

PRACTICAL WIRELESS

JANUARY 1966


2⁺

EXTRA *inside!*

16-PAGE
PULL-OUT
BOOKLET

SHORT
WAVE
DATA

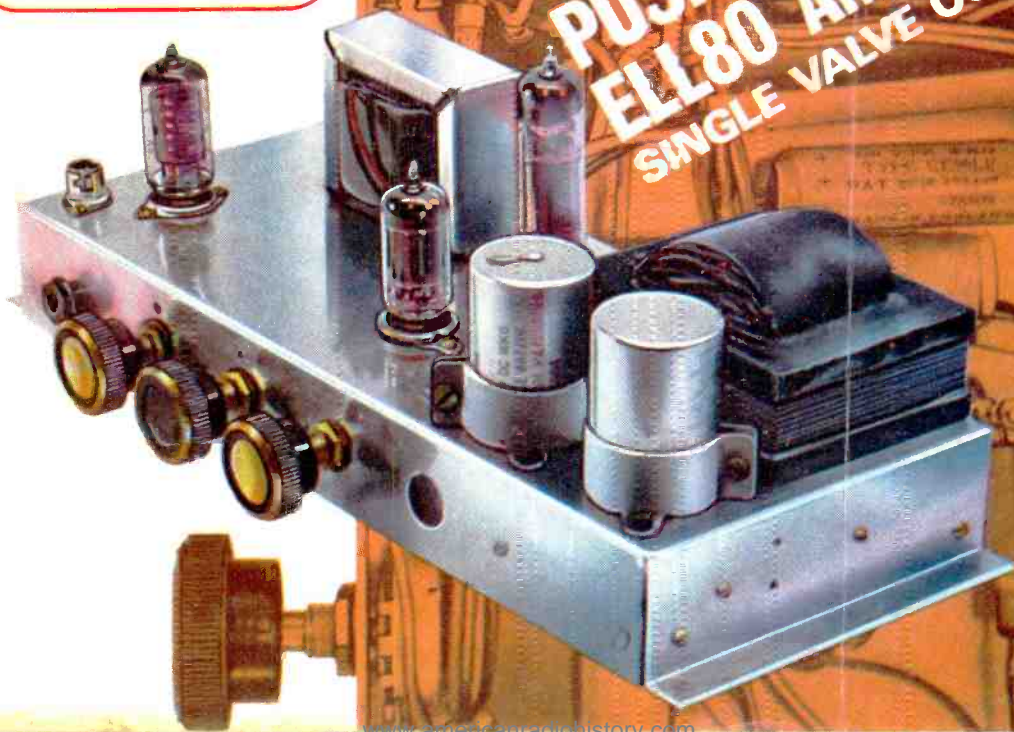
**PUSH-PULL
6X4
ELL80 AMPLIFIER**
SINGLE VALVE OUTPUT





SOLDERING EQUIPMENT

FOR THE RADIO CONSTRUCTOR

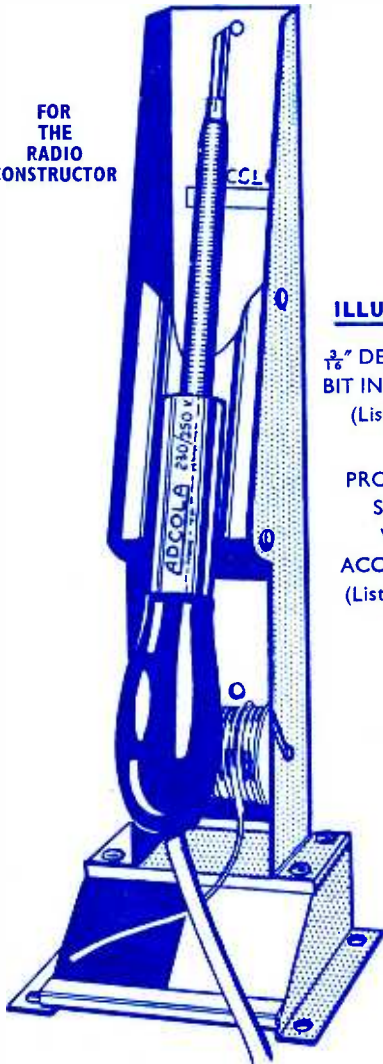

ILLUSTRATED

$\frac{3}{16}$ " DETACHABLE BIT INSTRUMENT (List No. 64)

IN PROTECTIVE SHIELD WITH ACCESSORIES (List No. 700)

FOR CATALOGUES APPLY DIRECT
ADCOLA PRODUCTS LTD.,
ADCOLA HOUSE,
GAUDEN ROAD,
LONDON, S.W.4

Telephones:
 MACaulay 3101
 4272
 Telegrams: "SOLJOINT" LONDON SW4

NOMBREX INSTRUMENTATION
TRANSISTORISED SIGNAL GENERATOR

Model 27 £9.16.9



Also available:

- ★ INDUCTANCE BRIDGE 66 ... £18.6.9
- ★ POWER SUPPLY UNIT 61 ... £6.14.6
- ★ C.R. BRIDGE 62 ... £8.11.9
- ★ AUDIO GENERATOR 63 ... £17.1.9

All Prices include Battery, Post and Packing.
 Prompt delivery

S.A.E. for Technical Leaflets

Trade and Export enquiries invited

NOMBREX LTD.

Phone: 3515

Estuary House, Camperdown Ter., Exmouth, Devon



For quick, easy faultless soldering

Ersin Multicore 5-core solder is easy to use and economical. It contains 5 cores of non-corrosive flux, cleaning instantly, heavily oxidised surfaces. No extra flux is required.



HANDY SOLDER DISPENSER

12 ft. of 18 s.w.g. SAVBIT alloy in a continuous coil, used direct from free-standing dispenser. **2/6 each**



LOW TEMPERATURE SOLDER

Size 9 pack contains 24 ft. of 60/40 high tin quality 22 s.w.g. **2/6 each**
 Size 10 pack 212 ft. 15/- each.



SAVBIT SIZE 1 CARTON

Contains approx. 30 ft. of 18 s.w.g. SAVBIT alloy. Also available in 14 and 16 s.w.g. **5/- each**




BIB WIRE STRIPPER AND CUTTER

Strips insulation, cuts wire cleanly. Adjusts to any size. **3/6 each**


Available from all Electrical and Hardware shops.
 If unobtainable write to:

MULTICORE SOLDERS LTD.

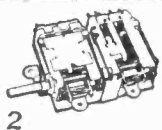
Multicore Works, Hemel Hempstead, Herts. Hemel Hempstead 3636 M.4




2

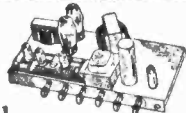

1

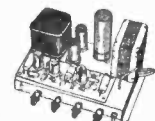


4

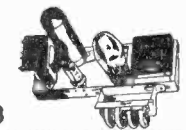


3




6

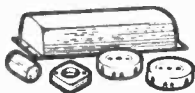


5

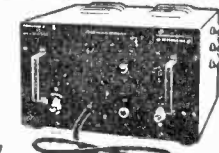


7

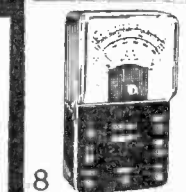

8

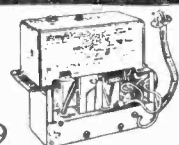

9

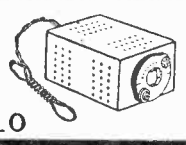

10




11




12



13

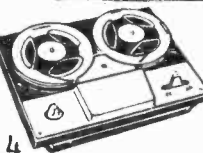

14

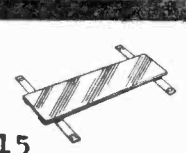

15

1. 6 VALVE 15 WATT PUSH-PULL AMPLIFIER. 15 x 7 x 1 1/2 in. A.C. Mains 200-250 volts. 4 inputs with controls for same and bass and treble lift controls. Tapped for 3 and 15 ohm speakers. Extra H.T. and L.T. for F.M. Tuner supplies etc. built and tested. 7 gns. P. & P. 13/6.
2. CYLON AM FM PERMEABILITY TUNERS FOR ALL TRANSISTOR OPERATION. Size 2 1/2 x 2 1/2 in. approx. By famous manufacturer. A.M. I.F. 470 Kc/s. F.M.-I.F. 10.7 Mc/s. A.M. coverage from 1020 Kc/s-525 Kc/s. F.M. coverage 108 Mc/s-88Mc/s. Circuit diagrams 2/6. FREE with Tuner, 1st, 2nd and 3rd A.M. I.F.'s, 1st, 2nd, 3rd and 4th F.M. I.F.'s V.H.F. Osc. choke, A.M. I.F. trap. All the above are the R.F. end of an A.M./F.M. receiver car radio etc. The above items £2.10.0.
3. AMPLIFIER KIT. 3 to 4 watt Amplifier Kit. Comprising chassis 3 1/2 x 2 1/2 x 1 in. Double wound mains transformer, output transformer, volume and tone controls, resistors, condensers etc. Valves 6V6, 6X05 and metal rectifier. Circuit 1/6, free with kit, 29/6 plus 4/6 P. & P.
4. 8-WATT 5-VALVE PUSH-PULL AMPLIFIER & METAL RECTIFIER. Size: 9 x 6 x 1 1/2 in. A.C. Mains, 200-250v. 5 valves. For use with 8rd. or L.P. records, musical instruments, all makes of pick-ups and mikes. Output 8 watts at 5 per cent total distortion. Separate bass and treble lift control. Two inputs, with controls for gain, and inke. Output transformer tapped for 3 and 15 ohm speech coils. Built and tested. £3.19.6. P. & P. 9/-.
5. 40W FLUORESCENT LIGHT KIT incorporating GEC Choke size 8 1/2 x 1 1/2 x 1 1/2 in. 2 bi-pin holders, starter and starter holder. 11/6. P. & P. 4/6. Similar to above: 80W Fluorescent Light Kit incorporating GEC choke size 11 1/2 x 1 1/2 x 1 1/2 in. 2 bi-pin holders, starter and starter holder. 17/6. P. & P. 5/6.
6. OSCILLOSCOPE FOR D.C. and A.C. APPLICATIONS. Push-pull X amplifier; Fly-back suppression; Internal Time-base Scan Wave form available for external use; pulse output available for checking T.V. line O/P Transformers, etc. Provision for external—1/P and C.R.T. Brightness Mod. Indicator. A.C. mains 200-250v. £15.15.0. P. & P. 10/- FULL 12 MONTHS' GUARANTEE INCLUDING VALVES and TUBE.
7. FIXED FREQUENCY SIGNAL GENERATOR. Crystal controls in metal case, size 10 x 6 x 6 in. Incorporating two FC13 valves, mains transformer, metal rectifier, choke, indicator, lamp, crystal and numerous components. Modulated and unmodulated output socket. Originally used for I.T.V. frequencies. Brand new, 39/6, plus 7/- P. & P. A.C. mains 200-250 volts. SILICON RECTIFIERS. 250v. P.I.V., 750mA. 81x for 7/6 post paid.
8. POCKET MULTI-METER. Size 3 1/2 x 2 1/2 x 1 1/2 in. Meter size 2 1/2 x 1 1/2 in. Sensitivity 1,000 O.P.V. on both A.C. and D.C. A.C. and D.C. volts. 0-15, 0-150, 0-1,000. D.C. current 0-150mA. Resistance 0-100k Ω. Complete with test leads battery and full instructions. 42/6. P. & P. 3/6. FREE GIFT to limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.
9. CHANNEL TUNER I.F. 16-19 Mc/s. Continuously tunable from 174-216 Mc/s. Valves required—PCP80 and PCC84 (in series). Cover BBC and ITA ranges. Also Police, Fire and Taxis, etc. Brand new by famous maker, 10/-, P. & P. 3/-.
10. POWER SUPPLY KIT in metal case, size 3 1/2 x 2 1/2 x 2 in. incorporating mains transformer, rectifier and condensers. 230/250 A.C. mains Output: 9v., 10mA. 10/6 plus 3/- P. & P.
11. B.S.R. MONARCH UA14 WITH FULL FI HEAD, 4-speed, plays 10 records, 12in., 10in., or 7in. at 16, 33, 45 or 78 r.p.m. Internixes 7in., 10in and 12in. records of the same speed. Has manual play position; colour brown. Dimensions: 12 1/2 x 10 1/2 in. Space required above baseboard 4 1/2 in., below baseboard 2 1/2 in. Fitted with full FI turnover crystal head. £5.19.6. P. & P. 7/6.
12. FIRST QUALITY PVC TAPE

5 1/2 in. Std. 550ft.	.. 9/-	5 in. L.P. 850ft.	.. 10/6
7 in. Std. 1200ft.	.. 11/8	5 in. T.P. 600ft.	.. 10/6
3 in. L.P. 240ft.	.. 4/-	5 in. T.P. 1800ft.	.. 25/6
5 1/2 in. L.P. 1200ft.	.. 11/8	5 1/2 in. T.P. 2400ft.	.. 32/6
7 in. L.P. 1800ft.	.. 13/6	7 in. T.P. 3600ft.	.. 42/6

 P. & P. on each 1/6. 4 or more Post Free
13. MAYFAIR 5-TRANSISTOR TAPE RECORDER. Capstan-driven, battery operated, 7 1/2 and 3 1/2 i.p.s. Precision made Push-button controls. High quality 2 1/2 in. speaker. Push-pull circuit. Output: 400 mw. Frequency response: 200-7,000 kc/s. Fast rewind. Up to 1 hour twin track playing time. Automatic crasing for re-recording. Dimensions: 8 in. x 11 in. x 3 1/2 in. Weighs only 7lbs. £11.11.0 plus 7/6 P. & P.
14. BSR TAPE DECK. AC 200/250v, tape speed 3 1/2 twin track. £5.5.0 P. & P. 7/6.
15. GEC FLAT HEATER ELEMENT 500 w. Can be used for wash boilers, washing machines, etc. Five or six elements can be used in parallel to give 2500/3000 watts. Size 5 1/2 x 1 1/2 in. copper enclosed, P. & P. 1/-, 4 or more Post Paid.

RADIO & TV COMPONENTS (ACTON) LTD.

21b High Street, Acton, London, W.3.

All enquiries Stamped Addressed Envelope.
Goods not despatched outside U.K.
Shop hours 9 a.m.—6 p.m. Early closing Wednesday

SPECIAL OFFER! FROM R. & T. V. LTD.



COMBINED PORTABLE & CAR RADIO


- 4in. **SPEAKER** The Radio with the STAR features
- ★ 7-transistor superhet. Output 350mWV.
 - ★ Grey wooden cabinet, fitted handle with silver coloured fittings. Size 12½ x 8½ x 3½in.
 - ★ Horizontal tuning scale, size 11½ x 2½in. in silver with black lettering.
 - ★ All stations clearly marked.
 - ★ Ferrite-rod internal aerial.
 - ★ I.F. neutralisation on each stage 460 kc/s.
 - ★ D.C. coupled output stage with separate A.C. negative feed back.
 - ★ All components, ferrite rod and tuning assembly mounted on printed board.
 - ★ Operated from PP9 battery.
 - ★ Full comprehensive instructions and point-to-point wiring diagrams.
 - ★ Printed circuit board, back printed with all component values.

ONLY **£4.4.0**

Plus 6/6 P. & P. Parts list & circuit diagram 2/6. FREE with parts.

SPECIAL OFFER—POWER SUPPLY KIT to purchasers of "Elegant Seven" parts, incorporating mains transformer, etc. A.C. mains 200-250V. Output 9v. 50mA. 7/6.

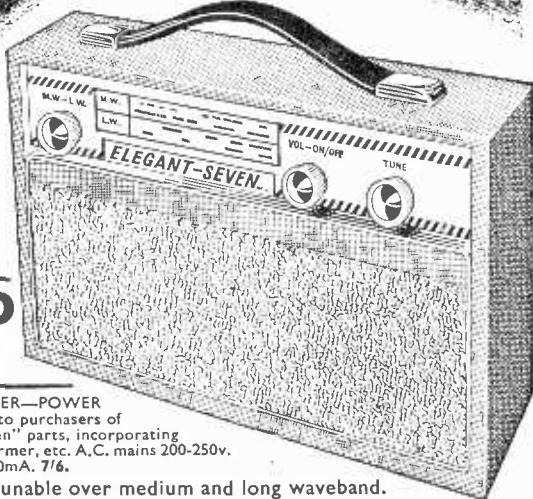- ★ Fully tunable over medium and long waveband.
- ★ Car aerial socket. Full after-sale service.



All enquiries Stamped Addressed Envelope.

RADIO & TV COMPONENTS (ACTON) LTD 21C High St., Acton, London W3

Open 9 a.m.—6 p.m. including Sats. Early closing Wed.

Goods not despatched outside U.K.

Terms C.W.O.

SURBITON PARK RADIO

MARTIN AUDIOKITS & RECORDAKITS

- F.M. TUNER UNITS** Nos. 15, 16 and 17..... Cash £12.17.6
 Or Dep. 51/6 and 12 m. pumts. of 18/10..... (H.P. Price £13.17.6)
- TRANSISTORISED AMPLIFIER** with 5 position input selector, pre-amp and con trols, 10 watt amplifier and Power Pack
 For 3 Ohm Speaker, Cash £14.5.0
 Or Dep. 57/- and 12 m. pumts. 20/10..... (H.P. Price £15.7.0)
 For 15 Ohm Speaker, Cash £15.5.0
 Or Dep. 62/- and 12 m. pumts. 22/6..... (H.P. Price £16/12/0)
- Two TRACK RECORDAKIT AMP. (Valve) FOR STUDIO DECK**, 6 valves, controls, self powered..... Cash £11.11.0
 Or Dep. 47/- and 8 m. pumts. 25/6..... (H.P. Price £12.11.0)
- COLLARO STUDIO DECK** 3 speed latest Two Track Cash £10.19.6
 Or Dep. 44/- and 8 m. pumts. 24/6..... (H.P. Price £12.0.0)
- COMPLETE KIT** with case, spkr., tape and mic..... Cash £29.19.6
 Or Dep. 120/- and 12 m. pumts. 44/-..... (H.P. Price £32/8/0)
- FOUR TRACK AMP.**, as above..... Cash £12.12.0
 Or Dep. 52/- and 8 m. pumts. 27/6..... (H.P. Price £13.12.0)
- FOUR TRACK COLLARO DECK** Marriot "X" Series heads, Cash £13.19.8
 Or Dep. 56/- and 12 m. pumts. 20/6..... (H.P. Price £15/2/0)
- COMPLETE KIT** with case, spkr., tape and mic. Four Track Cash £33.19.8
 Or Dep. 136/- and 12 m. pumts. 49/10..... (H.P. Price £36.14.0)
- TAPE PRE-AMP** for Studio Deck, self powered..... Two Track Cash £8.8.0
 Or Dep. 34/- and 6 m. pumts. 25/8..... (H.P. Price £9.9.0)
- TAPE PRE-AMP** as above..... Four Track Cash £9.9.0
 Or Dep. 35/- and 6 m. pumts. 26/4..... (H.P. Price £10.9.0)
- We are leading stockists for all Martin Constructional Kits.

SURBITON PARK RADIO LTD.

- ARMSTRONG 137 STEREO** as above Stereo amp..... Cash £37.10.0
 Or Dep. 150/- and 12 m. pumts. 55/-..... (H.P. Price £40.10.0)
- ARMSTRONG 227 MONO** 10W amp. with AM/FM..... Cash £38.15.0
 Or Dep. 147/- and 12 m. pumts. 53/10..... (H.P. Price £39.15.0)
- ARMSTRONG 227 STEREO** as above with Stereo Amp. Cash £52.15.0
 Or Dep. 211/- and 12 m. pumts. 77/4..... (H.P. Price £56.19.0)
- ARMSTRONG 226 STEREO** as above, but Mag. P.U. Filter Cash £81.0.0
 Or Dep. 260/- and 12 m. pumts. 88/-..... (H.P. Price £85.16.0)
- Teak Cases for all Armstrong Units**..... £3.10.0
- ROGERS CADEMK. 3** 10-10 watt Stereo Amp. Mag. P.U. Cash £29.10.0
 Or Dep. 118/- and 12 m. pumts. of 49/3..... (H.P. Price £31.0.0)
- CARRARD Model 3000 Stereo** LEAK STEREO 30 TRANSISTOR AMPLIFIER, Cash £49.10.0
 Or Dep. 198/- and 12 m. pumts. of 72/7..... (H.P. Price £53.9.1)

LOUDSPEAKERS: Selection

- FANE 122/10** Heavy Duty 12in. 20 watt..... Cash £5.5.0
- WHARFEDALE SUPER 8/RS/DD**..... Cash £7.0.0
- WHARFEDALE SUPER 10/RS/DD**..... Cash £11.13.4
- Or Dep. 47/6 and 8 m. pumts. 28/9**..... (H.P. Price £12.13.8)
- GOLDMANS MAXIM**..... Cash £17.10.6
- Or Dep. 70/6 and 12 m. pumts. 25/8**..... (H.P. Price £18.18.6)

MOTORS-PICK-UPS Selection

- GARRARD SRP10 Mono**..... Cash £5.10.0
- GARRARD Model 1000 Mono**..... Cash £7.10.0
- GARRARD Model 2000 Mono Large Table**..... Cash £8.10.0
- Or Dep. 34/- and 6 m. pumts. 28/-**..... (H.P. Price £9.10.0)
- GARRARD Model 3000 Stereo Lightweight arm**..... Cash £11.11.0
- Or Dep. 47/- and 8 m. pumts. 25/6**..... (H.P. Price £12.11.0)
- GARRARD S.P. 25** Less cart.; Single player..... Cash £12.10.0
- Or Dep. 50/- and 8 m. pumts. of 27/6**..... (H.P. Price £13.10.0)
- GARRARD A169** Less cart.; Heavy table..... Cash £13.0.0
- Or Dep. 52/- and 12 m. pumts. 19/-**..... (H.P. Price £14.0.0)
- GARRARD LA180** Push button oper., less cart..... Cash £27.10.0
- Or Dep. 110/- and 12 m. pumts. of 40/4**..... (H.P. Price £29.14.0)
- GARRARD 401** Transcription Table. No arm..... Cash £32.10.0
- Or Dep. 130/- and 12 m. pumts. 47/8**..... (H.P. Price £35.2.0)
- GOLDRING 446** Mono Single Player..... Cash £11.11.0
- Or Dep. 47/- and 8 m. pumts. 25/6**..... (H.P. Price £12.11.0)
- GOLDRING GL58** less cart.; Heavy table, single play Cash £17.1.0
- Or Dep. 69/- and 12 m. pumts. 24/11**..... (H.P. Price £18.8.0)
- GOLDRING GL70** trans.; Unit with arm, less cart. Cash £29.18.6
- Or Dep. 120/6 and 12 m. pumts. 43/9**..... (H.P. Price £32.5.6)
- Leaflets available upon receipt of 6d. stamp.

48-50, Surbiton Road, Kingstom-on-Thames, Surrey
 Phone KIN. 5549: Hours 9 a.m. to 6 p.m. daily (1 p.m. Weds.)



Offer the Finest Value and HOME CONSTRUCTORS

We wish all our customers old and new the Compliments of the Season and cordially invite you to select your Gifts from our huge selection of bargains.

THE "SKYROVER" RANGE

GENERAL SPECIFICATION

7 transistor plus 2 diode superhet, 6 waveband portable receiver. Operating from four 1.5 v. torch batteries. The SKYROVER and SKYROVER DE LUXE cover the full Medium Waveband and Short Waveband 31-94 M and also 4 separate switched band-spread ranges, 13M, 16M, 19M and 25M, with Band Spread Tuning for accurate Station Selection. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our easy to follow stage by stage instructions.



NEW—The SKYROVER Mk III

Now supplied with redesigned cabinet, edgewise controls, black and chrome plastic cabinet. Size 10 x 6 1/2 x 3 1/2 in. with carrying handle. **£8.19.6** Post 5/-
Can now be built for
H.P. Terms: 27/- dep. and 11 months at 15/8. Total H.P. Price £10.0.8.

The SKYROVER DE LUXE


Tone Control Circuit is incorporated with separate Control. In a wood cabinet, size 11 1/2 x 6 1/2 x 3 1/2 in., covered with a washable material with plastic trim and carrying handle. Car aerial socket fitted. **£10.19.6** Post 5/-
Can now be built for
H.P. Terms: 33/- dep. and 11 mths at 19/2. Total H.P.P. £12.3.10

A simple additional circuit provides coverage of the 1100/1950M. band (including 1500 M. Light programme). All components and detailed construction data. **Only 10/- extra** Post Free
This conversion is suitable for both models that have already been constructed.

Data for Receiver 278 extra. Refunded if you purchase the parcel. Four U2 batteries 3/6 extra. All components available separately.

The "REALISTIC" Seven


★ 7-Transistor Superhet. ★ 350 milliwatt output into 4in. high flux speaker.
★ All components mounted on a single printed circuit board. ★ Full medium and long wave cover. ★ Plastic cabinet with carrying handle, size 7 x 10 x 3 1/2 in. Blue/Grey or all Grey.
★ Socket for car aerial. ★ L.P. frequency 470 Kc/s
★ Ferrite rod internal aerial. Operates from PPG or battery. ★ Full data supplied. All coils and L.P.'s etc. fully wound ready for immediate assembly. An outstanding receiver.
Can be built for **£5.19.6**

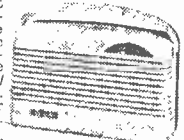

PPG Unit, 3/9. Data and instructions separately 2/6. Refunded if you purchase the parcel. All parts sold separately.

REALISTIC Seven DE LUXE

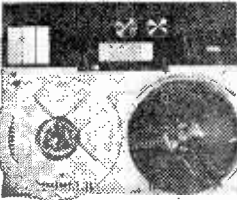With the same specifications as standard model—PLUS a superior wood cabinet in contemporary styling with full vision circular dial. **ONLY £1 EXTRA**



The Very Latest MAGNAVOX-GOLLARO 363 TAPE DECKS

3 speed model—11, 3 1/2, 7 1/2 i.p.s., available with either 1 track or 2 track heads. Features include: pause control; digital counter; fast forward and rewind; new 4 pole fully screened induction motor; interlocking keys. Size of top plate 13 1/2 x 11 x 5 1/2 in. deep below unit plate. For 200/250v. A.C. mains, 50 c.p.s. operation. New, unused and fully guaranteed.

LASKY'S PRICE with 1 track heads **£10.10.0** Carriage and packing 7/6 extra
LASKY'S PRICE with 2 track heads **£13.19.6**

SPECIAL for OVERSEAS CUSTOMERS—the new Magnavox-Gollaro 363 Deck for 110/125 v. 50 or 60 c.p.s. mains now available, prices as above. Post to any part of the World, 35/-.

Give a Lasky's Gift Voucher

The ideal gift for Christmas and all those other special occasions. Any value in multiples of 10/6 (min.) upwards.
Special Christmas Offer— Vouchers worth more than you pay! e.g. 1 Guinea Voucher for £1—10/6 Voucher 10/- etc.
You save money and give pleasure with a Lasky's Gift Voucher.

TRANSISTORS new & guaranteed

GET 81, GET 85, GET 86, 2/8; 87A, 87A/1, 8/8; OC45, OC71, OC81D, 4/6; OC44, OC70, OC76, OC81 (match pair 10/6) 5/6; AF17, OC75, OC200 6/8; OC43, OC43, OC78, OC82D 7/8; OC91, OC204 15/-; OC205, OC206 10/6; OC28 24/8.

TRANSFILTERS BY BRUSA CRYSTAL CO.

TO—01B 465 kc/s. ± 2 kc/s.
TO—01D 470 kc/s. ± 2 kc/s.
TO—02B 465 kc/s. ± 1 kc/s.
TO—02D 470 kc/s. ± 1 kc/s.
TF—01B 465 kc/s. ± 2 kc/s.
TF—01D 470 kc/s. ± 2 kc/s.

7/6 EACH
Post 6d.

B.S.R. AUTOCHANGERS—BRAND NEW AT LOWEST EVER PRICES

Brand new and fully guaranteed—complete with cartridge and stylus.

UA14 4 speed mains model £4.9.6
UA16 4 speed mains model £4.19.6
UA16 9v. battery model £5.19.6
UA20 4 speed mains model £5.19.6
Add 5/- carriage and packing on each

INTERNATIONAL TAPE

3in. Message tape, 150ft. 3 6
3in. Message tape, 225ft. 4 11
3in. Message tape, 300ft. 7 6
3 1/2in. Triple play, 600ft., Mylar base 15 0
4in. Triple play, 900ft., Mylar base 17 6
5in. Double play, 1,200ft., Mylar base 15 0
5in. Long play, 900ft., Acetate base 10 0
6in. Standard play, 600ft., PVC base 8 6
5in. Triple play, 1,800ft., Mylar base 25 0
5 1/2in. Double play, 1,800ft., Mylar base 22 6

Famous American Brand—Fully Guaranteed

5 1/2in. Long play, 1,400ft., Acetate base 12 6
9 1/2in. Standard play, 850ft., PVC base 11 0
9 1/2in. Triple play, 2,400ft., Mylar base 45 0
7in. Standard play, 1,200ft., Acetate base 10 0
7in. Standard play, 1,200ft., Mylar base 12 6
7in. Long play, 1,800ft., Mylar base 19 6
7in. Double play, 2,400ft., Mylar base 25 0
7in. Long play, 1,800ft., Acetate base 15 0
7in. Triple play, 3,600ft., Mylar base 58 6
P. & P. 1/- extra per reel; 4 reels and over Post Free.

GOODMANS OF ENGLAND CROSSOVER UNITS

XO/50 HALF SECTION CROSSOVER. For use with bass and treble speakers, 150 imp. to crossover at 750 c.p.s. Rated at 25 watts (British). In wood case 6 1/2 x 4 x 4 in. New and unused.

LASKY'S PRICE 29/- Post 2/6.

STEREOPHONIC FILTER. This is a frequency divider/mixer for use with a Stereo amplifier. Its function is to combine the bass frequencies up to 300 c.p.s. into a single bass speaker for both channels and to divide the frequencies above 300 c.p.s. into two separate mid/top range speakers. It can also be used as a 300 c.p.s. crossover for a mono system. 150 imp. Rated at 25 watts (British). In wood case 10 x 4 1/2 x 3 in. New and unused.

LASKY'S PRICE 19/6 Post 2/6.

SINCLAIR MINIATURES

We stock the complete range of Sinclair Super-miniature Kits.
THE MICRO-6 pocket radio 59/8
THE SLIMLINE pocket radio 49/6
THE X-20 Amplifier £7.19.6
Ready built and tested £9.19.6
THE X-40 Amplifier £25.19.6
Ready Built and Tested £25.19.6
See our Practical Wireless November '65 advertisement for details.

U.H.F. TUNERS

Only a few available. Complete with PCB6 and PCB8 valves. We regret no circuit or data is available. Knobs included

LASKY'S PRICE 79/6 Post 9/6.

GORLER UT 340 FM/VHF TUNING HEART

Permeability tunes—covering 87 to 108 Mc/s. For use with one ECC85 valve. In metal case, size 3 x 2 1/2 x 1 1/2 in. Circuit supplied.

LASKY'S PRICE 19/11 Post 2/6.
ECC85 valve 9/- extra.


LASKY'S FOR D.I.Y. CONSTRUCTION BARGAINS

Service in Great Britain to both & HI-FI ENTHUSIASTS

TAPE RECORDERS . RECORD PLAYERS . AMPLIFIERS ETC.
COMPLETE MONO/STEREO SYSTEMS TO YOUR SPEC.



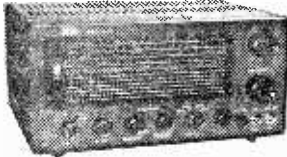NEW COMMUNICATION RECEIVERS MODEL KT 320 KIT




Supplied in sub-assemblies for easy building. Covers range from 540 Kc/s to 30 Mc/s. Ham Band is provided with a scale for direct reading and can also be band spread. 9 valves. Facilities: A.N.L., A.V.C. and M.V.C. Q Multiplier also serves as B.F.O. H.F. stage and two I.F. stages ensure high sensitivity and selectivity (all coils and I.F.s are supplied pre-adjusted). 2 Aerial Sockets. Stand-by position for use with a transmitter 8 meter fitted. 200-250V. A.C. mains. Steel cabinet, grey crackle finish. Size 13 x 8 x 10in. Dial 12 x 4in. All parts new and fully guaranteed. Complete with full construction data and operating manual.

LASKY'S PRICE 25 GNS. POST FREE
Also available ready built and tested 29 gns.
H.P. Terms available.

MODEL HE30 Still a few available—
as advertised June '66.
LASKY'S PRICE 33 GNS.
H.P. Terms available.

MODEL HE40

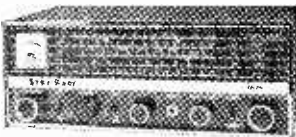

Covers medium wave band and 1.6-4.4 Mc/s, 4.5-11.0 Mc/s, 11.0-30.0 Mc/s, in separate switched band spread ranges. Controls include B.F.O. Sensitivity, A.N.L. Receiver—stand-by switch, Tone Switch, S-Meter. For 200-250V. A.C./D.C. Internal loop and telescopic antennae fitted. Valve line-up: 12BE6, 12BA6, 12AV6, 50C5, and metal rectifier. Size 13½ x 8½ x 5½in. Instruction manual included. No Kits available.

LASKY'S PRICE 19 GNS. POST 10/-
H.P. Terms £4.0.0. dep. and 12 months at £112.0.
Total H.P.P. £211.2.0.

MODEL HE80 14-valve super sensitive communication receiver. Freq. range 530 Kc/s—30 Mc/s, and 144-146 Mc/s. Dual conversion on 2 metres, with extra R.F. stage. Single R.F. stage, two I.F. stages on all other bands. B.F.O. and Q-multiplier circuits. Improved A.N.L. and voltage regulated powerpack. "8" meter dial with logging scale. All controls fitted. Output for speaker and phones. Valve line-up: 4 x 6AQ5, 3 x 6BA6, 2 x 6BE6, 1 x 6BL8, 6AL5, 6AQ5, 6A4, A.C. mains. Brand new with full instruction manual. No Kits available.

LASKY'S PRICE 59 GNS. POST FREE
H.P. Terms £12.19.0 dep. and 11 monthly payments of £4.18.0. Total H.P.P. £66.17.0.

SPECIAL ANNOUNCEMENT—Our Head Office and Mail Order Departments have now been transferred to our new building: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E.1

Telephones: STEPNEY GREEN 4281/2
All Mail Orders, correspondence, H.P. enquiries/accounts etc. should now be sent to the above address.

These premises have been especially designed for us to facilitate the handling of Mail Orders and continue our aim of rapid despatch coupled with good service, with which our name has been synonymous over the past 35 years.

Ideal Christmas Presents

TRANSISTOR POCKET RADIOS



All supplied complete with personal earpiece, battery and carrying case. Fully guaranteed—ready to use. POST FREE.
BOY'S 2 TRANSISTOR In attractive plastic case. Size only 4in. x 2½in. x 1in. Fitted 2½in. speaker. Socket for personal earpiece. Uses PP3 battery. Tunable over full medium waveband.
LASKY'S PRICE 35/-

BOY'S 4 TRANSISTOR MODEL **LASKY'S PRICE 45/-**

6 TRANSISTOR MODEL

Fully built in plastic case. 4in x 2½in. x 1½in. with 2½in. speaker. Uses single PP3 type battery. Tunable over full medium waveband.
LASKY'S PRICE 59/6

2 Waveband (Long and Medium) Model Size 6 x 3½ x 1½in. Cream/black plastic case. Incl. earpiece & carrying case. **LASKY'S PRICE 89/6**


THE "TRANSWAVE" DE LUXE TWO WAVEBAND RADIO

8 Sony transistors give super sensitive reception over the full Med. and Long wavebands. Internal ferrite and detachable chrome telescopic aerials. 2½" p.m. speaker. Sleek black plastic cabinet with metal trim—size 6½ x 3½ x 1½in. Uses 3 pen light batteries. Complete with leather case and shoulder strap. **LASKY'S PRICE 99/6**

3 WONDERFUL SETS FROM THE U.S.S.R.

THE "SELGA" 7 TRANSISTOR RADIO

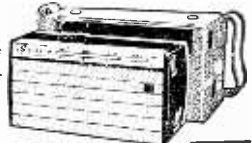High sensitivity circuit gives excellent reception over full Med waveband and powerful volume. P.M. speaker. Uses PP3 type battery. Black and ivory plastic cabinet size 7 x 4 x 2½in. Socket for external aerial. Complete with solid hule case and shoulder strap, earpiece and battery.



LASKY'S PRICE £5.9.6 Post 2/6


THE "SOKOL" 7 TRANSISTOR TWO BAND RADIO

Super quality receiver covering the full Med. and Long wavebands with exclusive rechargeable battery which can be recharged from any 110/250V. A.C. mains supply. Also operates on PP3 type dry battery. P.M. speaker. Ivory and black plastic cabinet 6 x 3½ x 1½in. Socket for external aerial. Complete with real leather case, rechargeable battery and charger, dry battery and earpiece. **LASKY'S PRICE £6.9.6** Post 2/6

THE "CONVAIR"

10 TRANSISTOR PORTABLE RECEIVER

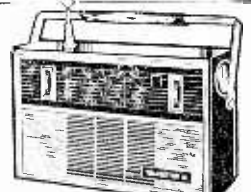Extremely well designed and made receiver covering the Long, Med and Short wavebands. The short waveband has switched hand spread on 13m., 16m., 19m., 25m., 31m., 41m. bands. Internal ferrite rod and telescopic aerials. Sockets for external aerial and earth and gram. pick-up. Strong cream and black plastic cabinet with carrying handle—size 10 x 7½ x 3½in. Uses six 1½ type batteries (supplied).



LASKY'S PRICE £12.19.6 Post 5/-

SPECIAL OFFER: GARRARD AT5 AUTOCHANGERS

4 speed mains model—brand new and fully guaranteed.
LASKY'S PRICE With mono crystal cartridge **£5.19.6** With stereo cartridge **£6.9.6** Post 5/-

207 EDGWARE RD, LONDON, W.2 Tel: PAD 3271/2
33 TOTTENHAM CT. RD., LONDON, W.1 Tel: MUS 2605
Both open all day Saturday. Early closing Thursday.

42 TOTTENHAM CT. RD., LONDON, W.1 Tel: LAN 2573
152/3 FLEET STREET, LONDON, E.C.4 Tel: FLE 2833
Both open all day Thursday. Early closing Saturday.

Please address all Mail Orders and correspondence to 3-15 Cavell St., Tower Hamlets, London, E.1.

LASKY'S FOR SPEEDY MAIL ORDER SERVICE



Heathkit models offer outstanding performance plus highest quality - at lowest cost

Anyone can build a Heathkit model. The easy-to-follow instruction manuals issued with each kit-set show you how. You will be proud of the professional appearance and performance of your finished model.

A KIT FOR EVERY INTEREST . . . FOR HOME, WORKSHOP, SERVICE & TEST DEPTS

NEW MODELS

PORTABLE SCOPE, Model OS-2. ★ Improved performance facilities and modern styling. ★ 'Y' bandwidth 2 c/s to 3 mc/s. ★ Automatic lock-in sync. ★ Mumetal C.R.T. shield. ★ P.C. Board. ★ Switched EXT/INT 'Y' plate connections. Size 5" x 7 3/4" x 12" deep. Weight 9 1/2 lb. Send for full specification. Kit £22.18.0. Assembled £30.8.0.

BERKELEY Slim-line LOUDSPEAKER SYSTEM. ★ Now from Heathkit, a loudspeaker kit with a fully finished walnut cabinet. ★ A 2 speaker system. ★ Modern, slim-line styling. ★ 30 c/s to 17 kc/s. ★ Only 7 1/2" thick. ★ Use it horizontally or vertically. ★ Stand it on the floor or in your bookshelf. Kit £18.10.0.

TEST INSTRUMENTS



10-12U

5in. **OSCILLOSCOPE Model 10-12U.** Laboratory quality at utility oscilloscope price. Wide band amplifiers essential for T.V. servicing, F.M. alignment, etc. T/B covers 10 c/s-500 kc/s in 5 ranges. £45.15.0 Assembled **£35.17.6** Kit

NEW! SINE/SQ GENERATOR, Model 1G-82U. Freq. range: 20 c/s—1 Mc/s in 5 bands. Simultaneous sine and square wave outputs. £36.10.0 Assembled **£24.10.0** Kit

REGULATED POWER SUPPLY Model IP-20U. Transistorised, 0-5-50 v. D.C. Up to 1.5 amps. Compact; 9 1/2 x 6 1/2 x 11 in. £47.8.0 Assembled **£35.8.0** Kit

VALVE VOLTMETER, Model V-7A. The world's best selling VTVM. Measures up to 1,500 volts (d.c. and r.m.s.) and 4,000 pk. to pk. Res. 0-1 Ω 1,000 MΩ. Centre zero dB scale, d.c. input resistance 11MΩ. 4 1/2 in. meter. Complete with test probes, leads and standardising battery. £19.18.6 Assembled **£13.18.6** Kit



V-7A

DE-LUXE 6in. VALVE VOLTMETER, Model 1M-13U. Similar spec. to mod. V-7A but with improved accuracy. Larger meter. Unique zimbal mount. £26.18.0 Assembled **£18.18.0** Kit

R.F. and H.V. probes available as extras.



DE-LUXE TRANSISTOR TESTER, Model 1M-30U. Many special features. Provides complete d.c. analysis of PNP NPN transistors and diodes. £35.10.0 Assd. **£24.18.0** Kit

HARMONIC DISTORTION METER, Model 1M-12U. Freq. cov.: 20-20,000 c/s. £34.0.0 Assembled **£24.15.0** Kit

TV ALIGNMENT GENERATOR, Model HFV-1 Covers 3-6 to 220 Mc/s fundamentals. £47.10.0 Assembled **£37.18.0** Kit


RF SIGNAL GENERATOR, Model RF-1U. Up to 100 Mc/s fundamental, 200 Mc/s harmonics. Up to 100 mV output on all bands. £19.18.0 Assembled **£13.8.0** Kit

MULTIMETER, Model MM-1U. Ranges: 0-1-5 v. to 1,500 v. a.c. and d.c.; 150 μA to 15 A d.c.; 0-2Ω to 20MΩ. 4 1/2 in. 50 μA meter. £18.11.6 Assembled **£12.18.0** Kit

A wide range of other test instruments available including: R/C Bridge C-3U £10.10.0. AF V/Volmeter AV-3U £16.10.0. Wattmeters AW-1U, £17.5.0. Capacitance meter CM-1U £15.15.0. Power supplies. Decade boxes etc.

AMATEUR EQUIPMENT

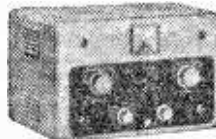
AMATEUR TRANSMITTER, Model DX-100U. Covers all amateur bands 160-10M. 150 w. d.c. input, self contained with power supply. Modulator, VFO **£79.10.0** Kit
Assembled £104.15.0



DX-40U

AMATEUR TRANSMITTER, Model DX-40U. Covers 80-10 m. Power inputs 75 w. C.W., 60 w. peak C.C. phone. Output 40 w. to aerial. Prov. for VFO. **£33.19.0** Kit
Assembled £45.8.0

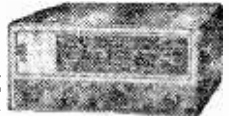COMMUNICATIONS TYPE RECEIVER RG-1. A high performance low cost receiver for the discriminating listener. Freq. cov. 600 kc/s-1.5 Mc/s and 1-7 Mc/s to 32 Mc/s. send for details. **£39.16.0** Kit
£53.0.0 Assembled



Other kits in the amateur range include: SSB Adaptor SB-10U £39.5.0. Variable freq. Oscillator VF-1U £10.17.6. Balun Coil Unit B-1U £4.15.6. Grid-Dip Meter GD-1U £10.19.6. Q Multiplier QPM-1 £8.10.0. Reflected Power Meter HM-11U £8.5.0.


HI-FI SPEAKER SYSTEMS

COTSWOLD STANDARD MODEL. Acoustically designed enclosure "in the white" 26 x 23 x 15 1/2 in. 12 in. bass speaker, elliptical middle speaker, 2 in. bass pressure unit. Covers 30-20,000 c/s. Complete kit with all controls.



MFS SYSTEM

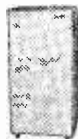A minimum floor space model for the smaller room. 26 in. high x 16 1/2 in. x 14 in. deep. Similar performance to standard model. Price either model **£25.12.0** Kit



SSU-1 SYSTEM

A practical solution to the problem of a moderately priced speaker suitable for Stereo Mono amplifiers where the equipment has to be compact. Two speakers, balance control, ducted port reflex cabinet. Horizontal or vertical (with matching legs). Incl. P.T. **£12.12.0** Kit



DAYSTROM LTD

Dept. PW1 GLOUCESTER, ENGLAND

**MODELS FOR HOME, TEST AND WORKSHOP.
BRITISH HEATHKIT MODELS USE BRITISH COMPONENTS**



HI-FI AMPLIFIERS

DE-LUXE ALL TRANSISTOR STEREO AMPLIFIER AA-22U.

At last, a British transistor amplifier with high power (20 + 20W) at a reasonable cost, capable of delivering full power at all frequencies in the audio band. Handsome fully finished walnut veneered cabinet available. Professional slim-line styling. Send for full specification. Kit (less cabinet) £39.10.0 Cabinet £25.0. Accessories for panel mounting £1.18.0.



6W DE-LUXE STEREO AMPLIFIER. Model S-33H. An inexpensive stereo amplifier with high sensitivity. Suitable for use with Decca Deram cartridge. £15.17.6 Kit

£21.17.6 Assembled

TAPE RECORD/REPLAY AMPLIFIER KITS. Will operate with most tape decks. Send for details.

TA-1M (Mono), £19.18.0 Kit. **TA-1S (Stereo),** £25.10.0 Kit.

STEREO CONTROL UNIT. Model USC-1. Ideal for use with MA-12 amplifiers. Kit: £19.10.0. Assembled £25.10.0.



S-33


6V STEREO AMPLIFIER Model S-33. 3 w/ch. Inputs for radio, tape and gram. Stereo/Mono ganged controls. Sensitivity 200mV. £18.18.0 Assembled **£13.7.6 Kit**

TRANSISTOR MIXER, Model TM-1. A must for the Tape enthusiast. £16.17.6 Assembled **£11.16.6 Kit**

5W HI-FI MONO AMPLIFIER. Model MA-5. A low priced amplifier based on the S-33. Printed circuit construction makes it easy to build. £15.10.0 Assembled **£10.19.6 Kit**

HI-FI MONO POWER AMPLIFIER. Model MA-12. Ideal for use with Models USC-1 and UMC-1, 0.1 THD at 10W. Wide frequency range. £15.18.0 Assembled **£11.18.0 Kit**

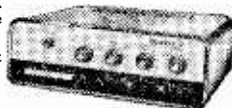18W STEREO AMPLIFIER. Model S-99. Ganged controls. Stereo/Mono gram, radio and tape record inputs. P/B selection. £38.9.6 Assembled **£28.19.6 Kit**




S-99

A range of R/players, T/Decks available.
Send for full spec. of any model

TRANSISTOR RECEIVERS

"OXFORD" LUXURY TRANSISTOR DUAL WAVEBAND RECEIVER.

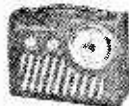The ideal domestic or personal portable receiver. 10 Semi-conductors. Solid leather case. Send for full details. Incl. P.T. **£14.18.0 Kit**



6 TRANSISTOR PORTABLE. Model UXR-1. Preamplified I.F. transformers. Printed circuit, 7in. x 4in. high flux speaker. Real hide case. Very easy to build. Incl. P.T. **£12.11.0 Kit**

"MOHICAN" GENERAL COVERAGE RECEIVER. Model GC-1U. Excellent portable or general purpose receiver for "amateur" or short wave listening. See full spec. leaflets. Assembled £45.17.5 **£37.17.6 Kit**



GC-1U

SPEAKERS FOR YOUR OWN ENCLOSURE

- 12" Heavy-duty Bass (ane 122/12) £7.7.0.
- 2" Tweeter (Fane 301) £3.1.6.
- (both as used in the Cotswold systems).
- 12" Bass speaker (Audiom-51) £9.12.5.
- 8" Goodman's General Purpose G8 £1.8.6.
- Two Speakers + Cross-over, System SCM-1.
- (As used in model SSU-1) with details for enclosure £5.5.0.

ELECTRONIC WORKSHOP KIT. Model EW-1. An outstanding experimental kit for children. £7.13.6 incl. P.T.

A WIDE RANGE OF BOOKS ON ELECTRONICS AND RADIO. PLEASE SEND FOR LISTS OR PRICES.

Many other models covering a wide range of equipment for HOME, OFFICE or Workshop.
SEND FOR FREE BRITISH CATALOGUE
American Catalogue sent for 1/- post paid

HI-FI TUNERS

Model FM-4U. Tuning range 88-108 Mc/s. Tuning unit (FMT-4U) with 10.7 Mc/s. I.F. (£2.15.0 incl. P.T.). I.F. Amp. (FMA-4U) complete with cabinet and valves (£13.13.0). Total **£16.8.0 Kit**



Assembly can be arranged.

FM-4U

AM/FM TUNER. Covers FM 88-108 Mc/s. A.M. 16-50, 200-550, 900-2,000 m. Tuning heart (£4.13.6 incl. P.T.), and I.F. Amp. (£22.11.6). Total **£27.5.0 Kit**

Send for leaflets. Assembly can be arranged.

EQUIPMENT CABINETS



A large range, in kit form or assembled and finished, available to meet most needs. Illustrated details on request.

Prices from **£8.8.0** to **£46.4.0**

PUBLIC ADDRESS AMPLIFIER, PA-1. 50 w. Amplifier, two heavy duty speakers, variable Tremolo. Ideal for use with guitars, etc. **£54.15.0 Kit**
£74.0.0 Assembled
Legs optional extra 17/6. Set of 4.



50 W POWER AMPLIFIER, MA-50 Ideal for PA work, electronic organs etc. **£27.18.0 Assembled £19.18.0 Kit**

STARMAKER '33. Transistorised PA/Guitar Amplifier. All transistor circuit gives full 20 watts r.m.s. output. Two heavy duty 12" speakers, Tremolo. Compact size 18" x 29" wide x 10" deep. Kit **£44.19.0.** Assembled **£59.10.0** available shortly.

FREE CATALOGUE of the BRITISH HEATHKIT RANGE
Gladly sent on request . . .

To DAYSTROM LTD. Dept. P.W.-1, GLOUCESTER ENG.

Please send me **FREE BRITISH CATALOGUE** (Yes/No)

Full details of model(s) _____


NAME _____

ADDRESS _____

ADAMIN

Micro Soldering Instruments

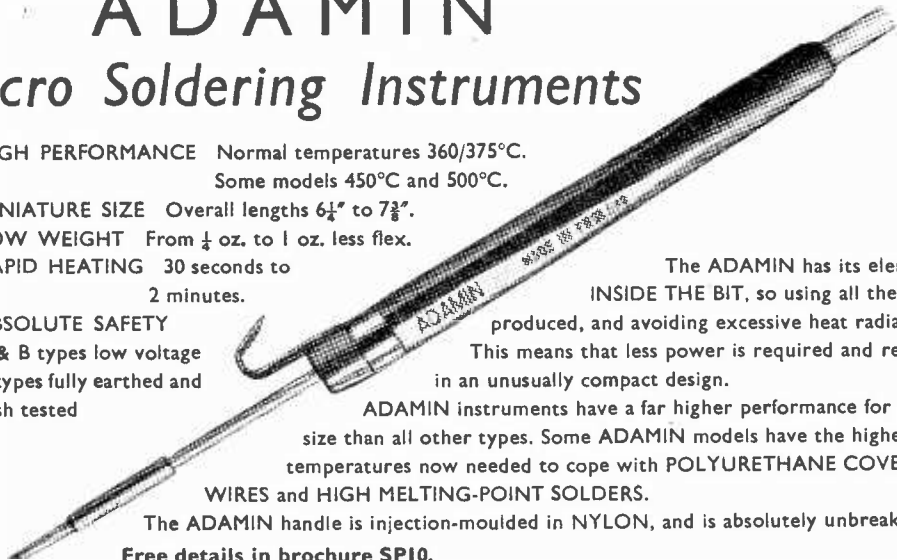- **HIGH PERFORMANCE** Normal temperatures 360/375°C.
Some models 450°C and 500°C.
- **MINIATURE SIZE** Overall lengths 6¼" to 7¾".
- **LOW WEIGHT** From ½ oz. to 1 oz. less flex.
- **RAPID HEATING** 30 seconds to 2 minutes.
- **ABSOLUTE SAFETY**
A & B types low voltage
C types fully earthed and flash tested



The ADAMIN has its element **INSIDE THE BIT**, so using all the heat produced, and avoiding excessive heat radiation. This means that less power is required and results in an unusually compact design.

ADAMIN instruments have a far higher performance for their size than all other types. Some ADAMIN models have the higher bit temperatures now needed to cope with **POLYURETHANE COVERED WIRES** and **HIGH MELTING-POINT SOLDERS**.

The ADAMIN handle is injection-moulded in **NYLON**, and is absolutely unbreakable.

Free details in brochure **SPI0**.


LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon, Surrey.

Telephone: CROydon 8589

EX-RENTAL TELEVISIONS

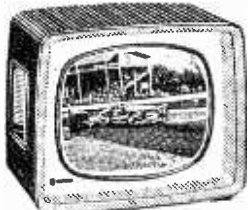14 in. 17 in.
£7.10.0 £11.10.0
12 months 3 star Guarantee
★Tubes★Valves★Components
COLOURED FREE LIST
Channels for all areas
Demonstrations daily from Large Selection.



Personal collection or insured
Carr. 14in. 20/-; 17in. 30/-.

AERIALS, BBC/ITA combined Loft and room aeriels—from 26/-
BBC/2UHF and colour aeriels—from 29/6, **SEND FOR FREE LIST**.

EX-MAINTENANCE TESTED TUBES

17in.—35/- Most makes and types available. 14in.—15/-
Guaranteed good picture. Carriage 5/- extra.

ONE YEAR GUARANTEED TUBES

21 in. 99/6
17 in. 79/6
15, 14 59/6
12 in.



100% **REGUNDED**
Add 10/- or old tube.
All 110°—99/6 plus
30/- refundable on
old tube. Carr. 10/6.
14in. Slimline 17 &
19 in. — overseas
posting 30/-.

VALVES £1 per 100. Assorted TV and Radio.
Surplus ex-rental dismantled receivers. Post 4/6.
Send for list

CONDENSERS 10/- per 100. New Assorted Electrolytics and pFs. P.P. 2/6.

RESISTORS 5/- per 100. New. Mostly High Stabs.
Assorted. P.P. 2/- Overseas 3/6.

SPEAKERS 7/6 6in., 8in., 7 x 4in., 8 x 3in. Ex-infd.
Salvage. P.P. 2/3. Overseas 4/-.

DUKE & CO. (LONDON) LTD.

621/3 Romford Road, Manor Park, E.12

Liverpool St.—Manor Pk.—10 mins.

Phone: ILFord 600/1/2/3. Stamp for Free List

TELEPHONE HAND-SETS

15/6

pair

G.P.O. pattern

House to Workshop

Garage, Inter-Office,
etc.

Works off any small
battery. P. & P. 4/6.

SPECIAL BARGAINS FROM RADIO EXCHANGE

THE SIG-GEN. A versatile Signal Injector. something no constructor should be without. This ingenious device generates an audible signal through the Audio and RF ranges. With variable output. Telescopic Probe. Pocket size slim line case measures 4½ x 3½ x 1½. Complete set of parts with full instructions. 19/6. P. & P. 1/6.

TUNING CONDENSERS. Air spaced one quality German manufacture with slow motion drive 0.0005. With oscillator section. **BRAND NEW** One 6/6. P. & P. 1/6.

1800mw TRANSISTOR AUDIO AMPLIFIER. Designed to give high quality at low cost. This superb amplifier uses 4 transistors including a special power type operating from a 1.5v. battery. Variable input impedance. Matches directly into 25-35 ohms loudspeaker. Special gain control circuit can also reduce noise to a minimum. All parts including transistors, printed circuit board, etc. 32/6. P. & P. 2/6. Easy build plans free with set of parts. 6x4in. 35 ohm speaker 12/6. P. & P. 1/6.

QUICK CHECK TRANSISTOR TESTER. Checks gain of RF and Audio Transistors. Also checks for noise level and dud. All parts ready to be assembled in attractive grey case with red grille complete with Dial, Knobs, and 2½in. Speaker. Simple assembly instructions free with set of parts. 39/6. P. & P. 3/6.

CYLDON PERMEABILITY TUNERS. By famous manufacturer. Full MW coverage. Fitted coupling coil oscillator coil, ferrite slug and slow motion tuning with cursor, etc. **GIVE AWAY PRICE** 10/- P. & P. 1/6. Switched type 2/6 extra.

HEADPHONES. Sonotone HS30 High Fidelity Headphones. Made by famous American manufacturer. Approx. 150 ohms impedance for direct matching into most transistor circuits. **BRAND NEW** in original sealed cartons 15/-, P. & P. 1/6. Matching transformers for higher impedance 2/6 extra.

RADIO EXCHANGE CO.

61, HIGH STREET, BEDFORD

See facing page for other items



Why NOT BUILD ONE OF OUR PORTABLE TRANSISTOR RADIOS...


BACKED BY OUR SUPER AFTER SALES SERVICE

All components used in our receivers may be purchased separately if desired. Parts price lists and easy build plans available separately at prices stated. Overseas post 10/-.

FIRST FOR QUALITY, PERFORMANCE & PRICE!

NEW ROAMER SEVEN Mk IV

7 WAVEBAND PORTABLE OR CAR RADIO
 ★ Now with PHILCO MICRO-ALLOY R.F. TRANSISTORS
 ● 9 stages—7 transistors and 2 diodes
 Covers Medium and Long Waves, Trawler Band and three Short Waves to approx. 15 metres. Push-pull output for room filling volume from rich toned heavy duty "Celestion" speaker. Air spaced ganged tuning condenser. Ferrite rod aerial for M & L waves and telescopic aerial for S Waves. Real leather look case with gilt trim and shoulder and hand straps. Size 9 x 7 x 4in. approx. The perfect portable and the ideal car radio. (Uses PPT batteries available anywhere.)
 ★ EXTRA BAND FOR EASIER TUNING Total cost of parts now only **£5.19.6** P. & P. 5/6
 OF PIRATE STATIONS etc Parts Price List and easy build plans 3/- (FREE with kit)

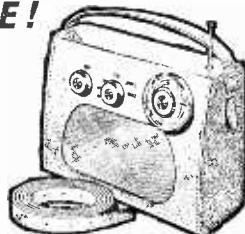


MELODY SIX

"... amazed at volume and performance... has really come up to my expectations."
 S.G. Stockton-on-Tees.

● 8 stages—6 transistors and 2 diodes

Our latest completely portable transistor radio covering medium and long waves. Incorporates pre-tagged circuit board, 3in. heavy duty speaker, top grade transistors, volume control, tuning condenser, wave change slide switch, sensitive 6in. ferrite rod aerial. Push pull output.

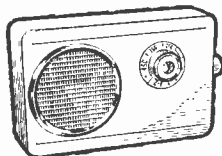Wonderful reception of B.B.C. Home and Light, 200 and many Continental stations. Handsome leather-look pocket size case, only 6 1/2 x 3 1/4 x 1 1/2in. approx. with gilt speaker grille and supplied with hand and shoulder straps.
 Parts Price List and Total cost of all easy build plans 2/- parts now only **£3.9.6** P. & P. 3/6 (FREE with kit)



New TRANSONA FIVE

"Home, Light, A.F.N., Lux. all at good volume."
 G.P. Durham.

● 7 stages—5 transistors and 2 diodes

Fully tunable over Medium and Long Waves and Trawler Band. Incorporates Ferrite rod aerial, tuning condenser, volume control, new type fine tone super dynamic 2 1/2in. speaker etc. Attractive case. Size 6 1/2 x 4 1/4 x 1 1/2in. 1289 battery available anywhere.)
 Parts Price List and easy build plans 2/- (FREE with kit)


with red speaker grille. (Uses 1289 battery available anywhere.)
 Total cost of all parts now only **42/6** P. & P. 3/6

TRANSONA SIX

● 8 stages—6 transistors and 2 diodes

This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade approx. 3in. speaker makes listening a pleasure. Push-pull output. Ferrite rod aerial. Many stations listed in one evening including Luxembourg loud and clear. Attractive case in grey with red grille. Size 6 1/2 x 4 1/4 x 1 1/2in. (Uses PP4 battery available anywhere.) Carrying strap 1/- extra.

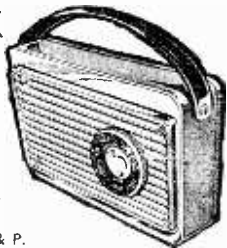Total cost of all parts now only **59/6** P. & P. 3/6
 Parts Price List and easy build plans 1/6 (FREE with kit)




POCKET FIVE

● 7 stages—5 transistors and 2 diode

Covers Medium and Long Waves and Trawler Band, a feature usually found in only the most expensive radios. On test Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round supersensitive Ferrite Rod Aerial and fine tone 2 1/2in. moving coil speaker, built into attractive black case with red speaker grille. Size 5 1/2 x 1 1/4 x 3 1/2in. (Uses 1289 battery available anywhere.)

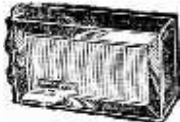Parts Price List and easy build plans 1/6 (FREE with kit)
 Total cost of all parts now only **42/6** P. & P. 3/6.





NEW ROAMER SIX

NOW WITH PHILCO MICRO-ALLOY R.F. TRANSISTORS
 ● 6 WAVEBAND !!

X8 stages—6 transistors and 2 diodes

Listen to stations half a world away with this 6 waveband portable. Tunable on Medium and Long waves, Trawler band and two Short Waves. Sensitive ferrite rod aerial and telescopic aerial for short waves. Top grade transistors. 3-inch speaker, handsome case with gilt fittings. Size 7 1/2 x 3 1/4 x 1 1/2in. Carrying strap 1/6 extra.

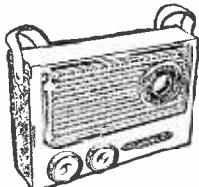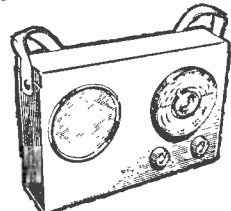★ EXTRA BAND FOR EASIER TUNING OF LUX, ETC.
 Parts Price List and easy build plans 2/- (FREE with kit)
 Total cost of all parts now only **£3.19.6** P. & P. 3/6



SUPER SEVEN

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band. The ideal radio for home, car or can be fitted with carrying strap for outdoor use. Completely portable—has built-in Ferrite rod aerial for wonderful reception. Special circuit incorporating 2 R.F. Stages, push-pull output, 3in. speaker (will drive large speaker). Size 7 1/2 x 3 1/4 x 1 1/2in. (Uses 9v. battery, available anywhere.)

Total cost of all parts now only **£3.19.6** P. & P. 3/6
 Parts Price List and easy build plans 2/- (FREE with kit)

RADIO EXCHANGE CO

61, HIGH STREET, BEDFORD

Telephone: Bedford 52367

Callers side entrance Barratts Shoe Shop open 9-5 p.m. Sats 10-12.30 p.m.
ALSO SEE FACING PAGE FOR OTHER ITEMS

STERN-CLYNE

HIGH FIDELITY EQUIPMENT



(1) Mullard "10 Plus 10" Stereo Amplifier
A High Fidelity design providing up to 10 watts per channel.
KIT OF PARTS £20.0.0.
Built and tested £24.0.0 (C. & I. 7/6).
We can also supply the Main Amplifier for operation with our Dual Channel Pre-amplifier.
KIT OF PARTS £27.0.0.
Built and tested £34.0.0 (C. & I. 10/6).



(2) Mullard Dual Channel Pre-Amplifier
A four-valve design for both Stereophonic and Monophonic operation.
KIT OF PARTS £12.10.0.
Built and tested £15.0.0 (C. & I. 5/-).



(3) The "Twin Three" Stereo Amplifier
Based on a recent design by Mullard Ltd. It is ideally suited for use in Portable Record Players.
Built and tested £9.0.0 (C. & I. 7/6).
To construct a Stereo Portable Record Player, we offer:
Assembled Amplifier with two 8 x 5 in. Loudspeakers and Portable Case for £16.10.0 (C. & I. 10/-).

Fully descriptive leaflets available on any of the above items.

Instruction Books and Detailed Price Lists are supplied Free with Kits of Parts but may be purchased separately if required.

Items 1, 2 and 14, 3/- each;
6 and 13, 3/6 each; 7, 8, 9, 10, 2/- each; 11, 2/6 each;
12, 5/-. All Post Free.




(5) Tudor AM/FM Tuner
Self-powered VHF/FM long and medium waves, FM 87.5-108.5 Mc/s AM MW 525-1,630 Kcs. LW 145-270 Kcs. Multiplex output.
Built and tested 24 Gns. (P. & P. 7/6).



(6) Mullard 3-Valve Pre-Amplifier Tone Control
Designed mainly for the Stern Mullard range of Monophonic Power Amplifiers.
KIT OF PARTS £10.0.0.
Built and tested £13.13.6 (C. & I. 5/-).



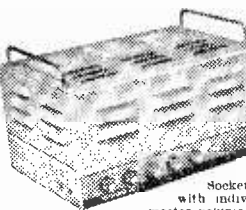(8) Mullard "5-10" Main Amplifier
For use with Mullard 2- or 3-valve pre-amplifiers with which an undistorted power output of up to 10 watts is obtained.
KIT OF PARTS £10.0.0.
Built and tested £13.10.0 (C. & I. 6/6).
Above incorporating Partridge Output Transformer £1.6.0. extra.




Socket with individual volume controls and with the master volume control the inputs may be mixed and balanced as required. Housed in a really robust steel case finished in smooth grey hammer finish with chrome handles and silver grey front panel with contrasting letters and knobs. Built-in Pre-amplifier and Control Unit, 30 watt Undistorted Output, Switched Output for 3 or 15 ohms Loudspeakers. Fully assembled and tested carriage and insurance 10/- Vented cover with chrome handles as illustrated, 35/- extra.



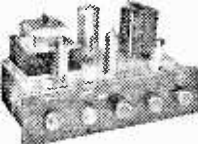(9) Mullard "5-10RC" Amplifier

The popular "5-10" complete incorporating Passive Control Unit providing up to 10 watts high quality reproduction with an input of 600mV
KIT OF PARTS £12.0.0.
Built and tested £16.0.0 (C. & I. 7/6).
With Partridge Output Transformer £1.6.0 extra.



(10) Mullard "3-3RC" Amplifier

A high quality Amplifier developed from the very popular 3-watt Mullard "3-3" design.
KIT OF PARTS £9.8.0.
Built and tested £11.10.0 (C. & I. 8/6).




(11) The "Mono-Gram" Amplifier

A small Amplifier of genuine high quality performance producing up to 3 watts undistorted output.
KIT OF PARTS £4.10.0.
Built and tested £6.0.0 (C. & I. 3/6).



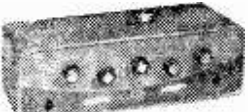(16) JL10 Power Amplifier
Incorporates the latest diode/pentode ECL86 valves in push-pull Partridge ultra linear output transformer. Partridge mains transformer and smoothing choke. 10 watts power output, surplus.
Built and tested £12.12.0 (C. & I. 7/6).



(17) Double Feature Pre-Amplifier

Inputs for microphone, crystal or magnetic pick-ups, tuner unit, and in addition offers full facilities for tape recording and high fidelity replay. This unique feature means that should you wish to include tape in your hi-fi system at a later date all that is required is a suitable tape deck.

Built and tested £18.13.0 (C. & I. 5/-).
Prices if both units purchased together:

Built and tested £30.9.0 (C. & I. 10/-).

VERITONE 30



A small versatile 3-4 watts Gram Amplifier suitable for Crystal Pick-up or Radio Tuner, ideally suited for a small domestic installation. Output imp. 3 ohms, volume control, treble control, bass control and middle control. Valve line-up: 6X4, 6P8, 6Z4.
Chassis size 8 1/2 x 4 x 1 1/2 in. Silver anodised finish. Attractive front panel silver grey finish with contrasting lettering and knobs. Size 8 1/2 x 2 1/2 in.

Fully assembled and tested 6 Gns. (C. & I. 5/-).

VERITONE 30 AMPLIFIER

A general purpose amplifier of outstanding quality, ideally suitable for Dance Bands, Clubs, Hotels, Factories, Indoor and outdoor Public Address requiring a powerful robust portable Amplifier which will provide high quality reproduction, distortion free. The Amplifier has two standard Jack Socket inputs, high gain and low gain with individual volume controls and with the master volume control the inputs may be mixed and balanced as required. Housed in a really robust steel case finished in smooth grey hammer finish with chrome handles and silver grey front panel with contrasting letters and knobs. Built-in Pre-amplifier and Control Unit, 30 watt Undistorted Output, Switched Output for 3 or 15 ohms Loudspeakers. Fully assembled and tested carriage and insurance 10/- Vented cover with chrome handles as illustrated, 35/- extra.

Price 18 Gns.



(7) MULLARD 2-VALVE PRE-AMPLIFIER
Employing two 6P8 valves and designed to operate with the Mullard MAIN AMPLIFIERS but also perfectly suitable for other makes. Now with new design front panel.
KIT OF PARTS £6.6.0.
Built and tested £9.10.0 (C. & I. 5/-).



(12) Stereo Tape Pre-Amplifier Model STP-1
For use with current Truon, Brenell or Collaro "Studio" 1- and 1-track Stereo Decks. Now with new design front panel.
KIT OF PARTS £22.0.0.
Built and tested £26.0.0 (C. & I. 8/6).



(13) Mullard Type "C" Tape Pre-Amplifier
Suitable for most 1-track Mono Tape Decks. Now with new design front panel.
KIT OF PARTS £14.0.0.
Built and tested £18.10.0 (C. & I. 7/6).



(14) Mullard Tape Amplifier Model HF/TR3
Based on Mullard's type "A" design and suitable for most 1-track Mono Tape Decks. Now with new design front panel.
KIT OF PARTS £13.13.0.
Built and tested £19.0.0 (C. & I. 7/6).

Introducing the new veritone saturn transistorised FM Tuner



Veritone bring to you a new design in
F.M. Tuners unique in both circuitry and styling
—designed for the modern-minded enthusiast

THE VERITONE SATURN TRANSISTORISED F.M. TUNER

Specifications:

Transistors:—1 x AF125, 1 x AF121, 4 x AF116 · Diodes:—1 x OA79 · 1 Variable Capacity Diode · Solid State Full Wave Bridge Rectifier, IOAZ212 Zener Diode · 4 I.F. Stages · Switchable A.F.C. · Tuning Meter · Tuning Range 87.5-108.5 Mc/s · Stabilised Power Supply Din Outlet Socket · Fully Variable Audio Output Attenuator · Sensitivity 4 mV for 30 dB signal to noise ratio. · Attractive Black and Silver Grey front panel with mirror strip top and bottom

Facility for Plug in Multiplex Stereo Adaptor (available at a later date)

PRICE 25 gas. (Inc. P.T.) TEAK CASE OPTIONAL EXTRA

Full technical information and details available on request

NOW ON DEMONSTRATION AT ALL BRANCHES

STERN-CLYNE

SEE FOLLOWING PAGE FOR ADDRESSES

STERN-CLYNE

ELECTRONIC CENTRES THROUGHOUT GREAT BRITAIN

TWO SPECIAL TAPE RECORDER BARGAINS



by
FAMOUS
MANUFACTURER



TR2 PORTABLE TAPE RECORDER. A truly first-class portable machine by famous manufacturer incorporating the renowned BSR single speed 2-track Tape Deck, 3 1/2 l.p.s. Tape Counter, Record Level Indicator, Volume and On/Off Tone Control, 3 watts output. Inputs for recording from Microphone and Radio. Tape Monitor socket. Extension Loudspeaker Socket. Attractive two-tone grey/cream rexine covered Portable Cabinet. Supplied complete with Microphone Reel of Tape and Spare Spool. Carriage and Insurance 15/- extra. Credit Terms Originally 23 Gns.
£2.18.0 deposit and 12 monthly payments of £1.9.4, total credit price £20.10.0. **OUR PRICE 18 Gns.**

TR3 PORTABLE TAPE RECORDER. A high quality Portable Tape Recorder for the discerning enthusiast incorporating the latest BSR TD10 8-speed Tape Deck 1 1/2, 3 1/2 and 7 1/2 l.p.s. 2-Track. Record interlock to prevent accidental erasure. Tape Counter. Record Level Indicator. 3-4 watt output. Volume and On/Off Tone Control. Inputs for recording from Microphone and Radio. Tape Monitor Socket. Extension Loudspeaker Socket. Attractive two-tone blue rexine covered Portable Cabinet with silver trimmings. Supplied complete with Microphone, Lead for recording from Radio or Record Player. Full Reel of Tape and Spare Spool. Carriage and insurance 15/- extra. Credit Terms: Originally 23 Gns.
£3.3.0, deposit and 12 monthly payments of £1.12.3. Total credit price £22.10.0 **OUR PRICE 20 Gns.**

FULLY AUTOMATIC TAPE SPLICER
14/6. P. & P. 1/6.

PLASTIC TAPE SPOOLS
3in., 1/8; 4in., 2/-; 5in., 2/-; 5 1/2in., 2/8;
7in., 2/6.

PLASTIC SPOOL CONTAINERS For
spool sizes 3in., 1/8; 5 1/2in., 2/-;
7in., 2/8. Any 4 single items plus 6d.
P. & P. Orders over £1 post free.

We carry fully comprehensive stocks
of Tape Recorders, Discs and Acces-
sories at all Branches or order with
confidence by mail.

AMERICAN RECORDING TAPE

5in.	600ft. Std. Acetate	5/6
5in.	900ft. LP Acetate	10/-
5 1/2in.	1,200ft. LP Acetate	12/6
3 1/2in.	600ft. DP Polyester	11/8
7in.	1,300ft. Std Polyester	12/6
5in.	1,200ft. DP Polyester	17/-
7in.	1,800ft. LP Polyester	20/-
5 1/2in.	1,800ft. LP Polyester	22/6
7in.	2,400ft. DP Polyester	25/-

P. & P. 1/- per reel. 4 or more reels
POST FREE

"the TRAVLER II"

TRANSISTORISED
CAR RADIO



★ MEDIUM AND LONG WAVES. ★ 12 VOLT
POSITIVE EARTH. ★ Push Button Wave Change.
★ SIZE: 7 x 2 x 7in.


9 1/2 Gns.

P. & P. 5/- all units and bolts and fitting instructions.

Options: Extra: Chromium plated weatherproof telescopic aerials. Type 1, 22in/50in., 19/8. Type 2, 12in/45in., 20/6. Type 3, fully retractable and locking in, 50in. Depth below wing, 14in., 39/8. All plus P. & P. 2/6, if purchased separately.

ETCH YOUR OWN PRINTED CIRCUITS

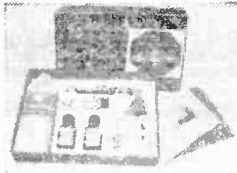A complete kit of parts to
make your own printed circuit
board to your own specifica-
tion, high quality materials
used to ensure perfect results.
Price complete with all neces-
sary chemicals and copper
clad laminated board, 19/6.
2/3 packing and postage.



LONDON

18 Tottenham Court Road, W.1. MUSEUM 5929/0095. Half Day Saturday.
23 Tottenham Court Road, W.1. MUSEUM 3451/2. Half Day Thursday.
309 Edware Road, W.2. PADDINGTON 9948. Half Day Thursday.
189 Fleet Street, E.C.4. FLEET STREET 5812/3. Half Day Saturday.
162 Holloway Road, N.7. NORTH 7941. Half Day Thursday.
9 Camberwell Church Street, S.E.5. RODNEY 2875. Half Day Thursday.
NOW ALSO OPEN AT:
220 Edware Road, W.2. PADDINGTON 5607 (New-Max).

CROYDON

12 Suffolk House, George Street, MUSEUM 3250. Half Day Wednesday.

BRISTOL

56 Merchant Street, Bristol 1. Bristol 20261. Open 6 days a week.

**ANOTHER
NEW CENTRE**

Now open
at
**EASTOWN
HOUSE
LINCOLN ST.
NOTTINGHAM**
Tel. 45889

LIVERPOOL

52 Lord Street, ROYAL 7450. Open 6 days a week.

MANCHESTER

20/22 Withy Grove, Manchester 4, BLAKIERS 5479/5246
Open 6 days a week

SHEFFIELD

125 The Moor, Sheffield, SHEFFIELD 29948. Half Day Thursday

MAIL ORDERS AND ENQUIRIES TO:

Dept. P.W. 3/5 Eden Grove, Holloway, London, N.7.
NQ8th 8161/5.



MAIL ORDERS TO: 54 WELLINGTON STREET, LEEDS 1

Terms: C.W.O. or C.O.D. No C.O.D. under £1. Postage 2/9 extra under £2. 4/6 extra under £5. Trade Supplied, S.A.E. with all enquiries please.

PERSONAL SHOPPERS WELCOME AT ANY OF THE BRANCHES BELOW. OPEN ALL DAY SATURDAY.

BRADFORD 10 North Parade Tel: 25349 (Half-day Wed.)

BRISTOL 14 Lower Castle Street (Half-day Wednesday) Tel: 22904.

BIRMINGHAM 30/31 Gt. Western Arcade, opp. Snow Hill Station. CENTRAL 1279. No half-day.

DERBY 26 Osmoston Rd., The Spot (Half-day Wed.) Tel: 41361

DARLINGTON 13 Post House Wynd (Half-day Wednesday) Tel: 68043

EDINBURGH 133 Leith Street, (Half-day Wed.)

GLASGOW 326 Argyle Street, Tel: City 4158 (No half-day).

HULL 51 Savile Street (Half-day Thursday) Tel: 20505

LEICESTER 32 High Street (Half-day Thurs.) Tel: 56420

LEEDS 5-7 County (Mecca) Arcade (No half-day) Tel: 28252

LIVERPOOL 73 Dale St. (No half-day) Tel: CENTral 3573

LONDON 238 Edgware Road W2 (Half-day Thursday) Tel: PADdington 1629

MANCHESTER 60A-60B Oldham St. Tel: CENTral 2778 (No half-day) New large store.

MIDDLESBROUGH (Half-day Wednesday) 106 Newport Road. Tel: 47096

SHEFFIELD 13 Exchange Street Castle Market Bldgs. Tel: 20716 (Half-day Thursday)

VACANCIES FOR STAFF AT VARIOUS BRANCHES SHOP EXPERIENCE UNNECESSARY Write to 54 Wellington St. Leeds 1

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Table listing various transformer models and specifications including primary/secondary voltages, current ratings, and prices.

TWEETERS R.A. 3 ohm 25/9 15 ohm 25/9

FANE HEAVY DUTY HI FI SPEAKERS 12" 20 watt. Type 123/10. Only 5 Gns.

R.S.C. POWER PACK, 39/9. Louvred metal case only 8 x 5 1/2 x 2 1/2 in. Stove enamelled. For 200-250 v.a.c. mains. Output at 4 pin plug and socket 250 v. 60 mA, fully smoothed at 6.3 v. 2a. Suitable for power requirements of almost any Pre-amp. or Radio Tuner.

ARMSTRONG, TRUYOX, LEAK, QUAD, ROGERS, LINEAR, W.B., FANE, WHARFEDALE, GOODMAN, GARRARD, GOLDRING, GRAMPAIN, LUSTRAPHONE, SHURE, RESLO, TANDBERG, FERROGRAPH Products stocked. Usual credit terms available.

AUDIO FIDELITY 10in. 15 WATT HI-FI LOUDSPEAKERS Heavy cast construction. Dual cone, smooth frequency response 40-15,000 c.p.s. Really outstanding performance at exceptional value at 5 GNS.

R.S.C. GRAM AMPLIFIER KIT, 3 watts output. Negative feedback. Control: Tone, Tone and switch. Mains operation 200-250v. A.C. Fully isolated chassis. Circuit, etc., supplied. Only 39/9. Carr. 3/9.

SCOOP PURCHASE OF HIGH QUALITY RECORD CHANGERS 11 GNS. Brand new Garrard 3000 LM. Very latest model. Normal Retail price approx. £22.50. Heavy Turntable and light-weight pick-up arm. High fidelity Stereo/Mono cartridge. Fully guaranteed.

R.S.C. 4 1/2 WATT AS HIGH GAIN AMPLIFIER

A highly sensitive 4-valve quality amplifier for the home small club etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest High-Fidelity Pick-up heads in addition to all other types of pick-ups and practically all 'mikes'. Separate Bass and Treble controls are provided. These give full tone playing record equalisation. Hum level is negligible being 71 dB down 15 dB of Negative Feedback is used. H.T. of 300v. 2mA and L.T. of 6.3v. 1.5a. is available for the supply of a Radio Feeder Unit or Tape-Deck pre-amplifier, or A.C. mains 200-250v. 50 c/s. Output for 2 ohms speaker chassis is complete in every detail with fully punched Gold Hammer finished chassis. Kit-to-point wiring diagrams and instructions. Exceptional value £4-15-0 or assembled ready for use 25/- extra, plus 3/6 carr., deposit 22/6 and 5 monthly payments of 22/6 (total £6.15.0) for assembled unit.



R.S.C. SUPER 15 HI-FI AMPLIFIER R.S.C. SUPER 30 STEREO AMPLIFIER

FULLY TRANSISTORISED 200-250v. A.C. Mains Operation. OUTPUT 10 WATTS R.M.S. into 15 ohms. OUTPUT 15 WATTS R.M.S. into 8-ohms. Maximum Instantaneous Peak Power Output 28 watts. PRINTED CIRCUIT CONSTRUCTION. L.A. BEST MULLARD TRANSISTORS AD149, AD149, OC127Z, OC81Z, OC44, OC44, OC81Z, OC44, AC107. 5 POSITION INPUT SELECTOR SWITCH. EQUALISATION to Standard R.I.A.A. and C.I.L.I. Characteristics for Gram and Tape Heads. FULL TAPE MONITORING FACILITIES. SENSITIVITIES: Magnetic P.U. 4 mV. Crystal or Ceramic P.U. 400 mV. Microphone 4.5 mV. Tape Head 2.5 mV. Radio/Aux or Ceramic P.U. 110 mV. FREQUENCY RESPONSE: 30-20,000 c.p.s. TREBLE CONTROL: +15dB to -14dB at 10 Kc/s. BASS CONTROL: +12dB to -15dB at 30 c/s. HARMONIC DISTORTION at 10 Watts R.M.S. 1,000 c.p.s. 0.29%. HUM LEVEL: 75dB. NEGATIVE FEEDBACK: 32dB. Complete kit of parts with full constructional details and point to point wiring diagrams. 91 Gns. Carr. 10/- If preferred printed circuit can be supplied with parts soldered in and tested for 21/- extra. Or unit factory built and tested, with our usual 12 months guarantee. Or Deposit £2 and nine monthly payments 27/9. Total £14.9. ALL COMPONENTS ETC. ARE OF A HIGH STANDARD AND SUPPLIED BY LEADING BRITISH MANUFACTURERS. Send S.A.E. for leaflet.

WE PROUDLY INTRODUCE TWO COMPLETELY NEW UNITS WITH TECHNICAL SPECIFICATIONS COMPARING MORE THAN FAVOURABLY WITH SIMILAR AMPLIFIERS OFFERED AT 2-3 TIMES THE COST.



IMPORTANT NOTE. Rated output figures are given in R.M.S. and not speech and music of 1:1:1. In other words we could obviously quote much higher outputs.

A DUAL CHANNEL VERSION OF THE SUPER 15. Employing Twin Printed Circuits. Close tolerance Ganged Pots. Matched Components. CROSSTALK: -50dB at 1,000 c.p.s. CONTROL: position Input Selector, Bass Control, Treble Control, Volume Control, Balance Control, Stereo/Mono Switch, Tape Monitor Switch, Mains Switch. INPUT SOCKETS (Matched Pairs): (1) Magnetic P.U. (2) Ceramic or Crystal P.U. (3) Radio/Aux. (4) Tape Head/Microphone. Operation of the Input Selector Switch assures appropriate equalisation. Rigid B.S.W.P. Chassis. Size approx. 12" wide x 7" high, and 9" deep. Attractive Face-plate and Matching Knobs. Neon Panel Indicator. Above facilities, etc., except for Ganging and Balance Control, apply also to Super 15. HI-FI UNITS ARE EMINENTLY SUITABLE FOR USE WITH ANY MAKE OF PICK-UP OR MICROPHONE. (Crystal, Ceramic, Magnetic, Moving Coil, Ribbon) COMPLETELY AVAILABLE. REGARDLESS OF THE COST SUPER SOUND OPTIMUM QUALITY CAN BE OBTAINED BY USING WITH FIRST RATE ANCILLARY EQUIPMENT. All required parts, point to point wiring diagrams and detailed instructions. 18 GNS. If required printed circuits can be supplied with appropriate components assembled, soldered and tested for 2 gns. extra. Terms: Deposit 6 gns. & 9 monthly payments 36/8 (total £22.14.6). Or unit completely assembled ready for use. Or Deposit £4.4.3 and 9 monthly payments 49/9. 23 GNS. Carr. 15/- Total £26.12.0.

R.S.C. STEREO 20/HIGH FIDELITY AMPLIFIER

PROVIDING 10/14 WATT ULTRA LINEAR PUSH-PULL OUTPUT ON EACH CHANNEL

SUITABLE FOR "MIKE", GRAM, RADIO OR TAP. INTENDED FOR THE HOME OR STUDIO BUT SUITABLE FOR LARGE HALLS OR CLUBS

- ★ Four-position tone compensation and Input Selector switch.
- ★ With amplify direct from Tape Heads.
- ★ Stereo/Mono switch so that peak monaural output of 28 watts can be obtained.
- ★ Separate Bass "Lift" and "Cut" and treble "Lift" and "Cut" controls.
- ★ Neon panel indicator.
- ★ Handsome Perspex Frontplate.

Based on a current Mullard design and employing valves: ECC83, ECC85, ECL86, ECL86, ECL86, ECL86, E281. Send S.A.E. for leaflet.

Output transformers are high-quality sectionally wound to required specification. Output matchings for 5 and 15 ohm speakers on each channel. **13 Gns.** Complete set of parts with point-to-point wiring diagrams and instructions, or Facto y assembled, tested and supplied with our usual 12 months guarantee for or DEPOSIT 57/- and 9 monthly payment of 39/10 (total £20.15.6). A protective wooden cabinet covered in a pleasing shade of leathercloth and fitted carrying handles and feet can be supplied for 59/6 extra. Carr. 5/6. Terms: DEPOSIT 6/9 and nine monthly payments 6/9 (Total 67/6).




FREQUENCY RESPONSE ± 24 B. 30-20,000 c.p.s.
HUM LEVEL 65dB down.
SENSITIVITY: 5 millivolts maximum.
HARMONIC DISTORTION (each channel) 0.2%.

AUDIOTRINE HI-FI TAPE RECORDER KIT 25 1 Carr. 17/6, 2 Gns.

REALISM AT INCREDIBLE LOW COST. CAN BE ASSEMBLED IN AN HOUR

Incorporating the latest Collaro Studio Tape Transcriber. The Audiotrine High Quality Tape Amplifier with negative feedback equalisation for each of 3 speeds. High Flux 12" Speaker, empty Tape Spool, a Reel of Best Quality Tape and a Handsome Portable Carrying Cabinet. Total cost if purchased individually approximately £40. Performance equal to units in the £60-£80 class. S.A.E. for leaflets. **TERMS:** Deposit 4 gns. and 12 monthly payments of 42/- (Total 28 Gns.)

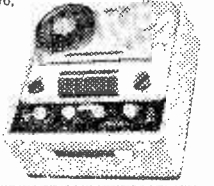

R.S.C. A10 30 WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER

A highly sensitive Push-Pull high output unit with self-contained Pre-amplifier, Tone Control Stage, certified performance figures or performance with most expensive amplifiers available. Hum level 70 dB down. Frequency response ± 3 dB 30-20,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 407 output valves. All components are chosen for reliability. Six valves are used: EPC8, EPC8, ECL86, 807, 807, 6Z4. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR FUNCTIONS, etc. For use with Electronic ORGAN, BASS, LEAD OR RHYTHM GUITAR, STRING BASS, etc. For standard or long-playing records. **OUTPUT SOCKET PROVIDES L.T. and H.T. for 14 Gns.**

RADIO FEEDER UNIT. An extra input with associated vol. control is provided so that two separate inputs such as Gram and "Mike" can be mixed. 200-250v. 50 c.p.s. Main output for 3 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and Carr. 10/- instructions. Supplied factory built with EL4 output valves and 12 months' guarantee. **11 Gns.** If required perforated cover with carrying handles can be supplied for 19/9. Send S.A.E. for leaflet, also speaker. **TERMS:** DEPOSIT 45/- and 9 monthly payments of 32/4 (Total 16 Gns.)

INTEREST CHARGES REFUNDED

on H.P. and CREDIT SALE Accounts settled in 6 months.


LINEAR TAPE PRE-AMPLIFIER. Type LP/1. Switched Equalisation. Positions for Recording at 12in., 3 1/2in., 7in. per sec. and Playback. EM84 Recording Level Indicator. Designed primarily as the link between a Collaro Tape Deck 9 1/2 Gns. and Hi-Fi amplifier, suitable almost any Tape Deck. S.A.E. for leaflet. **9 1/2 Gns.**

HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11


PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP STAGES

Two input sockets with associated controls allow mixing of "mike" and gram, as in A10. High sensitivity. Includes 5 valves, ECC83, ECC83, EL84, EL84, E281. High Quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. **INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut".** Frequency response ± 3 dB 30-20,000 c/s. Six negative feedback loops. Hum level 60 dB down. **ONLY 23 millivolts input required for FULL OUTPUT.** Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs for **STANDARD or LONG PLAYING RECORDS.** For **MUSICAL INSTRUMENTS** such as **STRING BASS, LEAD or RHYTHM GUITARS, etc.** **OUTPUT SOCKET** with plug provides 300v. 30mA. and 6.3v. 1.5a for supply of a **RADIO FEEDER UNIT.** Size approx. 12 x 9 x 1 1/2in. For A.C. mains 200-250v. 50 c.p.s. Output for 3 and 15 ohms speaker. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. **Only 8 Gns.** (Or factory built 51/6 extra). **10/-**

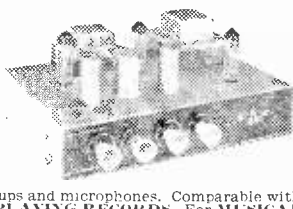If required louvered metal covers with 2 carrying handles can be supplied for 15/9. **TERMS ON ASSEMBLED UNIT: DEPOSIT 33/3 and 9 monthly payments of 21/1 (Total £12.10.0).** Send S.A.E. for illustrated leaflet detailing Cabinets, Speakers, Mikes, etc.



R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER

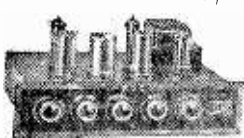

A complete set of parts for the construction of a stereophonic amplifier giving 5 watts high quality output on each channel (total 10 watts). Sensitivity is 50 millivolts. Suitable for all crystal stereo heads. Gained Bass and Treble Control give equal variation for "Lift" and "Cut". Provision is made for use as straight (monaural) 10 watt amplifier. Valve line-up ECC83, ECC83, EL84, EL84, E281. Outputs for 2-3 ohm speakers. Point-to-point wiring diagrams and instructions supplied. Send S.A.E. for leaflet. Full constructional details and price list 2/6. **8 Gns.** Carr. 10/-

Or supplied factory assembled with 12 months' guarantee for £11.7.6. **TERMS:** Deposit 2 gns. and 9 monthly payments of 24/2 (Total £12.19.6).

GL3A MINIATURE 2-3 WATT GRAM AMPLIFIER. For use with any single or auto-change unit. Output for 2/3 ohm speaker. For 200-250v. A.C. mains. Size 1 1/2 x 2 1/2 x 2 1/2in. Volume and Tone Controls with Switch. **59/6**

Always in Stock at record prices **SINGLE and AUTO RECORD PLAYING UNITS, PICK-UPS, CARTRIDGES, MICROPHONES, CABINETS VALVES and COMPONENTS TOO NUMEROUS TO LIST**

ONLY 3 PAIRS OF SOLDERED JOINTS PLAIN MAINS

12in. 10 WATT HIGH QUALITY LOUDSPEAKER

In walnut veneered cabinet. Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only **£4.19.6** Carr. 5/6

TERMS: Deposit 11/3 and 9 monthly payments of 11/3 (Total £5.12.6). **12in. 20 WATT HI-FI LOUDSPEAKERS IN CABINETS.** Size 18 x 18 x 10in. Finish as above. **£7.19.6** **TERMS:** Deposit 17/9 and 9 monthly payments of 17/9 (Total £17.6). Carr. 8/6.

W.B. "STENTORIAN" HIGH FIDELITY P.M. SPEAKERS EP1012, 10 watts rating. Where a really good quality speaker at a low price is required we highly recommend this unit with an amazing performance. Please state whether 3 or 15 ohms required. **£4.19.9**

R.S.C. JUNIOR BASS REFLEX CABINET. Designed for above speaker, but suitable for any good quality 5in. or 10in. speaker. Acoustically lined and ported. Polished Walnut veneer finish. Size 18 x 13 x 10in. Strongly made. Handsome appearance. Superb reproduction. Carr. 5/6. **£4.7.6**


R.S.C. STANDARD BASS REFLEX CABINET. For 12in. loud-speaker acoustically lined and ported. Size 20 x 14 x 13in. Beautiful wood veneer finish. Recommended for use with Audiotrine Speaker **£5.19.6**

AUDIOTRINE CORNER CONSOLE CABINETS Strongly made. Beautiful polished walnut veneered finish. Pleasing design. **JUNIOR MODEL** For up to 5in. speaker. Approx. 20 x 11 x 11 in. **49/9**

STANDARD MODEL. To take up to 10in. speaker. Size 27 x 18 x 15in. **5 Gns.** Carr. 7/6.

SENIOR MODEL. To take up to 12in. speaker and with Tweeter cut-out. Size approx. 30 x 20 x 15in. (Recommended for use with Audiotrine speaker system). Carr. 8/6. **8 Gns.** Terms available.

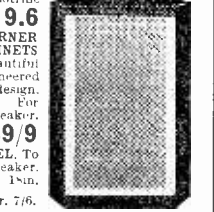AUDIOTRINE HI-FI SPEAKER SYSTEMS Consisting of matched 12in. 12,000 line, 15 ohm high quality speaker; cross-over unit (consisting of choke, condenser, etc.) and Tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. Standard 10 watt rating. **£4.19.9** Carr. 5/6. Or Senior 20 watt, £6.19.6. Carr. 7/6.




R.S.C. BASS-REGENT 50 WATT AMPLIFIER

AN EXCEPTIONALLY POWERFUL HIGH QUALITY ALL-PURPOSE UNIT

For lead, rhythm, bass guitar and all other musical instruments

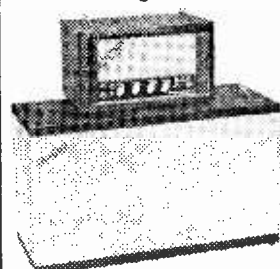For vocalists, gram, radio, tape and general public address



★ UNUSUALLY POWERFUL LOUDSPEAKER COMBINATION consisting of a FANE HIGH FLUX 15in. 30 watt unit PLUS FANE 12in. 20 watt unit with extended frequency response. 4 Jack Socket inputs and two independent Volume Controls for simultaneous use of up to 4 pick-ups or 'mikes'.

★ Separate cabinets fully covered in contrasting tones of Rexine/Vnair with gold trimming for speakers and amplifiers.

★ Separate Bass and Treble Controls giving 'Boost' and 'Cut'.

Send S.A.E. for leaflet. Or call at one of our many branches and compare the Bass-Regent with units at more than three times the cost.

49 Gns. Or deposit £7.16.0 and 12 monthly payments of 51/6 Carr. 25/- Total 54 Gns.

TRANSISTORISED SOUND MIXER

Enables mixing of up to 4 standard jack inputs, i.e. mic, tape, gram, tuner, etc., into single output. Compact and completely self-contained, uses standard 9 volt battery **49/9**

Full Range of FANE and GOOD-MANS Speakers in Stock and all types 'Mikes'. Credit terms if required.

R.S.C. B20 MULTI-PURPOSE AMP.

especially suitable for Bass Guitar

A highly efficient unit incorporating massive 15in. high flux loudspeaker specially constructed to withstand heaviest load conditions. Rating 25 watts. Individual bass and treble controls give ample 'Boost' and 'Cut'. Two jack socket inputs separately controlled. Cabinet is of substantial construction and attractively finished in two contrasting tones of Rexine and Vnair. Size approx. 24 x 21 x 18ins. Send S.A.E. **29 1/2 Gns.** Carr. 17/6 for leaflet. Or deposit £4.14.6 and 12 monthly payments of 49/- (Total 32 1/2 gns.).



R.S.C. G15 15 WATT AMPLIFIER for Lead or Rhythm Guitar, Mike, Gram or Radio

High-fidelity push-pull output. Separate bass and treble 'Cut' and 'Boost' controls. Twin separately controlled inputs so that two instruments or "mike" and pick-ups can be used at the same time. Loudspeaker is a heavy duty flux 12in. 20 watt model with cast chassis. Cabinet is covered in contrasting shades of Rexine/Vnair. Size approx. 18 x 18 x 8in. **19 1/2 Gns.** Carr. 12/6. Only 2 monthly payments of 39/6 and 12 monthly payments of 39/6 (Total £22.13.0). S.A.E. for leaflet

R.S.C. G5 AMPLIFIER

4 watt high quality output. Incorporating high flux 12in. 10 watt loudspeaker. Sensitivity 40 mv. High impedance jack input. Handsome cabinet (size 14 x 14 7/16 in. approx.) finished in Rexine/Vnair 200-250v. A.C. mains. Suitable for Lead or Rhythm Guitar in home or small club etc. **£9.19.6** Or Deposit 30/9 and 5 monthly payments of 22/3 (Total 11 Gns.). Carr. 7/6.

R.S.C. BATTERY CHARGING EQUIPMENT

Guaranteed 12 months



All for A.C. Mains 200-250 v., 50c/s
ASSEMBLED 6/12 v. 2 amps. Fitted Ammeter and selector plug for 6 v. or 12 v. Louvred metal cast finished attractive hammer blue. Fused, ready for use with mains and output leads **39.9** Carr. 3/6
 6/12v. 1 amp 27/9 Less meter

BATTERY CHARGER KITS

Consisting of Mains Transformer, F.W. Bridge, Metal Rectifier, well ventilated metal case. Fuses. Fuse holders Grommets, panels. Heavy Duty Clips, circuit. Carr. 3/6
 6v or 12v. 1 amp 22/9
 6v or 12v. 2 amps 25/9
 6v. or 12v. 2 amps, including of ammeter 35/9
 6v. or 12v. 4 amps with Ammeter and variable charge rate selector 52/9

CHARGER AMMETERS

0-1.5a. 0-4a., 0-7a., 8/9 each.

R.S.C. 4 WATT GRAM AMPLIFIER KIT.

Complete set of parts to build a high quality compact unit suitable for use with any record playing unit. Mains isolated chassis separate Bass and Treble controls. Output for 2-3 ohm speaker. For 200-250v. A.C. **59/9**

R.S.C. BABY ALARM or INTER-COMM KIT.

Complete set of parts with diagrams etc. Housed in two polished w/ut finished cabinets of pleasing design. High sensitivity. For 200-250v. A.C. mains. Fully isolated. Controllable at both units. An intercomm. of this class would normally cost £20-£30. Only 8/9d. carr. 5/- Ready for use. **8 Gns.**

R.S.C. BATTERY TO MAINS CONVERTER.

Type B311. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 1/2 in. approx. Completely replaces batteries supply 1.4v and 80v where A.C. mains 200-250v. 50 c/s is available. Suitable for all battery portable receivers requiring 1.4v and 80v. Complete kit with diagram 39/9 or ready for use 48/9

EX GOVT. SELENIUM RECTIFIERS 12v 15 AMP (BRIDGE) F.W. ONLY

19/9

FANNOY RE-ENTRANT LOUD-SPEAKERS.

For outdoor or Factory use. 8 ohms, 8 watts Plus 4/6 carriage **27/6**

HI-FI 12 WATT AMPLIFIERS

BRAND NEW **£7.19.9**

EX-GUITAR AMPLIFIERS

Manufacturers' discontinued Model. Push-pull output. Latest high efficiency valves. Dual separately controlled inputs for 'Mike' and gram. Separate Bass and Treble Controls. High Sensitivity. Output for 3 or 15 ohms speaker. Guaranteed tested and in perfect working order

JASON FMT1 V.H.F./F.M. Radio Tuner

design. Total cost of parts including valves, tuning dial escutcheon, etc. **£6.19.6**

SUPERHET FEEDER UNIT.

Design of a high quality Radio Tuner (specially suitable for use with our Amplifiers). Delayed A.V.C. Controls are Tuning, Wch. and Vol. Only 250v. 13mA H.T. and 1.7 of 6.3v. 1 amp required from amplifier. Size approx. 9 x 6 x 7in. high. Simple alignment procedure. Point-to-point wiring diagrams, instructions and priced parts lists with illustrations 2/8. Total building costs £5.5.0. S.A.E. for leaflet.

TRANSISTOR SALE

Mullard OC71 3/11 OC45 3/11 OC4 3/11 OC72 2/11 OC81 2/11 OC71 8/6. AP117 6/8. Ediswan XA101 3/8. XA112 3/8. XC101A 3/8. Postage 6d. for up to 3 transistors.

INTEREST CHARGES

REFUNDED ON H.P.

ACCOUNTS SETTLED IN

6 MONTHS



Addresses Page 749

R.S.C. COLUMN SPEAKERS

Covered in two-tone Rexine/Vnair. Ideal for vocalists and Public Address. Normally supplied for 15 ohm matching but can be supplied for 100v. line or 35/- extra.
 Type C88. 15-20 watts. Fitted five high flux speakers. Overall size approx. 42 x 10 x 5in. **12 1/2 Gns.** Carr. Or deposit 10/- and 9 monthly payments of 27/9 (Total £14.9.9)
 Type C42. 40 watts. Fitted four 12in. 12,000 line 10 watt speakers. Overall size 56 x 14 x 9in. approx. **19 1/2 Gns.** Carr. 15/- Or deposit of 3 gns. and 9 monthly payments of 43/2 (Total 23 1/2 gns.).

30 WATT HI-FI AMPLIFIER

FOR LEAD, RHYTHM BASS GUITAR and for VOCAL or INSTRUMENTAL GROUPS



A Four Input, two volume control Hi-Fi unit with separate Bass and Treble 'Cut' and 'Boost' controls. Designed for vocal or instrumental groups. For Bass, Lead or Rhythm Guitar. Mullard or Brimar latest type valves. Housed in strong Rexine covered cabinet with twin carrying handles. Attractive black and gold Perspex fascia plate. For 200-250 v. A.C. mains. Output for 3 or 15 ohm speakers. Carr. Send S.A.E. for leaflet.

17 Gns. or Deposit £3 and 9 monthly payments of 37/- (Total £19.13.)

HEAVY DUTY CHARGER KIT

6/12 v. 6 amps., variable output
 Consisting of Main Transformer 0-200-230-250 v. F.W. (Bridge) Selenium Rectifier; Ammeter, Variable Charge Rate Selector Panels, Plugs, Fuses, **59/9** Fuseholder and circuit. Carr. 5/6

SELENIUM RECTIFIERS F.W. (BRIDGE)

6/12v. 1a. 3/11 6/12v. 3a. 9/9 6/12v. 6a. 15/3; 6/12v. 2a. 6/11; 6/12v. 4a. 12/3; 6/12v. 10a. 26/9; 6/12v. 15a. 35/9.

COMPLETE POWER PACK KIT

Consisting of Mains Trans., Metal Rectifier, Double electrolytic smoothing choke, chassis and circuit. Output **19/11** 250 v. 60 mA, 6.3 v. 3a

COMMUNICATION RECEIVERS

RX. 69 DE LUXE

220/240v. 50/60 c.p.s. A.C. mains operation. Frequencies covered 1500 Kc/s to 30 Mc/s continuous. Incorporates 5in. speaker. Slide rule tuning dial 'S' meter. Internal ferrite aerial for medium wave. Telescopic whip aerial 58in. 10 section for short waves. Fitted sockets for optional outdoor aerial. Headphones, external speaker socket. Other features are electrical bandspread tuning. Noise Limiter, A.V.C., B.F.O., stand by switch. Size approx. 12 1/2 x 5 1/2 x 5 1/2 in. Handsome crackle finished metal cabinet. Brand new with full instructions manual **19 Gns.** Usual guarantee. Carr. 10/-

12in. 25 WATT HEAVY DUTY LOUDSPEAKERS

Famous make. Normal price approx. £12. **£7.19.9** Limited number. Fully guaranteed. Carr. 10/-

LINEAR TREMOLO PRE-AMP UNIT

Suitable for use with any of our Amplifiers. Controls are Speed (frequency of interruptions). Depth (or heavy or light effect). Volume and Switch. **4 Gns.**

12" R.A. DUAL CONE SPEAKERS

8 watt 3 ohm each **39/9**

LEARN ELECTRONICS

—AS YOU BUILD

over **40** **CIRCUITS**
EXPERIMENTS
TEST GEAR



including . . .

● CATHODE RAY OSCILLOSCOPE

- | | |
|--------------------------------|--------------------------|
| ● Valve Experiments | ● Square Wave Generator |
| ● Transistor Experiments | ● Morse Code Oscillator |
| ● Electro-magnetic Experiments | ● Simple Transmitter |
| ● Basic Amplifier | ● Electronic Switch |
| ● Basic Oscillator | ● Photo-electric Circuit |
| ● Basic Rectifier | ● Basic Computer Circuit |
| ● Signal Tracer | ● Basic Radio Receiver |
| ● Simple Counter | ● A.C. Experiments |
| ● Time Delay Circuits | ● D.C. Experiments |

The full equipment supplied comprises; valves, transistor, photo-tube, modern type chassis board; printed circuit board; full range resistors, capacitors and inductors; transformers; potentiometers; switches; transistors; valves; all hardware, wiring and every detail required for all practical work plus CATHODE RAY OSCILLOSCOPE for demonstrating results of all experiments carried out. All practical work fully described in comprehensive PRACTICAL MANUALS. Tutor service and advice if needed.

This complete practical course will teach you all the basic principles of electronics by carrying out experiments and building operational apparatus. You will learn how to recognise and handle all types of modern components; their symbols and how to read a completed circuit or schematic diagram. The course then shows how all the basic electronic circuits are constructed and used, and HOW THEY ACTUALLY WORK BY USING THE OSCILLOSCOPE PROVIDED. An application is given in all the main fields of electronics, i.e. Radio; control circuits; computers and automation; photoelectrics; counters, etc., and rules and procedure for fault finding and servicing of all types of electronic equipment.

- | | | |
|--------------------------------|---------------------------|--|
| ● NO PREVIOUS KNOWLEDGE NEEDED | ● NO MATHS USED OR NEEDED | ● REASONABLE FEE—NO EXTRAS REQUIRED |
| ● SENT IN ATTRACTIVE BOX | ● COMPLETE ADVICE SERVICE | ● EVERYTHING REMAINS YOUR OWN PROPERTY |

A completely **NEW** up-to-date home study experimental course by
BRITISH NATIONAL RADIO SCHOOL —
Britain's Leading Electronic Training Organisation.

POST NOW FOR FREE BROCHURE

To **BRITISH NATIONAL RADIO SCHOOL, READING, BERKSHIRE.** Please send free Brochure, without obligation, to:

NAME

ADDRESS

Block Capitals Please

OR WRITE IF YOU PREFER NOT TO CUT COUPON

PW 1.66

PRACTICAL WIRELESS

JANUARY 1966
VOL 41 NO 707

BEGINNING AND END

AN interesting fellow was Janus. A principal divinity in Roman mythology, he was primarily the god of All Doorways and, being blessed with two faces, could observe both the interior and exterior of a house. This handy physiognomical duality also enabled him to obtain the jobs of god of Beginnings and god of Departure. He also played an important role in the creation of the world. The first month of the year—Januarius—bore his name. In fact, a very versatile and busy lad.

Even so, he also held the position of god of All Means of Communication and it is a sobering thought that if we were still in the days of the Roman Empire he would not only be Minister of Transport and Postmaster General, but President of the RSGB and Governor-General of the BBC.

We shall never know what he would have thought about the RAE, the virtues of SSB or the prospects of 14 Mc/s DX, but we can be sure he would have quickly dealt with pirate radio stations, licence dodgers, Party Political Broadcasts and other ills of our time. He might even have got together with his buddy Jupiter (President of the Board of Trade) and banned the import of 27 Mc/s walkie-talkies!

Reluctantly returning to earth let us, like the double faced Janus, simultaneously look backwards and forwards by thanking you all for your interest during the past year and wishing you

A Happy Christmas and Successful New Year
from the Editor and Staff.

CONTENTS

	page
News and Comment	754, 784
Push-Pull ELL80 Amplifier	756
Understanding F.M.	760
On the Short Waves	763
Aerial Tuners	767
A Transistorised L.C.R. Bridge—Part 2	774
High Wattage Loads	778
Push Button Multimeter	780
Tape Terminology—Part 6	786
Electronic Pitch-Pipes	794
Practically Wireless	798
An Economy Two-Band Receiver	801
Club Spot—Basildon & Dist. A.R.S.	809

Short Wave Data in the Pull-Out Supplement

All correspondence intended for the Editor should be addressed to: The Editor, "Practical Wireless", George Newnes Ltd., Tower House, Southampton Street, London, W.C.2. Phone: TEMple Bar 4363. Telegrams: Newnes Rand London. Subscription rates, including postage: 29s. per year to any part of the world. © George Newnes Ltd., 1965. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproduction or imitations of any of these are therefore expressly forbidden. The FEBRUARY ISSUE WILL BE PUBLISHED ON JANUARY 6th

M.W.—D.X.

I FEEL I must compliment you on an excellent article called "M.W.—D.X." in the November issue of PRACTICAL WIRELESS. This is just the kind of text to encourage DX'ers against the streams of, "What's the point? . . . Why bother? . . . So what? . . ." people who just can't understand why we should stay up to 0400 for a few μ V's from New York.

A. Peake.

Great Yarmouth,
Norfolk.

Batteries Offer

ABOUT this time last year, you printed in PRACTICAL WIRELESS my offer of free h.t. batteries. You may be interested to know that the response was very good. I despatched 109 to 71 applicants and still get the odd letters from people who have been reading back numbers. I had to turn down a further 20 requests as I had exhausted my supplies. However, the main purpose of this letter is to make an offer of 6V dry batteries. The size is approximately 5in. x 4½in. x 2¼in. and the weight 3¼lbs. Each battery contains eight cells wired in series/parallel to give 6v, and they can easily be rewired for 3 or 1.5V operation. Connection is by PVC covered wires. I can most easily send these in batches of four at 6s. post. (5s. 6d. plus 6d. packing). Please send Postal Orders and do not cross.

These batteries are ex-U.S. Forces, thrown away due to the elapse of the makers' life expectancy. However, they are really as good as new. One person who tried one of these told me that it ran his transistor set for 14 months.

H. Humphries.

Old Rectory,
Gazeley, Newmarket,
Suffolk.

Mr. Methven Please


I WONDER if Mr. Methven (June 1965 issue, page 148) would get in touch with me, please, as I would like to communicate with him.

H. Seaton.

The Presbytery,
Foundry Hill,
Hayle,
Cornwall.

NEWS AND..

SLEEP-LEARNING EQUIPMENT

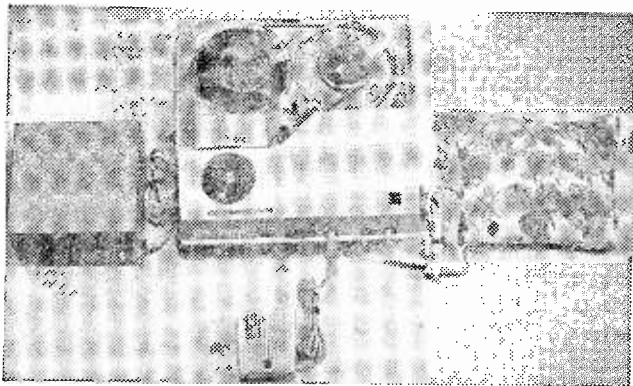

A number of researchers in America have laid great claims to the sleep learning method. It is particularly useful when a large number of facts have to be committed to memory, such as formulae, foreign languages etc.

The four simple basic requirements are a tape recorder, time switch, under-pillow speaker and a genuine desire to learn.

If you possess the latter requirement, then the first three can easily be obtained from R.C.S. Products, Ltd., 11 Oliver Road, London, E.17. £4 5s. 0d. buys the time switch with 14 day Swiss movement. The modified tape recorder complete with mic. and pre-recorded conditioning tape costs £23, and the pillow speaker 27s. 6d. The complete outfit may be obtained from R.C.S. Products at a cost of £29 10s.

PRACTICAL WIRELESS AND PRACTICAL TELEVISION FILM SHOW

The P.W. and P.TV. Filmshow is to be held on February 4th. 1966. For more details see the notice on page 783.

MASTERTAPE CHRISTMAS GIFTS

Mastertape (Magnetic) Ltd., announce that with every reel of Mastertape purchased over the Christmas period an empty spool of equivalent size will be provided free of charge.

The full reel and the empty spool will be packed together in a sealed polythene bag attractively over-printed with a Christmas motif.

BRITISH ELECTRONICS FOR AMERICAN AIRCRAFT

More British electronic equipment has been ordered by the Ministry of Aviation for the R.A.F.'s American Lockheed C-130 Hercules long-range transport aircraft.

Marconi Sixty Series transistorised airborne radio communications and navigation aids which are to be fitted, are already standard equipment in the majority of aircraft currently flying with the R.A.F.

Equipment specified includes the AD260 v.h.f. navigation system and the AD360 automatic direction finding system. The AD260 provides full v.h.f. navigation facilities and provides the instrument landing outputs used in the automatic landing system in the BEA Trident and also in the BOAC VC-10 aircraft. The AD360 is the standard Marconi airline automatic direction finding system. It features fully automatic crystal controlled tuning which was pioneered by the Company, and is still only available in Marconi ADF's.

.. COMMENT

EQUIPMENT FOR UK3 SATELLITE

UK3, the first all-British satellite, is being designed and built by the Guided Weapons Division of the British Aircraft Corporation.

At the Glenrothes, Fife, plant of Hughes International (UK) Ltd., microglass diodes are welded on to printed circuit boards to be used in the telemetry ground equipment of the project. These diodes form part of the microminiaturisation of the decoding matrices used in the telemetry ground equipment.

EMBOSSED PLASTIC CALLSIGN PLAQUES

We have received from F. W. Harris & Co. Ltd., Town Hall Chambers, Lydney, Gloucestershire, a specimen callsign plaque. Inch-high letters are heat embossed into the white plastic background which measures 4in. x 2in.

The plaque, which is washable and easily drilled for fixing, costs 3s. inclusive. A free-standing version is priced at 4s.

CIVIL SERVICE RADIO SOCIETY

The Civil Service Radio Society will be pleased to welcome members of H.M. Civil Service and associated organisations to their meetings at the Science Museum, South Kensington. The meeting on 7th December featured films on amateur radio, and on the 21st there will be an informal meeting and a Christmas party. For further details, please contact the Secretary, Mr. G. Lloyd-Dalton, 2 Honister Heights, Purley, Surrey, or H. E. Reeve, G3JXZ, 284a Barking Road, East Ham, London, E.6.


SOLID STATE AMPLIFIER

Messrs. Henry's Radio Ltd., 303 Edgware Road, London, W.2., are fast making a name as being one of the transistor people as far as the constructor is concerned.

Their latest offering is a ready built audio amplifier with a frequency response 30 c/s to 16kc/s. The sensitivity is 6 mV into 1k Ω for a push-pull output of 5W r.m.s., 10W peak with less than 1% distortion.

Despite the output, and the six transistors plus diode, the unit measures only 2 $\frac{1}{2}$ in. x 2in. x 1 $\frac{1}{2}$ in. and is available ready built and tested at £3 19s. 6d. plus 2s. post and package.

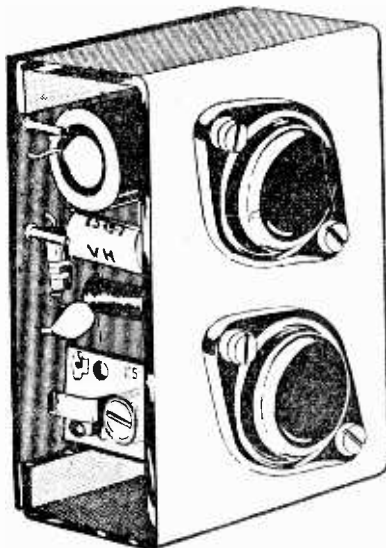It uses a transformerless design, with outputs for 3, 4 or 5 Ω speakers. An optional mains unit is available at 54s., and for the hi-fi enthusiasts, a full-function pre-amplifier at 79s. 6d.



more News and Comment on page 784

To Make, or To Buy?

WHEN reading the 'Editorial' and 'News and Comment' in the December 1965 issue of PRACTICAL WIRELESS, I felt that one point had been missed; the factor of technical advances in radio.

When most Amateurs were building their own equipment, the circuits and techniques were very elementary compared with the complexity of knowledge and highly advanced techniques of today. In the old days very good results were possible with simple equipment, since this equipment was norm. Today, however, one has to build modern first-class equipment to compete with the commercial product. This requires a great deal of knowledge and skill of the sort which is available to the professional. For the Amateur who does not earn his living in the radio or electronic industry these techniques are sometimes felt to be far too difficult to master, and who is to blame him for buying the commercial article?

B. Otter,

Durham City.

Thank-you Letter

IN reply to the request for the "Regency" blueprint which you kindly published for me, many readers sent copies. Some even enclosed the relevant issues of PRACTICAL WIRELESS, and one gentleman not only sent these but also enclosed the "Citizen" blueprint with the oscillator section completely wired and tested!

Will you through the medium of your columns thank all readers who helped me?

J. Owens.

Dolgellau,
N. Wales.

Correspondent Wanted

I AM interested in most branches of electronics. I would like to correspond with anyone who has the same interests and who is about the same age as myself (17).

David Higgins.

3 Woolgreaves Drive,
Milnthorpe,
Wakefield.



Push-Pull ELL80 Amplifier

3 VALVES ★ 8 WATTS

ALTHOUGH it uses only three valves and a minimum of other components this amplifier has an output of 8W and will reproduce records and radio programmes, etc., at high quality.

The Circuit

Referring to Fig. 1 it will be seen that the output stage employs only one valve, ELL80, which contains two pentode assemblies with a common cathode. Although rather expensive at present it is not unduly so when it is remembered that it takes the place of two and eliminates the problem of finding a matched pair of valves for the conventional push-pull circuit. The valve has a slope of 6mA/V and with 250V on anodes and screens and a bias resistor of 180Ω it provides a power output of 8.5W in return for a signal of

24V peak grid to grid. The signal currents through the two halves of the valve cancel out at the common cathode and the bias resistor does not have to be by-passed. Resistor R14 is included in the supply to the screens to ensure that, taking into account the voltage drop in the output transformer primary, the screen voltage will not exceed that at the anode.

The optimum load for the ELL80 is 11,000Ω. The specified output transformer is advertised for use with 6V6 or EL84 output valves but the manufacturers state that it is designed for a load of 10,000Ω and it is therefore suitable for the ELL80.

Phase Inversion

The valve V2 is a double triode, ECC83, one half of which is used to provide the two signals of opposite phase required by the output stage. Allowing for the decoupling provided by resistor R11 and capacitor C10 the supply voltage to the stage is 245V and with a total load of 200kΩ (R12+R13) the valve has an output capability of 27V r.m.s. This meets the requirement of the output stage with something in hand.

It will be noted that the cathode of V2b is about 120V above earth, which permits the grid to be directly coupled to the anode of V2a, so saving a coupling capacitor, grid and bias resistor. With this circuit the voltage across R13 is a little higher than that at the anode of V2a, thus providing working bias for the valve, a state of affairs which is automatically maintained irrespective of variations in supply voltage, etc. A further advantage is that direct coupling eliminates phase shift at extreme frequencies, which can be troublesome when feedback is applied over several stages as it is in this amplifier.

Heavy negative current feedback due to the large un-bypassed cathode load gives excellent linearity but the gain, as might be expected, is low, 0.9 each side or 1.8 times overall. For full loading the inverter therefore requires a signal of

$$\frac{24}{1.8} \text{ — or 14V approximately.}$$

by V. E. HOLLEY

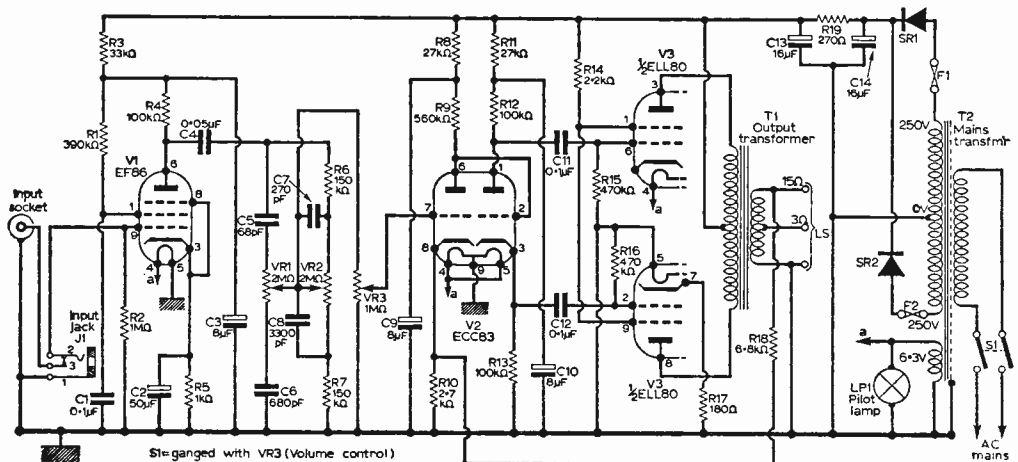


Fig. 1: Circuit diagram of the amplifier.

Voltage Amplifier

This signal is provided by V2a arranged as a conventional resistance coupled amplifier with decoupling provided by resistor R8 and capacitor C9. The bias resistor R10 is not by-passed, which saves a component and provides a convenient point for the injection of negative voltage feedback derived through resistor R18 from the secondary of the output transformer. This feedback compensates for deficiencies in the transformer, reduces harmonic distortion and improves loudspeaker damping.

The values of resistors R10 and R18 are so chosen that in parallel they provide the correct bias for the valve, while in series they cause the desired percentage of the output voltage to be fed back. It will be seen that V2a operates with both current and voltage feedback and consequently with excellent linearity.

Preamplifier and Tone Controls

The gain of the amplifier from the grid of V2a onwards is insufficient for most purposes, especially when the losses due to the introduction of tone controls are taken into account. A fairly high gain preamplifier stage is therefore needed.

The valve V1, in a conventional resistance coupled circuit with anode load of 100k Ω , gives a stage gain of 120 times. A gain of 180 can be had here by increasing R4 to 220k Ω , R1 to 1.2M Ω and R5 to 2k Ω , but if this is done the signal handling capacity of the valve will be reduced and it will be necessary to replace the grid resistor R2 by a 1M Ω potentiometer so that overloading with large inputs can be avoided.

With the circuit of Fig. 1 overloading will not occur with any normal gramophone or radio tuner input. The radio signal input is taken from a coaxial socket through the closed circuit jack J1 to the grid. Insertion of the jack plug disconnects the radio input and connects any other desired input.

The preamplified signal from V1 is fed into a Mullard-type tone control network consisting of the potentiometers VR1 and VR2 and their associated resistors and capacitors and thence to the volume control VR3, which incorporates the mains switching. Insertion of the controls at this point in the circuit ensures that they are not liable to electrostatic hum pick-up and that any noise voltages originating in the first stage are reduced along with the signal when the volume is turned down. The values of the capacitors C5, C6, C7 and C8 gave a good range of control in the prototype but tone control is very much a matter of individual preference and the capacitor values can be varied as desired.

Power Supply

The amplifier requires an h.t. supply of 75mA at 265V under full load conditions and 2A at 6.3V for the valve heaters and indicator lamp. This is provided by a double-wound mains transformer and two silicon rectifiers, SR1 and SR2. Fuses are included to protect the transformer winding in

COMPONENTS LIST

Resistors (all $\frac{1}{2}$ w. unless otherwise stated)

R1	390k Ω
R2	1M Ω
R3	33k Ω
R4	100k Ω
R5	1k Ω
R6	150k Ω
R7	150k Ω
R8	27k Ω
R9	560k Ω
R10	2.7k Ω
R11	27k Ω
R12	100k Ω
R13	100k Ω
R14	2.2k Ω
R15	470k Ω
R16	470k Ω
R17	180 Ω 2w.
R18	6.8k Ω
R19	270 Ω 1w.
VR1	2M Ω log. (Treble)
VR2	2M Ω log. (Bass)
VR3	1M Ω log, with switch.

Valves

V1	EF86, B9A base.
V2	ECC83, B9A base.
V3	ELL80, B9A base.

Capacitors (350v. working unless otherwise stated)

C1	0.1 μ F
C2	50 μ F 25v. electrolytic
C3	8 μ F electrolytic
C4	0.05 μ F
C5	68 pF
C6	680 pF
C7	270 pF
C8	3,300 pF
C9	8 μ F electrolytic
C10	8 μ F electrolytic
C11	0.1 μ F
C12	0.1 μ F
C13	16 μ F electrolytic
C14	16 μ F electrolytic

Transformers

Mains	250-0-250v. 80 mA. 6.3v. 2 amp.
Output Push-pull	10/12 watts, 6V6 or EL84 to 3 and 15 ohms. R.S.C. (Manchester) Ltd.

Rectifiers

SR1, SR2	—Silicon, BY100 or similar
----------	----------------------------

Fuses

F1, F2	150 mA.
--------	---------

Indicator Lamp

	6.3v.0.3 amp. and holder.
--	---------------------------

Miscellaneous

	co-axial socket, closed circuit jack socket, aluminium for chassis, mains cable and plug, 22 s.w.g. tinned copper wire, sleeving, hardware, etc.
--	--

event of a rectifier breakdown. The reservoir capacitor is virtually C14+C13; resistor R19 has little smoothing effect and is included only to reduce the h.t. line voltage to the required figure of 265V. Each of the earlier stages is provided with separate decoupling and smoothing, while in the output stage hum is almost completely cancelled out by push-pull operation. What little

is left is very effectively suppressed by negative feedback and cannot be detected 12in. from the speaker.

There is, of course, no reason why a valve rectifier should not be used if preferred and the fuses F1 and F2 need not then be fitted. The only requirements are that the valve should be capable of passing the required current and that a heater supply for it is available on the mains transformer. The advantage of the silicon rectifiers is that they do not generate heat, which is a consideration if the amplifier is to be installed in a cabinet with limited ventilation.

Construction

The amplifier is constructed on a chassis of 16 s.w.g. aluminium sheet, 12in. x 5in. x 1 1/4in., details of which are shown in Fig. 2. This allows plenty of room for everything, simplifies the construction and wiring and enables the constructor to make use of some of the older and bulkier components from the spare box. The wiring, for which 22 s.w.g. tinned copper covered with sleeving is suitable, is shown in detail in Fig. 3.

Note that in this diagram the positions of the components are approximate and the wiring has been opened out to make the connections clear. In construction all wiring should be kept to a reasonable length, particularly in the early stages, and if this is done no screening will be necessary anywhere in the amplifier. The positioning of the components is not critical.

Components

If silicon rectifiers are used the h.t. voltage will come on before the valves are warmed up and

ready to receive it and all capacitors except C2 must therefore be 350V working.

The accuracy of balance in the inverter stage depends entirely on the values of the resistors R12 and R13. Close-tolerance components are not necessary but the two must be balanced as closely as possible to ensure that their values are identical. Alternatively 1% resistors can be used. These remarks apply also to resistors R15 and R16 in the output stage. The wattage rating for resistors is given in the components list.

Testing

First check that the valves are in the correct positions. The connections to V2 and V3 are such that if the valves are accidentally transposed a dead short will appear on the h.t. line. Next check with a meter on a high-resistance range between C14 and chassis to see that there are no shorts. The lead carrying the positive voltage from the meter battery should be applied to C14, when a large deflection should be observed, dropping back slowly to a reading of 1MΩ or more as the capacitors become charged from the meter battery. Now connect a speaker and apply power. If as the valves warm up there is instability, reverse the connections from the output transformer primary to the ELL80 anodes to make the feedback negative.

The following voltages should be found at the points indicated using a 20,000 o.p.v. meter. Any substantial departure from these figures should be investigated.

C3 to chassis	230V
C9 " "	255V
C10 " "	245V
C13 " "	265V

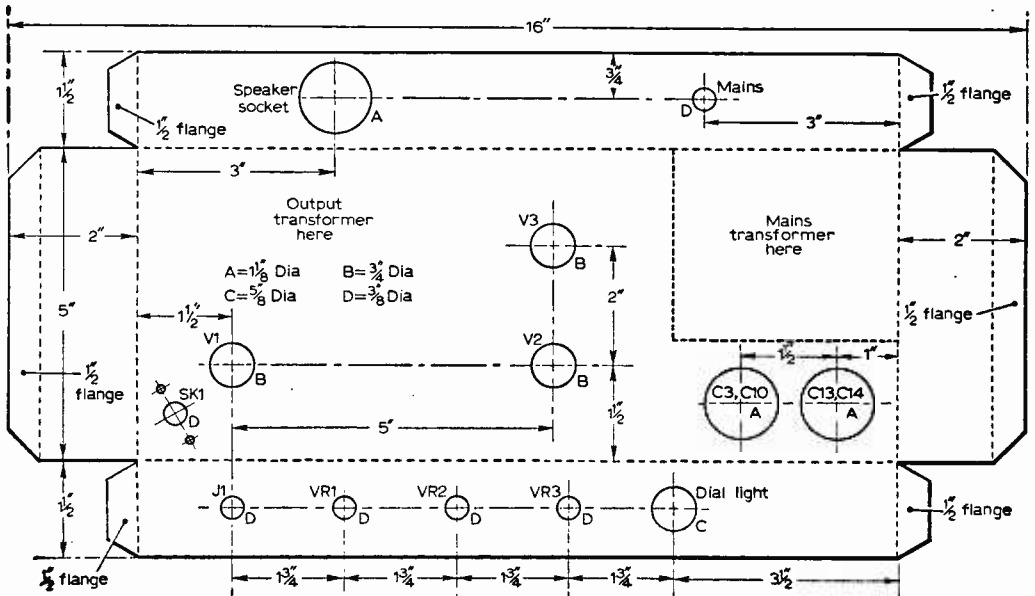


Fig. 2: Chassis drilling dimensions.

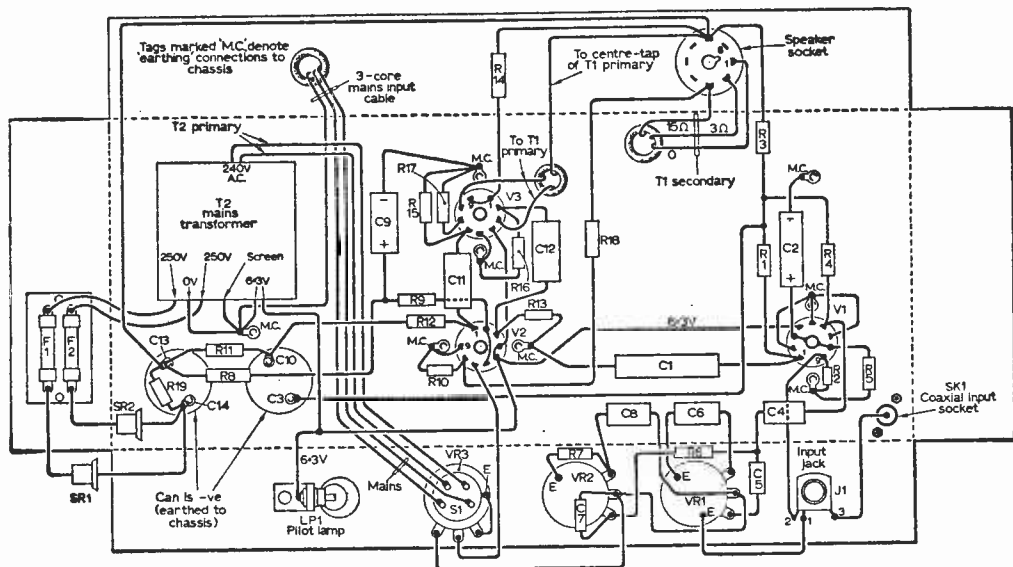


Fig. 3: Wiring diagram of the amplifier—underside view.

V3	anodes and screens	255V
V1	cathode	1.8V
V2a	"	1.4V
V2b	"	122V
V3	"	12.2V

speaker should be suitably housed. The prototype gave excellent results with an 8in. column speaker fitted in a 9in. glazed ceramic drainpipe. Domestic objections to the pipe can be overcome by painting it with metallic paint. Another point to note is that while the tone controls have a good range they cannot be relied upon to compensate for large deficiencies in the input signal. The output from a pick-up, for instance, must be corrected for recording loss if the best results are to be achieved. ■

Operation

A good amplifier is of little use without a good speaker and it is equally important that the

**BUMPER ISSUE
THIS MONTH!**

**SIMPLE DIGITAL COMPUTER
ELECTRONIC SERVO SYSTEM
PIPE AND CABLE LOCATOR**

These are just some of the features
in the **JANUARY** issue of
PRACTICAL ELECTRONICS
ON SALE 16 DECEMBER
SEE FOR YOURSELF!

**PRACTICAL TELEVISION
DECEMBER**

**CIRCULAR TV AERIAL
FOR BBC-2**

Full constructional details for compact indoor aerial for set top. Easily rotated for optimum performance.

**SINGLE-GUN COLOUR
TV TUBES**

**THE NEV-ICON CCTV
CAMERA**

THE SHORT-CIRCUIT

On Sale now Price 2s.



UNDERSTANDING F.M.

by W. Groome

RADIO is a progressive hobby. Sooner or later you will turn to frequency modulation for high quality, interference-free reception and will want to build your PW design with an understanding comparable with your knowledge of amplitude modulation. The main difficulty seems to be that of visualising the behaviour of the carrier and this impedes the study of the discriminator. Despite technical and mathematical proof most of us like to have a mental image of what goes on; we like to "get the picture" first and then proceed to advanced details. In this article much of the picture is aimed at your imagination, but there is no childish simplification and nothing that will conflict with any contemplated further study.

The basis of all signalling is change. Something must wave, wag, flash, flicker, hoot—there must be some noticeable or detectable change of a normally steady state. A radio carrier alternates at a high frequency but can be said to have a steady state when the frequency and radiated power are constant, producing—by rectification in the receiver—an unvarying voltage. It is easy to appreciate that changes in the transmitted power will produce corresponding changes in the rectified voltage and that such changes can follow the waveform of the audio signal.


This is amplitude modulation, with which we can take the carrier frequency for granted (as we do with most dependable things) and regard the easy relationship between carrier amplitude changes and rectified signal amplitude changes. With frequency modulation the carrier power is constant; the waveform and dynamic range of the audio signal are represented by changes of carrier frequency. Here lies one of the problems. The audio signal begins in the studio as a current or voltage varying in amplitude and it must emerge at some stage of the receiver in the same form. How can these changes of energy be conveyed by a carrier of constant power? A quick answer, which we shall develop later, is that they are not

conveyed, they are represented. Another question arises from a glance at transmitter characteristics. How can we relate carrier frequency swings as wide as 150kc/s with the frequency and amplitude of audio signals in the region under 20kc/s?

Here I call upon your imagination. Fig. 1 represents the dial of a receiver. It is calibrated vertically in kc/s and has a pointer driven by the usual knob (not shown). A certain frequency is marked at the middle of the scale (f_c) and others are shown by the amount by which they are higher or lower than f_c . The receiver is selective and has a visual indicator (not shown) to tell you when a carrier is tuned in.

Imagine that a carrier has been located at f_c but it seems wayward; it is drifting and you have to re-tune. Still it drifts and as you manipulate the knob to follow it the pointer is driven up to +30kc/s, then you have to tune downwards to follow the carrier to f_c and then further down as far as -30kc/s. Here it drifts up again until the pointer finally returns to f_c .

Let us check what happened. The carrier drifted by a large amount — from f_c up to +30kc/s, then down to f_c and beyond to -30kc/s, finally returning to f_c . One whole cycle of change. Yes, just one cycle of change. Despite all the kc/s your pointer moved up and down in only one cycle, and if you like to go over it again in imagination you will find that the pointer movement agrees well with the rise and fall of a sine wave. You will also realise that the pointer, following deviations of frequency, had a certain *amplitude* of movement, which suggests the possibility of such conversion although not normally by a mental-mechanical process!

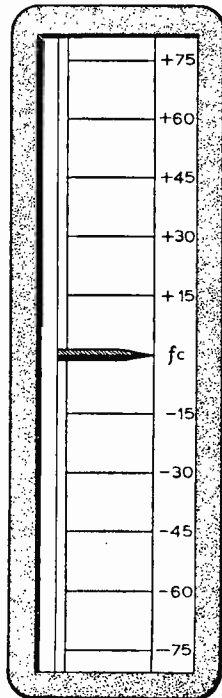

If the response of the imaginary receiver is broadened to cover the entire bandwidth of 150kc/s a frequency meter scaled as in Fig. 1 can indicate the deviations directly without knob-tiddling. Now we watch the pointer go through the same change of plus and minus 30kc/s five times in one second. If the pointer had a pen over a moving band of paper the five cycles would be recorded as in Fig. 2.

Rolling the paper back for one further imaginary experiment we find that the deviations are much wider—the pointer swings 60kc/s each way instead of 30kc/s—but still at the same rate of five cycles per second. These are drawn in broken line in Fig. 2.

From all this it is clear that the *rate* of change

Fig. 1: You can follow the explanation of frequency deviation with this diagram.


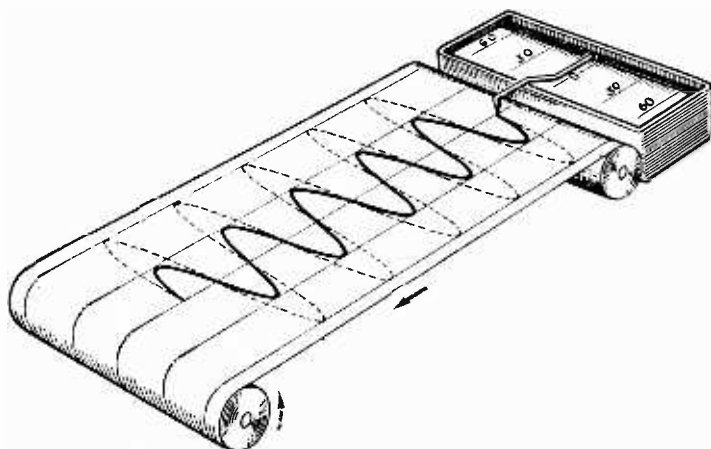


Fig. 2 (above): Carrier frequency deviations converted into modulation wave form.

Fig. 3 (below): Slope of LC circuit produces amplitude modulation from frequency modulated carrier.

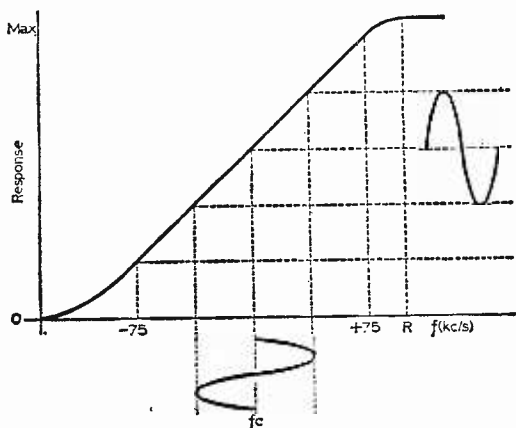

of carrier frequency is the modulation frequency (five cycles per second in our slow-motion picture, audio frequencies in reality) while the *amount* of deviation represents the amplitude. Unlike the a.m. signal, frequency modulation does not transmit real amplitude changes ready-made. It represents them, it provides their patterns, it supplies signal designs from which the receiver must recreate the amplitude changes of audio tones. There must be built into the receiver some means of "knowing" what the frequencies "mean", some way of recognising that it must supply amplitude changes of voltage or current as instructed by the swinging carrier.

A tuned LC circuit does "know" this, for it is inherently frequency-sensitive, having a response that is maximum at the resonant frequency but falls away gradually to frequencies on either side. Fig. 3 shows one side of the kind of response we would like to have. A carrier arriving with constant amplitude will suffer varying losses as its frequency swings between the resonant peak and the point of lowest response, and will therefore

emerge with an amplitude modulation. An ordinary a.m. detector will then demodulate the amplitude changes and lose the residual (and now unwanted) f.m. content in its r.f. filter.

This arrangement, the "slope" detector is merely a mis-tuned a.m. circuit. The straight slope of Fig. 3 is not attainable in practice and the normal curve brings serious distortion. For this reason, and because the degree of off-tuning is critical, the arrangement is rarely used.

If we broaden the response of a tuned transformer sufficiently it will no longer be frequency-sensitive within the flat bandwidth and will therefore fail to act as a slope detector. It will, however, be phase sensitive.

There is some difficulty in describing the action of phase discriminators without assuming the reader is familiar with the nature and effects of phase relationships. The subject is worthy of an article to itself but for the present we must settle for the statement that phase means the positions of a.c. cycles in time. For example, two trains of cycles may have the same frequency but the cycles of one may commence earlier or later than those of the other. Their result would depend on the amount (expressed in angular degrees) of "lead" or "lag".

The Foster-Seeley discriminator works by comparison of a signal after it has passed through two routes, of which one introduces phase shift and the other does not. In Fig. 4 the direct route via capacitor C1 produces no phase shift. The transformer secondary conducts it equally to the diodes for rectification and it appears in opposition across the total load R1 R2. In the absence of aid or opposition from elsewhere the two outputs would cancel.

In addition to this reference the signal also arrives via the tuned transformer with changes of phase dependent upon frequency. At the central, resonant frequency it is a quarter of a cycle ahead of the reference signal at one diode—it leads by

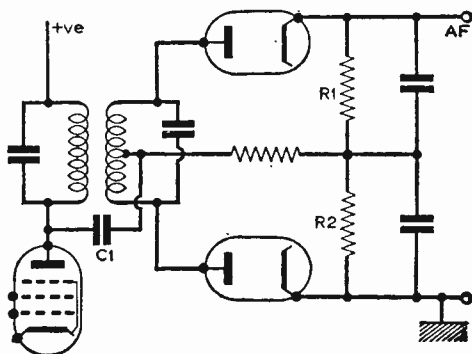


Fig. 4: Foster-Seeley discriminator.

90°—and at the other it lags by 90°. It can be shown by vector diagram that this combination in exact quadrature produces diode inputs greater than those of the reference signal alone, but they are still equal and therefore the diode outputs still cancel. This condition exists only for the resonant frequency. At all other frequencies the phase of the tuned transformer signal changes increasing the angle at one diode input and decreasing it equally at the other. The balance that produced equal aid to the reference signal is now disturbed and the total signal is now shared unequally between the two diodes. The rectifier outputs cannot cancel but must leave a difference. This difference voltage, varying as changing phase angles bring changing unbalance, is the a.f. signal.

The circuit is sensitive to amplitude modulation (which for practical purposes includes interference) and must therefore be preceded by a limiter. This is usually an over-driven i.f. stage which clips the tops and bottoms of the carrier waves to a uniform level, removing interference "spikes" in the same process.

This additional stage can be eliminated by re-arranging the circuit to make the diodes serve the dual roles of rectifiers and dynamic limiters. Fig. 5 shows a simple version of the ratio detector, the most popular system today. Although the reference signal is derived from the tertiary transformer winding instead of via a capacitor the signal conditions are much the same as in the Foster-Seeley circuit as far as the rectifiers. The diodes, you will notice, are connected to make their outputs additive across the load instead of subtractive. As the unbalance produced by phase shifts brings an increased input to one diode and an exactly corresponding decrease to the other the sum of the two outputs is always the same. The difference voltage is therefore due to the changing ratios by which the diodes contribute their shares to the total sum, and can be taken as an a.f. signal across either of the capacitors C2 C3 or either of the resistors R1 R2.

We have established the total diode-to-diode voltage as being (ideally) constant, and it can be

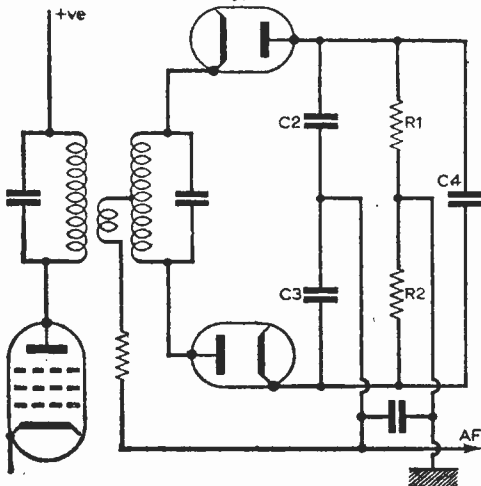


Fig. 5: Ratio detector.

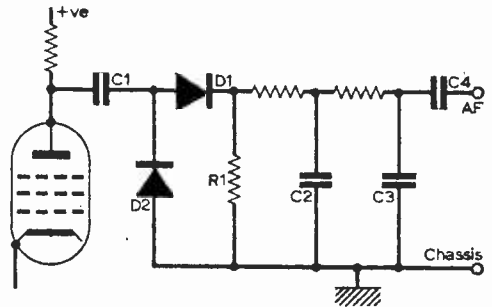


Fig. 6: Pulse-counter discriminator.

stabilised by a large capacitor C4, which charges to a level set by the average carrier amplitude and also absorbs some of the spurious signals that may be riding above the carrier. The diodes are tied to this steady bias and variations of carrier strength (and these include interference that "lifts" the carrier level) change the working points, varying their resistance inversely with the changes of carrier level. The diode resistance damps the tuned circuit, therefore a rise of carrier amplitude is countered by heavier damping and is unable to attain more than about 15% of its true worth.

The ratio detector is now seen to be a phase discriminator in which unbalanced diode output resulting from the phase shifts of frequency deviations in a tuned transformer provide an a.f. signal by their voltage differences and, by their sum voltage, a bias that enables the diodes to serve also as dynamic limiters. Although limiting is less effective than that of a separate stage it is adequate for most ordinary needs, and is achieved with economy.

Both discriminators depend upon accurate alignment of tuned transformers and upon the maintenance of this alignment once it has been attained. The conversion of frequency deviations to phase-shifts, thence to diode unbalance and difference voltages is reasonably accurate and distortion is variously claimed as being between 1% and 3%, which is below the standard required for transmitter monitoring and certain other high quality needs. For such purposes there is a system which gives a more direct and linear conversion of frequency deviations to a.f. voltages. The system is aperiodic—it has no tuned network—therefore the alignment problem does not exist and there is no long-term deterioration of the performance.

The receiver gives each carrier cycle a fixed value and adds them to obtain an output that is continuously proportional to their number. At the higher deviations the number of carrier cycles per given small period of time is obviously larger than the number arriving with the lower deviations and in an additive circuit these varying numbers of cycles will produce varying voltages. These constitute the a.f. signal. To give each cycle the same value regardless of frequency the carrier (i.e., i.f.) sine waves are converted into pulses, and this can be achieved in a simple overdriven limiter stage. In Fig. 6 clipped waves from the preceding limiter are passed through the differentiator network C1 R1 through diode D1 which passes pulses of one

—continued on page 783

on the Short Waves

MONTHLY NEWS FOR DX LISTENERS

All times are in G.M.T.

All frequencies are in kc/s.

The Broadcast Bands—by John Guttridge

ON November 7 most international stations introduced their winter schedules. Details of some of these are amongst this month's information.

Japan: *Nippon Hoso Kyokai* (Radio Japan, Tokyo) is using new frequencies for some General Service transmissions in English and Japanese. Between 1200 and 1730 9,505/9,560/11,815 are used. The 1800 and 1900 transmissions are on 9,505/9,560/9,605. From 2000—2030 9,560/9,605/15,195 are used.

Philippines: *Far East Broadcasting Co.* (Box 2041, Manila) replaced 15,385 by 11,850 for the 2330—0100 section of its English transmission on December 1. This transmission is also carried on 17,810. Other portions of the English service with new frequencies are 0830—0900 9,715/11,920/15,440/15,300/17,810 and 0900—1145 15,440/17,810. Full QSL.

Ryukyu Islands: *Voice of America* relay on Okinawa, can be heard in London until 1600 on 7,235 in Chinese. Station identification is given at 1600 in English.

Australia: *Radio Australia* (P.O. Box 428G, G.P.O., Melbourne) now transmits in English to British Isles from 0815—0915 on 9,570/11,710.

Canada: *Canadian Broadcasting Corporation* (P.O. Box 6000, Montreal) now uses 15,320/11,720 for the 1055—1315 segment of its European Service.

U.S.A.: *Voice of America* (U.S. Information Agency, 330 Independence Avenue, S.W., Washington 25, D.C.) now has following European English schedule: On 1,196 Munich 0400 0430, 0500—0730, 1600—1830, 2200—2345; 3,980 Munich 0300—0700, 1400—2345; 5,965 Tangier, 5,995 Greenville, 7,200 BBC and 7,250 0300—0730; 5,995 Tangier 1630—2245; 6,040 0500—0730; 7,205 Thessaloniki 1500—2300; 9,540/9,740 0430—0730; 9,760 1430—2245; 9,565/9,710 1900—2245; 11,760 1800—2215; 15,205 Greenville 1400—2215; 15,290 Tangier 1400—1800; 15,295 0600—0730; 17,780 Greenville 1400—1800.

Radio New York Worldwide (4 West 58th Street, New York City 19, N.Y.) has following new English schedule: 1200—1400 15,290 or 15,295/17,710 (plus 15,385 Saturdays and Sundays); 1400—1500 17,845/15,440 (plus 15,385 Saturdays and Sundays); 1500—1900 17,845/15,440/17,730; 1900—2000 15,440/11,970/17,845/17,730; 2000—2100 15,440/11,970/11,880/17,730; 2100—2145 11,970/9,740 or 9,570/11,880/17,730/15,440; 2145—2200 9,740 or 9,570/11,725 or 11,790. A new QSL card is now being issued. The Dx programme is now at 1330 and 2130 on Saturdays.

Cuba: *Radio Habana* (Apt. Postal 7026, Habana) transmits to Europe in English from 2010—2040 on 11,735.

Mexico: *Radiodifusora Comerciales* (Quemada 40, Col. Narvarte), can be heard during the evening over

XEWW on 15,110 with interference from Radio Iran on 15,112.

Netherlands Antilles: *Trans World Radio* (Bonaire), has been heard with English test transmissions at 0140 on 11,825; 1430 on 11,820 and 1825 on 15,180.

Brazil: *Radio Farroupilha* (Rua Vigarario José Inacio 263, Porto Alegre, Rio Grande do Sul) has been heard as early as 1900 with excellent signal over ZYU60 on 15,335.

Austria: *Osterreichischen Rundfunk* (Wien IV, Argentinierstrasse 30a) transmits to Europe from 0500—2200 on 6,155; 0900—1900 7,245; and 0600—1700 on 9,770.

Bulgaria: *Radio Sofia* (Sofia) has an English transmission to Africa from 1905—1930 on 11,715/15,320.

Denmark: *Radio Denmark* (Shortwave Department, Radio House, Copenhagen V) has now returned to 15,165 for its transmission from 0900—1000.

France: O.R.T.F. (116 Avenue du Président Kennedy, Paris 16) has English for the U.K., Monday—Saturday on 6,175 at 2000—2015.

Germany: *Deutsche Welle* (Bruederstrasse 1, Postfach 344, 5 Köln) has now brought its Kigali, Rwanda, 250kW relay into full service. English transmissions are 0630—0715 on 11,905; 1215—1300 17,765; 1745—1830 17,805; 0430—0500 6,045; 1015—1045 9,735; 1545—1615 9,695. The new schedule for English programmes transmitted from Julich, Germany, is 0300—0340 5,980/7,175; 0845—0940 17,845/11,925/15,275; 2110—2200 5,980/7,175; 1550—1620 7,175/9,735; 0645—0715 9,605/11,785/15,275; 1015—1030 11,930/15,280/17,870; 1555—1630 9,610/11,890; 0130—0250 6,075/9,640; 0500—0540 6,145/9,735; 1510—1550 9,545/9,640/11,795. A new QSL card is being issued.

Greece: *Radio Athens* (Mourozi Street 16, Athens) may be heard on 9,605 during its 1030—1300 transmission except for 1045—1100 when there is a special transcription broadcast for North America on this channel from Deutsche Welle. Although all programmes from Athens are in Greek, the station (a rare catch) may be identified by its flute and bell interval signal.

Holland: *Radio Nederland Wereldomroep*, P.O.B. 222, Hilversum, now has six English transmissions (daily except Sundays). Details are 0730—0820 9,715/11,730/11,790 and 19m.b.; 1430—1520 17,810/15,425/6,020; 1900—1950 9,590/6,020 and 25m.b.; 2000—2050 19,25 and 31m.b. and 6,020; 2100—2150 9,590/6,085; 0130—0220 9,600 (Bonaire relay). Happy Station programmes on Sunday are 0600—0720 11,730, 9,715; 0730—0850 9,525/11,970 and 19m.b.; 1030—1150 9,710/5,980/6,020; 1430—1550 17,810/15,425/6,020; 1800—1720 19 and 25m.b.; 1900—

2020 11,730/9,590/6,085; 2030—2150 6,020 and 25, 31m.b.; 2200—2320 15,220/9,715.

Portugal: *Radio Lisbon* (Rua Sao Marcal 1A, Lisbon) has the following new English transmissions 0300—0345 5,975; 0730—0815 and 0815—0900 7,130/9,645; 2015—2100 6,025/7,225.

Switzerland: *S.B.C.* (3000 Berne 16) has completely new schedule. English to the U.K. is now at 1145—

1315 on 9,665/11,865. Full details of the other English transmissions will be given next month.

Thanks this month go to John Sawyers (Ilford), J. W. Smith (Anstruther), Roy Patrick (Derby), Brian Burling (Rotherham), R. J. S. Gilchrist (Bristol), Radio New York Worldwide, S.B.C., and the International Short Wave Club.

The Amateur Bands—by David Gibson G3JDG

ANOTHER excellent month for the DX fans, especially on the h.f. bands. Twenty-one "megs" has opened with a real vengeance at times and the majority of logs received this month were for this band.

Yours truly was operating in the "Jamboree on the Air" event using the call G3GJX/A from Leverstock Green. At 0700 hours 21Mc/s proved a hive of industry and no trouble was experienced in raising JA stations in Tokyo and Osaka. It must be confessed that this was with 400W p.e.p. of s.s.b. to a two-band cubical quad.

My best on 20m from the home QTH was VK3ATN. Imagine my feelings when an s.w.l.'s report contained the same call—only the s.w.l. was using a t.r.f.! Brethren I am choked.

If you hear 3A2DA then you are listening to a pirate. **Geoff Haynes**, the real 3A2DA, would like any reports on this call. Time, band, etc. Geoff's address is Sans Nom, Fir Tree Road, Leatherhead, Surrey.

The L.F. Bands

Eighty looks very promising for the winter months. **James Brown** (Llandaff), 19 set, a.t.u. dipole, reports hearing some 20 W stations and 23 VE's, including VEØMS//MM (Baffin Is.). Others heard include K2GO, UA2KAN, ZB2AO, ZD8HL, 4X4AS, 7X2AH. **Peter Hickey** (Pinner), t.r.f. hooked K2KPM, K8HIR, T12IO (Costa Rica), VE1IE, W—2ZPO, 3WJO, 3WPG, 4BW, YV5BMR ZL2BCG, ZL4LM, all around 0600 hours G.M.T. **A4238**, QTH unknown: RX107+PR30, 132ft long wire running SE/NW, DL, EA, HA5, HB9, HVI (Vatican City), LX1, LZ, OH, OK, ON, SM, VE, VO, W4/P, YU, YV, 4U1, all on sideband. **D. M. Howarth** (Bolton), PCR3, 20ft vertical on 7Mc/s, DJ, LA5, OK, ON, PAØ, plus two nice ones, SVICC, VK5VA.

14Mc/s and Higher

Dennis Goh using a transistor receiver with the P.W. add on b.f.o. raised DU, JA, KA, KG6, VK, VS6, VS9, XW8, 9M6. Not DX to him because Dennis is in Singapore. **Chris Freeman** (Nuthall), HE80+PR30, a.t.u. ground plane, CN8, FM7 (Martinique), FP8 (St. Pierre and Miquelon), KG4, LA2/MM, OD5, U18, VK3, VK4, VP7, YS1, ZD8, 4X4, 5Z4. **Dave Hidmore** (Belper), HE40, dipole, CN8, CR4, CR6, EP2, FG7, HI8, HK, IØ, K7/VO2, KZ5, LU, OD, PY-1, 2, 5, 7, SVØ, TG9 (Guatemala), VP6, VP9, XE, YV3, ZB. All these logs are for 20 and the last 14Mc/s report comes

from **Bernard Hughes** (Worcester), 84OC+Codar preselector, dipole, KL7, KX6 (Marshall Is.), MP4 SVØ, JA9, VP9, VK-2, 3, 4, YV, ZL. **Stephen Beal** (Muswell Hill), P.W., May, 1964, t.r.f. 66ft long wire, 21Mc/s, AP3 (Pakistan), OD, SV, UB, VE, VP2 (St. Vincent), K1, W-1, 2, 3, ZB2, 4X4, S. **Barnes** (Newthorpe), PCR2, 30ft long wire, W-1, 2, 3, 4, 8, 9, K-2, 4, WA, WB, 4X4. **A. Smith** (Highbury Barn), HE30, Joystick, G3, K1 OD5, UA3, VE3, W-1, 3, 8, 9, Ø, 6W8 (Senegal).

28Mc/s

Paul Baker (Pontypool), HE30, 45ft long wire plus 14ft whip, CR6CZ, CR7FR, DJ, DL, GW5XN, 11, K2, LUIDAB, SM, SV1DB, W2AZD, ZS1BV, 9G1DM, 9J2DL. **R. Iball** (Worksop), SX28+PR30, 80ft long wire end fed with 35ft coaxial, CR7FR, CR7IZ, ZS1BV, ZS2CB, ZS2ND, ZS6MM. **Christopher Clarke** (Farnham), 10-valve s/het, 33ft wire around picture rail, CR7, CT1, DJ, DL, EA, ET3, G's, 11 U, OD5, OE, OH, SV1, UQ2, VK2NN, W1, YV5, ZC4, ZS1, 5A1, 7X2, 9J2, all a.m. or s.s.b.

In General

Listen to the low end of 160 for W1BB/1. On 20m phone KW6 (Wake Is.), KM6 (Midway Is.), KJ6 (Johnson Is.), KR6 (Okinawa), all very active. K1ZBR/MM is the U.S.S. Calcaterra cruising around the Antarctic, whilst a VK9 is reported operating from Papua Territory.

One piece of news perhaps not generally known is the RSGB news bulletin broadcast on Sunday mornings. The London area has a transmission on 3.6Mc/s at 0930 hours.

The Severn area at 1000, Belfast 1015, North Midlands 1030, North West England 1100, South West Scotland 1130, North East Scotland 1200. All these on 3.6Mc/s.

For the two metre enthusiasts the news is also broadcast on Sunday mornings as follows:— 145.1Mc/s beaming North from London. 145.1Mc/s beaming West from London. 145.8Mc/s 1015 beaming South from Belfast. 145.3Mc/s 1030 beaming North West from Sutton Coldfield. 145.3Mc/s 1100 beaming South West from Sutton Coldfield. 145.5Mc/s 1130 beaming North from Leeds. 145.5Mc/s 1200 beaming East from Leeds.

That's it for this year. Thanks to all who sent in logs. Please keep them coming. Best 73, Mri Christmas es cuagn next year.

Sheet

Paxolin

Ideal for transistor projects
Special offer
12 panels 6 x 8 in. 5/-.



Bargain of the Year

A complete kit of parts to build
6 transistor
2 wave
superhet
receiver
at only
39/6.
Post
and
Ins. 3/6.




"CORONET" Mk. IV

It fully covers the medium waveband and that part of the long waveband to bring in B.B.C. Light. The circuit includes a highly efficient slab aerial and 2 1/2 in. P.M. speaker. Overall size approximately 4 1/2 x 2 1/2 x 1 1/2 in. Supplied complete with carrying case and instructions.

MAINS POWER PACK

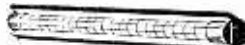Designed to operate transistor sets and amplifiers. Adjustable output 6v-12 to 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PPI-PP3-PP4-PP6-PP7-PP9 and others. Kit comprises: mains transformer-rectifier, smoothing and load resistor, 5000 and 500 mfd condensers, zener diode and instructions. Zeal snip at only 14/6 plus 3/- post.



INFRA RED HEATER

Make up one of these latest type heaters. Ideal for bathroom, kitchen, bedroom, etc. They are simple to make from our easy to follow instructions—use silica enclosed elements designed for the correct infra-red wavelength (3 microns). Price for 750 watt element and metal casing as illustrated, 19/6 plus 2/9 post and insurance. Full switch 3/- extra.

This Month's new Bargains

Note A complete list of our bargains is being prepared it will be over 100 pages. If you would like a copy please send 2/6, also if you would like advance news of each month's bargains please send S.A.E. to reach us by first of the month.

Tubular Heater New & unused by G.E.C.—60 watt per foot leading—ideal in home, office or shop—curtains, papers etc. can drop on them without catching fire—connect these on off peak rate and a warehouse may be kept damp free for the min. cost and trouble—supplied complete with fixing brackets—all lengths from 2ft to 22ft—only 2/9 per foot (less than half price) carriage extra at cost.

Beethoven Coil Pack. Covers medium wave and two shorts (regret exact coverage not known) uses 6 coils 6 trimmers and 4 pole wave change switch and it is aligned ready for use. 7/6 plus 2/6 post.

Wall Mounting Thermostat. By Satchwell intended for use to control tubular or any type of space heaters indoors or in a greenhouse—Adjustable over 40/50. Of complete with mounting screws 29/6 plus post 2/9 (normal price is at least twice this).

Morganite Sealed Pairs. Another batch of these has arrived and we can now offer quite a range namely; 5K, 50K, 100K, 250K, 1/2 meg, 1 meg, 2 meg, all at 8/- per dozen per value, plus 2/9 post on first dozen, then 1/- per dozen. Less than one dozen price is 9/- each even this is only about 1/10 of the catalogue price and this is undoubtedly one of the best spots available.

Tuning Condensers. 2 gang .0005 mfd air space standard size with good length spindle 30/- doz. or 3/9 each post 2/9 up to six, 3/6 per dozen.

Tuning Condenser. Bakelite type. .0005 mfd for tuning or reaction 1/4 inch spindle 25/- per doz. or 3/- each, post 2/9 per doz.

Where postage is not definitely stated as an extra then orders over £3 are post free. Below £3 add 2/9.




CIRCLE-LITE

Brings sunshine into your home. 150 watts of light but uses only 40 watts. Beautiful fittings with glass, not plastic centre, fluorescent tube and choke control. Made by Philips. Will give a lifetime of service. Regular price £4.15.0.

Special Bargain Price **65/-** plus 8/6 carriage and insurance. Please state colour of glass centre white, pink, blue, red, black, yellow or cream. Also whether plug into lamp holder or ceiling, mounting model 80 watt model 99/6.

See in the Dark
INFRA-RED BINOCULARS

These if fed from a high voltage source will enable objects to be seen in the dark, providing the objects are in the rays of an infra-red beam. Each eye tube contains a complete optical lens system as well as the infra-red cell. These optical systems can be used as lens for TV camera—light cell etc. (details supplied). The binoculars form part of the army night driving (Tabby) equipment. They are unused and believed to be in good working order, but sold without a guarantee. Price £2.17.6 plus 10/- carriage and insurance. Handbook 2/6.

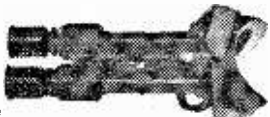

750 mW TRANSISTOR AMPLIFIER




4 transistors including two in push-pull input for crystal or magnetic microphone or pick-up—feed back loops—sensitivity 5 m/v.

Price 19/6

Post and insurance 2/6.
35 ohm Speaker 12/6 extra

THIS MONTH'S SNIP

CAPSTAN DRIVEN
Tape Recorder

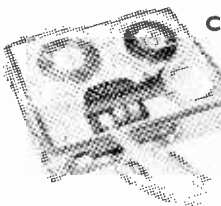

Although some well made spool driven machines give remarkably good results there is no doubt that to achieve anything like perfection and to have versatility a Capstan Driven Tape is essential. Now at last we can offer you a Capstan Driven, completely portable, battery operated instrument at a remarkably low price. So low in fact that you can easily afford to have a second machine for use in your car, office, home etc. or to give to reps or relations to exchange tapes.

SPECIFICATION—260/7000 C.P.S.—400 MW output—double track—two speed 1 (3) and 7 1/2 fast rewind time—5" spool gives one hour playing with standard tape weight 7 lb., size 8 x 11 x 5/2. Complete with batteries, microphone, tape spool and instruction manual. Nothing to go wrong if you use a good tape and keep heads clean. Demonstration gladly given at our Croydon shop.

Special Snip Price This Month. £11.11.0. Post & Insurance 6/6.

AUTOCHANGER BARGAIN

Garrard Auto Record
Player Model A.T.5




This is undoubtedly the finest Auto changer made in fact its large, heavy, non-magnetic, die cast turntable, die cast compensated constant pressure styli, together with its laboratory series motor with balanced rotor, make it almost a transcription unit. Other special A.T.5 feature are:— Will take 8 records which may be playing a record without rejecting same record—fitted with latest pick-up for playing stereo or mono records.

OFFERED AT THE AMAZING PRICE OF £8.15.0 plus 6/6 carriage and insurance.

Speaker Bargain

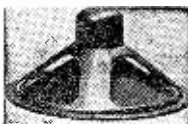12in. High-fidelity loudspeaker. High flux magnet type with either 3 ohm or 15 ohm speech coil. Will handle up to 10 watts. Brand new by famous maker. Price 29/6 + 3/6 post and insurance.



SPOT OR FOG LAMP

Made by Lucas. Flat o pencil beam. 36 watt. Suitable for car, boat, caravan, etc. Complete with 6 or 12v bulb, flex, cables and fixing bolt. Remarkable bargain. Price 12/6 + p. & p. 3/6



SELF ENERGISED TELEPHONES



These require no batteries: in fact they have only to be connected by a pair of wires. They can thus be fitted into existing bell circuits. Results are extremely good and maintenance costs are nothing. Handsets only 15/- each. Post etc. 2/6. Two, post free.

THERMOSTATS

Type 'A' 15 amp for controlling room heaters, greenhouse, airing cupboard. Has spindle for pointer knob quickly adjustable from 30°-80°F. 9/6 plus 1/- post. Suitable box for wall mounting. 5/-, P. & P. 1/-.

Type 'B' 15 amp. This is a 17in. long rod type made by the famous Sunvic Co. Spindle adjusts this from 50°-500°F. Internal screw alters the



setting so this could be adjustable over 30° to 1,000°F. Suitable for controlling furnace, oven, kiln, immersion heater or to make flamestat or fire alarm. 8/6 plus 2/9 post and insurance

Type 'C' is a small porcelain thermostat as fitted to electric blankets, etc. 1 1/2 amp. setting adjustable by screw through side. 3/6, P. & P. 6d.

Type 'D' We call this the Ice-stat as it cuts in and out at around freezing point, 2/3 amps. Has many uses, one of which would be to keep the hot pipes from freezing if a length of our blanket wire (16 pds. 10/-) is wound round the pipes. 7/6, P. & P. 1/1.

Type 'E' This is a standard refrigerator thermostat. Spindle adjustment covers normal refrigerator temperature. 7/6, plus 1/- post

9-Way push-button switch

Each way having two single pole change over and one shunting switch, good length push rods 30/- per doz. 3/8 each, post 2/9 per doz.

Waterproof Heater Wire

18 v.d.s. length 70 watts, self regulating temperature control. 10/-, post free.

Three Unusual Items

OZONE OUTFIT—for removing smells and generally improving any oppressive atmosphere. Kit consists of Philips Ozone Lamp and mains unit, only needs box 19/6 plus 3/6 postage and insurance.

BLACK LIGHT UNIT. 40 watt intensity, comprises lamp, lamp holder and 40 watt choke. Only 19/6 plus 6/6 carr. & ins.

TIMER KIT. Special offer of all components except metal box to make mains operated interval timer for photography etc. 12/6 plus post 2/6.

ELECTRONICS (CROYDON) LTD

Callers to: 266 LONDON ROAD, WEST CROYDON, SURREY
Post orders to: Dept. P.W. 4 Springfield Road, Eastbourne, Sussex

Make Your Ability PAY

UNLIMITED OPPORTUNITIES exist today for "getting on" . . . but only for the fully trained man. Let ICS's tuition develop your talents and help you to succeed.

STUDY IS EASY with ICS guidance. The courses are thorough. Printed manuals, fully illustrated, make study simple and progress sure.

YOUR ROAD TO SUCCESS can start from here—today. Complete this coupon and post it to us, for full particulars of the course which interests you. MODERATE FEES INCLUDE ALL BOOKS.

Take the right course now . . .

- | | |
|--|--|
| <p>ADVERTISING & ART
 Copywriting, Cartooning
 Layout and Typography
 Commercial Illustrating
 Oil & Water Colour</p> <p>BUILDING & CIVIL ENG'NG
 Architecture, Bricklaying
 Building Construction
 Builders' Drawings
 Builders' Quantities
 Interior Decoration
 Quantity Surveying
 Heating & Ventilation
 Carpentry & Joinery</p> <p>COMMERCE
 Book-keeping
 Accountancy & Costing
 Business Training
 Office Training
 Purchasing, Storekeeping
 Secretaryship
 Shorthand & Typing
 Computer Programming
 Small Business Owners</p> <p>DRAUGHTSMANSHIP
 Architectural, Mechanical
 Drawing Office Practice</p> <p>ELECTRONICS
 Computers
 Electronic Technicians
 Industrial Electronics</p> <p>FARMING
 Arable & Livestock
 Pig & Poultry Keeping
 Farm Management & Accounts</p> <p>GENERAL EDUCATION
 G.C.E. subjects at Ordinary & Advanced Level
 Good English
 Foreign Languages</p> | <p>HORTICULTURE
 Home Gardening
 Park Gardening
 Market Gardening</p> <p>MANAGEMENT
 Business Management
 Hotel Management
 Industrial Management
 Office Management
 Personnel Management
 Public Relations (I.P.R.)
 Transport Management
 Work Study
 Foremanship</p> <p>MECHANICAL & MOTOR ENG'NG
 Engineering Maths.
 Diesel Engines-Welding
 Industrial Instrumentation
 Workshop Practice
 Refrigeration
 Motor Mechanics, etc.</p> <p>POLICE
 Entrance Examination
 Police-Promotion (Educ. Sub.)</p> <p>PHOTOGRAPHY
 Practical Photography
 RADIO, TV & ELECTRICAL
 Servicing & Engineering
 Radio-Construction (with Kits)
 P.M.G. Certificates
 Telecommunications
 Elect. Jobs</p> <p>SELLING
 Electrical Contractors'
 Company Reps.
 Sales Management
 Marketing</p> <p>WRITING FOR PROFIT
 Television Scriptwriting
 Short-story Writing
 Free-lance Journalism</p> |
|--|--|

INTENSIVE COACHING for all principal examinations —G.C.E., Secretaryship, Accountancy, Engineering, Work Study, Management, Radio, Architecture and Surveying. Special course for G.C.E. French Oral Test.

Member of the Association of British Correspondence Colleges

Start today the ICS way!

INTERNATIONAL CORRESPONDENCE SCHOOLS
 (Dept. 172)
 Intertext House, Parkgate Rd., London, S.W.11

Send FREE book on.....

Name.....

Address.....

Occupation.....

1.66

INTERNATIONAL CORRESPONDENCE SCHOOLS

RETURN-OF-POST

ON CASH OR C.O.D. ORDERS

● GARRARD GRAMOPHONE EQUIPMENT

RECORD CHANGERS	Cash Price	Deposit	Credit Terms	
			Monthly Payments	Total Credit
Model 50 (GCS Mono PU)	£9.9.6	£1.9.6	12 of 16/5	£11. 4.6
Model 1000 (GCS Mono PU)	£8. 9.6	£1.9.6	12 of 13/5	£9.14.6
Model 3000 (STAILO Stereo Mono PU)	£12.15.0	£2.12.0	12 of 19/-	£14. 0.0
AT80 (GCS Mono PU)	£12.19.6	£2.12.8	12 of 19/5	£14. 5.6
A70 (Deram PU)	£25.19.6	£5. 3.6	12 of 39/-	£28.11.6
LAB80 (Deram PU)	£31.19.6	£6.19.6	12 of 47/9	£35. 2.6

SINGLE RECORD PLAYERS

SP25 (GCS Mono PU)	£12.15.0	£2.12.0	12 of 19/2	£14. 0.0
SP25 (Deram PU)	£12.10.0	£2.10.0	12 of 24/8	£12. 2.0

IMPORTANT—When ordering units with the Decca Deram Pick-Up, please state whether Stereo or Mono required.

● ARMSTRONG CHASSIS

127M AM/FM Tuner Amplifier	£28.10.0	£5.10.0	12 of 39/4	£29. 2.0
224 FM Tuner	£22.10.0	£4.10.0	12 of 33/9	£24.15.0

● MULLARD AMPLIFIER KITS

We have full stocks of all components for the Mullard 510, 3-3, Two and Three Valve Pre-Amplifiers, Tape Pre-Amplifier, Stereo Pre-Amplifier, Seven Watt and Three Valve Stereo Amplifiers all as described in the Mullard Manual for Audio Circuits. We can supply this publication for 9/8, post free.

● PARMEKO TRANSFORMERS

We stock Parmeko Transformers for the popular Mullard Valve Amplifier circuits. All the transformers are fully shrouded and fitted with tag panels. Exactly as specified by Mullard.

MAINS

510, P2630 (100mA H.T.)	63/-, Post 4/-
P2644 (120mA H.T.)	88/3, Post 4/6
3-3, P2631	40/9, Post 3/6
Seven Watt Stereo, P2631	85/8, Post 4/-
Three Valve Stereo, P2930	47/6, Post 3/6

OUTPUT

510, P2629 (pentode 6,000 and 8,000 load)	55/-, Post 3/6
P2642 (UL, 43% taps, 8k load)	62/3, Post 3/6
P2943 (UL, 20% taps, 6k load)	55/-, Post 3/6
3-3, P2641	34/-, Post 2/9
Seven Watt Stereo, P2932	47/8, Post 3/-
Three Valve Stereo, P2928 (not shrouded)	18/6, Post 2/9

● ILLUSTRATED LISTS

Illustrated price lists are available free on Loudspeakers, Gramophone Equipment, Martin Audio Kits and Test Equipment. Please send 4d. stamp for postage.

● MARTIN AUDIO KITS

Complete transistorised Hi-Fi Pre-Amplifier and Main Amplifier comprising Unit 1, (Five-way input selector), Unit 4 (Pre-Amp. with volume, bass and treble controls), Unit 7 (10 watt Main Amplifier, 15 ohm output), Unit 8 (Power Unit) and smart plastic Enclosure. All units are assembled and tested and the constructor has only to link the various units together. Full instructions supplied. Cash Price £15.8.0. Credit terms. Deposit £3.2.0 and 12 monthly payments of £1.3.0. Total Credit Price £16.18.0. Stereo and other Mono Units available. Full list free on request.

● MARTIN FM TUNER KIT

Transistorised FM Tuner Kit for use with the above Martin Audio Kit and most other Amplifiers. Supplied ready assembled in unit form and tested. The constructor has only to link together and mount the units. Full instructions supplied. Cash Price £12.17.6. Credit terms. Deposit £2.11.8 and 12 monthly payments of 19/4. Total Credit Price £14.3.6.

● LOUSPEAKERS

	Cash Price	Deposit	Credit Terms	
			Monthly Payments	Total Credit
GOODMANS Axiom 201 12in. 15 watts.	£11. 8.9	£2. 5.9	12 of 17/4	£12.13.9
GOODMANS Axiom 10 10in. 10 watts.	£6.12.4	£1.12.4	6 of 20/-	£7.12.4
GOODMANS Axiote 8 8in. 6 watts.	£5.10.11	£1. 7.11	6 of 17/8	£6.10.11
WBHF1012, 10in. 10 watts	£5. 1.3			
WBHF1016	£8. 1.9	£2. 1.9	6 of 23/4	£9. 1.9
WBHF1016 Major	£10. 7.6	£2. 0.6	12 of 16/-	£11.12.6

● LATEST TEST METERS

All the latest models from current production. Illustrated list available. Credit terms

	Cash Price	Deposit	12 monthly Credit terms	
			Monthly payments	Total Credit
AVO 8, Mk. 3	£24. 0.0	£4.18.0	£1.16.0	£28. 8.0
AVO Multimeter Mk.4	£8.10.0	£1.18.0	14. 9	£10.15.0
Taylor Model 88B	£24.10.0	£4.18.0	£1.16.10	£27. 0.0
Taylor Model 127A	£10.10.0	£2. 3.0	16. 0	£11.15.0
TMK Model 500	£3.19.6	£1.16.6	14. 0	£10. 4.6

All Cash and COD orders are dealt with on day of receipt. Credit orders are subject to only the minimum of delay.

WATTS RADIO (Mail Order) LTD

54 CHURCH STREET,
 WEYBRIDGE, SURREY

Telephone: Weybridge 47556

Please note: Postal business only from this address



AERIAL TUNERS

by R. F. Graham

A TUNER is essential with some aerial systems and optional with others. It may offer some of the following benefits:

- Increased receiver signal strength.
- Proper loading of a transmitter.
- Reduced harmonic output.
- Transformation from an unbalanced (coaxial) circuit to balanced feeders.
- Multi-band working with an aerial otherwise unsuitable.

Use of whips or very short wires. Increased signal strength and proper loading are often a matter of securing an impedance match between aerial or feeder and receiver or between transmitter and aerial or feeder. This is easily arranged for the impedances likely to be encountered.

Reduction of harmonic output may be incidental with the use of the tuner for other purposes or may be sought to alleviate television interference. Transformation from unbalanced to balanced feeders is necessary when working a transmitter pi-output into balanced feeders—that is, open wire tuned or untuned lines and 300Ω, 75Ω and similar twin-lead feeders. The balanced system may also reduce TVI or BCI. The change from twin balanced feeders to coaxial feeder may also be needed for best working of a receiver not having twin or dipole aerial sockets.

For multi-band working with the usual types of aerial a tuner is almost essential. It allows best results from a simple wire.

As the tuner often matches impedances (Z) it is sometimes called a Z -match. In general any tuner can be made to perform satisfactorily with any aerial, receiver and transmitter if the inductance and capacity values are suitable. The construction and components can be varied enormously with no significant change in results.

Fig. 1 shows the method adopted to investigate tuners used with various aeriels and transmitters. The transmitters had pi-output (unbalanced

coaxial) circuits of usual type. A standing wave bridge indicates what is happening between transmitter and tuner but is otherwise often relatively unimportant. The r.f. meter indicates aerial current. A useful field strength indicator is a pick-up aerial very remote from the transmitting aerial with diode rectifier and giving readings through a long, buried feeder, a microammeter being visible from the operating position.

It was generally found that field strength was the same with *any* tuner provided it was correctly adjusted. Also that the standing wave ratio on a short coaxial line from the transmitter to the tuner might have no significance from the point of view of maximum radiated signal strength. (This is expected because the transmitter pi-tank can handle high standing waves.) It was also noted that maximum field strength coincided with maximum aerial current through the r.f. meter provided nothing was done to change the feed point impedance. So tuning for maximum aerial current corresponds to tuning for maximum radiated signal strength.

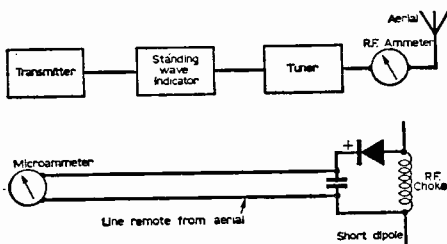


Fig. 1: Equipment to test tuner and coupling efficiency.

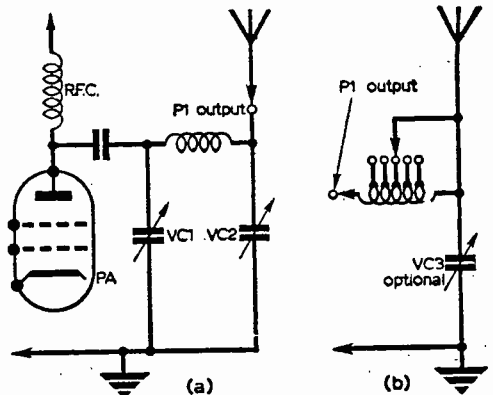


Fig. 2: Operating directly from the transmitter.

Single Wire Feed

The end of the aerial or its download is the feed point with an end-fed aerial. In the simplest possible system the aerial is taken directly to the transmitter pi-tank (Fig. 2a). This allows correct loading of the p.a. only if the aerial presents an impedance within the pi-tank range.

TABLE

Band	Coil	Capacitor	Purpose
160	40 turns. 20swg. $1\frac{1}{2}$ in. dia. Link 11 turns.	300pF	Fig. 7A, 7B.
80	26 turns. 16swg. $2\frac{1}{2}$ in. dia. $3\frac{1}{2}$ in. long. 3-turn link	150pF 150+150pF	Fig. 4, 5A Fig. 5B, 8
40	7 turns each side centre tap of above	150 or 100pF 150+150pF	Fig. 4, 5, 6 Fig. 5B, 8
20/15	3 turns each side centre tap of above	100 or 50pF or 100+100pF	Fig. 4, 5, 6
10	7 turns. 14swg. $1\frac{1}{2}$ in. dia. 2in. long. Link 1 or 2 turns	50pF or 100+100pF	Fig. 4, 5, 6
80	28 turns. 14swg. $4\frac{1}{2}$ in. dia. 4in. long	—	Base loading 10ft. Whip Fig. 7C
80/40/ 20/15/ 10	26 turns. 18swg. $2\frac{1}{2}$ in. dia. $3\frac{1}{2}$ in. long. Clip tap any turn.	150pF optional.	Fig. 2B
80/40/ 20/15	30 turns. 26swg. enam. side by side. $\frac{3}{4}$ in. dia. Tapped at 3, 5, 7, 12 and 20 turns.	150pF	Receiver only Fig. 4, 5, 7B
80/40/ 20/15/ 10	30 turns. 14 swg. $2\frac{1}{2}$ in. dia. Clip tap any turn	Optional in parallel, 150pF for 80, 50pF for 40/10	Whip or short wire. Fig. 5A, 7C
80/40	30 turns. 14swg. 4in. dia. $5\frac{1}{2}$ in. long. Tapped 7 turns each side centre	200+200pF or 100pF	Fig. 5, 6
20/15	14 turns. 14swg. 2in. dia. 3in. long. Tapped 4 turns each side centre	100+100pF or 50pF	Fig. 5, 6

If the aerial is resonant at the working frequency the impedance is resistive because current and voltage are in phase. The impedance $Z=V/I$ (voltage divided by current). Fig. 3 shows the distribution of current and voltage on a $\lambda/2$ (half-wave) aerial. At each end current is small and voltage high. At the centre current is large and voltage small. Therefore the end impedance is high and the centre impedance is low. Typically the end impedance may be some thousands of ohms while the centre impedance is about 70Ω . If the aerial is a $\lambda/2$ -wave fed at X, the feed impedance into which the pi-tank must operate is high. If the aerial is $\lambda/2$ and the feed point is Y, then the impedance is low. At interme-

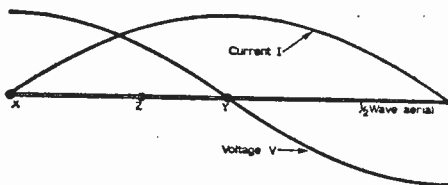


Fig. 3: Distribution of current and voltage on an aerial.

mediate lengths such as Z the impedance has some intermediate value.

When the aerial is not resonant at the working frequency its feed point has capacitive or inductive reactance. If the reactance and impedance values fall within the range of the pi-tank, then the transmitter can be loaded directly into the aerial, Fig. 2a.

The usual pi-output circuit can be adjusted to work into impedances from about 50 to 300 or 500 Ω , actual limits depending on component values. Therefore a transmitter will quite often work into a random length of wire. If the impedance falls outside the range of the pi-tank, the transmitter cannot be loaded correctly, and if the feed impedance is high the voltage across VC2 is large, and it may spark over, especially on modulation peaks.

If difficulty arises with a given length, the addition of a loading coil Fig. 2b may cure this. Tappings allow the feed point impedance to be adjusted until the pi-tank can operate into it successfully. The variable capacitor VC3 (additional to aerial capacity) is optional. It allows fine adjustment with few tappings, coil and capacitor forming an L network.

The use of this type of tuner will allow any

ordinary pi-tank to work into any aerial length from a few feet up to long wires which are many multiples of a $\lambda/2$. It is thus quite a convenient circuit to employ.

Parallel Tuned Circuits

An end-fed aerial or single wire feeder can be worked from a parallel tuned circuit (Fig. 4). L1 is a coupling link, usually two or three turns, connected by coaxial feeder to the pi-tank. L2 is tuned to the working frequency by VC1. Point X or point Y is earthed. The aerial tapping is near earth on L2 for low impedances and far from earth (near the coil top) for high impedances. Almost any impedance can be fed, the tapping being moved from the earthed point a turn or so at a time until correct loading is obtained.

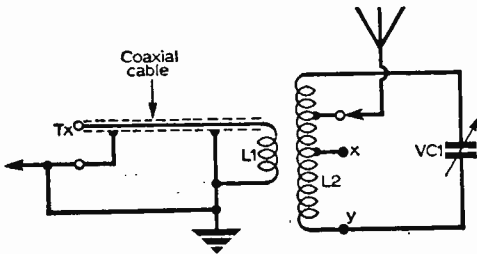


Fig. 4: Parallel tuner for end-fed aerials.

Fig. 4 has the advantage that L1 is grounded to the transmitter chassis and the p.a. h.t. can never reach the aerial, even if the anode blocking capacitor failed. L2 tuned by VC1 gives some suppression of harmonics.

The use of a tapped coil, L1 in Fig. 5a, gives similar results. With medium and high power the voltage across VC1 will be very high. Fig. 5b has the advantage that the voltage across sections of the two-gang capacitor VC2a and VC2b is halved. Point X may be earthed instead of the coil centre tap. If X in Fig. 4 or Fig. 5b is earthed the link is wound on the centre of the main coil.

With receivers the same circuit can be used. Adjustment is then for maximum signal strength. Where the aerial impedance was a bad match for the receiver input impedance at some frequency the tuner may increase signal strength some S points at this frequency.

Single wire feeders include the end of Marconi

($\lambda/4$) and end-fed Hertz ($\lambda/2$) aerials and the download of systems such as the Windom. All random length end-fed aerials also terminate in a single feed point.

Coaxial to Balanced Feeder

Most transmitters have a coaxial output socket. This can be transformed to balanced feeder by using a tuner as in Fig. 6. L1 and L2 can be the same as in Fig. 4 or 5. If the single capacitor VC1 in Fig. 4 is used it should be operated through an insulated extension. The two-gang capacitor (Fig. 6) helps to maintain balance.

The twin feeder may be 75Ω flat twin, 300Ω flat twin or an open wire line. The coil centre tap Y may be earthed or the capacitor at X. The feeder taps are near Y for low impedance and farther from Y for high impedance. With an open wire tuned line having high impedance the feeders may be connected to the ends of the coil.

A $\lambda/2$ centre-fed dipole can be used in this way with a balanced twin feeder instead of having a coaxial feeder from the pi-tank. Harmonic output is reduced and the balanced system may help avoid TVI.

Series Tuning

Low-impedance feed points can be handled by tappings near the earthed point of a parallel tuned coil. For very low impedances the tapping becomes critical and may be awkward. So series tuning is then often employed.

This is quite popular with a $\lambda/4$ Marconi and similar short aerials. The capacitor VC1 in Fig. 7a is in series with the coil L2. L1 is a coupling link from the transmitter. Using a tap on L2 b gives similar results. The aerial is series tuned against ground and a good earth is required for best results.

It will be seen that the circuits in Figs. 4 and 5 can be used for series tuning by placing the capacitor in series with the main coil. Series tuning is often employed on 160m where it is impracticable to erect a $\lambda/2$. Whips and short aerials can be fed by this means. The capacitor may sometimes be omitted, Fig. 7c. The tapping positions are then more critical as there is no other means of adjustment.

When a Zepp or tuned doublet is used and has a low impedance feed point, series tuning is often used (Fig. 8a). The centre tap Y may be earthed. One capacitor is sometimes omitted. Occasionally the coil is divided by cutting the centre turn and a single capacitor is placed here, Fig. 8 (B). This maintains the balanced system with a single capacitor. A coaxial line can also be fed by series tuning (C, Fig. 8).

Other Circuits

Most tuners are derived from the circuits given. The coil may have tappings for multi-band operation. Tests made with an efficient 80m coil, tapped for 15 and 20m, showed no measurable

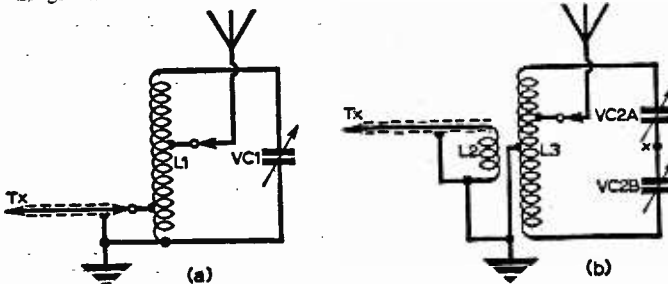


Fig. 5: Alternative systems of coupling and tuning.

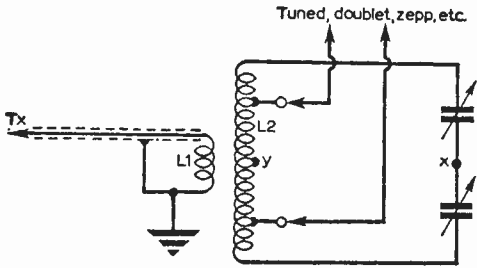


Fig. 6: Coupling to twin feeders.

loss in signal strength compared with a coil wound for 15 and 20m only.

In any of the circuits a capacitor is sometimes included in series with the link so that the reactance of this may be tuned out.

Various particular circuits are seen and aim to avoid band switching or secure some other advantage. One is shown in Fig. 9a. VC1 and VC2 allow series tuning of L2, VC3 being set at minimum. If parallel tuning is required VC3 is used. Another circuit is that at B. VC3 and VC4 are in series across L3, L4 being high impedance at this frequency. When the frequency is that covered by L4, VC4 is effectively in parallel with VC3, the few turns of L3 having little effect. The aim is to cover two or more bands without switching. In general the circuits shown earlier give at least equivalent results.


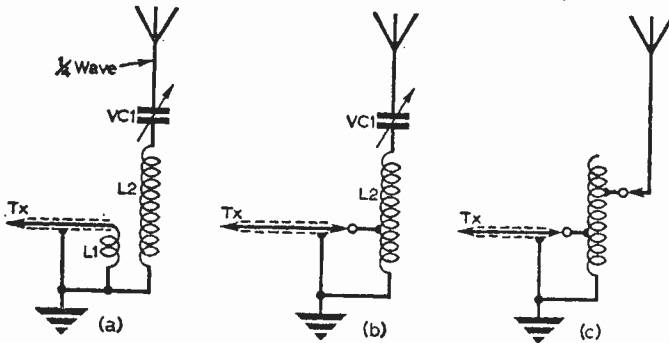


Fig. 7 above): Series tuning for Marconi aerials.

Fig. 8 (below): Circuits using series tuning.

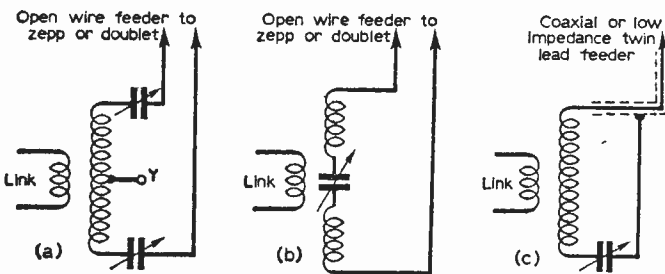

Practical Construction

For receiving only, receiver-type coils and variable capacitors may be used. A 100pF or 200pF air-spaced variable capacitor and coil having about 30 turns of 22 s.w.g. wire will allow coverage of 15 to 80m bands in most cases. It is necessary either to use bare wire with spaced turns or to provide tappings so that clips can be attached at several points. Using the circuit in Fig. 5a one clip may be used for aerial, one for receiver and one to short turns on L1 to allow the required band to be reached by VC1. Other circuits may be used in the same way.

For transmitting with other than low power the coil must be of generous size, wound with stout wire. Many surplus self-supporting and similar coils are satisfactory. An Eddystone ceramic $2\frac{1}{2} \times 5$ in. former is obtainable which takes up to 26 turns of 12 s.w.g. wire and is suitable for 10-80m with power up to 150W. For 160m more turns will be required, but power is low, so a solenoid of cotton or enamel covered wire is often used.

With series tuning receiver-type variable capacitors may be used as voltages are low here. These capacitors spark over with other than low power in parallel tuned circuits, so components with spacing similar to that found in the transmitter pi-tank anode position are necessary. The capacity is often not too important as larger values to hand may be fitted.

Some typical coils and capacitor values are given in the table. Any reasonable s.w.g. and coil size can be satisfactory, the number of turns being adjusted if necessary. Coils should be efficient—self-supporting or on low-loss formers and of large diameter and stout wire.

The simplest method of construction is a flat base-board, carrying coil and variable capacitor. Clips on short leads will allow capacitors to be in series or parallel as wanted. An obvious development is to add a multi-way switch to give band selection. For Fig. 2b a single pole 12-way switch is suitable. Other circuits can use a two-pole, five-way switch for five bands, tappings being soldered to the coil. Components may be housed in any convenient cabinet. For coaxial input a coaxial socket allows the transmitter to be connected, using a short length of 75Ω or similar cable equipped with plugs.

Adjustments

For receiving only, adjustments are directed towards securing the best signal strength. A tuning or signal strength meter should be fitted to the receiver if not present. Adjustments can be

Brand new individually checked and guaranteed

V ALVES

Table listing vacuum tube types, their manufacturers, and equivalent types. Includes entries like AC/HL 4/6, AC/P 4/6, AC/PE 5/5, etc.

Table listing vacuum tube types, their manufacturers, and equivalent types. Includes entries like KRA 30/1, KTC3 22/1, KT 82 8/1, etc.

Table listing vacuum tube types, their manufacturers, and equivalent types. Includes entries like 6L4WA 10/1, 6AB6 6/1, 6AG7 6/1, etc.

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. All U.K. orders below £1, P. & P. 1/- over £1, 2/- over £3, P. & P. free.

MARCONI COMMUNICATION RECEIVERS CR. 150. Frequency coverage 2-60 Mc/s in 5 bands... P.C. RADIO'S mains P.S.U. for above, 90%.

H.R.O. SENIOR TABLE MODEL in excellent, fully checked and tested condition together with set of 8 general coverage coils and mains P.S.U. £28.

ORIGINAL MAINS POWER SUPPLY UNIT FOR H.R.O. RECEIVER, 260/115v. Brand New 65%, P. & P. 5/-.

VERY HIGH CLASS COMMUNICATION RECEIVER TYPE BRT 402E. 150kc/s-385 kc/s., 510 kc/s-30 mc/s. Fully tested £60. Carriage 30/-.

EVERSHED MEGERGER CIRCUIT TESTER. 2 ranges 0 to 1,000Ω, 100Ω to 200,000Ω. With test leads, leather carrying case. Tested £4.19.6. P. & P. 3/6.

PANEL METERS (round) 500mV 3 1/2" DC 32/6 500mV* 3 1/2" DC 35/1 500mA* 2 1/2" DC 22/6 500 microamp 2 1/2" AC 22/6 500 microamp* 2 1/2" DC 19/1 0-500 microamp 2 1/2" DC 22/6 25-0-25 mA 2 1/2" DC 45/1 0-500-1500 mA 3" DC 29/1 0-500 mV 3 1/2" DC 32/6 0-15 V 2 1/2" DC 17/6 0-50 V 2" DC 28/1 0-150 V 2 1/2" AC 24/1

2 KW ULTRASONIC GENERATOR together with power supply unit for 200-250v. A.C. Complete two chassis with interconnecting cables. Frequency 37 to 43 kc/s adjusted by fine control. Peak output 2kw, average output 500w. Completely new with valves and manuals £65.

VARIOMETER for No. 19 set, 17/6, P. & P. 3/-.

ARR88 RECEIVERS. Fully reconditioned, £55, rebuilt models £85. Carriage paid U.K.

TELEPHONE HANDSET. Standard G.P.O. type, new 12/-, P. & P. 2/-.

NEW DHR. HIGH-RESISTANCE HEADPHONES. 14/-. P. & P. 1/6.

WIRELESS SET No. 52 (CANADIAN) Complete station consisting of Transmitter. Receiver, supply unit for 12 V. All contained in special carrier. 1.75-16 mc/s in 3 bands. 813 as output valve.

P.G. RADIO LTD

170 GOLDHAWK ROAD, W.12.

Shepherd's Bush 4946

Open 9.5-30 p.m. Thursday 9-1 p.m.

THERMAL PLUS MECHANICAL CIRCUIT BREAKER FOR A.C. & D.C. Current 1 amp. Protects against shorts (instantaneous cut-out...)

SEMI-AUTOMATIC BATTERY CHARGER "Baby Esstron". Initial charging rate 3-5 amps DC automatically reducing to 1-5 or lower (depending on specific gravity of battery acid).


ARR88 INSTRUCTION MANUALS, 20/-. P. & P. 2/6.

TELEPHONE HANDSET. Standard G.P.O. type, new 12/-, P. & P. 2/-.

NEW DHR. HIGH-RESISTANCE HEADPHONES. 14/-. P. & P. 1/6.

WIRELESS SET No. 52 (CANADIAN) Complete station consisting of Transmitter. Receiver, supply unit for 12 V. All contained in special carrier. 1.75-16 mc/s in 3 bands. 813 as output valve.

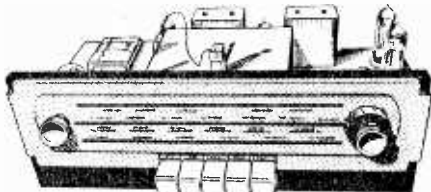BRAND NEW AM FM (V.H.F.) RADIO GRAM CHASSIS AT £13.13.0 (Carriage Paid)



Chassis size 15 x 8 1/2 x 3 1/2 in. high. New manufacture. Dial 1 1/4 x 4 in. in 2 colours. Pre-amplifier available. 200-250V. A.C. only. Pick-up. Ext. Speaker. Ae. D. and Dipole Sockets. Five push-buttons—OFF, L.W., M.W., F.M., and Gram. Aligned and tested. O.P. Transformer. Tone control. 1000-1500 Mc. 2000-350 Mc. 80-98 Mcs. Valves 1Z80 rect.; EC115, 1P9, KA150, EL4, RU35, 3-ohm speaker required. KITS, 1P9, KA150, EL4, RU35 to purchasers of this chassis. 9 x 6 in. ELLIPTICAL SPEAKER 20/- to purchasers of this chassis. TERMS: (Chassis) £3.10.0 down and 5 monthly payments of £2.4.0. Cheap Room Dipole for V.H.F. 12/6. Feeder 6d. per yard. ALTERNATIVE DESIGN. Similar to above chassis. With addition of shortwave 6-17 Mc/s. Price £25.15.0 (curr. paid). TERMS: £3.10.0 down and 6 monthly payments of £2.4.0. Total H.P. price £16.14.0. Circuit diagram 2/6. Carriage to N. Ireland 20/- extra.

2-VALVE GRAMOPHONE AMPLIFIER Price 37/6 (P. & 2/6)

Overall size 4" wide x 5" high x 2 1/4". Volume and tone controls. Mains lead. Screened lead input. With output transformer for 3-ohm. For series connection to Garrard and B.E. Autochangers and Players, having 90v. tapping. Valves UY85 and UCL82. Can also be supplied on fabric covered board with mains transformer and 6" x 4" speaker. Valves EZ80 and ECL82 at 55/- (P. & P. 6/-). 3-valve Gram. Amp. Board 14" x 7 1/2" x 2 1/4" overall. UY85, UOC86 and UL84 with Speaker 7" x 4". Price 70/- (P. & P. 6/-).

BATTERY ELIMINATOR


For 4 low consumption valves (90 range) 90v. 10mA and 1.4v. 125mA, 42/6. (4/- post), 200-250V. A.C. Also for 250 mA, 1.4v. and 90v. 15 mA at same price. Two units each 31" x 3 1/2" x 1 1/2".

TAPE RECORDER AMPLIFIER

Fully built. Front panel 12 1/2 x 3 in. Chassis size 10 1/2 x 4 in. Valves EP88, EC083 and 2EL84. Controls (1) Mic. Vol. (2) Tuner/P.U. Vol. (3) Play back or monitor, (4) Tone, 2 jack sockets for Tuner/P.U. and Mic-switch for superimpose. Separate power pack containing trans. and rectifier. For Coliaro studio deck only. Price £3.14.0 (6/- P. & P.)


SELF-POWERED V.H.F. TUNER CHASSIS

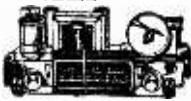Covering 88-95 Mc/s. Dims. 8 x 6 x 6 in. high. Valves EC083, EABC80 and 2-EP88's with metal rectifier. Mains 2-EP88's with metal rectifier. Mains transformer. Fully wind and tested. ONLY £3.17.6 (curr. p.d.). Room dipole 12/6. Feeder 6d. per yard.



8 WATT PUSH-PULL O.P. AMPLIFIER £5.5.0 (6/- Carr.)

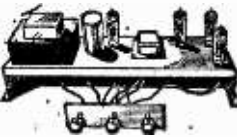200-240 A.C. mains. Bass, treble and v.o. controls. EZ80, EC083 and 2-EL84. Chassis 12 x 3 1/2 x 3 1/2 in. With o.p. trans. for 2-ohm speaker. Front panel (normally screwed to chassis) may be removed and used as flying panel. With Cream/Black control panel whole length of front chassis.



4-SPEED AUTOCHANGERS

GARRARD AUTOSLIM	£5.10.0
GARRARD AUTOSLIM STEREO	£6.0.0
GARRARD A.T.6	£10.0.0
GARRARD A.T.6 STEREO	£12.10.0
GARRARD 3000	£9.19.6
GARRARD 3000 STEREO	£9.9.0

Carr. 5/- each

TRANSISTOR SUBSTITUTION HANDBOOK

New 6th Edition by S.A.M.S. British, American, Jap. etc. 12/6. P. & P. 1/-.
Amateur Radio Call Book, new 1966 ed. by R.S.G.B. 6/-, P. & P. 8d.
Servicing Electronic Organs by Pittman. 30/-, P. & P. 1/6.
Troubleshooting with Test Meters (VOM and VTVM) by Middleton. 21/-, P. & P. 1/-.
Solid State Power Supplies and Converters by Lytel. 20/-, P. & P. 1/-.
101 Ways to use your Oscilloscope by Middleton. 21/-, P. & P. 1/-.
Transistor Electronic Organs for the Amateur by Douglas. 18/-, P. & P. 1/-.
Where possible 24 hours service guaranteed

UNIVERSAL BOOK CO.
12 LITTLE NEWPORT STREET,
LONDON, W.C.2
(adjoining Lisle Street)

WHEATSTONE BRIDGE KIT Set of 18 W.W. 1% Resistors and 18 switches. Measures 10 to 1.1M Ω With circuit, instructions, 67/6.

PRECISION WIREWOUND RESISTORS 1 Watt. 10 to 5K 1% 3/-; to 20K 4/6; 1% add 8d. Your value wound to order.

HIGH STABILITY RESISTORS 1% 1W, 2/- each. Full range 10 Ω to 10M Ω , plus many special multimeter values.


NOUGHTS AND CROSSES MACHINE Uses switches and lamps only, cannot be beaten. Circuit, wiring diagram, instructions, 3/6.

BINARY ADDER/SUBTRACTOR Another switch and lamp design to make a demonstration model, 3/6.

MULTIMETERS EP10K, 10K Ω /V, 67/6 post 2/-; EP30K, 30K Ω /V, 105/- post 2/6; EP30K, 50K Ω /V, 145/- post 2/6. Avro Multimotor £9.10.0 post free.

PLANET INSTRUMENT CO.
25 (W) Dominion Avenue, Leeds 7

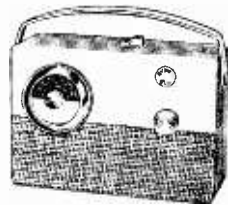The SUPER 6 LONG & MEDIUM WAVE TRANSISTOR RADIO



A quality radio available as a kit or ready built. The sparkling performance and superb finish of the completed receiver give you value equivalent to a £12, 12, 0 commutator model.

★ All new parts. ★ 6 transistors and diode. ★ 350mV output. ★ Superhet circuit. Ferrite rod aerial. ★ Weymouth Radio printed circuit board
★ Component positions and references printed on back of board. ★ Nicely styled wooden cabinet. 11 x 7 1/2 x 2 1/2 in. ★ Vinyl covered in various colours. ★ 6 x 4 in. speaker giving good bass and treble response. ★ Full instruction booklet 2/6. Free with kit. ★ I.F. frequency 470 kc/s. ★ Lining up service u required. ★ All parts supplied separately. Write for list, S.A.F. please. ★ 9v. battery required. VT9 or P.P.9 (8.9 with kit).
PLS 3/- POST COMPLETE KIT ONLY £4.0.0
OR FULLY BUILT 28.17.6 Tax & Carr. Paid

V.H.F. Pre-amplifier with high signal-noise ratio and gain of at least 3:1 under average fringe area conditions. Metal container 3 1/2 x 3 1/2 x 1 1/2 in. high, with strap for carry, top or skirting fixing. 9 volt battery operated, using transistor AF114. Covers all British and some continental stations. 8 to 108 Mc/s. Order with confidence of improved reception. Price 32/6 (3/- P. & P.)

TRANSISTORS

Packet of 3 coded RF transistors (equivalent of OC44/5) 7/6 post paid. Set of 6 transistors and diode with circuit diagram. Newly packed in foam-lined box: useful for presentation. 15/- post paid.



4 TRANSISTOR MINIATURE PUSH-PULL AUDIO AMPLIFIER HIGH IMPEDANCE

PRINTED CIRCUIT. 4 in. x 2 1/2 in. x 1 1/2 in. over transformers. Output for 3-ohm speaker. Suitable for microphone, record player and intercom. 9 volt battery required. Frequency range 100 cps. to 25 Kcps. Push-pull output class B. Instruction sheet provided. Fully wired ready for use. Three types, 200mV 35/-; 500mV 41/-; 1.2W 57/6. (P. & P. 2/6 each).

AMERICAN BRAND RECORDING TAPES FULLY GUARANTEED AT RECORD LOW PRICES

MYLAR BASE				
7in. Stand. play, 1,200ft.	19/6		
7in. Long play, 1,800ft.	19/6		
5in. Double play, 1,200ft.	15/-		
5 1/2 in. Double play, 1,800ft.	22/6		
7in. Double play, 2,400ft.	25/-		
5in. Triple play, 450ft. (Plain white boxes)	12/6		
5 1/2 in. Triple play, 600ft. (Plain white boxes)	14/-		
4in. Triple play, 900ft. (Plain white boxes)	22/6		
5in. Triple play, 1,800ft. (Plain white boxes)	42/6		
7in. Triple play, 3,600ft. (Unboxed)	76/-		
ACETATE BASE				
5in. Stand. play, 600ft.	8/-		
7in. Stand. play, 1,200ft.	11/-		
5in. Long play, 900ft.	10/-		
5 1/2 in. Long play, 1,200ft.	12/6		
7in. Long play, 1,800ft.	15/-		
			MESSAGE TAPES	
			5in. Stand. play, 150ft.	3/6
			5in. Long play, 225ft.	4/11
			5in. Double play, 300ft.	7/6

Postage 1/- per reel (4 or more post free)

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.
(2 mins. from Station and Buses). Aldershot 22240
CLOSED WEDNESDAY AFTERNOON
CATALOGUE 6d.
Regret overseas orders cannot be executed

N.S. KITS

No Soldering — No Drilling

High performance Medium Wave Radio you can really build yourself. Unique kits that really work with add-on kits to increase power and range.

Kit No. NS.IVM, 47/6
Postage & Packing, 3/3

Full details sent on receipt of stamped addressed envelope.

Circuit diagrams and details send 2/6. (deductible on order).

G. A. TAYLOR LTD.
21 HYDE ROAD, DENTON
MANCHESTER

on a strong signal in the band, the tuner then being left alone. If tappings are marked or selected with a switch this allows easy resetting for a band in conjunction with a variable capacitor with numbered dial.

The benefit secured from a tuner may be

be adjusted for maximum aerial current on the r.f. meter if fitted. If a field strength meter is available this naturally offers a means of tuning up.

It will probably be found that the transmitter pi-tank can be operated into a wide range of impedances which may be available by different adjustments of the tuner. All these may result in a similar radiated signal, though some produce high standing waves on a coaxial line from transmitter to tuner. If this line is short losses are negligible and the transmitter pi-tank can return the reflected power as if operating directly into an aerial. On these grounds the presence of a low standing wave ratio in the position in Fig. 1 indicates power is flowing from the transmitter to the tuner and aerial; but a high standing wave ratio does not mean there is necessarily any measurable loss in radiated signal strength.

The readings of the r.f. meter will depend on frequency, aerial and power and will thus change from one band to another or if modifications are made to the aerial-earth system. However, the meter is useful to check that usual output is obtained and because more current here corresponds to more power radiated provided frequency and aerial-earth system are unchanged.

With average wire aerials the length in feet for a $\lambda/2$ at any particular frequency is:

$$\frac{468}{\text{Mc/s.}}$$

The length for a $\lambda/4$ is:

$$\frac{234}{\text{Mc/s.}}$$

It is thus easy to calculate the length needed for a $\lambda/2$ or $\lambda/4$ aerial for any band. ■

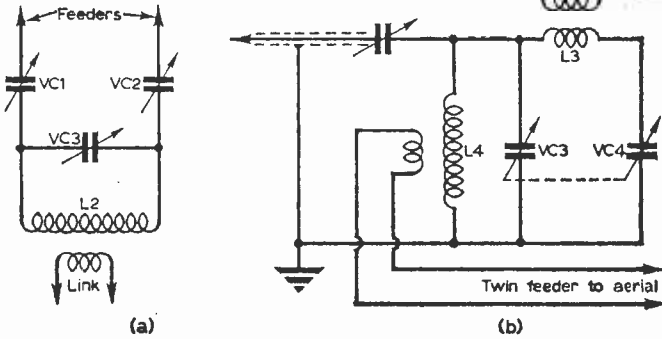


Fig. 9: Two multi-band systems.

considerable if bad mismatching otherwise exists. Numerous communications receivers have 75Ω coaxial input and, using a circuit like that in Fig. 4, can give a great increase in signal strength with a $\lambda/2$ end-fed aerial. When using the receiver with a Zepp or tuned doublet the tuner is practically essential for maximum results.

With a transmitter several methods of adjustment are possible. One is to load the transmitter into a 75Ω carbon resistor of sufficient power rating, then leave the transmitter tuning as nearly as possible untouched while setting the aerial tuner. Another method, useful with a receiver having 75Ω input, is to adjust the tuner for best receiver signal strength with some station heard in the band, then to load the transmitter into the tuner with its pi-output controls. The same tuner may be in use for both transmission and reception.

Another method is to tune for minimum reflected power, using a standing wave indicator as in Fig. 1. Or the transmitter and tuner may

STILL TIME TO SEND PRACTICAL WIRELESS FOR CHRISTMAS

It's still not too late to send fellow radio enthusiasts a Year's Subscription to PRACTICAL WIRELESS for Christmas... a gift that will renew your good wishes month after month throughout 1966, and bring them repeated help and pleasure.

But hurry! You must send now to make sure that first copies arrive in time for Christmas. Simply send your friends' names and addresses, together with your own and remittance to cover each subscription to The Subscription Manager (G.2), PRACTICAL WIRELESS, Tower House, Southampton Street, London, W.C.2. An attractive Christmas Greeting Card will be sent in your name to announce each gift.

RATES (INCLUDING POSTAGE) FOR ONE YEAR (12 ISSUES): UK AND OVERSEAS £1 9s; USA \$4.25.


To make sure of your own copy why not place a regular order with your newsagent?

PRACTICAL WIRELESS BINDERS

The Practical Wireless Easi-binder is designed to hold normally 12 issues, but it will accommodate two additional copies quite comfortably.

A new version of the Easi-binder with a special pocket for storing blueprints and data sheets is now available. The price is 11/6d inclusive of postage.

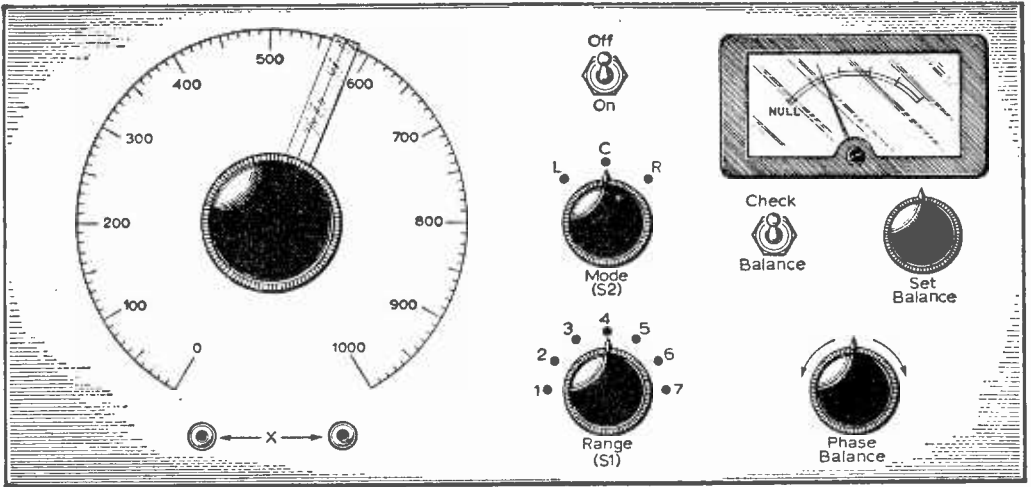Order your binder from: Binding Department, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.



A Transistorised L.C.R. Bridge – Part Two

By Mike Fisher

CONSTRUCTION of the basic bridge circuitry is quite straightforward but care should be taken to keep the connecting leads fairly short and a reasonably heavy gauge wire should be used. The inevitable resistance of the circuit wiring will necessitate the adjustment of the 1Ω standard resistor on test. The $0.1\mu\text{F}$ standard capacitor will be difficult to obtain to a high standard of accuracy but this snag can be overcome by using a normal type of component and adjusting its value by wiring additional capacitors in parallel on test. The procedure for adjusting these two

components is as follows:

1Ω resistor. Build the complete bridge unit and calibrate the main balance control by its resistance against a suitable test instrument. If no test instrument is available the dial can be set up by placing 1% test resistors across the "X" terminals and adjusting the bridge to balance. The scale is then marked at the balance point with the appropriate value. This calibration is best carried out on the 0-1,000 Ω to 0-100k Ω ranges. When the dial calibration is complete connect a 1% or better resistor of value between 2 and 10 Ω across

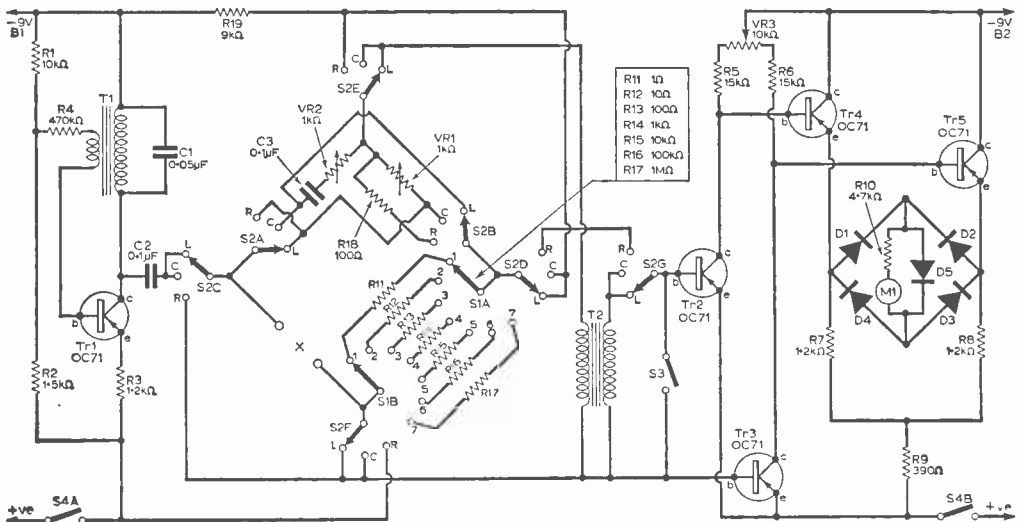


Fig. 10: Circuit diagram of the complete unit.

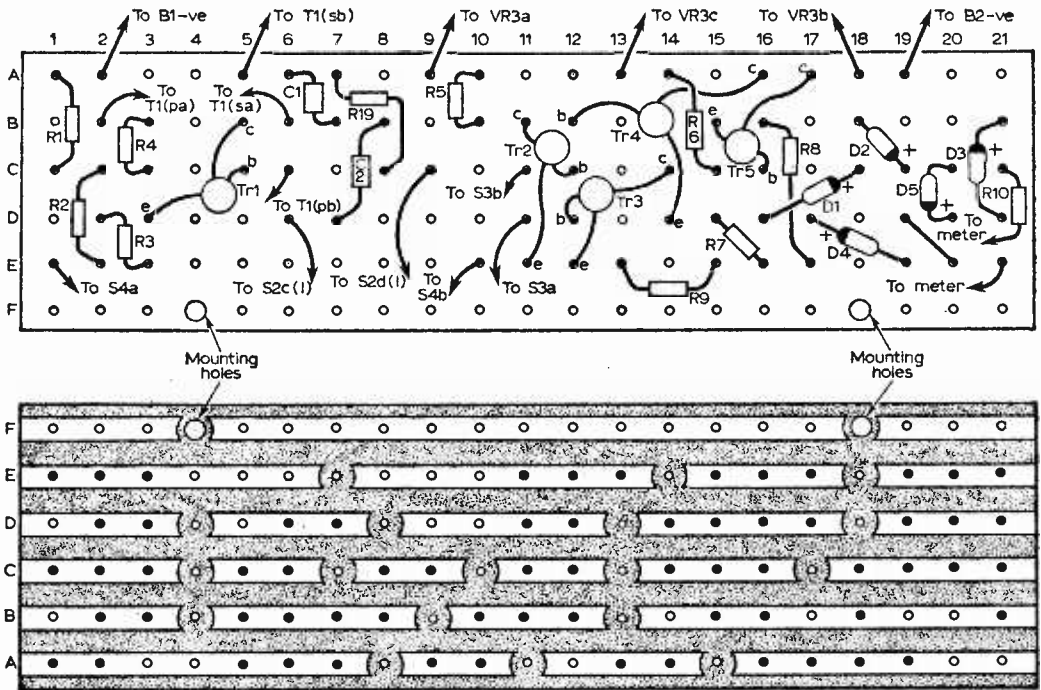


Fig. 11: Component layout of Veroboard circuit.

the "X" terminals, set the range switch to the 0-10Ω range and set the dial to the point at which balance *should* be obtained. The value of the 1Ω standard resistor is then adjusted until a true balance is obtained at this point.

0.1μF standard capacitor. A close-tolerance test capacitor, preferably of either 0.05 or 0.005μF value, is connected across the "X" terminals and the instrument switched to the required range. The dial is set to the point at which balance should be obtained, as above, and the standard capacitor is then adjusted until a balance is obtained at this point. Calibration, etc., is now complete.

The detector circuit. Component values and layout are not critical. OC71 transistors were used for the simple reason that they were at hand but it will probably be found that OC70, etc., types will work quite well in the circuit.

The oscillator circuit. Considerable variation of component values and working voltages is permissible with this circuit; it will continue to function at voltages of less than 1.5V.

The ratio of the transformer seems to be of little real importance. 3:1 ratio was used on the test circuit but it was found that a far too powerful feedback signal resulted and the 470kΩ resistor to the base of the transistor had to be introduced to stop squegging which resulted. The

value of this resistor should be adjusted as follows to suit the particular transformer used (it will probably be found that the circuit will still work even if a transformer with a ratio of 40:1 is used).

Wire up the circuit, leaving the 470kΩ resistor shorted out, and connect the 0.05μF capacitor across the transformer primary (connected as the collector load). A pair of headphones is now connected via a blocking capacitor to the transistor collector and the negative rail. A strong audio signal should be heard. This signal will probably seem to be fairly pure in tone but this may be a delusion caused by the high volume level. The tone frequency should be about 1kc/s; if not the frequency may be adjusted by changing the value of the capacitor in parallel with the primary winding. When this adjustment has been completed a fairly high value resistor should be connected in series with the phones, resulting in a very low volume level to them. It will probably be found that at this low level the frequency of the signal seems to be considerably different from that formerly heard; in fact it may even sound like a motor-boat running at low speed. This is symptomatic of "squegging", caused by too high a feedback factor. The short across the 470kΩ resistor should now be removed. Should oscillation now cease completely reduce the value of the resistor until oscillation starts again. The resistor effec-

tively reduces the magnitude of feedback and it will be found that as the resistor value is increased so the squegging frequently rises until finally, when the correct degree of feedback has been obtained, only the pure tone of the oscillator will remain. It may be necessary to readjust the frequency of oscillation during the setting up.

If it is found to be necessary to use a very high value of R4, such as the 470kΩ shown in Fig. 7, it will be found that the base bias chain, R1 and R2, will have no effect on circuit operation. R1 and R2 can therefore be removed from the circuit. Inspection of the waveform on a scope will show, in the above case, that distortion is taking place; as long as squegging is not taking place, however, the oscillator may still be used to energise the bridge.

It is felt that ideally the transformer T1 should have a ratio of about 20:1 if a pure sinewave is to be obtained from the circuit.

It should be noted that if the above adjustments are not made poor detector response and faulty balance reading may be obtained.

A suitable front panel layout for the instrument is shown in the heading and the final circuit of the complete instrument.

Components List

The 50μA meter is available from Radio and TV Components (Acton) Ltd., price 25s.

If difficulty is experienced in obtaining S1, the two-pole, seven-way switch, an alternative would be a two-pole, ten-way type modified as follows: Drill and tap a 6BA hole in the switch front plate in such a position as to fall between the seventh and eighth position locator recesses. A short 6BA screw can then be inserted in the hole and will act as a stop, reducing the number of available switch positions to seven.

S2 the seven-pole three-way switch, may be adapted in similar fashion from an eight-pole, four-way switch, available from Radio Component Specialists, of 337 Whitehorse Road, West Croydon, price 6s. 6d. Alternatively a Wearite 12-pole, three-way switch, price 7s. 6d. may be used with the five unwanted poles left blank. This switch can be obtained from L. Wilkinson (Croydon) Ltd., Longley House, Longley Road, Croydon, Surrey.


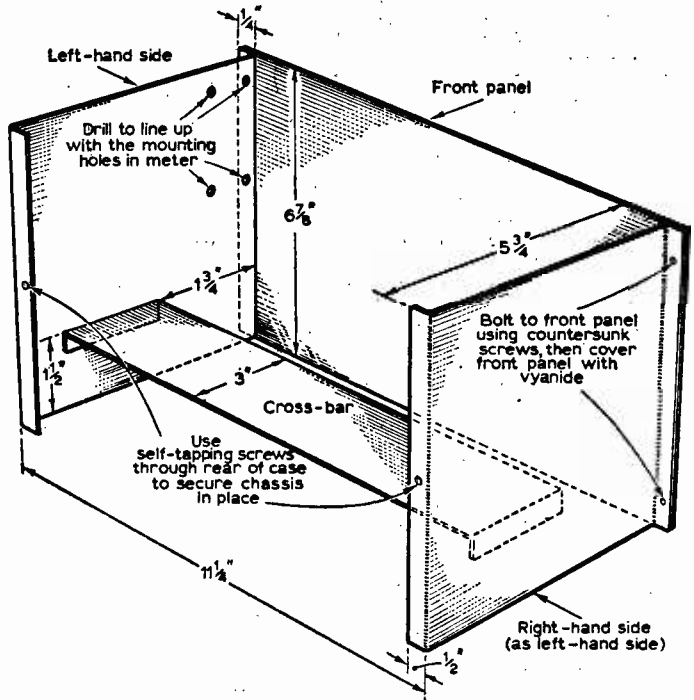


Fig. 12 (above): General layout of metalwork.

Fig. 13 (below): Wiring diagram of front panel etc.

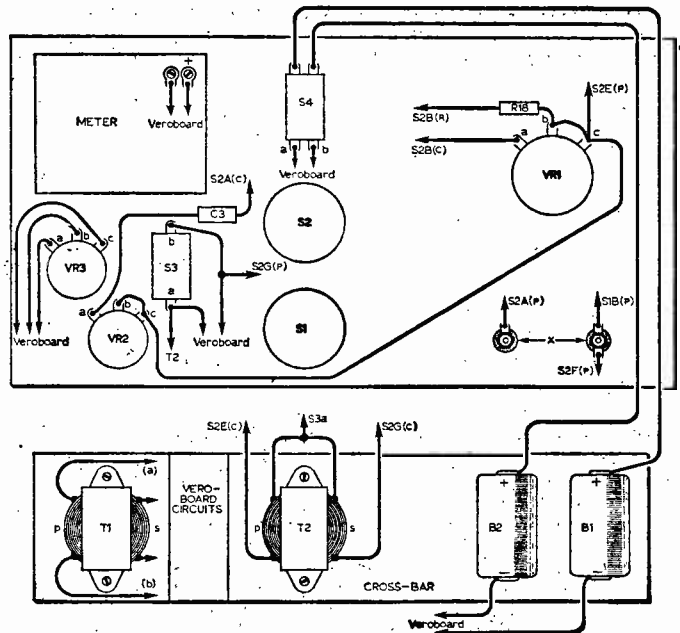


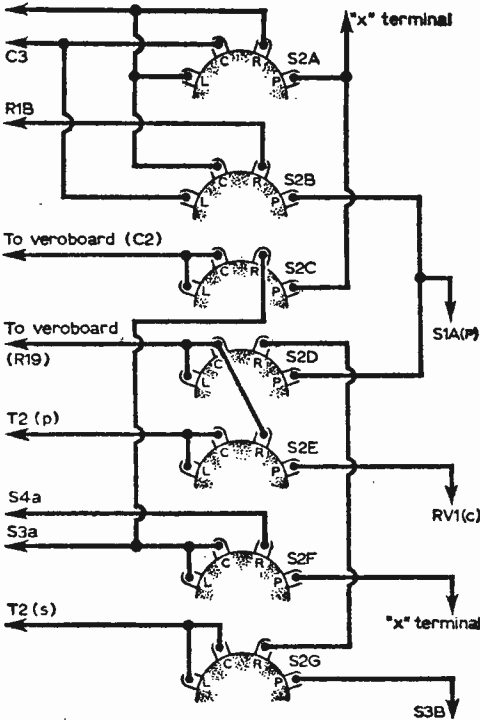


Fig. 14: Wiring of S2 (mode).

Fig. 15: Wiring of S1 (range).

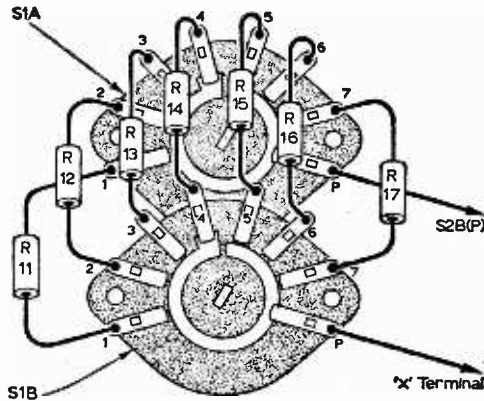

Position of S1 (Fig. 10)	L	Range C	R
1	0-100μH	0-100μF	0-10Ω
2	0-1mH	0-10μF	0-100Ω
3	0-10mH	0-1μF	0-1kΩ
4	0-100mH	0-0.1μF	0-10kΩ
5	0-1H	0-0.01μF	0-100kΩ
6	0-10H	0-1000pF	0-1MΩ
7	1-100H	0-100pF	0-10MΩ

Front Panel and Chassis Assembly

The prototype instrument was designed, from the mechanical point of view, to fit into an instrument case that was available at the time and no effort was made to miniaturise. While it is unlikely that the same mechanical dimensions will be used in any instrument built by the reader the general constructional details used in the proto-

COMPONENTS LIST

Resistors

R1 10kΩ 10%	R11 1Ω	} see text
R2 1.5kΩ 10%	R12 10Ω	
R3 1.2kΩ 10%	R13 100Ω	
R4 470kΩ see text	R14 1kΩ	
R5 15kΩ 10%	R15 10kΩ	
R6 15kΩ 10%	R16 100kΩ	
R7 1.2kΩ 10%	R17 1MΩ	
R8 1.2kΩ 10%	R18 100Ω	
R9 390Ω 10%	R19 9kΩ 10%	
R10 4.7kΩ 20%		

All resistors 1/8W minimum

Potentiometers:

VR1 1kΩ w/w linear 1%	} large diameter
VR2 1kΩ w/w linear 1%	
VR3 10kΩ Carbon Linear	

Capacitors:

C1 0.05μF (see text)
C2 0.1μF
C3 0.1μF 1% (see text)

Semiconductors:

Tr1	} Red Spot, OC71, etc.	D1	} Any Germanium Diode
Tr2		D2	
Tr3		D3	
Tr4		D4	
Tr5		D5	

Miscellaneous:

T1 20:1 to 3:1 (see text)	} Veroboard 3 1/4 x 1in.
T2 1:1	
S1 2P 7W	
S2 7P 3W	
S3 1P 2W self return	
S4 2P 2W	
M1 0-50μA	
B1 9v	} Separate batteries must be used
B2 9v	

type may be of interest.

The dimensions of the front panel are 11 1/4 x 6 3/8 in. This panel may be cut from sheet aluminium, plywood or hardboard.

The two side members are cut from aluminium, and bolted to the front panel as shown in Fig. 12. The securing screws should be countersunk flush into the front panel. The right-hand side member has the meter bolted to it as shown. Clinch nuts are secured to the rear flanges of the side members and holes cut in the rear of the case to line up with them; the chassis can then be held secure in the case by screws at the rear, leaving the front panel free from unsightly screws.

Resistors R11 to R17 should be soldered directly to the contacts of switch S1.

HIGH WATTAGE LOADS

by C. L. Jones, B.Sc.

THE most common types of resistors used in electronics are designed to dissipate a comparatively small quantity of energy. Occasionally higher voltage components are required, for example as "loads" when testing equipment. The problem resolves itself into two categories—that of comparatively small currents at high voltages and that of high current at low voltages.

Low Current—High Voltage

The original need for such a load occurred when the voltage-current curve for a power pack of maximum power output, about 30W (300V at 100mA), was required. A rheostat to cope with this would be expensive and so the circuit given in Fig. 1 was used.

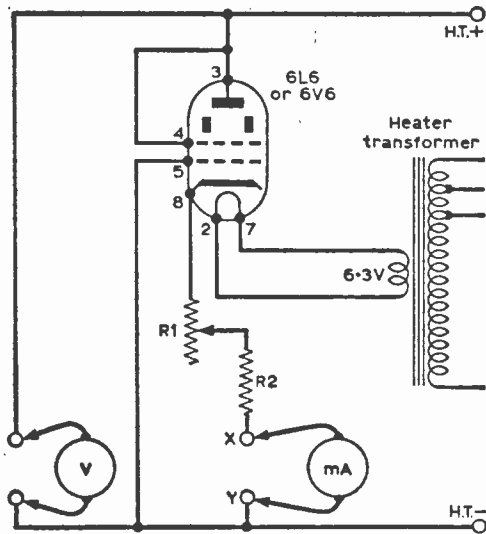


Fig. 1: This circuit eliminates the use of a rheostat. The transformer is optional as heater supplies can be obtained from the transformer under test.

Almost any output valve can be used but the original rig employed a 6L6 which had been discarded because of a broken spigot. The current taken by the valve is varied by means of R1, the fixed resistor R2 limiting the current when R1 is at minimum.

The values of R1 and R2 will depend on the use to which the circuit is put. R1 limits the current when R2 is at minimum. When assessing the value of R2 the following points should be borne in mind:

- (a) If R2 is too low then the minimum current taken by the valve is high.
- (b) If R2 is too high adjustment of the current is difficult, especially when the current is high.

The maximum current for the valve has been exceeded by as much as 50% but only for short periods. Since valves which are past their best are used the risk is felt to be justified. Readings can be taken very quickly so that prolonged overloading can be avoided.

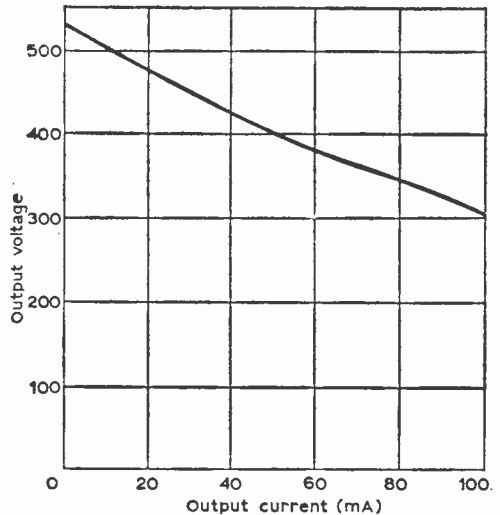


Fig. 2: The graph obtained by using the circuit of Fig. 1.

Fig. 2 shows a graph obtained using the circuit. It could be used to provide data to stabilise the power pack. The power pack in question is used with different pieces of test equipment which are used too infrequently to make it worth while providing each with its own power supply. The test instruments have widely different h.t. requirements and the graph is used to find a suitable resistor to put in series with the supply. Thus each piece of equipment has a built-in h.t. dropper and a decoupling capacitor which enables it to be plugged directly into the power pack and provides additional smoothing.

A second unit has been built employing a 6V6 to test the regulation of a power pack designed to operate an amplifier and a tuner, the latter being switched off when the amplifier is used for records. The effect of switching one load off or on can be determined by setting R2 so that the valve takes

the same current as the equipment it is simulating. The circuit can be wired up when required or built into a small self-contained unit. The transformer shown in Fig. 1 is optional as heater supplies can be taken from the transformer under test.

Multi-range meters can be used to measure the current and voltage. They provide a "fixed" load; R2 can be adjusted until the millimeter registers the required current, then the meter can be replaced by a "short" across X and Y.

Details of R1 and R2 are given below but should only be used as a rough guide as the exact current depends on the h.t. voltage and individual requirements may enable more suitable values to be used. The last two columns were determined using the power pack from which Fig. 2 was drawn.

	R1	R2	Min. Current	Max. Current
6V6	100Ω	10kΩ	6mA	130mA
6V6	500Ω	10kΩ	6mA	60mA

The maximum power dissipated by R2 in the case of 6V6 is just over 1W. An old standard size (1½ in. diameter) wire-wound potentiometer should be used rather than the more modern miniature type.

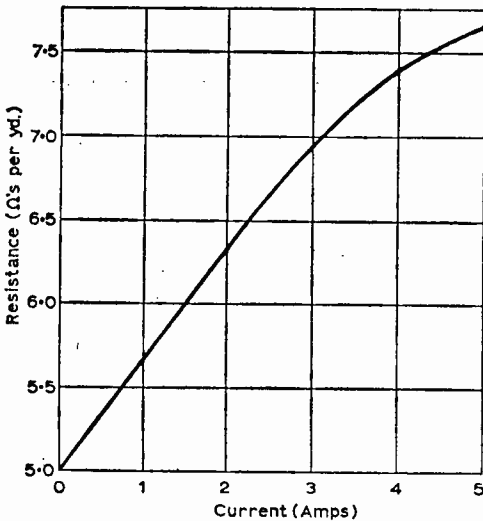


Fig. 3: Graph showing how resistance of metallic conductors increases with rise in temperature.

High Current—Low Voltage

Testing power amplifiers can be a noisy business if the outputs are fed into a loudspeaker, so that dummy loads are required if the family or neighbours are not to be disturbed. Further, if feedback loops are connected the wrong way round sensitive speakers can be damaged, so that some less delicate load is required. Resistors as described below have also been used in series with a power supply when charging small accumulators at a constant current.

There are several different types of "resistance" wire available, each with properties suited to

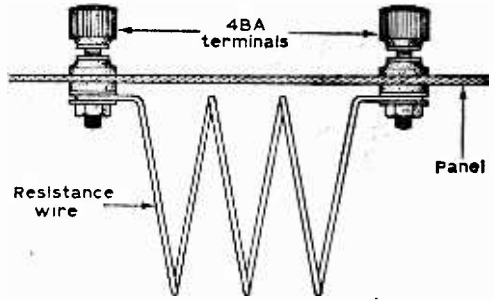


Fig. 4: Method of connecting resistance wire.

particular applications. Convenient sources of resistance wire are electric fire elements, especially the type obtained as tight coils, which are then stretched backwards and forwards over a rectangular ceramic former. A 1kW element of this type is made from about 10yd of 25 s.w.g. "nichrome" wire. This is a nickel-chromium alloy which can stand up to high temperatures. The resistance of this particular gauge of wire is almost exactly 5Ω per yard at room temperature. Thus the length for any particular resistance is easily calculated.

The resistance of metallic conductors increases with increase in temperature and a sample has been tested to determine the heating effect of current passing through it. The results are shown in Fig. 3. The length of wire can be adjusted to give correct resistance at any particular current. For these tests the wire was kept stretched out horizontally and it should be remembered that if it is coiled tightly heating will increase.


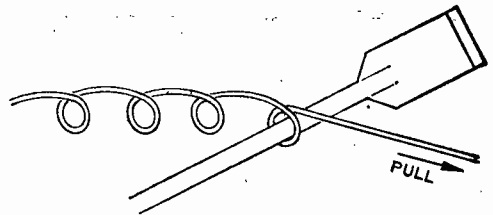


Fig. 5: Method of eliminating "kinks" in wire.

The temperature of the uncoiled wire rises above the melting point of solder with currents as low as 2A, so that connections are best made as shown in Fig. 4. In any case it is difficult to solder this type of wire. The ends of the wire can be clamped between washers under 4BA brass terminals; these help to dissipate the heat generated in the wire. Large diameter coils should be made and if housed in a container this must have well-ventilated sides.

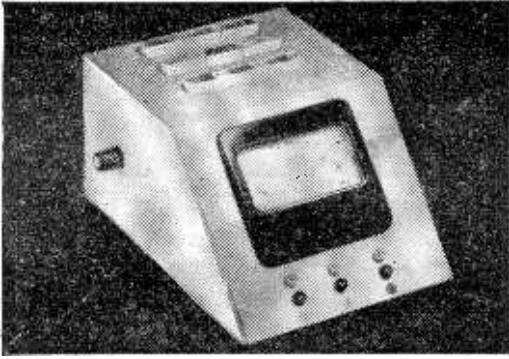Resistors made in this way are not "non-inductive", but at low frequencies this should not be much of a problem. The wire may be freed from kinks by looping one turn around the shaft of a large screwdriver and pulling the wire as shown in Fig. 5.



PUSH-BUTTON MULTIMETER

D. FANSHAWE

THE meter was primarily designed for use in transistor experiments connected with the design of apparatus. It is often required to monitor base and collector currents, and also collector voltage. These three jobs can be done with only one meter provided three switched inputs are available. The total cost of the instrument is around £3.

INPUTS

This meter has three pairs of input sockets on the front panel (marked 1, 2 and 3) and each input can be selected in turn simply by pressing the appropriate input push button.

The basic meter movement is an ex-government meter of $50\mu\text{A}$ f.s.d., available from one of the advertisers in this magazine, price 25s. The switch-

ing is by push-buttons, three banks of three-way units are used. When the meter is being used as a general purpose multimeter, the test leads can be used in any input; but if it is desired to monitor two currents and a voltage in turn, the current inputs should be plugged into inputs 1 and 2. The voltage input should be plugged into input 3. The reason for this is that inputs 1 and 2 are both short circuited when they are not selected so that the circuit under observation will not be broken. Fig. 2 shows the meter being used in this way.

RANGES

The meter ranges are: $50\mu\text{A}$; 1mA; 25mA; 500mA; (all d.c.). 1V; 10V; 50V; 500V (all d.c.). 1k Ω ; 100k Ω ; 10M Ω .

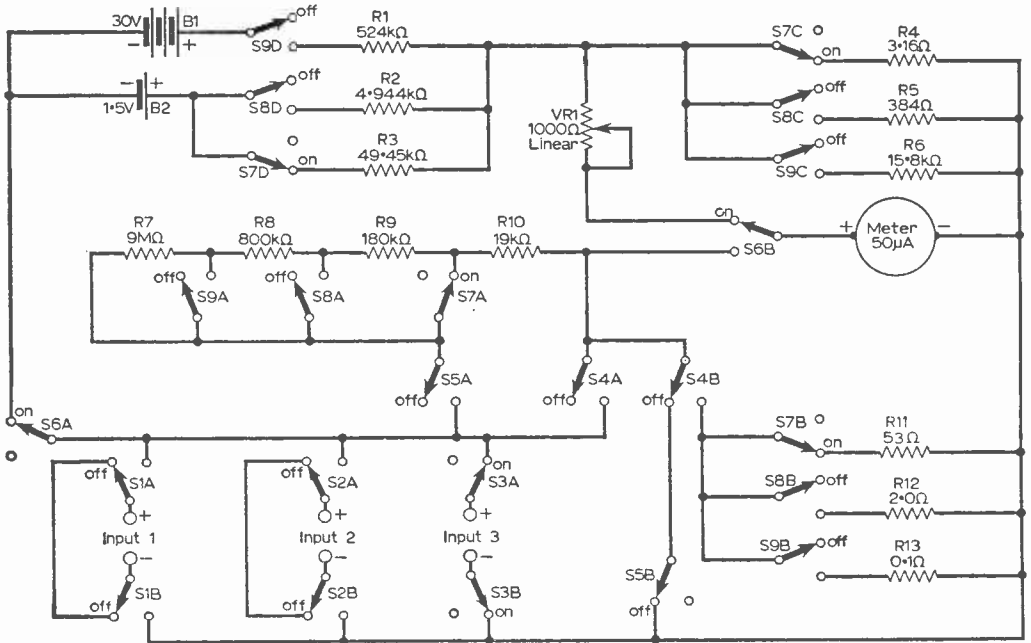


Fig. 1: Complete circuit of the multimeter.

PRACTICAL WIRELESS

***SHORT
WAVE
DATA**

POCKET GUIDE

presented with the January 1966 issue

CUT HERE

49m band: During daylight, stations up to about 1,000 miles distant should be well received. During darkness, reception will be excellent for DX stations—in fact during the winter it may be one of the best bands for after-dark reception.

41m band: Similar to 49m but noisier—although both bands will suffer interference due to the extensive use of these bands, particularly after dark.

31m band: This will provide good short distance (up to 1,000 miles) reception during daylight. During darkness, good long distance reception will often be possible, notably during the summer months.

25m band: Excellent for daylight reception of stations up to around 2,000 miles. Late afternoons and early evening will produce long distance reception but it may fade out during hours of darkness, particularly in the winter.

19m band: During hours of daylight this band will produce excellent DX reception from all over the world. Conditions should normally hold up to early evenings, but will then fade out.

16m band: Capable of producing strong DX signals, this band is best between autumn and spring during daylight hours but the summer may be relatively bleak.

13m band: Of little use at present, though the winter may bring a few stations in.

11m band: Until the sunspot cycle swings back there will be very little activity on this band.

Station Information

Various lists of short wave broadcasting stations are available, but the most comprehensive is the *World Radio TV Handbook*, published in Denmark but obtainable in the U.K. through booksellers at 23s. 0d. Apart from a complete listing of stations, it contains notes on programmes, identification and other essential information.

WHEN AND WHERE TO LISTEN

It is impossible to more than generalise in the space available. Conditions may change from day to day, month to month. Generally speaking, the high frequency bands are best during daylight and the low frequency bands during darkness. In any given year, conditions will vary from season to season,

LISTENING TO SHORT WAVE STATIONS

The newcomer to the short wave bands may understandably become rather confused; strange jargon, unpredictable reception, and other frustrations. It is not the intention of this pocket guide to present a treatise on the mysteries of the short wave bands but rather to collect in a handy form much of the basic essential data and reference material useful in day-to-day short wave listening.

The Amateur Bands

Here is a brief summary of what to expect from the amateur bands most likely to be tuned by the newcomer:

1.8Mc/s (160 metres). "Top Band" is used mainly for local communications between stations up to about 100 miles apart during daylight hours but for British Isles coverage after dark. During winter months, European contacts are possible and under very favourable conditions British stations have worked Transatlantic stations and even the Antipodes.

3.5Mc/s (80 metres). This band is favourable for hearing all the British Isles and Europe. During the hours of darkness, particularly in the winter, stations further afield are not uncommon.

7Mc/s (40 metres). Much patience is needed in listening on this band due to interference from broadcasting stations and other intruders. Though basically a "local" band, much longer distant reception is possible, notably on morse, and particularly during the winter after darkness.

14Mc/s (20 metres). The most popular "DX" band of all. It is open for world-wide reception most of the year, though it sometimes "closes" early in the evening during the winter. Sometimes, according to conditions, European stations are heard at outstanding strength.

21Mc/s (15 metres). Potentially a good band for long distance signals, much patience is required. It is best during summer months and when sunspot activity is high. Openings may be of comparatively short duration, but they are often very productive.

28Mc/s (10 metres). Much the same as 21Mc/s. When the band is really "open", stations from all over the world are often heard at remarkable strength; at other times the band may appear to be completely "dead".

General: Space does not permit a comprehensive survey of the various bands but a very good idea of current reception conditions can be obtained from reading the monthly notes *On the Short Waves* published in each issue of *Practical Wireless*.

2

but an influencing factor is the sunspot cycle. Years of high sunspot activity favour the high frequency bands, years of low sunspot activity (we are in a "trough" at the moment) favour the low frequency bands. Thus, whereas the 28Mc/s amateur band is relatively poor this year, in several years' time it may be excellent. With these reservations in mind, the following notes should be accepted as a *guide* to reception. Times in GMT.

North America/Caribbean

Best times are 1500-2300, peaking in winter around 1800 and in summer around 2030. Western N. America is more difficult but try around 1500-1800 and breakfast time. Broadcasting stations: 19m afternoon, 25m after dark (winter), in summer 19m band is best. Amateurs: 20m most reliable throughout the year—East Coast possible all through the day. After dark, 40 and 75m bands and in winter 1.8Mc/s.

Central America

On broadcast bands, try 49m around dawn, or late night in winter (when the 60, 75m bands may also be productive). Amateur bands: 20m is best bet after dark and around dawn.

South America

Best times are 0900-1100 and 1700-0100. On broadcast bands (except summer) 19m is best for morning period, 25 and 31m evenings. Also try the 60-75m section. In summer, this area is more difficult to hear—25 and 31m is usually best, evenings. Amateur bands: again 20m and 40m after dark. Also 15m early evenings.

Central/South Africa

Best general times are between 1300-2200. On broadcast bands, 19m during daylight hours and 25/31m after dark especially during winter. On amateur bands try 20m around 1700-2000. Usually good when 28Mc/s is "open".

Asia

For S and SE Asia, best times are 1100-1700, starting off with 16 and 19m bands, then 25m. During winter, the best period may hold till around 2100 on 31 and 41m bands. For amateurs, 20m is again about the best bet. Best times for Northern Asia 0600-0900 and again around 2000. The 19m and 25m broadcast bands are best.

The Antipodes

Peak times are 0600-1000, with 1400-1700 and around 2200 during winter. New Zealand is best

6

Modes of Operation

The main system used by amateurs is amplitude modulation. The beginner will listen mainly to stations using a.m. telephony ("phone") which is receivable in the normal way on any receiver. However, thousands of stations operate on telegraphy (Morse code, "cw"), because (a) the language barrier is reduced owing to the use of internationally understood codes and abbreviations, and (b) under comparable reception conditions a faint c.w. signal can be copied easily whereas a phone signal would be unintelligible. To receive c.w. signals it is necessary to have a receiver with a beat frequency oscillator (b.f.o.) which heterodynes with the incoming signal, thus making it audible. Much of the more exotic DX is heard on c.w., particularly on the lower frequency bands and the newcomer is urged not to overlook the facilities to receive c.w. stations.

To overcome the severe crowding on the amateur bands, various forms of a.m. single sideband telephony are gaining popularity. To receive such transmissions properly, the receiver should have a product detector. Frequency modulation is also permitted, but is not used extensively.

THE HAM LANGUAGE

Callsigns

For identification purposes, every amateur station has a call sign, issued by the licensing authority. This consists of a prefix (establishing the country of origin) followed by a suffix (establishing personal identity). Sometimes a numeral indicates regional significance; for example—VE2AAA is in Quebec, because VE is the Canadian prefix and 2 is the identification for the Province of Quebec.

The competitive element is strong in both listening and transmitting. Most societies issue certificates for DX achievements—mainly on the basis on the number of countries, counties, "zones", etc. The prefix list on pages 10-13 is that currently recognised by our national society, the RSGB, for country "scoring" purposes.

Abbreviations

In order to avoid ambiguity and to save time, the pioneer operators gradually devised a system of codes and abbreviations still used today. These comprise (a) signal reporting systems, (b) the Q Code, (c) general abbreviations. The greatest benefit is felt by c.w. operators who are able to convey intelligent messages to any other station regardless of nationality. In the pages that follow, the basic ingredients of this international "ham language" are outlined.

3

around 0900-1100. Summer is poor compared with other seasons. Best broadcast bands are 25 and 31m in morning, 31 and 41m in afternoon, and 19m for evening. For amateurs 20m is best, though 40m can be good during winter mornings.

Pacific Area

A difficult area to hear. Best time is between 0600-1100 on the 19 and 25m broadcast bands and 20m amateur band.

Europe/North Africa/Near East

Little need to elaborate as it is possible to hear all these areas almost around the clock.

THE "Q" CODE

One of the ingredients of the "ham language" is the Q Code, adapted from the professional communications code. Each set of symbols can be used as a question or as an answer, or in general context. For example, QTH? means "what is your location?" and QTH London means "my location is in London". An operator may also say, e.g., in conversation: "My QTH is poor for reception". Here are some of the more commonly used Q signals.

QRA	Full address	QRQ	Send faster	QSO	Contact
QRB	Distance (miles)	QRS	Send slower	QSP	Pass on a message
QRC	Frequency (kc/s)	QRT	Closed down	QSV	Send series of V's
QRJ	Weak signals	QRU	Nothing further to say	QSX	Listen for
QRH	Your frequency varies	QRV	Ready to operate	QSY	Change frequency
QRK	Signal strength	QRX	Wait	QSZ	Double sending
QRL	Busy	QSA	Readability of signal	QTC	Telegram, message
QRM	Man-made interference	QSB	Fading	QTH	Location
QRN	Atmospheric interference; static	QSL	Acknowledgement of receipt; confirmation of contact	QTR	Time check (exact time)
QRO	High power				
QRP	Low power				

7

QSL Cards

Two stations which have maintained a two-way contact may exchange "QSL" cards. These prominently display the call sign and contain data on the equipment used and confirmation details of the contact. The QSL card is the proof, normally required in claiming certificates.

Short wave listeners may also attempt to obtain QSL cards from transmitting stations by sending reception reports. But whereas in the early days most amateurs welcomed such unsolicited reception reports the fact must be faced that with such high activity on the bands today most amateurs already know how they are getting out and many SWL reports are virtually useless. In fact many stations will not even send cards to stations they have "worked" unless they are specifically requested.

We would therefore advise prospective QSL collectors to concentrate on sending reports mainly to genuinely unusual stations, such as long distant signals on the harder bands (1.8, 3.5 and 7Mc/s). Also, in any case, it is only courtesy to enclose return postage in the form of reply coupons obtainable from any Post Office.

THE BROADCASTING BANDS

Many broadcasting stations have regular programmes and/or announcements in English; indeed more and more countries are establishing "international" services, with propaganda programmes beamed to all parts of the world. There are, however, a large number of stations which never, or rarely, give English announcements. Some use call signs for identification, though these are being dropped by many broadcasters. Luckily, most of the "local" stations, particularly Latin Americans, still retain the callsign in the prominent station announcements, together with the various station slogans.

Regular readers of *Practical Wireless* can obtain monthly news of broadcast band happenings in the feature *On the Short Waves*. The newcomer may, however, find the following summary of the various bands of great use in learning what to expect.

60 and 75 metres: These bands are used almost exclusively for local regional broadcasting. The 60m band (in fact it ranges from approx. 50-63m) is a happy hunting ground for Latin Americans. Between 50-140m are several "tropical" bands, used for local broadcasting, and there is something of interest all through this range. Reception should be good on these frequencies for several years (being as we are in a period of low sunspot activity) and the Latin Americans should be plentiful during hours of darkness, notably during the winter months. Static interference may be troublesome during the summer.

4

SIGNAL REPORTING SYSTEMS

Of the various signal codes evolved through the years, the RST system is the only one to have gained universal acceptance.

Readability:

- R1 Unreadable
- R2 Only just readable, and only occasional words heard
- R3 Readable, but with considerable difficulty
- R4 Readable with almost no difficulty
- R5 Perfectly readable

- S2 Very weak signals
- S3 Weak signals
- S4 Fair signals
- S5 Fairly good signals
- S6 Good signals
- S7 Moderately strong signals
- S8 Strong signals
- S9 Extremely strong signals

- T3 Rough, low pitched note
- T4 Rather rough note
- T5 Musically modulated note
- T6 Modulated note, slight whistle
- T7 Fairly good note, smooth ripple
- T8 Good note, slight ripple
- T9 Pure DC note

Signal Strength:

- S1 Signals only just perceptible

Tone:

- T1 Extremely rough note
- T2 Very rough note

(If the note seems to be crystal controlled, an "x" is added, if the note is chirpy, a "c" is added.)

Thus an extremely strong, perfectly readable c.w. signal with a pure d.c. note would be reported as RST 599. On telephony the accepted form is R5 S9, but the same signal could be reported as QSAS R9 (or Q5 R9) owing to the persistence of an earlier system with a QSA1-5 readability scale and an RI-9 strength scale. Quality of modulation scales have been evolved but are never used.

The readability/strength code can be used for reporting to broadcasting stations, but a better system for this purpose is the **SINPO** code. This has five scales, each of 1 to 5, as indicated by the letters S (Signal Strength), I (Interference), N (Noise, i.e. static), P (Propagation Disturbance, i.e. fading) and O (Overall quality of reception).

The scale for signal strength is: 1—barely audible; 2—poor; 3—fair; 4—good; 5—excellent. The scales for Interference, Noise and Propagation Disturbance are: 1—extreme; 2—severe; 3—moderate; 4—slight; 5—nil. The scale for overall quality is: 1—unusable; 2—poor; 3—fair; 4—good; 5—excellent. Thus, in the SINPO code, a perfectly received signal would be given 55555.

8

VU	India	ZF1	Cayman Is.	5T5	Mauretania
VU	Laccadive Is.	ZK1	Cook Is.	5U7	Niger Republic
VU	Andaman and Nicobar Is.	ZK1	Manihiki Is.	5V	Togo Republic
W	U.S.A.	ZK2	Niue	5W1	W. Samoa
XE, XF	Mexico	ZL	New Zealand	5X5	Uganda
XE4	Revilla Gigedo	ZL	Auckland and Campbell Is.	5Z4	Kenya
XT2	Voltaic Republic	ZL	Chatham Is.	6N	see HL
XW8	Laos	ZL	Kermadec Is.	6W8	Senegal Republic
XZ2	Burma	ZL5	see CE9	6Y5	Jamaica
XU	Cambodia	ZM6	Samoa	7G1	Guinea Republic
XV5	see 3W8	ZM7	Tokelau(Union) Is.	7Q	Malawi
YA	Afghanistan	ZP	Paraguay	7X2	Algeria
YI	Iraq	ZS1, 2, 4,		8J1	See CE9
YJ	see FJ8	5, 6	South Africa	8Z	see HZ
YK	Syria	ZS2	Prince Edward and Marion Is.	8Z4	Saudi Arabia/Iraq Neutral Zone
YO	Nicaragua			8Z5	Saudi Arabia/ Kuwait Neutral Zone
YN	Roumania	ZS3	S.W. Africa		San Marino
YS	Salvador	ZS8	Basutoland	9A1	Ghana
YU	Yugoslavia	ZS9	Bechuanaland	9G1	Malta
YV	Venezuela	3A	Monaco	9H1	Kuwait
YV0	Aves Is.	3V8	Tunisia	9K2	Saudi Arabia/ Kuwait Neutral Zone
ZA	Albania	3W8	Vietnam	9K3	Sierra Leone
ZB2	Gibraltar	4M	Venezuela		W. Malaysia
ZC3	Christmas Is	4S7	Ceylon		E. Malaysia
ZC6	Palestine	4U1ITU	I.T.U. Geneva		Nepal
ZD3	Gambia	4W1	Yemen	9L1	Congo
ZD5	Swaziland	4X4	Israel	9M2, 9M4	Burundi
ZD7	St. Helena	5A	Libya	9M6, 9M8	Rwanda
ZD8	Ascension Is.	5B4	Cyprus	9N1	
ZD9	Tristan da Cunha and Gough Is.	5H3	Tanganyika	9Q5	
		5N2	Nigeria	9U5	
ZE	Rhodesia	5R8	Madagascar	9X5	

13

AMATEUR ABBREVIATIONS

In order to save time, the pioneer operators gradually evolved a series of abbreviations which have now become an accepted part of amateur radio operating. Most of these were devised to reduce the number of morse code characters but some are still used verbally and in written characters. Their derivation is fairly obvious; contraction by omitting vowels (i.e., HRD=HEARD, RPT=REPORT), by phonetics (i.e., SED=SAID, GUD=GOOD), by using initials (i.e., SWL=SHORT WAVE LISTENER), by general contraction using first and last letters or by using an X as termination (i.e., VY=VERY, TX=TRANSMITTER). Here are some of the more common abbreviations in use.

ABT	About	FB	Fine business (excellent)	OT	Old timer
AGN	Again	FD	Frequency doubler	PA	Power amplifier
ANI	Any	FER	For	PSE	Please
ANT	Antenna	GA	Go ahead, good afternoon	R	All received correctly
BC	Broadcast	GB	Goodbye	RCVD	Received
BCI	Broadcast interference (by an amateur transmitter)	GE	Good evening	RPT	Report
BCNU	Be seeing you	GLD	Glad	RX	Receiver
BK	Break	GUD	Good	SA	Say
CK	Check	HI	Laughter, high	SED	Said
CKT	Circuit	HPE	Hope	SIGS	Signals
CLG	Calling	HR	Hear/Here	SWL	Short wave listener
CO	Crystal oscillator	HRD	Heard	TKS	Thanks
CQ	General call	HV	Have	TNX	Thanks
CONDX	Conditions	LID	Bad Operator	TVI	Television interference
CUL	See you later	MNI	Many	TX	Transmitter
DE	From	MO	Master oscillator	U	You
DF	Direction-finding	ND	Nothing doing	UR	Your, you are
DX	Distance (long distance reception)	NW	Now	VFO	Variable frequency oscillator
ERE	Here	OB	Old boy	VY	Very
ES	And	OM	Old man	WX	Weather
		OP	Operator	WID	With

FREQUENCY AND TIME CHECKS

A number of stations operate in order to provide accurate time and frequency checks, mainly on 2500, 5000, 10,000, 15,000, 20,000 and 25,000 kc/s. Many of these stations operate continuously with audio tones and interruptions in Morse and voice. WWV also gives radio propagation forecasts.

ATA, New Delhi, India, 10,000kc/s.	MSF, Rugby, England, 2500, 5000 and 10,000kc/s.
BPV, Peking, China, 5000, 10,000 and 15,000kc/s.	OMA, Prague, Czechoslovakia, 50 and 2500kc/s.
CHU, Ontario, Canada, 3330, 7335 and 14,670kc/s.	OLB5, Prague, 3170kc/s.
DCF77, Mainflingen, Germany, 77.5kc/s.	OLD2, Prague, 18,985kc/s.
FFH, Paris, France, 2500kc/s.	RWM, Moscow, U.S.S.R., 5000, 10,000 and 15,000kc/s.
HBN, Neuchatel, Switzerland, 5000kc/s.	WWV, Washington, U.S.A., 2500, 5000, 10,000, 15,000, 20,000 and 25,000kc/s.
IAM, Rome, Italy, 5000kc/s.	WWVH, Hawaii, 5000, 10,000 and 15,000kc/s.
IBF, Turin, Italy, 5000kc/s.	ZLFS, Lower Hutt, New Zealand, 2500kc/s.
JJY, Tokyo, Japan, 2500, 5000, 10,000 and 15,000kc/s.	ZUO, Johannesburg, South Africa, 5000 and 10,000kc/s.
LOL, Buenos Aires, Argentina, 5000, 10,000 and 15,000kc/s.	

Apart from the above-mentioned stations, the following transmitters can be used as accurate frequency checks; since the frequencies are maintained within a tolerance of better than ± 1 part in 10^6 : GBR, Rugby, 16kc/s; Droitwich, 200kc/s; GRO, Skelton, 6180kc/s; GSB, Daventry, 9510kc/s; GSV, Daventry, 17,810kc/s. (GSV, GSB and Droitwich are broadcasting stations).

HOW TO BECOME A RADIO AMATEUR

Having acquired experience in listening on the amateur bands, many SWL's aspire to owning and operating their own amateur station. In the interests of all users of the air space, and to prevent absolute chaos, it is necessary to control the conditions under which amateur transmitting stations must operate.

In the U.K., applicants for an amateur licence must (a) be over 14 years of age, (b) be a British subject, (c) pass the Radio Amateur Examination, (d) pass the Post Office Morse Test. The R.A.E.

14

WKD Worked	XTAL Crystal	YL Young lady
WL Will	XYL Wife (ex-YL)	73 Best regards
WUD Would	YF Wife	88 Love and kisses

AMATEUR CALL SIGN PREFIXES

The following list of call sign prefixes is arranged to indicate where a common prefix is shared by areas which can be counted as separate "countries" for scoring purposes. This list has been prepared by the Radio Society of Great Britain, our national radio society.

AC3 Sikkim	CT1 Portugal	FH8 Comoro Is.
AC4 Tibet	CT2 Azores	FK8 New Caledonia
AC5 Bhutan	CT3 Madeira Is.	FL8 French Somaliland
AP W. Pakistan	CX Uruguay	FM7 Martinique
AP E. Pakistan	DJ, DL, DM Germany	FO8 Clipperton Is.
BV Formosa	DU Phillipine Is.	FO8 French Oceania
BY China	EA Spain	FP8 St. Pierre and Miquelon
C9 Manchuria	EA6 Balearic Is.	FR7 Reunion Is.
CE Chile	EA8 Canary Is.	FR7 Gloriseuses Is.
CE9, VP8 Antarctica	EA9 Ifni	FR7 Juan de Nova
CE0 Easter Is.	EA9 Rio do Oro	FS7 French St. Martin
CE0 Juan Fernandez	EA0 Spanish Guinea	FU8 New Hebrides
CM, CO Cuba	EI Eire	FW8 Wallis and Futuna Is.
CN8 Morocco	EL Liberia	FY7 French Guiana
CP Bolivia	EP Iran	G England
CR4 Cape Verde Is.	ET2 Eritrea	GC Jersey
CR5 Portuguese	ET3 Ethiopia	GC Guernsey and Dependencies
CR5 Guinea	F France	GD Isle of Man
CR5 Principe, Sao Thome	FB8 Amsterdam and St. Paul Is.	GI N. Ireland
CR6 Angola	FB8 Kerguelen Is.	GM Scotland
CR7 Mozambique	FB8 Tromelin Is.	
CR8 Portuguese Timor	FC Corsica	
CR9 Macao	FG7 Guadeloupe	

10

requires a knowledge of fundamental receiving and transmitting theory and a knowledge of amateur licence regulations. The Morse Test is at 12 words per minute.

Sources of Information

How to Become a Radio Amateur: This is an invaluable pamphlet giving details of the R.A.E., licence conditions, etc. It can be obtained on request from: Radio Services Department (Radio Branch), General Post Office, Headquarters Buildings, St. Martins-le-Grand, London, E.C.1.

Pamphlet No. 55 (Radio Amateurs' Examination): This contains the syllabus upon which the examination is set and can be obtained, price 1/-, from The City and Guilds of London Institute (Publications), 76 Portland Place, London, W.1. Also obtainable from the same address, price 2/-, are copies of the question papers set during the last three years.

The Radio Amateurs' Examination Manual: This is designed for those studying for the R.A.E. and covers the whole syllabus. Price is 5/6 from Radio Society of Great Britain, 28 Little Russell Street, London, W.C.1. Other useful publications by the RSGB include *A Guide to Amateur Radio* (price 4/-) and *Morse Code for Radio Amateurs* (price 1/9).

PHONETIC ALPHABET

In order to convey a call sign or other information through interference, amateurs may resort to phonetic words. This may lead to confusion with newcomers since a popular phonetic alphabet uses geographical locations (such as A=America, H=Honolulu)! Although there is no compulsion, U.K. operators are encouraged to use the alphabet contained in the Radio Regulation, Geneva 1959, and adopted by NATO Services and other bodies, viz.:

A Alfa	H Hotel	O Oscar	V Victor
B Bravo	I India	P Papa	W Whisky
C Charlie	J Juliet	Q Quebec	X X-ray
D Delta	K Kilo	R Romeo	Y Yankee
E Echo	L Lima	S Sierra	Z Zulu
F Foxtrot	M Mike	T Tango	
G Golf	N November	U Uniform	

15

GW	Wales	KC6	E. Caroline Is.	M1	San Marino
HA	Hungary	KC6	W. Caroline Is.	MP4B	Bahrain Is.
HB	Switzerland	KG1	see OX	MP4Q	Qatar
HC	Ecuador	KG4	Guantanamo Bay	MP4T	Trucial Oman
HC8	Galapagos Is.	KG6	Mariana Is.	MP4M	Muscat and Oman
HE	Liechtenstein	KG6	Guam	OA	Peru
HH	Haiti	KG6	Marcus Is.	OD5	Lebanon
HI	Dominican Rep.	KG61	see KAØ	OE	Austria
HK	Colombia	KH6	Hawaii	OH	Finland
HKØ	San Andres and Providencia	KH6	Kure Is.	OHØ	Aaland Is.
HKØ	Malpelo Is.	KJ6	Johnston Is.	OK	Czechoslovakia
HKØ	Bajo Neuvo	KL7	Alaska	ON4, 5, 8	Belgium
HM	Korea	KM6	Midway Is.	OX, KG1	Greenland
HP	Panama	KP4	Puerto Rico	OY	Faeroe Is.
HR	Honduras	KP6	Palmyra Group;	OZ	Denmark
HS	Thailand	KR6	Jarvis Is.	PAØ, PJ1	Netherlands
HV	Vatican City	KS4	Ryukyu Is.	PJ	Netherlands
HZ	Saudi Arabia	KS4B	Swan Is.		W. Indies
I1, IT1	Italy		Serrana Bank and Roncador Cay	PJ2M	Netherlands
IS1	Sardinia	KS6	U.S. Samoa	PK	St. Martin Is.
JA, KA	Japan	KV4	Virgin Is. (U.S.)	PX	Indonesia
JT1	Mongolia	KW6	Wake Is.	PY	Andorra
JY	Jordan	KX6	Marshall Is.	PYØ	Brazil
K	see W	KZ5	Canal Zone		Trinidad and Tobago
KA	see JA	LA	Jan Mayen	PYØ	Vaz. Is.
KAØ, KG61	Bonin and Volcano Is.	LA, LB	Norway		Fernando de Noronia
		LA	Svalbard	PZ	Netherlands
KB6	Baker, Howland and American	LH	Bouvet Is.		Guiana
	Phoenix Is.	LU	Argentina	SL, SM	Sweden
KC4	see CE9	LU-Z	see CE9	SP	Poland
KC4	Navassa Is.	LX	Luxembourg	ST2	Sudan
		LZ	Bulgaria	SU	Egypt

11

AMATEUR BANDS (U.K.)

Frequency Band (Mc/s)	Classes of Emission	Maximum d.c. Input Power
1.8-2.0	A1, A2, A3, A3A, F1, F2, F3	10 watts
3.5-3.8 7.0-7.10 14.0-14.35 21.0-21.45 28.0-29.7		150 watts
70.2-70.4		50 watts
144-145 145-146 420-450 1,215-1,325 2,300-2,450 3,400-3,475 5,650-5,850 10,000-10,500 21,000-22,000		150 watts
2,350-2,400 5,700-5,800 10,050-10,450 21,150-21,850	PID, P2D, P2E, P3D, P3E	25W (mean), 2.5kW (peak)

Note: A—classes of emission are forms of amplitude modulation, F—frequency modulation and P—pulse modulation.

16

----- CUT HERE -----

SV	Greece	UM8	Kirghiz	VP5	Turks and
SV	Crete	UO5	Moldavia		Caicos Is.
SV	Dodecanese	UP2	Lithuania	VP6	Barbados
TA	Turkey	UQ2	Latvia	VP7	Bahamas
TF	Iceland	UR2	Estonia	VP8	see CE9
TG	Guatemala	VE, VO	Canada	VP8	Falkland Is.
TI	Costa Rica	VK	Australia	VP8	S. Georgia
TI9	Cocos Is.	VK	Lord Howe Is.	VP8	S. Orkney Is.
TJ	Cameroun	VK	Willis Is.	VP8	S. Sandwich Is.
TL8	C. African Rep.	VK9	Christmas Is.	VP8	S. Shetland Is.
TN8	Congo Republic	VK9	Cocos Is.	VP9	Bermuda Is.
TR8	Gabon Republic	VK9	Nauru Is.	VQ1	Zanzibar
TT8	Tchad Republic	VK9	Norfolk Is.	VQ7	Aldabra Is.
TU2	Ivory Coast Rep.	VK9	Papua Territory	VQ8	Cargados Carajos
TY	Dahomey Rep.	VK9	New Guinea	VQ8	Chagos Is.
TZ	Mali Republic	VK0	see CE9	VQ8	Mauritius
UA1, 3, 4, 6,		VK0	Heard Is.	VQ8	Rodriguez Is.
UNI	European S.F.S.R.	VK0	Macquarie Is.	VQ9	Seychelles
UA1	Franz Josef Land	VP1	British Honduras	VR1	British Phoenix Is.
UA2	Kaliningradsk	VP2	Anguilla	VR1	Gilbert and Ellice
UA9, Ø,		VP2A	Antigua, Barbuda		and Ocean Is.
UW9	Asiatic S.F.S.R.	VP2V	British Virgin Is.	VR2	Fiji Is.
UB5, UT5,		VP2D	Dominica	VR3	Fanning and
UY5	Ukraine	VP2G	Grenada and		Christmas Is.
UC2	White Russian		Dependencies	VR4	Solomon Is.
	S.S.R.	VP2M	Montserrat	VR5	Tonga Is.
UD6	Azerbaijan	VP2K	St. Kitts, Nevis	VR6	Pitcairn Is.
UF6	Georgia	VP2L	St. Lucia	VS5	Brunei
UG6	Armenia	VP2S	St. Vincent and	VS6	Hong Kong
UH8	Turkoman		Dependencies	VS9	Aden and Socotra
UI8	Uzbek	VP3	British Guiana	VS9	Maldives Is.
UJ8	Tadzhik	VP4	Trinidad and	VS9	Sultanate of Oman
UL7	Kazakh		Tobago	VS9K	Kamran Is.

12

These ranges are selected by pressing a function button (mA, V or Ω) and also a range button. Each of the three range buttons will select a current range, a voltage range or a resistance range. Thus the left-hand range button will give ranges of 0-1mA; 0-1V or 0-1k Ω , depending on which function button is depressed. Thus three range buttons allow us to select 3 current ranges, 3 voltage ranges and 3 resistance ranges. The fourth current range (0-50 μ A) is obtained by pressing the mA function button and releasing all the range buttons. (This can be done by slowly pressing a button half-way in until it unlocks the other buttons, and then releasing it.)

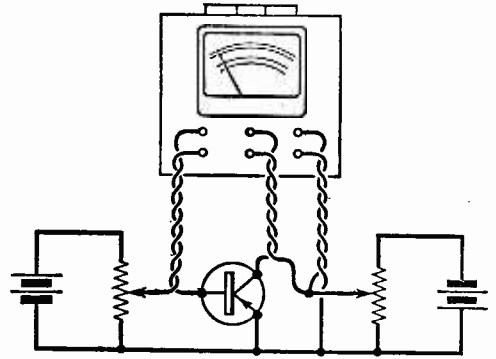


Fig. 2: Checking transistor performance.

V FUNCTION BUTTON

The fourth voltage range (0-500V) is obtained by pressing the V function button and releasing all the range buttons. It is suggested that the buttons be colour coded, using red for current, green for voltage and yellow for resistance. Thus buttons "input 1", "input 2" and "mA" will be coloured

red; buttons "input 3" and "V" will be coloured green; and button " Ω " will be coloured yellow. The three range buttons are each divided into three equal areas which are coloured red, green and

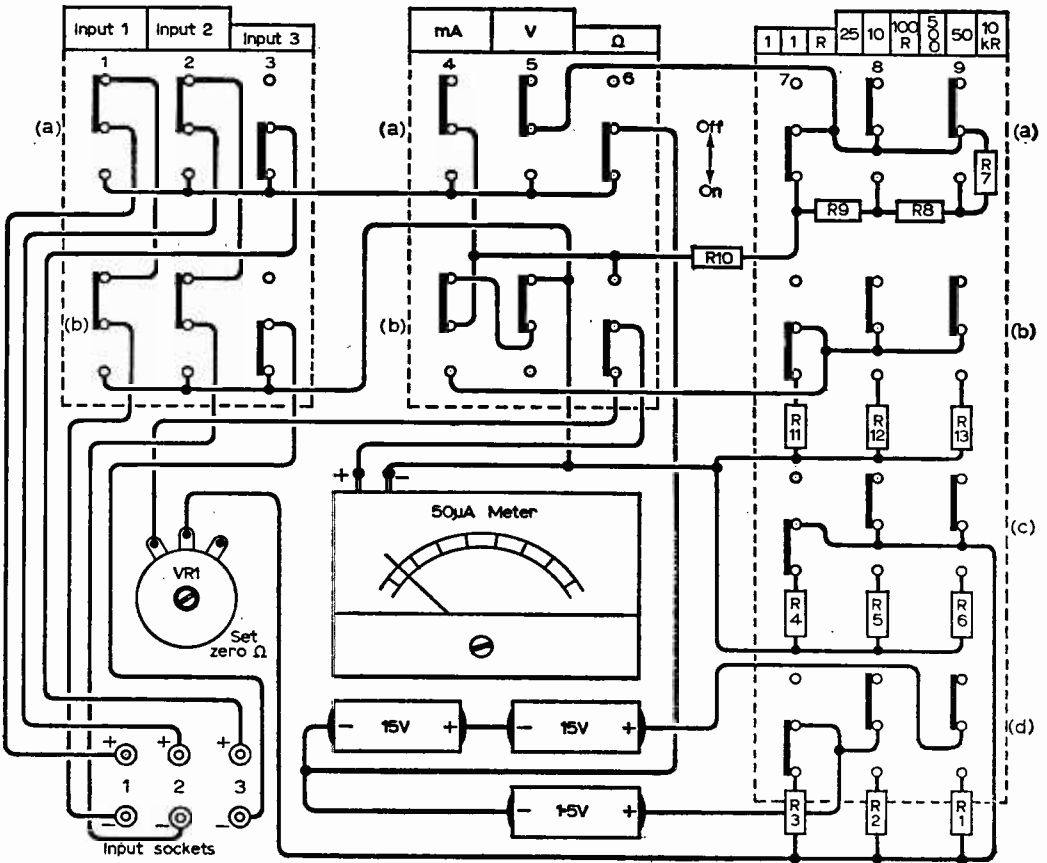


Fig. 3: Wiring and layout diagram.

yellow respectively. Thus for each button the appropriate current, voltage and resistance range can be written on the red, green and yellow panels. When all the function buttons are released the meter movement is short circuited, and the meter should be left like this when not in use.

Each button operates a 4-pole 2-way switch. The circuit diagram is given in Fig. 1 and the layout in Fig. 3. The case is made from plywood bonded with epoxy resin (Araldite etc). The resistances are nearly all non-standard values. If you are on good terms with your dealer he may let you go through his stock of 10% resistances with his meter until you find ones near enough. This way means that your meter will be slightly inaccurate on some ranges, but it should not be enough to worry about.

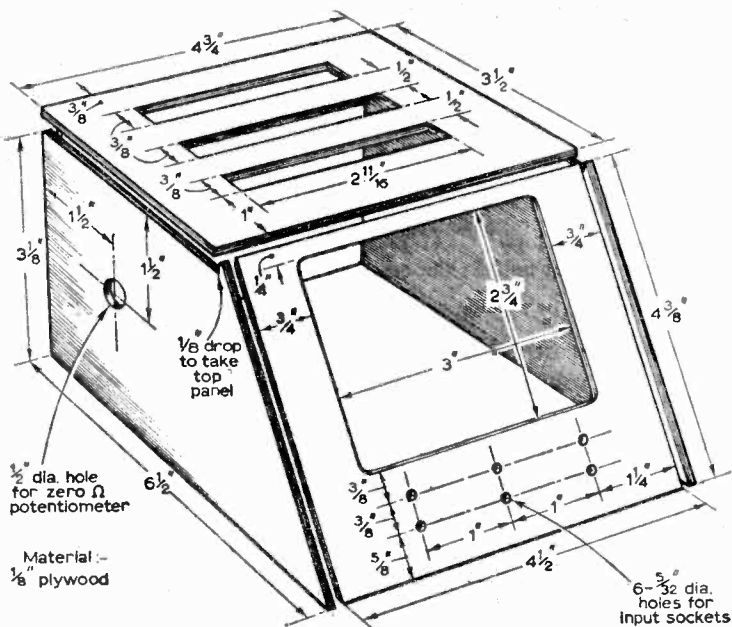


Fig. 4: Cabinet drilling and constructional details.

SPECIAL RESISTORS

The very low value resistances are best made from lengths of electric-fire element. Pull out a few feet of element to remove the kinks, measure this length accurately (in inches) and borrow an ohmmeter to measure its resistance. Divide the length by the resistance and you will get a number which represents the length which has a resistance of 1Ω. Multiply this by the resistance you want. This will give you the length of wire you will need (in inches). Remember to cut off a piece slightly

longer than this to allow for the soldered ends. The 0.1Ω resistance may be best made out of copper wire. If you use fire element for this one, it will be about 1/4 in. long and may be a bit too small to handle easily. If you use Welco spiral element, 230/250V 500W, a 6.5mm length has a resistance of 1Ω, and you will find the suggested lengths for each resistance in the components list. The wire should be insulated with a varnish.

CONSTRUCTION

Construction should be started around the banks of switches, leaving leads about 6 in. long for connecting to the meter, the batteries, the potentiometer and the input sockets. The four screws at the back of the meter are removed and the cover can then be lifted off. The existing scale should be

COMPONENTS LIST

Resistors:

All selected from 10%, 1/2 watt

Resistance	Value	Nearest standard value
R1	524kΩ	560kΩ
R2	4.944kΩ	4.7kΩ
R3	49.45Ω	47Ω
R5	384Ω	390Ω
R6	15.8kΩ	15kΩ
R7	9MΩ	8.2MΩ or 10MΩ
R8	800kΩ	820kΩ
R9	180kΩ	180kΩ
R10	19kΩ	18kΩ
R11	53Ω	56Ω

The following resistors are made from resistance wire:

Resistance	Value	Length of 230/250v 500 watt fire element (Welco Ltd)
R4	3.16Ω	202mm
R12	2Ω	130mm
R13	0.1Ω	6.5mm


Other Components

- VRI 1000Ω linear w.w. pre-set potentiometer
- B1 Two 1.5V batteries in series (Ever Ready B154)
- B2 One 1.5V baby cell battery (Ever Ready LPU 11)
- Three 3-way pushbutton units, each operating a 4-pole, 2-way switch (Broadway Electronics Ltd., Tooting).
- 50μA meter, ex-government (Radio & TV Components (Acton) Ltd.).
- Six sub-miniature sockets and plugs.
- One piece of 1/8 in. plywood, 12 1/2 in. x 11 in.
- Two pieces of leathercloth for covering 18 in. x 5 in.; 15 in. x 4 in.

Fig. 5: Scale calibration for the new dial (see text).

removed, and the scale shown in Fig. 5, copied on to thin card, mounted in its place. The pointer can be lengthened, if desired, by gluing a short length of very fine wire to the end of it. If this is done, it must be counterbalanced very carefully so that the position of the pointer does not change when the meter is horizontal and vertical.

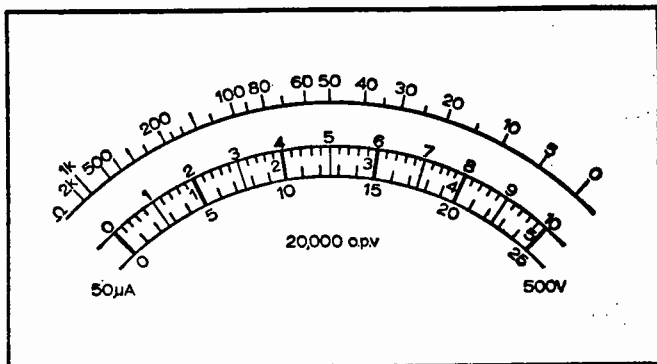The wooden case can be covered with leathercloth. ■



UNDERSTANDING F.M.

—continued from page 762

polarity only. The pulses "pile up" additively in C2, but not indefinitely because there is a drain into the following a.f. circuit through C4. Allowing for the smoothing effect of C2 C3 and the time constants of the network it will be realised that the pulses lose their separate identities but set up voltages that change with their rate of arrival. The smoothing network includes the adjustment required for de-emphasis. D2 eliminates pulses of opposite polarity.

To produce distinct pulses the carrier must be converted to a very low intermediate frequency between 100 and 500kc/s and the gain of the receiver is consequently low. Nevertheless, it provides a simple system of the highest quality and a 'successful' valve version appeared in the April 1965 issue of this journal. It is well suited to transistor circuitry and a design is in development at the moment.

As the object of this article has been to explain the nature and behaviour of the f.m. carrier in order that the discriminators likely to be encountered can be understood, such matters as the relationship between frequency modulation and phase modulation, pre-emphasis and de-emphasis, limiter circuitry, and interference, have not been included because these can be pursued after the information in these pages has been understood. ■

ECONOMY FM TUNER (October 1965 P.W.)

Fig. 1 shows the screen grid (pin 8) of V2 connected to the junction of R2/C2. This should have been shown connected to the junction of R1/C1 only.

MINIATURE OSCILLOSCOPE (November 1965 P.W.)

Henry's Radio Limited, 303 Edgware Road, London, W.2. have informed us that they are able to supply new, from stock, the ACRI10 (VCRI39A) c.r.t. We understand that this will replace the VCRI39 without any changes to the circuitry. The price is 25s. 0d. plus 2s. 6d. post and packing.

BUILT-IN TUNER FOR TAPE RECORDERS (September 1965 P.W.)

The H402 coil kits are now being supplied with two different codings. The colour coding of the cores given in the article is correct where the transformers have part numbers viz: E360—S301—S203 etc., and where the ferrite rod aerial has only three leads.

Where the ferrite rod aerial has four leads, the GREEN and BLACK leads should be joined together and taken to chassis (+ve). Also where the transformers do not have part numbers, the colour coding of the cores are as follows: Oscillator—Black. 1st i.f.t.—Yellow. 2nd i.f.t.—Red. 3rd i.f.t.—Grey.

A circuit diagram supplied by the coil kit manufacturers, is included with each set of coils, and reference to this before construction will clarify the connections.

PRACTICAL WIRELESS AND PRACTICAL TELEVISION FILM SHOW

The Film Show, which is held annually, is to be held as before, at Caxton Hall, Caxton Street, Westminster, London, S.W.1. The date of the Show, which is arranged in collaboration with Mullard Limited, is Friday, 4th February, 1966, at 7.30 p.m. sharp. The films to be shown are "Electromagnetic Waves, Part II" and "Thin Film Microcircuits" and the illustrated talk will be on "Transistor Topics". Refreshments will be provided. The talk will be given by Mr. I. Nicholson of Mullard Limited, and in the chair will be Mr. W. N. Stevens, Editor of "Practical Wireless" and "Practical Television". Applications for free tickets should be made to FILM SHOW, "Practical Wireless", Tower House, Southampton Street, W.C.2 and not to Caxton Hall. A stamped addressed envelope must be enclosed.

Dealings with the G.P.O.

I ENCLOSE part of recent correspondence between myself and the G.P.O. Radio Services Branch.

From the University of Sheffield Amateur Radio Society:

Q1 . . . Can Sound 'B' licensees operate on any amateur frequency provided that they use a Sound 'A' call sign, the holder of which is present?

A1 . . . The holder of an amateur (Sound) licence 'B' is permitted to operate an 'A' station under the direct supervision of the licensee on all amateur frequencies. Operation, however, is restricted to telephony only.

Q2 . . . Can Sound 'B' licensees operate a club (Sound 'A') station as authorised operators, unsupervised, on frequencies higher than 420Mc/s?

I appreciate that the use of Morse is not allowed when a Sound 'B' licensee is transmitting.

A2 . . . The holder of an Amateur (Sound) licence 'B' cannot be authorised to act as an additional operator of an 'A' club station.

I feel that these answers could be of sufficient significance for comment in PRACTICAL WIRELESS.
J. P. Billingham.

Ardley,
Barnsley.

Tape Terminology


THE remark in Mr. Read's letter (November 1965 issue) has been somewhat anticipated. On the 20th of October, George Newnes published a short work, "Questions and Answers on Radio and Television", putting technical matters into language that, I hope, will be both instructive to the layman and helpful to the accomplished. Also published on that date was my more ambitious work on the subject that appeals to Mr. Read, "Tape Recording Service Manual". Although this is a volume costing three guineas and containing technical data on a great many tape recorder mechanisms and circuits, it also contains a section dealing with the principles of tape recording and general servicing procedures in which Mr. Read may be interested.

H. W. Hellyer.

Bargoed,
Glamorgan.

NEWS AND..

THE WORLD'S MOST PRECISE "RADIO EYE"

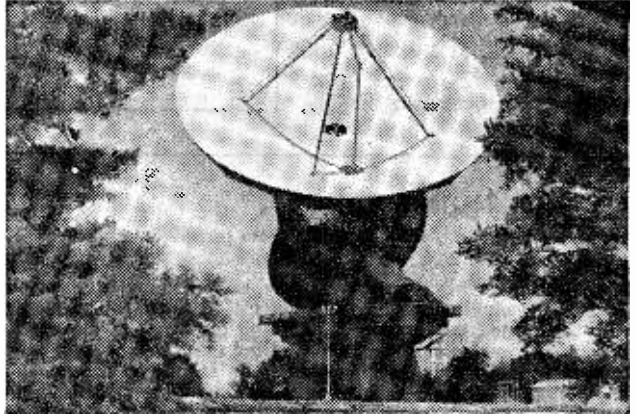

A new 140 ft. diameter radio telescope is now operational in Green Bank, (West Virginia) USA. It is being used by astronomers to detect sources of noise in outer space. Unique feature of the telescope is a Westinghouse metal bearing which pivots 2,600 tons on a film of oil only the thickness of a hair.

Built at a cost of \$13 million the station, known as National Radio Observatory, is designed to be the world's most precise instrument for pinpointing waves from outer space.

THE COLDEST PLACE ON EARTH

In a recent issue of the Mullard Outlook, details were given of the Mullard Cryomagnetic Laboratory located at Oxford, England. This forms part of the internationally known Clarendon Laboratory which has become famous for its contributions to research in the field of magnetic fields at very low temperatures.

Mullard scientists in their new laboratory with its source of very high power magnetic fields have recently been testing many new types of semi-conductor material. This may, in time, lead to revolutionary methods of generating, transforming and distributing electric power. In the course of studying aspects of solid state physics, the scientists have been able to achieve temperatures as low as a millionth of a degree above absolute zero—almost as cold as the conditions found in outer space.

The Mullard Cryomagnetic Laboratory is believed to be the only one in the world to have reached so far down the temperature scale and thus earned for itself the title of "The Coldest Place on Earth".

LASER TELEPHONE LINE IN MOSCOW

The first laser telephone communication system linking two districts in Moscow is being put into operation. Special transmitting equipment converts telephone signals into impulses which are superimposed on a laser ray. The receiving equipment directs the ray to a large parabolic mirror which reflects it into a system of filter and photo transformers where it becomes a telephone signal again.

.. COMMENT

INTERNATIONAL RADIO COMMUNICATIONS EXHIBITION

Now fairly established as a regular event in the radio calendar, this year's exhibition at the Seymour Hall fully lived up to the reputation of its predecessors.

The home-constructed units bore witness to the very high standard attained these days by Amateurs, and with some exhibits it was difficult to define the borderline between these units and some of the commercial items. Of particular note was the solid state mobile equipment built by G3LOK and the superb s.s.b. transceiver constructed by G3SBA.

The British Amateur TV Club displayed an impressive array of gear with a triple-turret TV camera with built-in monitor screen televising the exhibition from the balcony.

In the professional field, K.W. Electronics displayed their KW2000A s.s.b. transceiver while across the hall Brian J. Ayres & Co. were showing a range of National equipment. Highlight here was the much talked of solid state receiver, the HRO-500 costing about £705. Needless to say, this is not a t.r.f.!

The manufacturers award this year was presented to Tom Withers of T.W. Electronics for their solid state v.f.o. for 144 Mc/s. Messrs Imhofs offered an impressive display of cabinets of all shapes and sizes, and Electroniques offered their very excellent coils and receiver front-ends for the serious amateur. J. Beam aeriols showed a number of their time proven v.h.f. and u.h.f. arrays, plus the able assistance of Vic. Hartopp to answer the numerous queries.


The accent this year was clearly two things—the increase in solid state circuitry, and s.s.b. Next year might even see greater marriages between these two.

MARCONI SOLID SWITCHES

The photograph shows the final stage in the production of one of the new range of Marconi high-speed solid-state switches.

Hard black Araldite, an extremely tough epoxy-resin, is being poured into the body of the switch to provide complete encapsulation. This technique provides the maximum possible protection for solid-state electronic circuits. After curing at 60°C, the switch becomes an entirely solid unit which is capable of operating under extreme environmental conditions.

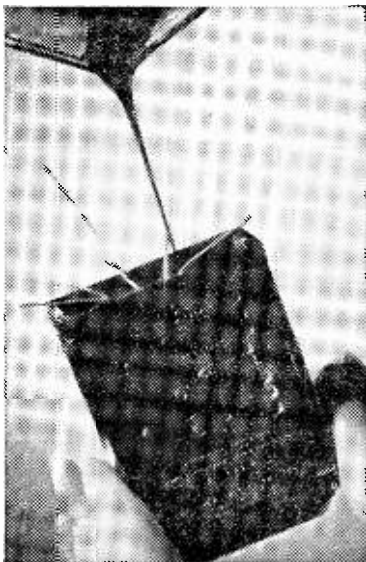These new switches are fully transistorised and can be used as direct replacements for electro-mechanical relays. They are virtually indestructible and will operate almost indefinitely.



Thumbnail History of Radio

I WOULD like to thank the many old-timers who have helped me in my researches for the above-mentioned article. Most of this information has been passed on to me by the old operators on 80m whose ranks are sadly diminishing all the time. I feel that it is especially important to collect all this information before it is lost.

R. F. Farley, G3SSJ.

Mytchett,
Nr. Aldershot,
Hampshire.

The Meaning of Amateur

Do your correspondents think that amateur footballers should knit their own jerseys and socks, or that amateur cyclists should construct their own cycles?

So why should amateur radio enthusiasts be any different? Why should they not have the benefit of commercially-made equipment as much as amateurs in any other field?

R. G. Hasler.

Birmingham, 28.

I do not think we should take too seriously the letter on this subject from Mr. Heathfield in the December issue—he generalises too much on only a few observations. Will he now do us the favour of visiting those of his friends whose hobby is photography and then tell us how much of their apparatus (cameras, lenses, light meters, rangefinders, print-driers, etc.) they have made for themselves, and if he considers it a bad thing that they should buy commercial gear.

Has it escaped his notice that a commercial-looking piece of equipment may in fact have been built from a kit of parts such as those offered by K. W. Electronics, or Heathkit?

Our hobby is perhaps unique in that so much of the apparatus used in it can be built at home to save heavy outlays if one is so inclined; that so much is published to enable this to be done, and that so many people (despite what Mr. Heathfield would like us to believe) still do "roll their own" and enjoy doing it.

W. E. Thompson, G3MQT.

St. Leonards-on-Sea,
Sussex.

TAPE TAPE TAPE TERMINOLOGY TAPE

PART SIX

by H. W. Hellyer

THREE-HEAD SYSTEM

Using separate Erase, Record and Play Heads.

TOPE CONTROL

Used during playback to "tailor" the response of the tape recorder to suit listening conditions. Can consist of a simple top-cut network or a more complicated bass and treble constant-control, using feedback networks and balanced controls.

TRACK

The magnetised path of the recording after it has passed the recording head. Trackwidth depends on the gap length. Fig. 19 shows actual and proposed track dimensions on standard quarter-inch (average) tape. Figures given are in inches, and some tolerance is allowed for most measurements, depending on head manufacture. The diagram is not to scale.

- (a) Half-track operation, BS. 1568.
- (b) International half-track standard.
- (c) Original Continental quarter-track standard, now discontinued.
- (d) Proposed "compatible" standard.
- (e) American MRIA quarter-track standard.

Note that various standards have been proposed, and the latest attempt is to ensure compatibility, i.e. the replaying of two-track recordings through a four track machine for stereo reproduction, without losses and also to be able to replay quarter-track recordings on a half-track machine, which is at present not satisfactory. Spaces between tracks and at edges are called "safety lanes".

TWIN TRACK

Correctly referring to a stacked head with two gaps, one above the other, for simultaneous recording and playback of two tracks. (As opposed to two-track, where a single gapped head is used for recording and replay of two tracks by tape inversion at the end of the reel.) Similarly, quarter-track recording is made on a four-track machine having two gaps, and employing the tape inversion principle. Track numbering is normally 1 and 4 for the outer tracks and 2 and 3 for the inner tracks, giving a numbering 1 to 4 from top to bottom. But some manufacturers favour different numbering systems.

TRANSDUCER

A device which is actuated by waves from one transmission system and supplies related waves to other media. Practically, a microphone or loud-speaker which converts sound waves to electrical impulses, or vice versa.

TWEETER

Small loudspeaker specially designed to handle the higher audio frequencies. Normally connected via a filter which cuts off tones below about 2,000c/s.

ULTRASONIC FREQUENCY

A frequency lying above the audio frequency range; usually employed to indicate the frequency range of the bias oscillator. This is not strictly accurate, bias frequency is usually in the radio frequency part of the spectrum.

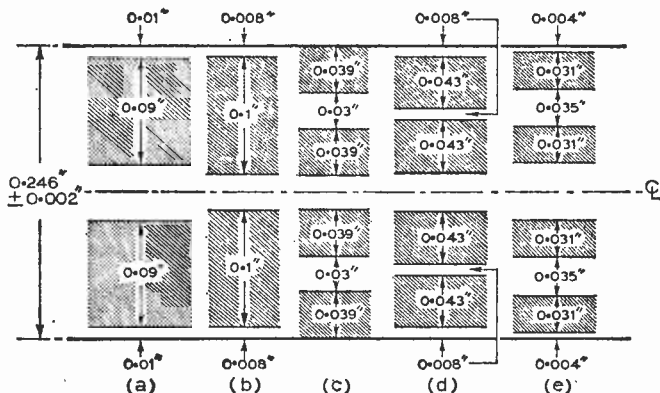


Fig. 19: Track dimensions on standard $\frac{1}{4}$ " tape.

VARIABLE BIAS

Method of altering bias gradually to obtain good tone balance, usually during superimposition when the action of cutting out erase power can affect bias conditions, and when reduced bias is needed for the later signal to prevent over-riding the original.

VARIABLE SPEED WIND

In some machines (professional types mainly) the speed of winding can be potentiometer controlled for special applications.

EXCLUSIVE TO PRACTICAL WIRELESS READERS

TRANSISTOR POCKET RADIOS



BULK PURCHASE ENABLES US TO MAKE THIS FANTASTIC OFFER AND WITH MONEY BACK GUARANTEE !!!

The "SAN REMO" . . . so tuned that it brings the voices of star entertainers and vocalists dramatically to life—in your home, office, etc. Only 4 1/2 x 2 1/2 x 1 1/2 in. Fits easily into your pocket or handbag. Works for months off 1 1/2 battery. Should last a lifetime, anyone can assemble it in an hour or two with our easy plan. Miniature speaker, carrying case—everything only 28/6, 2/6 P. & P. (Parts can be bought separately.) Limited period—so rush your order before it's too late. DEMONSTRATIONS DAILY.

ONLY 28/6
NO MORE TO PAY

into your pocket or handbag. Works for months off 1 1/2 battery. Should last a lifetime, anyone can assemble it in an hour or two with our easy plan. Miniature speaker, carrying case—everything only 28/6, 2/6 P. & P. (Parts can be bought separately.) Limited period—so rush your order before it's too late. DEMONSTRATIONS DAILY.

DON'T WALK—JUST TALK!!




INTERCOM OUTFIT & BABY ALARM

LIMITED QUANTITY SAVE £3.13.1

ONLY 49/11 Robustly made, brand new current models. You get 2 separate, fully transistorised intercommunicating sets—each can speak or listen to the other—complete with 60 ft. connecting wire. Fixed in a flash. Ends baby-crying worries. Ideal for Workshop to House, Sickroom, hundreds of uses! Hangs on wall or stands up. Our absurd price 49/11, battery 2/6, extra Post, etc. 3/7. Money refunded if not 6 gns. value!

MAKE 5 DIFFERENT TRANSISTOR RADIOS

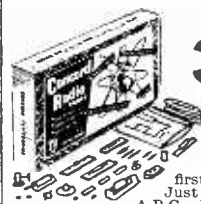

FOR **35/-**

NO EXPERIENCE NECESSARY. No Soldering. Only 8 connections for first radio to work. Just look, you get A.B.C. Plans, Cabinet, 4 Semi-conductors, Coils, Condensers, Resistors, Tuner, Switch, Screws, etc. **YES—EVERYTHING!** Loud clear English and Foreign reception. As supplied to Educational Authorities, H.M. Forces, etc. **TESTIMONIALS GALORE.** Mr R O'D of Londonderry, writes: ". . . I received your components and I must say that I am very satisfied with them! I have it already set up." **COMPLETE HOME RADIO COURSE.** Originally £8 SEND **ONLY 35/-** plus 3/6 post, etc.

IT HAD TO COME EVENTUALLY! THE "SKYSCRAPER" PERSONAL COMMUNICATIONS RECEIVER. Highly sensitive. World-wide short-waves reception including news in English and countless other broad-casts from RUSSIA, AMERICA, etc., etc. Take it anywhere—it's featherweight! 6in. x 3 1/2in. x 1 1/2in. Bandspread Tuning, Vernier Dial, Miniature Valve Circuits, Plug-in Coils, Own Rod Aerial, etc. 50% of production to be exported. Anyone can assemble it within 2 hours—only a few connections to make—experience unnecessary. Parts Incl. Case, Personal phone. Easy-to-follow plan—49/6 plus 2/6 Post, etc.

TRANSISTOR RADIO KITS
SOLD IN DEPARTMENT STORES AT £5.8.0.
OUR PRICE **37/6**
P. & P. 3/6
Extra

Well-known brand Transistor Radio Kits—YOU SAVE £3.10.6. Covering all medium/long wave with parts including Mullard Semi Conductors. 48 page instruction manual. Entertaining and educational. No soldering, just plug in, making many different Radios in a few mins.

CAR CIGARETTE LIGHTER DISPENSER

High Class Stores sell at 3 gns. save £2.4.8
Top quality chromium. Car cigarette Lighter Dispenser. Fixed in a jiffy—Pressing Button delivers ready-lit Cigarette into your hand! Takes 10 cigarettes—King size or any size! As fitted to luxury cars. Safe, fool-proof. 4 1/2 x 4 x 1 1/2 in. Lifetime tested, ready to use. Refund if not worth 3 gns., 750 only. 18/6 plus 1/6 P. & P. (state 6 or 12v.).

FABULOUS ST. TROPEZ MK. 6 The Sensational Pocket Radio

This fantastic offer will amaze you—the beautifully compact ST. TROPEZ, measuring 4 1/2 x 3 x 1 1/2 in. receives perfectly in bedroom, office or gardens—over all medium waves including Luxembourg. Under 1d. per hour running cost. ANYONE can assemble it in one or two hours using our simple A.B.C. plan. 25/- (P. & P. 2/6 extra). Case extra. Parts can be bought separately.

Read what just a few of our satisfied customers say
R.C. of Harringay writes Received with thanks Skyroma . . . Very pleased. Working well.
B.M. of Harrogate writes . . . I would like to thank you . . . It was a real bargain.
L.S. of London W.8 writes . . . given it a good try out and I am very pleased with the results.
S.B. of Somerset writes . . . delighted with this radio . . . glad if you could send one more.
T.F. of Stevenage writes . . . I would just like to say how pleased my son is with this radio.

MORE TERRIFIC OFFERS FROM CONCORD!

10 TRANSISTOR PERFORMANCE HI-FI RADIO

ONLY 55/-
POST 3/6

LIQUIDATION PURCHASE 500 ONLY
Made to sell at 54 gns. — Save £3.0.6. Latest camera style radio. Big-Set tone from tone-chamber moving coil speaker. New device plucks in Station after Station including Luxembourg, Caroline, etc. Fantastic coverage — 187-577 metres! Expensive looking finish, simulated leather, black and chromium. Size 4 1/2 x 2 1/2 x 1 1/2. 7 semi-conductors. 55/-+2/6 batt. + 3/6 P. & P. Refund if not delighted.

NEW RADIO VOLKSRADIO

ANYONE CAN BUILD IN 2-3 HOURS!
19/6

EVEN THE OLDER CHILDREN BUILD THEM! . . . no soldering—only 16 connections! then hear it reach out bringing in station after station, loud and clear. Palm-of-hand size 4 1/2 x 2 1/2 x 1 1/2 in. Many Testimonials: M.H. of Bradford, writes: ". . . I have just completed one of your sets successfully. It is the first time I have ever tackled anything like a radio, and I must state here and now, I am amazed how easy it is to a layman like me. Your instructions and plan have obviously been very carefully thought out so that even the most dim can follow them . . ." Direct from Manufacturers to You. Send 19/6 plus 2/6 post, etc.
PARTS AVAILABLE SEPARATELY

AMAZING CIGARETTE RADIO

ONLY 18/6

Yes, a perfectly ordinary packet of cigarettes! — but watch your friends' astonishment on hearing it fetch in station after station, loud and clear! Still holds 10 Cigarettes—yet cleverly conceals highly sensitive, fully transistorised circuit (including tiny battery). Even a young boy can assemble it in under 2 hours. No soldering. No experience necessary; only 16 connections to make. Ideal for taking to work with you. From our bulging testimonial file, Mr. D. B. of Huddersfield, writes: ". . . I have fitted the parts in and it is working wonderfully . . ." **ALL PARTS** including Semi-Conductors, A.B.C. Plans, etc. **ONLY 18/6** plus 2/6 post etc.
PARTS AVAILABLE SEPARATELY

TRANSISTOR ELECTROLYTICS

COMPARE THESE PRICES!

32µF	1.5 volt	25µF	6 volt	4µF	15 volt
25µF	3 volt	30µF	6 volt	5µF	15 volt
2µF	3 volt	50µF	6 volt	6µF	15 volt
3µF	3 volt	100µF	6 volt	8µF	15 volt
8µF	3 volt	2µF	9 volt	16µF	15 volt
10µF	3 volt	10µF	9 volt	32µF	15 volt
12µF	3 volt	20µF	9 volt	50µF	15 volt
20µF	3 volt	2µF	12 volt	64µF	15 volt
30µF	3 volt	3µF	12 volt	2.5µF	25 volt
40µF	3 volt	4µF	12 volt	16µF	25 volt
25µF	6 volt	10µF	12 volt	32µF	25 volt
2µF	6 volt	20µF	12 volt	2µF	30 volt
3.2µF	6 volt	25µF	12 volt	16µF	30 volt
4µF	6 volt	30µF	12 volt	25µF	30 volt
8µF	6 volt	1µF	15 volt	1µF	50 volt
10µF	6 volt	2µF	15 volt	5µF	70 volt

All the above at 1/2 each.

320µF	2.5 volt	250µF	15 volt	150µF	25 volt
200µF	3 volt	500µF	15 volt	100µF	30 volt
250µF	6 volt	100µF	18 volt	200µF	30 volt
400µF	6 volt	64µF	25 volt	50µF	150 volt

All the above at 1/6 each.

1,000µF	6 volt	750µF	15 volt	1,000µF	25 volt
1,000µF	12 volt	1,000µF	15 volt	500µF	50 volt
4,000µF	12 volt	500µF	25 volt	1,000µF	50 volt

All the above at 2/- each.

200/100µF, 257V or 200/200µF, 275V ... 6/6 each

CONDENSERS

Silver Mica, 3-3pF to 6,800pF. Including High Voltage Disc Ceramics (normally 3/- each) ... 10/- per 100 Paper Condensers: .001µF, .001µF, .002µF, .005µF, .02µF and .04µF, all at 7/6 per 100. £3 per 1,000; .1µF, .25µF, .5µF, 10/- per 100.

RESISTORS

1/10th, 1/6th, 1/4th, watt ... 10/- per 100 Mixed wattages ½ watt to 3 watt. Close Tolerance. Assorted Values. Polythene wrapped on cards of 10. Give-away price, 50/- per 1,000, plus 5/- post and packing.

TRANSISTORS (At a price you can afford)

OC71 equivalent, 1/- each, 25 for £1, 100 for £3. NKT124 or NKT125. Switching transistors, 2/- each, 6 for 10/- Large Car Radio type Output Transistors, OC25, OC35, NKT405, 10/- each.

Packet containing: three 2G417, two 2G371, one 2G381, one 2G339, one diode (for making superhet with complementary symmetry transformerless output stage) ... £1 complete Diodes, 1/- each. Zener Diodes, ZE12, ZB4-3, 5/- each. BY100 Mains Rectifiers for TV Sets. 7/6 each.

SIGNAL INJECTOR. R.F./I.F./A.F. Transistors, components and circuit to make. Only 10/- complete.

LOUDSPEAKERS. Brand New, 4 inch. Excellent reproduction. 10/- each.

- Midget Earpieces, complete with plug and lead ... 5/- each
- Magnetic Lapel Microphone with plug and lead ... 10/- each
- Transistor Holders ... 1/- each
- Miniature Soldering Irons, complete with Bit ... 30/- each
- Set of 5 assorted Bits to suit any job ... 20/- set
- Crystal Set kits ... 15/- each
- POCKET-SIZE MULTIMETERS.** AC/DC/Ohms ... £3
- Transistor Intercomm. Units ... 55/- pair
- FLUORESCENT FITTINGS:** 5ft. with choke and starter, 39/6; 4ft. with choke and starter, 32/6. Carriage 10/- per fitting.

ACOS PICK-UP HEADS. COMPLETE WITH NEEDLES
This is the price you would expect to pay for the needles only!

Monaural	14/-
Stereo	21/-
Diamond Stereo	28/9

Will fit most record changers. Can be very profitable!

RELAYS


700 ohm or 2,500 ohm coil. Transparent dust cover. 2 pairs of change-over contacts. PLUG-IN TYPE. Base included in price. 25/- each.
For orders less than 10/- please add 6d. towards postage.

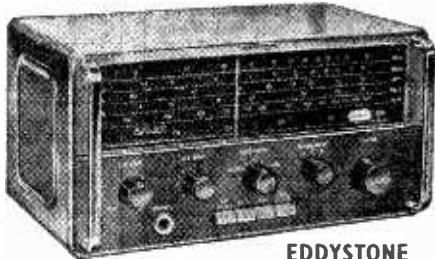G. F. MILWARD

17 PEEL CLOSE, DRAYTON BASSETT
Near TAMWORTH, STAFFORDSHIRE
Tamworth 2321 Post only



The Sensational
ALL-TRANSISTOR!
Communications Receiver



EDDYSTONE EC10


for use in the home, caravan, car or boat, H.P. facilities. Only £48 Part exchanges.

Write for brochure

170-172 CORPORATION STREET
BIRMINGHAM 4
Telephone CEN 1635

GUITAR AMPLIFIERS with TREMOLO

12 months' guarantee (valves 3 months)

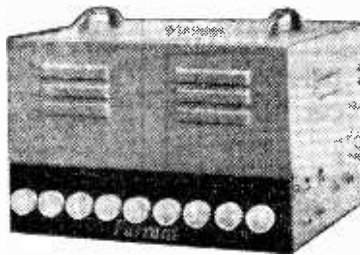

Five jack socket inputs with four separate mixing volume controls. High gain of 10 millivolts makes it suitable for all types of guitars and microphones. Separate Bass and Treble controls. Master gain control. Tremolo speed and depth controls. Remote tremolo switch socket. 7.5 and 15 ohms outputs. 30 and 50 watt valves

EOC83, EOC88, EL34, EL34, GZ31. 15 watt valves EOC83, EOC88, EL34, EL34, EZ81. Two extra valves EOC85 used in the tremolocircuit. Tremolo operates on one input only. Black and gold front panel (fitted tremolo type only at present). Chassis finished silver/grey hammer. Cover with chrome handles 45/- extra.


PRICES

50 watt with tremolo	£21.17.6
50 watt less tremolo	£18.10.0
30 watt with tremolo	£18.17.6
30 watt less tremolo	£14.10.0
15 watt with tremolo	£13.17.6
15 watt less tremolo	£11.10.0

Add carriage 10/- any amplifier. Descriptive leaflet free, stamp appreciated. Suitable speakers, Bakers 12" Guitar L.S. 5 gns. Bakers 15" Group 10 L.S. 18 gns. Carriage free.

Cash with order only regret no C.O.D. "No trade or Export"
STROUD AUDIO
CASHES GREEN ROAD, STROUD, GLOS. STROUD 788.

Fig. 20 depicts (a) original circuit of wind-on and re-rewind motors of typical three-motor machine, with loading resistor used to balance torque during Record or Playback. (b) Modified circuit using variable resistor to form bridge. (c) Motor torque varies as resistance (and hence applied voltage) is varied. Suitable for single-phase induction motors with no electrical connection between stator and rotor. Speed of motor is less than synchronous speed, the difference being the "slip" which increases as rotor speed decreases. The circuit allows relative torque variation. At point of intersection of curves, which depend on motor characteristics, motors are balanced and at standstill.

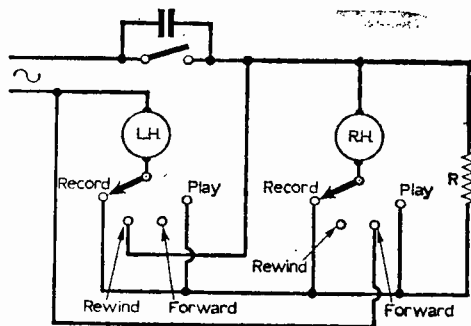

VARIABLE RELUCTANCE MICROPHONE

Older types of moving iron microphone come into this category, and are rarely used for present purposes. (See Microphones.)

VELOCITY MICROPHONE

A microphone in which the electric output substantially corresponds to the instantaneous particle velocity in the impressed sound wave. An example is the ribbon microphone, in which pressure gradient principle is employed, the difference in pressure between the two faces of the ribbon causing movement and electrical output. (See Microphones.)

VIDEO TAPE RECORDING

Method of recording television pictures on magnetic tape for subsequent replay. Problems involved are caused by the need for large bandwidth—at least 2 Mc/s—which calls for high speed of tape past heads. This can be achieved either by fast tape speed or by rotating a sequence of switched heads as the tape is moved. Fig. 21 shows basic rotating head system used for video tape recording. Two-inch Mylar tape is used at 15 in/sec. Headwheel spins at 15,000 r.p.m., giving relative head-to-tape speed of 1570 in/sec. Vision track is modulated on to an f.m. carrier from 42.2 to 6.8Mc/s before recording and demodulated after replay. There are four heads, and four channels, with each head having a 120 degree arc of tape contact—30 degrees of overlap. Each head is switched electrically during contact, and "killed" during out of contact period to reduce stray responses. Synchronising is supplied from servo control of motor and sync pulses are recorded on tape. Switching gate is controlled by photocell from motor into switching module.

The multiple head system scans the tape vertically with the tape at relatively slow speed. A tape speed of 7½ in/sec. will produce a track speed of 200 in/sec. or greater with rotating heads. As the tracks are nearly vertical, and in rotation, the tape must be wider than standard, and mechanical problems of speed regulation, head wear and synchronisation are encountered. Two such machines recently marketed have tape speeds of 12.6 and 19 cm/sec. and tape width of 50.8mm and 25.4mm respectively.

The alternative technique, of a stationary head

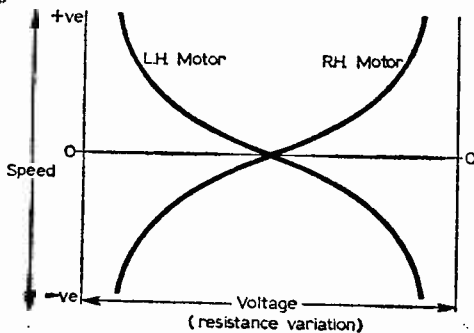
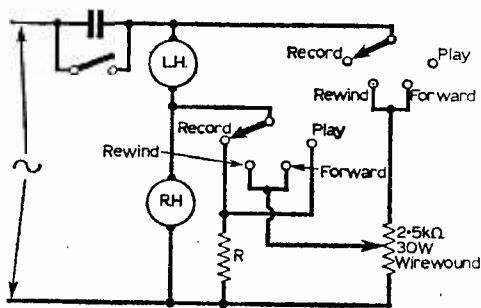


Fig. 20: Circuits of wind-on and rewind motors and motor torque graph.

and fast-moving tape, uses speeds of up to 150 in/sec., and a standard ¼in. tape, on which one track of video and another of f.m. sound are recorded. Typical head gap sizes are less than micron. (One example is the American Fairchild V-5000, using a tape speed of 120 in/sec., a standard ¼in. tape, and movable heads to scan four tracks. A single track is used with multiplexed video and audio signals. The record head has a relatively wide gap but the playback head gap is only 0.000039in. wide. Instrumentation tape is used, of 9,000ft. length on a 10½in. standard NAB spool.)

Later developments include thermoplastic video recording, first developed for radar equipment. A tape is prepared with a positively charged thermoplastic layer, which has a low melting point. The

basic negatively charged tape has a higher melting point. Thermoplastics soften when heated and return to normal condition on cooling.

The principle involves heating the whole tape to the melting point of the charged thermoplastic layer by passing it through a vacuum and applying a dielectric heater. Ripples are formed on the tape in proportion to the moving electron beam of the cathode ray tube through which it passes, the beam being modulated by the video information. The dielectric process causes the thermoplastic layer to "freeze" temporarily in its ripple formation as it passes through and this modulated tape is replayed by passing light through a condenser lens, the transparent tape and an apertured plate, using the Schlieren optical system. A very wide bandwidth (up to 50Mc/s) is possible. The drawback is the elaborate vacuum pumping equipment, but development of a special tube with a mosaic of fine wires in place of the normal phosphor screen is still taking place. The wires are embedded in the glass and pass right through, forming a virtual extension of the electron beam, and eliminating the complication of vacuum sealing of the tape at the point of modulation.

Recently announced was a video-disc method of recording with parallel principles, but using a method of repeated "stills" instead of a moving picture, stored on disc. The great advantage of such a system, if it can be developed beyond the slow-scan 25 frames per second limitation, is the simplicity of the playback conversion equipment.

VOLUME

Correctly, an acoustic, rather than electrical term. Measurement refers to the pressure of the sound wave in terms of dynes/square centimetre. The louder the sound, the greater the pressure, but

loudness, as a term, depends also on the frequency and waveform. Convenient form of volume expression is in decibels, this scale being nearer to the aural range than any linear form.

VOLUME COMPRESSION

System of sound recording where the level of the signal passing through an amplifier is arranged to control the gain in such a way that high sound levels are amplified less than low sound levels.

VOLUME UNIT (VU) METER

Type of modulation level indicator which measures electrical signal voltages and records relative levels of sound. This type of meter responds to average values but does not indicate peaks. Professional recording authorities favour peak programme meters for correct setting of modulation levels. American machines favour VU meters, the British and many Continental machines have various forms of peak reading meters or indicators (such as the magic eye) or modified forms of these, with rise times flattened slightly by charge circuits to give a compromise system.

A typical VU meter would be a rectifier-fed, moving-coil meter with a low total series resistance so that the non-linear forward characteristic of the rectifier makes it almost a square-law instrument, measuring energy or power rather than voltage or current. The scale is marked in volume units, each being approximate to one decibel with the instrument measuring a pure steady tone. But peaky waveforms will produce only the "averaged" response, sometimes referred to as the r.m.s. reading (not quite accurately, except with pure sine waveforms).

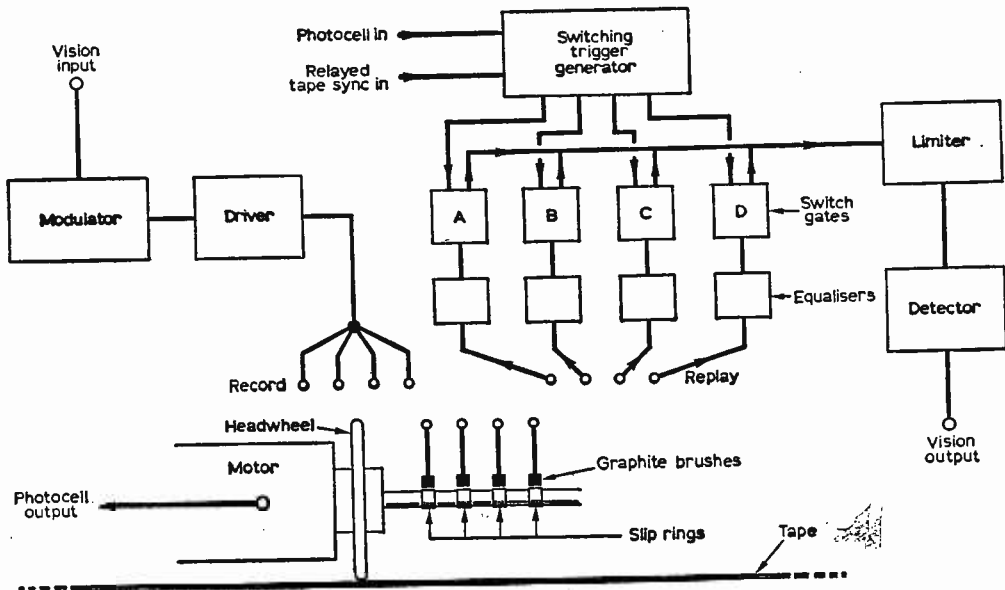


Fig. 21: Basic rotating head system for video recording.

CODAR - QUALITY

ANOTHER CODAR TRIUMPH!

THE NEW 1966 CR.70A COMMUNICATION RECEIVER

This completely new receiver sets a new high standard for performance and finish unequalled at the price, and is a worthy addition to the outstanding range of CODAR quality communication equipment. Frequency range: 560 Kc/s-30 Mc/s (540-10 metres) in four ranges: 560 Kc/s-1.5 Mc/s; 1.5 Mc/s-4.2 Mc/s; 4.2 Mc/s-11.5 Mc/s; 11.5 Mc/s-30 Mc/s. Slide rule scales for each band, calibrated in frequencies plus an additional logging scale in degrees. Two speed vernier tuning control with reverse slow tune action. Unique aerial input stage exclusive to the CR.70A employing High 'Q' Air-spaced CODAR-COIL inductor giving extremely high gain with low noise level. Panel aerial trimmer for peaking weak signals. Double tuned I.F. Iron core transformers. 470 Kc/s with EF83 frame grid valve for maximum gain and selectivity. 5 valves (including two twin triodes) giving 7 valve lineup. Separate B.F.O. stage for CW and SSB reception. Calibrated signal strength 'S' meter, illuminated. Automatic Volume control. Panel phone jack for "private" listening. 2-8 ohm output for external speaker. Superb styling, metal cabinet in the new Organosol Satin lustre finish. Size 13" x 5 1/2" x 7 1/4". For A.C. 200/250 v. Ready built. Not a kit at the fantastic low price of £19.10.0. Carr. 7/6.


CODAR R.F. PRE-SELECTOR MODEL P.R.30. Considerably improves the performance of any superhet receiver over 1.5-30Mc/s. Uses EF83 Frame Grid Valve, and provides up to 20dB gain plus substantial image rejection, improved signal/noise ratio and selectivity. Selector switch for either dipole or single wire antenna. Power requirements 180-250 volts 12mA H.T. 6.3v. 0.3 amp L.T. Size 8 1/2 x 5 x 4 1/2 in. Ready built, complete with cables, plugs and instructions, £5.10.0. Carr. 3/6. **MODEL P.R.R.30X.** Self powered version for 200-250v. A.C. Also provides 25mA at 20v. H.T. and 6.3v. 1 amp L.T. for other accessories £7.4.0. Carr. 3/6.

CODAR "Q" MULTIPLIER MODEL R.Q.10. For use with any superhet receiver with an I.F. between 450 and 470 Kc/s. Provides considerable increase in selectivity for either peaking or rejecting a signal on AM, CW, or SSB, BFO. Size 8 1/2 x 5 x 4 1/2 in. Power requirements 180-250v. H.T. at 5mA 6.3v. 3 amp L.T. Ready built complete with cables, plugs and instructions, £6.15.0. Carr. 3/6. **MODEL R.Q.10X.** Self powered version for 200-250v. A.C. and also provides 25mA at 20v. H.T. and 6.3v. 1 amp L.T. for other accessories £8.8.0. Carriage 3/6.

CODAR A.T.S. 12 WATT 2 BAND TRANSMITTER. The newest most compact transmitter for fixed or mobile use on 160-80 metres. "The tiny TX with the BIG voice" Size only 8 1/2 x 5 x 4 1/2 in. (Base area is less than two-thirds of this page!) High stability new type calibrated VFO. 1.8-2.0 Mc/s and 3.5-3.8 Mc/s (up to 4 Mc/s export). Air-spaced CODAR COIL Pi-net output. P.A. Plate current meter plus neon indicator. Plate-Screen modulator. AM/CW switch and Panel key jack. Plug changeover for 6 or 12 volts heater supply. Ready built £16.10.0 Carr. 4/- **A.T.S. POWER SUPPLY UNITS.** For 200/250v. A.C. and 12v. Solid state for Mobile use, complete with all Transmit/Receive changeover switching available.

CODAR-KIT CR.45K MAINS T.R.F. SHORT-WAVE RECEIVER. World wide reception—North and South America, Russia, India, Australia, Far East, Amateurs, Shipping, etc. ★ Separate electrical bandsread. ★ 3 slow motion vernier drives. ★ Low loss polystyrene plug-in coils, factory aligned. ★ Dials calibrated in frequencies and degrees. ★ Power output 2Watts for 2/8 ohm speaker. Valve line-up: ECC81, EL84, EZ80. Size 12 x 5 1/2 x 7 1/4 in. **CODAR-KIT CR.45k** complete with valves, 3 coils (10-28, 25-75, 60-176 metres) and 11 page instruction manual, £9.10.0. Carr. 5/6. Extra coils 4/9 each. Instruction manual only 4/- (credited on order). (Can also be supplied ready built—price on request).

CODAR-KIT MINI-CLIPPER—OUR FAMOUS SHORT-WAVE RECEIVER. Can be built in one evening ready to switch on and bring the World to your fingertips very low cost. ★ Supplied complete with valve, one coil 25-75 metres and 4-page instruction manual. PRICE 39/6. Carr. 3/-, Extra Coils 4/9 each. Instruction Manual only 2/- (credited on order). Electrical Bandsread available. Provision to add 2 transistor amplifier.

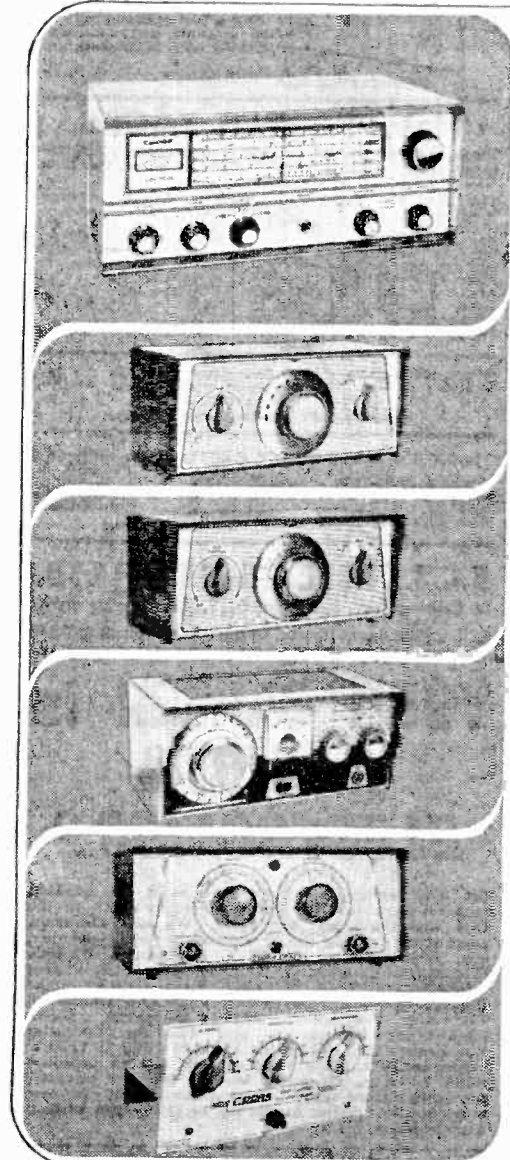

SEND 6d. IN STAMPS FOR ILLUS. LEAFLETS OF THE CODAR RANGE • H.P. TERMS AVAILABLE • WORLD-WIDE MAIL ORDER SERVICE




CODAR

CODAR RADIO COMPANY
 BANK HOUSE, SOUTHWICK SQUARE
 SOUTHWICK, SUSSEX. Tel. 3149
 G3JRE G3HGQ

Canada: Codar Radio of Canada, Tweed, Ontario.

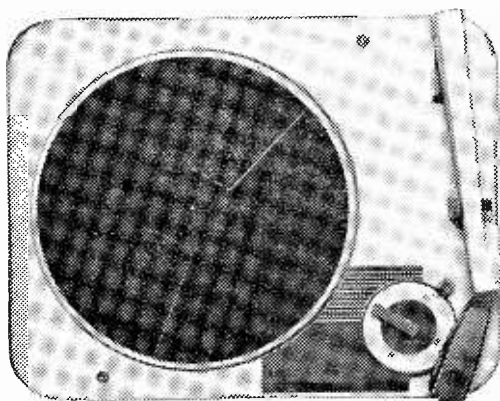An integrated hi-fi turntable unit from only 11 gns?



YES!

Only Goldring's 60 years of experience of making gramophone turntables and pick-ups could lead to a unit like this... the ideal integrated turntable, arm and pick-up for do-it-yourself hi-fi aspirants... at such a modest price. Just look at the features of this remarkable G.66 unit:

Silent, specially made Swiss mains motor. Pressed steel turntable on precision bearings evens out mains current fluctuations. Die-cast light alloy arm with full stylus pressure adjustment. Plug-in head shell, wired for mono and stereo, takes alternative pick-up cartridges. Eddy-current speed control (as fitted on some professional units) varies the four standard speeds by $\pm 10\%$. Pick-up raising/lowering device coupled to on/off switch and idler-wheel disengagement mechanism. Deck size $12\frac{1}{2}'' \times 10''$.

See the Goldring G.66 at your dealers—or write for descriptive leaflet.


THE GOLDRING G.66

G.66/MX.2 £9.18. 8 + £1.12.4 P.T. £11.11.0
 G.66/CS.80 £10.10. 0 + £1.14.2 P.T. £12. 4.2
 G.66/CS.90 £12.12.10 + £2. 1.2 P.T. £14.14.0



Goldring Manufacturing Co. (GB) Ltd.,
 486-488 High Road, Leytonstone, London E11
 Telephone: Leytonstone 8343

"TELSTAR" OUR EVER-POPULAR I-VALVE

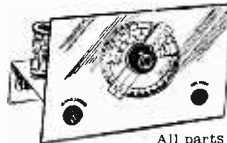

SHORT WAVE RADIO
 Receives speech and music from all over the world. Price includes valve and one coil covering 40-100 metres. Can be extended to cover 10-100 metres. Can be converted to 2 or 3 valve and all-mains speaker use. Total Building

All parts available separately **Costs 35/-** P. & P. 2/-

Mains POWER PACKS

The ideal economical and safe way of running any Transistor Radio, Record Player, Tape Recorder, Amplifier, etc. from A.C. Mains with complete safety.

The MAJOR "Power Plus" for 9v.; 6v.; 4.5v.; Single Output. P. & P. 2/6
 For 9v.+9v.; 6v.+6v.; 4.5v.+4.5v. Two separate outputs. P. & P. 2/6
Please state outputs required.
 All "Power Plus" units are completely isolated from mains by double wound transformer ensuring 100% safety.

The BLOU "Power Plus". For the smaller set using PP3 type battery. Supplied complete with special adaptor enabling you to reactivate your existing PP3 type battery. **17/6**

P. & P. 2/6.

The "POP-6" 6 Transistor Portable complete with battery, case and earpiece. **62/6**
 P. & P. 2/6

Really pulls in those pirate stations.

READY TO USE POCKET RADIO

Covers Medium waveband. No batteries needed. Complete with earpiece. **ONLY 9/11**
 P. & P. 2/-



R.C.S. PRODUCTS (RADIO) LTD.

11 Oliver Rd., London, E.17. (Mail Order only)

Export Trade Enquiries Invited

YOUR CAREER in RADIO & ELECTRONICS?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the **CITY & GUILDS EXAMS**, (Technicians' Certificates); the Grad. Brit. I.R.E. Exam.; the **RADIO AMATEUR'S LICENCE**; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have **OVER 20 YEARS'** experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronic subjects only. Full details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.
 Please send FREE BROCHURE to:

NAME.....Block

ADDRESS.....Caps.

..... Please 1.66

BRITISH NATIONAL RADIO SCHOOL

WATT

The unit of electrical power. Defined as the energy expended per second by an unvarying electric current of one ampere across a potential difference of one volt. For audio purposes, both the peak power and the average power must be considered. Electro-acoustic efficiency is less than purely electrical measurement may indicate. Electro-acoustic efficiency ratio may be as much as 30:1 with commercial equipment. A speaker efficiency is only some 3 to 5% under normal domestic conditions, so that an amplifier with an average audio output of 10 watts is adequate for domestic purposes, even if transient peak powers are as much as 40 watts. Most domestic tape recorders with inbuilt speakers are only intended to give about 2-5 watts audio output, which is quite sufficient for normal purposes.

WAVELENGTH

In tape recording, directly related to the speed and frequency of the medium; i.e. the frequency of signal and the speed at which the tape passes the head gap, which determines the physical wavelength of the recorded "magnet" on the tape. Wavelengths become shorter as the frequency of the applied signal increases, but longer as the speed of tape transport increases. This is important during playback, where the higher speed permits use of a wider gap for a given frequency due to the extended wavelength, or, conversely, allows a higher frequency response for the same gap when the tape is recorded and replayed at a higher speed.

WOW

Distortion caused by periodic variation of tape speed. Although there is no standard, variations of up to twenty times a second in pitch of the sound are generally considered as "wow" while variations in the band 20-200c/s are called "flutter". Wow is more evident with sustained notes and music with "dying tones" such as piano and organ music. It is usually caused by eccentricity in moving parts. Regularity of the wow may be a clue to its origin. Flutter has the effect of making the tone harsh, and is often more difficult to determine. Its results sometimes sound like an overloaded amplifier due to frequency modulation of the recorded signal. Wow and flutter figures are stated as an R.M.S. measurement, typical specification being "less than 0.2% total r.m.s.". More than 0.5% is poor.

In Table 1 reel sizes in inches, tape length in feet, playing times in minutes and seconds for principal types of tape in general use. There are variations of tape length, and playing time between manufacturers. Figures given are common to the largest number of companies. Playing time is for a single track at $3\frac{1}{2}$ in./sec. For alternative speeds divide and multiply by factors of 2. For complete tape playing time on more than one track multiply by number of recorded tracks (except for stereo).

End of Series

FREE INSIDE NEXT MONTH'S PRACTICAL WIRELESS

DOUBLE-SIDED BLUEPRINT to build a PROGRESSIVE SHORT WAVE RECEIVER

Includes full constructional details, with instructions for the following additional facilities:— Tuned r.f. Amplifier Stage, I.F. Regeneration, Bandsread Tuning, Send/Receive Switching and Tuning Indicator.

Other Constructional Features include:—
QUIZ MACHINE FOR EXPERIMENTORS,
CLUBS AND SCHOOLS
MINI MODULATOR
ADD-ON TRANSISTOR STAGE



ORDER YOUR COPY NOW!

ELECTRONIC PITCH-PIPES

by

R. Bebbington

Grad. I.E.R.E.

ANYONE who has had anything to do with training or conducting choirs will appreciate the value of a set of pitch-pipes. Pianos are not always situated conveniently adjacent to the choir and to pitch the notes of the initial chord for unaccompanied singing can be something of a problem. The author knows from bitter experience that the notes you play on the piano and the notes you sing to the choir on your return—after knocking over a few music stands and negotiating several rows of seats—are not always the same. Usually the tenors will be quick to point this out to you, that is if the effort of reaching a top A that should only have been a top F has not permanently strained their vocal chords. The electronic pitch-pipes to be described have been used successfully for male voice singing and have been particularly useful for open-air activities.

Circuit Theory

The transistorised version of the well-known Hartley oscillator is employed as a high degree of stability can be obtained. Even with battery ageing there is no discernible variation in pitch, which means that the device may also be used as

a pitch or frequency standard for other purposes. The output of the oscillator is fed straight into a high-impedance miniature loudspeaker which serves as the collector load. Sufficient volume is obtained to allow the unit to be operated inconspicuously in a coat pocket and still be heard. Should extra volume be required an output stage can easily be added and a resistor substituted for the oscillator collector load. In its simplest form the unit can be really compact, the prototype measuring 4in. x 3in. x 1½in. The frequency determining components are the tapped coil, the capacitors across it and, in the simplified version, the series variable resistor.

For accurate pitch control a capacitor for each note is preferable and this requires a single-pole, 12-way switch to cover every semitone in a complete octave or musical scale. It is extremely

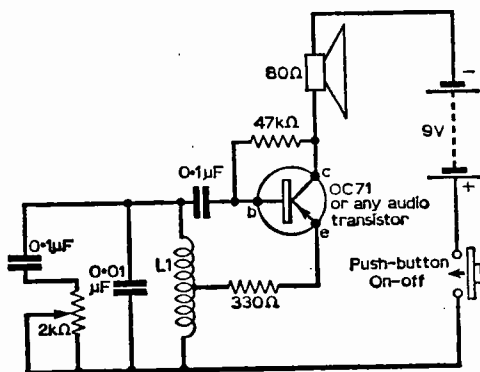


Fig. 2: Tones selected by potentiometer (see Fig. 4).

unlikely that exact values of capacitors will be found to tune each note in the scale and padding by smaller values will have to be done. If you are incapable of doing this, even with the aid of a piano, borrow the ear of a musical friend. If extreme accuracy is not so important the variable resistor is an easier and cheaper method of frequency control and can be quickly calibrated.

With the components listed in Fig. 2 the 2kΩ variable control has a frequency range of one octave from E flat to E flat.

Choice of coil will obviously influence the precise location of the frequency range, but this is immaterial as long as a complete octave is covered, since this is bound to embrace all the notes in any musical scale. However, as the coil is the only item that is not standard some details are perhaps called for at this stage. Many tapped coils have been tried and the circuit oscillated freely with most of them. These included inter-valve transformers, television blocking oscillator transformers, the tapped primary of a standard output transformer,

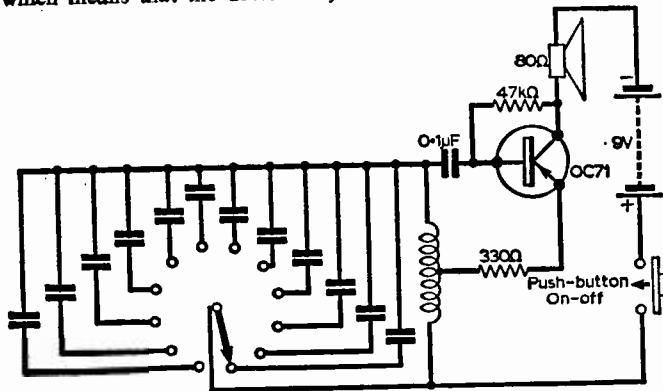


Fig. 1: Tones selected by switched capacitors.

IMPROVED

STANDARDS OF

ACCURACY AND RELIABILITY

Improved internal assemblies.

Re-styled scale plate for easy rapid reading. 2 basic scales, each 2.5 inches in length.

New standards of accuracy, using an individual calibrated scale plate: d.c. ranges 2.25% f.s.d. a.c. ranges 2.75% f.s.d.

Available accessories include a 2500V d.c. multiplier and 5, 10 and 25A shunts for d.c. current measurement.



Mk 4

MULTIMINOR

The instrument is supplied in an attractive black carrying case, which also houses a pair of leads with interchangeable prods and clips, and an instruction booklet. It is packed in an attractive display carton. Robust real leather cases are available, if required, in two sizes, one to take the instrument with leads, clips and prods, and the other to house these and also a high voltage multiplier and a d.c. shunt.

As from 1st November 1965, Avo are operating a new net Price List. Full details on request.

D.C. Current: 100µA f.s.d.—1A f.s.d. in 5 ranges
A.C. Voltage: 10V f.s.d.—1,000 f.s.d. in 5 ranges
D.C. Voltage: 2.5V f.s.d.—1,000 f.s.d. in 6 ranges
D.C. Millivolt range: 0 —100mV f.s.d.

Resistance: 0-2 MΩ in 2 ranges using 1.5V cell.
Sensitivity: 10,000Ω/V on d.c. Voltage ranges.
1,000Ω/V on a.c. Voltage ranges.

● For full details of this pocket-size instrument, write for descriptive leaflet.

AVO LTD

AVOCET HOUSE - 92-96 VAUXHALL BRIDGE ROAD - LONDON, S.W.1 - Phone: VICTORIA 3404



MM17

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronic Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

SATISFACTION OR REFUND OF FEE.

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £20 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.,
Electrical Eng.,
Civil Engineering,
Radio Engineering,
Automobile Eng.,
Aeronautical Eng.,
Production Eng.,
Building, Plastics,
Draftsmanship,
Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

A.M.I.Mech.E.
A.M.I.C.E.
A.M.I.Prod.M.
A.M.I.M.I.
A.I.O.R.
E.S.O.
A.N.I.E.R.E.
City & Guilds
Gen. Cert. of Education
Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V., Electronics Etc., A.M.I.E.R.E., City & Guilds
Radio Amateur's Exam
R.T.R.E. Certificate
P.M.G. Certificate
Practical Radio
Radio & Television Servicing
Practical Electronics
Electronics Engineering
Automation

INCLUDING TOOLS!

The specialist Electronic Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details

B.I.E.T. SCHOOL OF ELECTRONICS



POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES" (Write if you prefer not to cut page)

NAME

ADDRESS

.....

SUBJECT OR EXAM THAT INTERESTS ME..... (SE/21).

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
(Dept. SE/21), 29 Wright's Lane, London, W.8

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

etc. The latter was used successfully without laminations and a tapping was soldered on after exposing the primary layers by bending back one of the end cheeks. The exact position of the tap was not found to be critical.

Practical Layout

No hard and fast rules are given as regards size of unit as this will be dictated by the components available to the constructor. If a 2 1/2 in. loudspeaker is used an extremely portable unit may be built around it, particularly if resistance tuning is employed. Readers who are used to working from a theoretical diagram will no doubt have their own ideas about the practical layout and this should not present any problems. However, for the less experienced constructor and those who prefer to work from a wiring diagram a suitable layout is given.

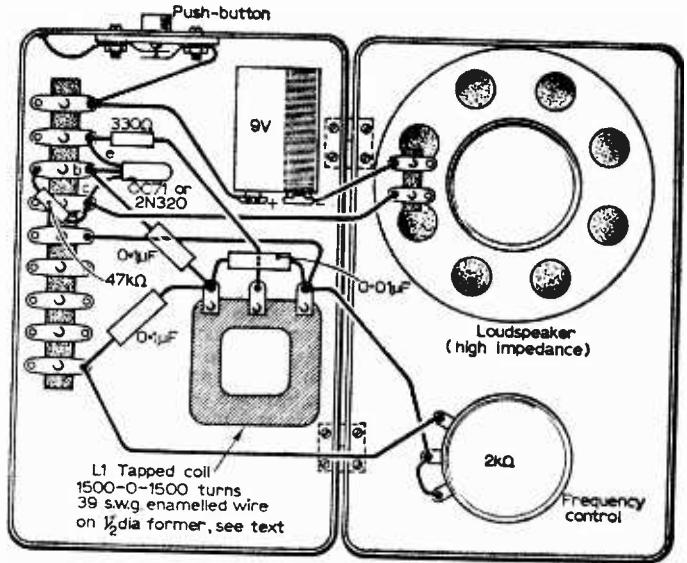


Fig. 3: Wiring diagram and layout of Fig. 2.

A small tin box was used to house the experimental model, the loudspeaker and tuning control being attached to the lid. Construction was simplified as the tagstrip and the "earthy" side of components could be soldered directly to the case. One slight drawback was that initial tuning and calibrating had to be carried out with the lid closed as the proximity of the metal lowered the pitch about a semitone by increasing the inductance of the coil. With a plastic case the problem of hand capacity might arise.

A 9V battery such as the Vidor VT3 was chosen because these are physically small but there is no reason why external batteries should not be used. Where space is no criterion a larger speaker may be utilised and this may have the more usual low-impedance speech coil if it is connected through a transistor output matching transformer.

Advantage was taken of the case being metallic to solder one of the push-switch contacts to it, the other contact being soldered to one of the adjacent points on the tagstrip. A half-inch length of thick copper wire soldered to the "earthy" contact and fitted with a small length of sleeving serves admirably as a push button. A hole should be suitably drilled, as indicated in the diagram, for this to protrude slightly through the side of the case.

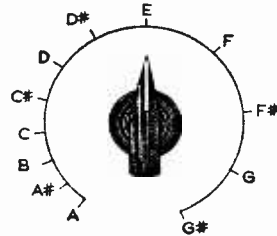


Fig. 4: Dial for the 2kΩ potentiometer in Fig. 2.

Calibration

Once the capacitors have been selected in the switched version a permanent scale can be accurately scribed as the 12 semitones will be equidistant on the positions of the switch. If the simpler resistor method of tuning is used, then there will be cramping towards the lower notes which could result in some slight pitch inaccuracies due to difficulties in reading the scale. Generally these would be too small to be serious.

Should the frequencies covered be too high in the musical range these may be lowered by increasing the fixed capacitor across the coil or, alternatively, inserting an iron core in the coil.

(Chromatics) A# C D# F G

Diatonic Notes	A	B	C#	D	E	F#	G#	A
Capacitor (μF)	0.2	0.17	0.14	0.12	0.1	0.08	0.06	0.05

Approximate values of the switched capacitors for the scale of A Major (3 sharps). The values for the chromatic semi-tones lie approximately half-way between adjacent notes.

A COMMENTARY BY HENRY

PRACTICALLY WIRELESS

No. 17

Illogical Conclusions

THAT hilarious pantomime "The March of Progress" has earned a few deft sideswipes from Henry's bladder. Any jester worth his cap and bells could hardly miss a target so wide.

In the field of telecommunications it would seem that Progress—with a capital—is marching onward with the relentless determination of a hungry rhinoceros. Every trade magazine we pick up heralds new approaches, developments, devices and even ideas. Editors delight in crystal gazing or, unforgivably, reminding us how accurate their predictions of a half-century ago have turned out to be.

Boffins—not to be outdone—brush up their syntax and publish the intimate details of their experiments. Scribes like me absorb the gist and breathe out hot air about "The Sets of Tomorrow" or less precisely, "New Concepts". The innocent bystander may be forgiven for thinking us all a dynamic class of citizens, leading the backward plodders of Industry and Commerce into some brave new world beyond the horizon.

One has only to read the dismal history of Colour TV to see what is meant. In the November issue of *Practical Television* the Editor recounted his remarkable dream—which ended with a delegate to one of those interminable Colour Television Standards Conferences crying: "But do we really need colour TV?"

Mr. Sidney Bernstein and Lord



... the relentless determination of a hungry rhinoceros.

Thomson, chairmen of Granada and Scottish Television respectively, have come out against premature launching. This does not mean that either of these extremely astute gentlemen is a reactionary diehard. Their kick is not against progress, so much as against the effect mistiming of decisions may have upon their profits.

And to be sure, decisions are not likely to be timed at all if the last breakdown of talks, following hard on a hasty "final" SECAM demonstration, is indicative.

The ironic fact that Henry is trying to wrinkle out and lay before you, dear Reader, is that technical magazines were running series of articles on Colour TV Principles, or Servicing Colour Receivers as much as ten years ago.

These were based on American experience, to be sure. Yet it is worth remembering that it is only as lately as 1964 that the larger companies in the States were able to make Colour TV pay. Last year, for the first time, colour TV sales overtook black-and-white receivers. What price Progress?

Getting away from radio's founding, let's ask each other: "What sort of wireless signal are you getting?" Short of stringing the surrounding rooftops with piano-wire pigeon traps and digging below plastic water-main level for the earth return, can you pick up interference-free programmes?

I being naive in suggesting that a logical conclusion is some form of communal aerial system? To indulge in another Progress Prediction, the future should bring all communication services, radio, TV, what-have-you to the house via a single pipeline. Water, Gas, Electricity, Telecoms, each with its inaccessible stop-cock and horrible quarterly bill.

Rather like the Editor's dream, you may say. And after



Digging for the earth return.

reading of the furore at Cwmbran New Town last autumn, I'd be inclined to agree. There, the Corporation decided to be in the van of progress by wiring their beautifully planned houses for all services and putting a one-and-sixpenny charge on the rates. But the concession was given to a relay company and the local traders came out strongly in protest to the local press. One can hardly blame them when the pipeline people are also their greatest rivals in the set retail business. There's not much living left in selling radiograms and tape recorders. Even if (see last month) Dame Progress hands us videotape on a plate.

The joke is that BBC2 had just then opened in the area and both radio dealers and pipeline technicians were chasing madly up and down the Welsh Mountains in search of the u.h.f. signals. Considering the ban on rooftop aerials that is imposed in the New Town, developments should be of some interest to followers of the pantomime called Progress.

When colour TV does come along, we wonder what the residents who voted against the levy on the rates will say. Possibly: "I don't care about the bloke down the road, Jack, My 'Coronation Street' comes through OK".

That should please Mr. Bernstein, at least.

BENTLEY ACOUSTIC CORPORATION LTD. Suppliers to H.M. Government. 38 CHALCOT ROAD, LONDON, N.W.1 Telephone: PRIMROSE 9090

NEAREST UNDERGROUND: CHALK FARM. ALL GOODS ARE NEW, BEST QUALITY BRANDS ONLY, AND SUBJECT TO MAKERS' FULL GUARANTEE. PLEASE NOTE THAT WE DO NOT SELL ITEMS FROM USED EQUIPMENT NOR MANUFACTURERS' SECONDS & REJECTS, WHICH ARE OFTEN DESCRIBED AS "NEW AND TESTED" BUT HAVE A SHORT AND UNRELIABLE LIFE.

Table listing electronic components such as resistors, capacitors, and diodes with their respective part numbers, values, and manufacturers.

WE REQUIRE FOR PROMPT CASH SETTLEMENT ALL TYPES OF VALVES, LOOSE OR BOXED, BUT MUST BE NEW METAL RECTIFIERS, 6X4, 6X5, 6X6, 6X999, 6X1000.

EXPRESS POSTAL SERVICE! ALL ORDERS DESPATCHED SAME DAY AS RECEIVED

Terms of business—Cash with order only. Post/Packing 6d. per item. Orders over £5 post free. No C.O.D. All orders cleared day of receipt. Any parcel insured against damage in transit for 6d. extra. We are open for personal shoppers 9.00—5 p.m. Sat. 9.00—1 p.m. Complete list of models and obsolete valves, resistors, condensers, transformers, potentiometers, microphones, etc. with terms of business 6d. Please enquire for any item not listed with S.A.E.

R.S.T. VALVE MAIL ORDER CO.

211a STREATHAM ROAD, MITCHAM, SURREY

Mon—Sat. 9 a.m.—5.45 p.m.
 Wednesday 1 p.m.—Open Daily to Callers
 Tel. MITcham 6202

0A2	5/3	6BR7	10/8	6L1	9/8	10LD11	10/-	30C1	6/6	ATP4	1/8	EB91	3/-	EF98	10/-	N78	15/-	PY83	6/-	UC183	8/9	
0C3	5/3	6BR8	7/6	6L6G	7/-	10P13	12/6	30P17	12/-	ATP5	7/-	EB93	6/8	EF103	6/8	N108	15/-	PY800	5/9	UCF41	7/9	
1A7	7/9	6BS7	15/-	6L14	7/6	12A18	10/6	30P5	5/-	ATP7	4/6	EB94	4/6	EF184	6/8	SG11	3/-	PY801	6/3	UCF99	6/1-	
105	6/1	6BW6	8/6	6Q7G	5/6	12A76	4/6	30P11	10/6	AU2	30/-	EB96	3/6	EL22	3/-	SGT	25/-	R2	4/-	UL41	6/9	
1H5	7/6	6RW7	8/6	6Q7HT	9/-	12A77	3/3	30L15	12/-	A15	6/-	EBF60	5/-	EL33	17/6	OZ4	4/-	R19	7/-	UL84	5/6	
1N5GT	9/-	6C4	1/9	6R47	7/-	12A78	5/9	30L17	12/6	A21	8/9	EBF83	7/3	EL34	9/6	PC86	10/-	R05/500	UM80	7/-	UM80	7/-
1R5	5/-	6C6	3/6	6R67	4/-	12A79	4/6	30P19	14/-	CB11	12/6	EBF89	5/9	EL41	7/3	PC88	9/3	59/-	UT6	13/6	UT6	13/6
184	3/5	6C8G	6/-	6R7	2/6	12A80	6/6	30P11	11/-	CK502	5/-	EBL1	17/6	EL42	7/6	PC97	7/6	S130	10/-	UT7	10/6	
185	3/5	6C8GG	22/6	6R7	2/6	12A81	5/-	30P11	12/6	CL33	12/6	EBL21	10/6	EL43	4/6	PC98	5/6	SP4	9/-	UT9	8/-	
174	2/6	6C9H	3/-	6R7	2/6	12A82	4/6	30P11	12/6	CV31	10/-	ECC81	3/3	EL93	6/1	PC99	8/6	SP41	1/6	UY21	7/6	
344	3/6	6C9W4	14/-	6R15GT	4/9	12A83	7/6	30P14	12/6	DA32	7/6	ECC82	5/6	EM34	9/-	PCF80	6/6	SP81	1/-	UY41	4/6	
305	6/6	6D	5/9	6R97	10/-	12A84	5/6	35L6	5/9	DAF91	3/3	ECC83	4/6	EM30	6/1	PCF82	6/6	SU25	18/6	UY85	4/9	
384	4/9	6F1	9/-	6U4GT	6/-	12A85	2/3	35W4	4/9	DAF96	6/-	ECC84	5/6	EM81	7/-	PCF84	8/-	T41	8/-	VCR517B	30/-	
3V4	6/-	6F5G	9/-	6U5G	7/6	12A86	3/1	35ZAGT	3/9	DF33	5/6	ECC85	5/9	EM84	6/1	PCF86	8/6	T44	20/-	VCR517C	30/-	
3E4G	8/-	6F6	4/6	6V	8/-	12A87	8/3	35Z	5/6	DF70	5/6	ECC86	6/8	EY51	6/6	PCF802	9/9	U10	7/-	VMP4G	17/-	
5U4G	4/-	6F8G	4/6	6V6G	3/6	12Q7G	3/3	37	5/6	DF91	2/6	ECC87	6/1	EY86	6/3	PCF806	10/6	U14	7/-	VR105/305	5/-	
5V4G	8/-	6F11	12/6	6V6GT	7/6	12A87	6/6	42	4/6	DF92	2/6	ECC88	10/6	EY85	4/9	PCF808	12/6	U25	10/-	VR150/305	5/-	
5Y3GT	4/6	6F13	5/-	6X4	3/6	12A88	3/6	50B5	6/6	DF96	6/-	ECC89	13/6	EZ40	5/6	PCF808	12/6	U26	10/-	VT25	12/6	
5Z4GT	8/-	6F14	12/6	6X5G	4/9	12A89	2/9	50C5	6/3	DK17	3/6	ECC90	8/6	EZ41	6/1	PCF82	6/6	U26	10/-	VT25	12/6	
630L2	19/-	6P23	9/6	6X5GT	7/6	12A90	3/9	50C6G	24/9	DK32	7/9	ECC91	5/6	EZ80	5/6	PCF82	8/-	U78	3/6	VT81	59/-	
6A7	15/-	6G6	2/6	7B6	11/-	12A91	2/9	50D6G	24/9	DK91	5/6	ECC92	6/6	EZ81	3/6	PCF84	7/6	U191	11/-	VU11	6/-	
6A8G	6/6	6H6	1/3	7B7	7/6	12A92	5/6	75	5/6	DK92	7/9	ECC93	6/6	EZ82	8/6	PCF86	8/9	U301	12/-	VU508	25/-	
6AC7	3/-	6J5M	6/6	7C5	10/-	1487	20/-	78	4/6	DK96	6/6	ECC94	9/9	EZ84	9/9	PCF84	20/-	U403	6/6	W81M	5/6	
6AK5	4/6	6J6	2/6	7C6	6/6	15A45	7/6	80	5/6	DL70	7/-	ECC95	8/6	EZ86	22/6	PCF84	20/-	U403	18/6	X78	28/6	
6AL5	3/-	6J6GT	4/3	7D5	8/-	2011	10/-	813	80/-	DL92	4/6	ECC96	8/6	EZ86	22/6	PCF84	20/-	U403	18/6	X78	28/6	
6AM6	2/9	6J7M	8/6	7H7	5/-	20P2	11/-	85A2	8/6	DL93	3/6	ECC97	20/-	KT61	17/6	PCF86	20/-	U403	18/6	X78	28/6	
6AQ5	6/-	6J7G	4/3	7H7	5/6	20P4	14/-	150B2	11/6	DL94	6/-	ECC98	20/-	KT66	12/6	PCF86	20/-	U403	18/6	X78	28/6	
6A87	22/6	6J7GT	7/-	7Y4	5/-	20P5	12/-	801	5/6	DL95	6/6	ECC99	8/6	KT74	9/6	PCF86	20/-	U403	18/6	X78	28/6	
6AT6	3/6	6K8GT	5/-	9BW6	8/-	25A6	6/6	807	7/9	DM70	5/6	ECC99	8/6	KT76	12/6	PCF86	20/-	U403	18/6	X78	28/6	
6A06	6/-	6K7M	5/-	10C1	9/-	25L6GT	4/6	866	10/-	DY36	7/6	ECC99	8/6	KT76	12/6	PCF86	20/-	U403	18/6	X78	28/6	
6B8G	2/-	6K7G	1/3	10C2	12/-	25Y5	6/-	954	4/-	DY87	7/9	ECC99	8/6	KT76	12/6	PCF86	20/-	U403	18/6	X78	28/6	
6BA8	4/9	6K7GT	4/6	10P1	12/6	35Z4	6/3	925	5/6	EB88C	14/-	ECC99	8/6	KT76	12/6	PCF86	20/-	U403	18/6	X78	28/6	
6BE6	4/9	6K8M	8/6	10P3	12/6	35Z5	7/6	4022AB	5/-	EASO	2/6	ECC99	8/6	KT76	12/6	PCF86	20/-	U403	18/6	X78	28/6	
6BE6	7/-	6K8G	3/6	10P9	9/9	25Z6	8/6	5763	10/6	RABC80	5/6	ECC99	8/6	KT76	12/6	PCF86	20/-	U403	18/6	X78	28/6	
6B76	6/6	6K8GT	8/3	10P18	9/-	28D7	5/-	7193	1/6	EAF42	7/6	ECC99	8/6	KT76	12/6	PCF86	20/-	U403	18/6	X78	28/6	
6BQ7A	7/6	6K25	20/-	10L1	10/-	30C15	9/6	7475	2/6	EB41	4/6	ECC99	8/6	KT76	12/6	PCF86	20/-	U403	18/6	X78	28/6	

SPECIAL 24 HOUR SERVICE

OBsolete TYPES A SPECIALITY

QUOTATIONS FOR ANY VALVE NOT LISTED

Postage 6d. per Valve. C.W.O. No C.O.D.

Special 24 Hour

Express Mail

Order Service

SETS OF VALVES

DAF91, DF91, DK91, DL92, DL94	Set of 4, 19/-
DAF96, DF96, DK96, DL96	Set of 4, 25/-

BRAND NEW TRANSISTORS

OC35	9/6	OC72	6/-	OC81D	4/-
OC44	4/6	OC81	4/-	OC82	6/-
OC45	3/6	OC81m/pr	12/6	OC82D	6/-
OC71	4/6				



HOME RADIO LTD

187 LONDON RD., MITCHAM SURREY. *Phone MIT 3282

Santa appreciates a good catalogue when he sees one, so perhaps he can be forgiven for getting so absorbed in a HOME RADIO Catalogue that Rudolph has to remind him how time is slipping by! Perhaps one of the copies in that pile on the floor is earmarked for you, but to be on the safe side send off the coupon below with your cheque or P.O.* Time is slipping by... act now!


Please write your name and address in block capitals

NAME _____

ADDRESS _____

HOME RADIO LTD., DEPT. P.W. 187 LONDON ROAD, MITCHAM

AN ECONOMY TWO-BAND RECEIVER

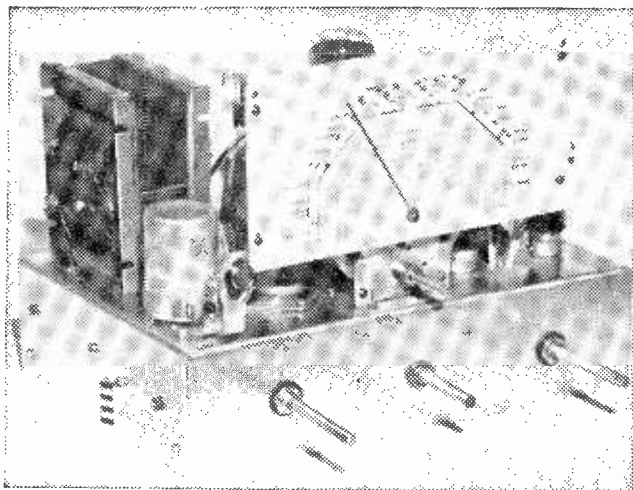

by J. B. WILLMOTT

IN a recent article in this magazine, describing the numerous uses to which the EF50 type valve, now so widely obtainable from advertisers in this magazine at give away prices (frequently as little as 1s. 6d. each), the author made reference to a receiver designed and constructed over 10 years ago. This has given completely trouble free service, and accordingly a further prototype has now been constructed, using components currently obtainable. The receiver described here follows closely along the lines of the original design: it is capable of giving really good quality reproduction of local Medium and Long Waveband BBC programmes in good reception areas.

Obviously no "straight" (or superhet) receiver can give the same freedom from background noise or interference by Continental stations after dark.

as an f.m. receiver; but in areas of good BBC reception, extremely good results are assured, at a fraction of the cost of purchasing or assembling an f.m. receiver. In areas where the Light Programme is strongly received on Medium Waves, such for example as London, the Long Wave tuning coils and the attendant complication of wavechange switching, can be omitted entirely.

A double-wound mains transformer is specified and thus the chassis of the completed receiver is completely isolated from the mains supply and therefore safe to handle. A direct earth connection is recommended and it is surprising how much improvement in performance and lowering of background noise results from this often neglected connection.

Layout is not unduly critical apart from the

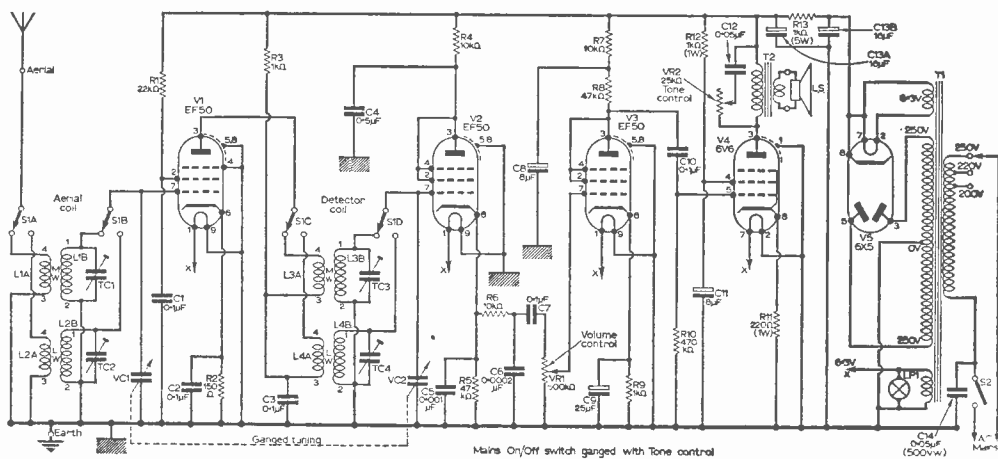


Fig. 1: Complete theoretical circuit diagram.

essential need to separate the r.f. and detector tuning circuits (achieved by mounting the respective tuning coils above and below chassis respectively) but it is suggested that the layout shown in Figs. 2 and 3 would be difficult to improve upon as it results in a neat and symmetrical disposition of components as well as ensuring shortness of wiring. A full list of all components required is given and there should be no difficulty in obtaining any of them from component stockists.

Briefly the circuit comprises an r.f. amplifier stage (V1), followed by an infinite impedance detector (V2), noted for its low distortion. Then follows an a.f. amplifier stage (V3), feeding into the power output stage (V4) power being supplied from the mains through a double-wound mains transformer with full-wave rectification provided by V5.

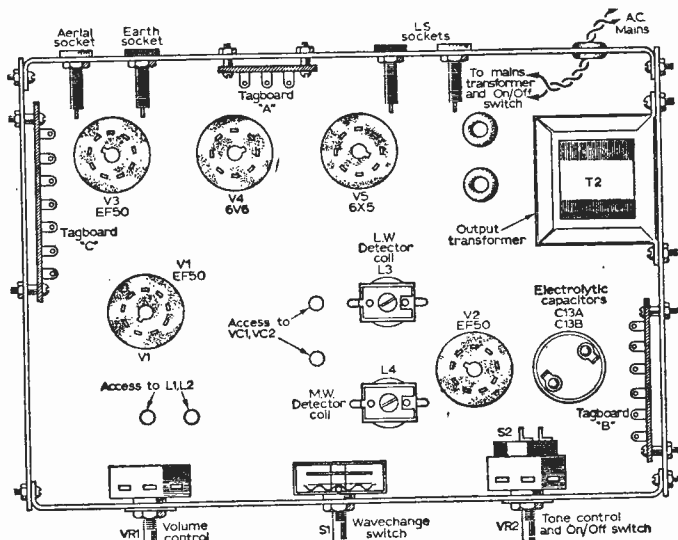


Fig. 2: Suggested underchassis layout.

Preparation of Chassis and Component Mounting

A ready-made four-sided aluminium chassis, dimensions 10in. x 7in. x 2½in., which is a "standard" size, is specified and the details of drilling to be carried out are clearly shown in Fig. 3. The sizes of the various holes can be found by reference to the chart at the top of the diagram. The large valvholder cutouts are not all of the same size, a point which must be borne in mind, those for V1, V2 and V3 being 1½in. diameter, V4 and V5 are 1¼in. diameter and the hole to accommodate C13 should be 1¼in. diameter. Established constructors will no doubt have the necessary range of screw-up-type hole cutters for the purpose but with patience these holes can be made by drilling a series of small holes around the circumference of each large hole, pushing out the centre blank and cleaning up with a file. This is admittedly somewhat tedious and investment in a set of hole cutters is strongly advised if any quantity of constructional work is envisaged in the future.

It will be noted that three of the holes marked "D" on the upper chassis surface and a further hole on the rear chassis should be fitted with rubber insulating grommets. It is through these holes that leads carrying mains supply or mains transformer connections will pass. The exact position of fixing holes for valvholders and the mains transformer are best marked out on the chassis surface, using the actual components as a template. Make certain that the valvholders are positioned so that the locating spigots take up the direction indicated by the spigots in Fig. 2. The fixing holes for the two-gang tuning capacitor and the "I.B. Full Vision Dial Assembly" are clearly shown. Obviously if any other make of tuning capacitor or dial assembly is used the position of these fixing holes will need to be amended. The


two holes "D" near the centre of the area occupied by the gang capacitor provide for connecting wires to the lower tags on the fixed plates of this component passing through the chassis to the wavechange switch.

Mounting of components can begin as soon as all drilling is completed and it is recommended that all valvholders be fitted first, using 6BA nuts and bolts. A solder tag should be secured under the chassis to the fixing bolt nearest pins 1 and 9 on V1 to V3 inclusive and nearest to pins 1 and 8 on V4. A further solder tag should be secured above chassis on the fixing bolt of V1 valvholder nearest the holes "E" midway between L1 and L2 positions and also to the fixing bolt of valvholder V5 nearest to the mains transformer.

Attention should now be turned to fixing the full vision tuning dial assembly. This dial provides three-waveband indication but the short wave band is, of course, ignored in this design. The two-gang tuning capacitor is mounted on long 4BA bolts, using additional nuts (or brass spacers) to support it at the correct height above chassis for the spindle to accurately register with the driving boss on the drive assembly. Check to ensure that the drive operates smoothly and without strain before finally tightening the mounting bolts of the gang. It is advisable to solder a 6in. length of connecting wire to each of the two-gang lower tags before mounting the component, these wires being fed through the appropriate holes "D". Ultimately they will be cut to length and covered by insulating sleeving when wiring-up is carried out.

Next mount the mains transformer, seeing that the primary winding tags are nearest the side of the chassis. This will ensure that mains supply leads coming up through the single hole "D" are conveniently placed for connection to the primary winding, whilst secondary winding connections

**INCREASE
YOUR
KNOWLEDGE**



**RADIO
TELEVISION
ELECTRONIC
ENGINEERING**

MEMBER OF THE ASSOCIATION
OF BRITISH CORRESPONDENCE COLLEGES

CHOOSE THE RIGHT COURSE FROM:

RADIO AND TELEVISION ENGINEERING, INDUSTRIAL TELEVISION, RADIO AND TELEVISION SERVICING, ELECTRONICS, COMPUTERS AND PROGRAMMING, ELECTRONIC TECHNICIANS, SERVOMECHANISMS, TELEMETRY, COLOUR TV, INSTRUMENTATION, AND PRINCIPLES OF AUTOMATION.

ALSO EXAMINATION COURSES FOR:

Inst. of Electronic and Radio Engineers
C. & G. Telecommunication Techns'. Cert.
C. & G. Supplementary Studies
R.T.E.B. Radio/TV Servicing Cert.
P.M.G. Certificates. Radio Amateurs' Exam.

LEARN AS YOU BUILD

Practical Radio Courses: Gain a sound knowledge of Radio as you build YOUR OWN 5-valve superhet Receiver and Transistor, Portable Signal Generator and High Quality Multitester. At the end of the course you have invaluable practical equipment and a fund of personal knowledge and skill. ICS Practical Radio Courses open a new world to the keen amateur.


THERE IS AN ICS COURSE FOR YOU

Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialised knowledge, ICS can help you with a course individually adapted to your requirements. There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

**FILL IN AND POST THIS COUPON
TODAY**

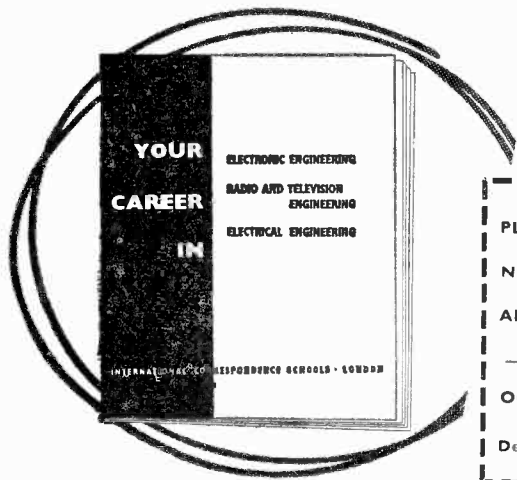You will receive the FREE ICS Prospectus listing the examinations and ICS technical courses in radio, television and electronics. PLUS details of over 150 specialised subjects.



PLEASE SEND FREE BOOK ON _____


NAME _____

ADDRESS _____

OCCUPATION _____ AGE _____

INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept. 170, INTERTEXT HOUSE, PARKGATE RD, London SW11
1.66

TEST METERS

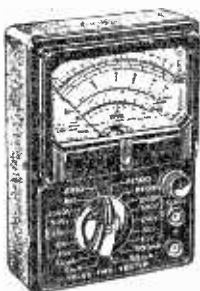

20,000 O.P.V. MODEL TP 58. Reads voltage up to 1,000 D.C. at 20,000 ohms per volt and A.C. at 10,000 O.P.V.; D.C. Current to 500mA; Resistance to 10 Megs.; Capacitance to 0.1µF; Decibels from -20 to +38. Size 3 1/2 in. x 5 1/2 in. x 1 1/2 in., £5.19.6.

2,000 O.P.V. MODEL TP 10. Reads A.C. and D.C. Volts up to 1,000 D.C. Current to 500mA; Resistance to 1 Meg.; Capacitance to 1µF; Decibels from -20 to +38; Output jack for Audio Measurements. Size 3 1/2 x 5 x 1 1/2 in. £3.19.6.

20,000 OHMS PER VOLT MODEL 500. Reads voltages up to 1,000 D.C. at 20,000 ohms per volt and A.C. at 15,000 O.P.V.; D.C. current to 12 amp. Resistance to 60 Megs.; Decibels from -20 to +56; incorporates internal buzzer for audible warning of direct shorts and blocking condenser for A.F. output measurements. Size 3 1/2 x 6 1/2 x 2 1/2 in., £8.19.6.

20,000 OHMS PER VOLT TESTMETER MODEL 700. Reads A.C. and D.C. voltages up to 5,000. Alternating and Direct Current up to 10 amps. Resistance up to 50 Megohms, Decibels from -10 to -42dB. Internal buzzer for audible warning of short circuits or continuity and fitted with automatic overload protection for movement. Meter size 4 1/2 in. x 3 1/2 in., overall dimension 7 1/2 in. x 5 1/2 in. x 3 1/2 in. Has rigid handle which can be swivelled for use as a tilt support. ONLY £17.10.0.

TRANSISTORISED TEST EQUIPMENT. Fully guaranteed, brand new. By NOMBREX: 160 Kc/A.—350 Mc/s. Signal Generator, £9.10.0. Resistance-Capacitance Bridge, £8.5.0. 1-15 volts D.C. Power Supply, £6.10.0. Audio Generator 10/100,000 c/s., £16.18.0. Inductance Bridge, £18.0.0.

VALVE VOLTMETER. D.C. Input Impedance 11 Megohms. 7 Voltage ranges, D.C. to 1,500 A.C. to 1,500 B.M.S., 4,200 Peak to Peak, Resistance 2 ohm to 1,000 Megohms. Centre zero setting for receiver alignment. Complete with A.C./D.C. probe and leads. Full illustrated details on request. ONLY £13.19.6 (Post 3/6).

FREQUENCY METERS TYPE LM. Frequency range 125-20,000 kc/s. in 2 bands. This is the United States Navy Model of the well-known BC221 Frequency Meter, but has many additional features which increase its usefulness. Voltage stabilisation circuits and Crystal control ensure extreme accuracy and in addition it is fitted with an Internal Modulation switch to allow use as a Signal Generator. Size only 8 1/2 in. x 8 in. x 8 1/2 in. ONLY £15.

VARIABLE VOLTAGE TRANSFORMERS. Fully shrouded. Input 250 v. A.C. 50/60 cycles. Output 0-250 v. 2.5 amps. type £5.17.6. 5 amps. type £9. 10 amps. type £16.10.0. 20 amps. type £32.10.0.

STANDARD TRANSFORMERS
Vacuum impregnated, interleaved E.S. screen. Universal mounting. Size 4 in. x 3 1/2 in. x 2 1/2 in. ALL BRAND NEW 18/6 each. Post 2/6.
Type 1. 250-0-250 v. 80 mA., 6.3 v. 3 a. tapped at 1 v. 4 a. 6.3 v. 1 a. tapped at 4 v. and 5v. 2 a.
Type 2. An above but 250-0-350 v. 80 mA.
Type 3. 30 v. 2 a. tapped at 12, 15, 20, and 24v. to give 3-4-5-6-8-9-10 v., etc.

HARRIS ELECTRONICS
(London) LTD.

138 GRAY'S INN ROAD
LONDON, W.C.1


Telephone: T E R m t n s 7037

Please include carriage cost on ALL items.

Trading hours 9 a.m.—6 p.m., Monday—Friday. Closed Saturday. We are 2 mins. from High Holborn (Chancery Lane Station) and 6 mins. by bus from King's Cross.

FAMOUS FOR THIRTY YEARS for
SHORT-WAVE EQUIPMENT of QUALITY

H.A.C. SHORT-WAVE KITS

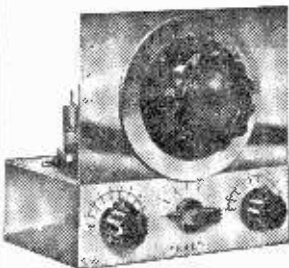

H.A.C. were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army Hams, etc.

IMPROVED 1966 RANGE

1-Valve model 'CX', complete kit, Price 34/6
Customers say: 'Definitely the best one-valve S.W. kit available at any price'. This kit contains all genuine Short-Wave components, a drilled chassis, accessories and full instructions. Ready to assemble and of course, as all our products, fully guaranteed. FULL RANGE of other kits still available including the famous model 'K', price 77/-.
Before ordering call and inspect a demonstration receiver or send for a descriptive catalogue and order form to—

"H.A.C." SHORT-WAVE PRODUCTS
(Dept. T.H.), 44 Old Bond St., London W.1

4-STATION INTERCOM



Solve your communication problems with this new 4-station Transistor Intercom system (1 Master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Operates on one 9v. battery. On/off switch. Volume control. Ideally suitable for Office, Factory Workshop, Warehouse, Hospital, Shop etc. to keep instant inter-departmental contacts. Complete with long connecting wires and other accessories. Nothing else to buy. P. & P. 5/-

INTERCOM/BABY ALARM



Usually £9.95—
Our Price ONLY

57/6

Modernize your Office, Shop, Warehouse, Workshop, Surgery, Nursery and Home with this latest two-way Transistor Intercom, consisting of two units, Master and Sub, in strong plastic cabinets with chromium stands. Elegantly designed to use as two-way instant communication system—call/talk/listen—between two persons anywhere indoors or outdoors. Operates on one 9v. battery. Complete with 60 ft. wire Battery 2/6. Ready to operate. P. & P. 2/6.


BATTERY ELIMINATOR & CHARGER, 27/6

Use your Transistor Radio or Intercom from domestic A.C. mains and charge dry battery PP3 9v. to boost battery's life many times. Unbeatable value. Save your pounds on batteries. P. & P. 1/6. Complete with Plug, Lead and Snap cord.

Full price refunded if not satisfied in seven days.
WEST LONDON DIRECT SUPPLIES (PW/11)
8 Obignell Place, West Ealing, London, W.18

PRICE SPECIAL RADIO CHASSIS OFFERS

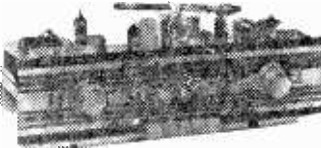HI-FI CONTINENTAL STEREPHONIC RADIOGRAM CHASSIS



Magnificent 'Continental' Stereophonic Radiogram Chassis with piano key switches, built-in ferrite rod aerial. Complete with two 10" elliptical loudspeakers, plus a mono/stereo 4-speed autochanger. Complete £29.19.6. Chassis only 19/6 gns. Special terms available of £4.10.0 deposit followed by 18 monthly payments of £1.13.0 (total H.P. of £34.4.0) + 15/- P. & P. Send £5.5.0 now.

IMPERIAL HI-FI STEREPHONIC RADIOGRAM CHASSIS



The Imperial stereophonic 4 waveband chassis has the most advanced specifications yet offered in this country. There is a built-in ferrite rod aerial, seven piano key buttons. Long-Medium-Short and VHF bands. Complete with two 10" loudspeakers plus a mono-stereo 4 speed automatic record changer. Complete 39/6 Gns. Chassis only 29/6 gns. Special terms available of £6.4.6 deposit followed by 24 monthly payments of £1.15.10 (total H.P. £44.4.6) + 17/6 P. & P. Send £7.2.0. now.

HI-FI EMPRESS RADIOGRAM CHASSIS



This fabulous 'Empress' Hi-Fi radiogram chassis is offered complete with 10" loudspeaker plus 4 speed autochanger. At only 23 gns. this is the bargain of the year. Chassis only 15/6 gns. Special terms available of £3.12.6 deposit followed by 18 monthly payments of £1.6.7 (total H.P. £27.11.0) + 15/- P. & P. Send £4.7.6. now.

All Lewis Radio equipment including valves are fully guaranteed for one year. Send your cheque or P.O. today while stocks last to Dept. P.125.

LEWIS radio

LEWIS RADIO, 100, CHASE SIDE, SOUTHGATE LONDON, N.14. Telephone: PAL 3733/9666

Holes marked "A" are $1\frac{1}{2}$ " dia
 Holes marked "B" are $1\frac{1}{8}$ " dia
 Holes marked "C" are $1\frac{1}{4}$ " dia
 Holes marked "D" are $\frac{5}{8}$ " dia
 Holes marked "E" are 4BA clearance
 Unmarked holes 6BA clearance
 Exact fixing positions for valveholders not shown, use component as template
 Shaded holes to be fitted with rubber grommets

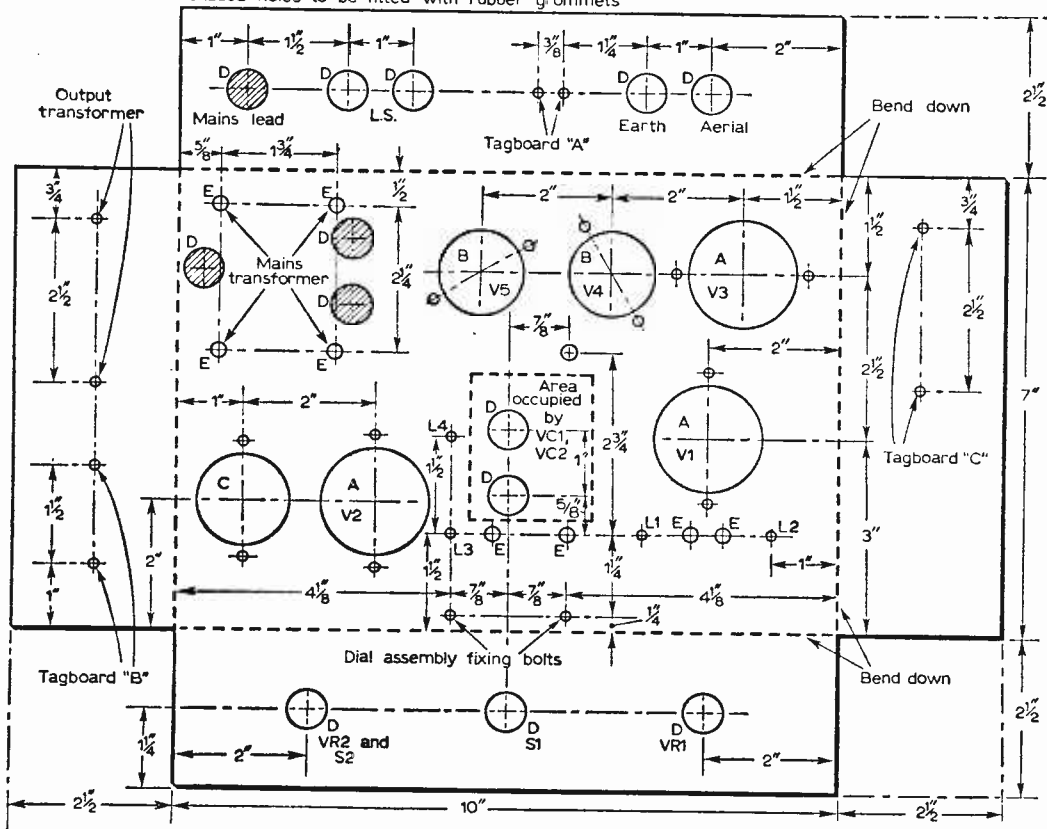


Fig. 3: Chassis drilling details.

utilise the two "D" holes to the right of this component. Now mount the electrolytic smoothing capacitor C13, using the clip specified in the components list, with its tags projecting through the hole "C". Before wiring is commenced check that all components are in their correct position and firmly bolted down.

Testing and Alignment

Before inserting valves and connecting to the mains supply the following check tests with an ohmmeter are highly desirable: First connect the meter across the receiver mains supply leads and check that when the on/off switch is turned to "on" the resistance of the primary winding of T2, some 20 to 50Ω, is indicated. Now connect the negative meter lead to chassis and the positive to pin 8 of V5, a momentary "kick" of the needle (indicating charging up the reservoir and smoothing capacitors), followed by a fall to almost open-circuit reading, should result. A reading of 50kΩ or less indicates an unwanted path between h.t.

positive and chassis and must be investigated before proceeding further.

Retaining the meter negative lead on the chassis, place the positive test prod on the cathode pins of V1 to V4 in turn and in each case a resistance indication corresponding to the value of the relative cathode resistor (see Fig. 1). Now remove the negative clip from the chassis, place the positive meter prod on the cathode (pin 8) of V5 and connect the meter negative in turn to the anode and screened grid pins of V4, the "anode" of V3 and V2 (comprising pins 2, 3 and 4 linked together in each case) and the anode pin of V1. In each instance continuity should be established and a resistance reading reflecting the value of the various dropping and decoupling resistors in circuit at the points tested.

If all the foregoing tests are carried out with satisfactory results the receiver can be connected to the mains with confidence. Remove test meter connections, ensure that on/off switch is in the "off" position. Insert all valves, connect loud

COMPONENTS LIST

Resistors:

R1	22k Ω	R8	47k Ω
R2	150 Ω	R9	1k Ω
R3	1k Ω	R10	470k Ω
R4	10k Ω	R11	220 Ω 1 watt carbon
R5	47k Ω	R12	1k Ω 1 watt carbon
R6	10k Ω	R13	1k Ω 5 watt w/w
R7	10k Ω		

All resistors $\frac{1}{2}$ W 10% except where otherwise stated.

Capacitors:

C1	0.1 μ F 350V paper
C2	0.1 μ F 350V paper
C3	0.1 μ F 350V paper
C4	0.5 μ F 350V paper
C5	1000pF mica
C6	200pF mica
C7	0.1 μ F 350V paper
C8	8 μ F 350V electrolytic
C9	25 μ F 25V electrolytic
C10	0.1 μ F 350V paper
C11	8 μ F 350V electrolytic
C12	0.05 μ F 350V paper
C13a/b	16 + 16 μ F 450V electrolytic
TC1	50pF trimmer
TC2	50pF trimmer

TC3	50pF trimmer
TC4	50pF trimmer
VC1	500pF J.B. 2 gang
VC2	

Potentiometers:

VR1	500k Ω carbon
VR2	25k Ω carbon with switch

Valves:

V1	EF50	V4	6V6
V2	EF50	V5	6X5
V3	EF50		

Miscellaneous:

L1	Wearite PA2
L2	Wearite PA1
L3	Wearite PHF2
L4	Wearite PHF1
T1	Mains Transformer "Douglas", 250-0-250V 80mA, 6.3V 3.5A, 6.3V 1A.
T2	Output transformer 5000 Ω :3 Ω Speaker 3 Ω 8-10in. dia. Chassis 10 x 7 x 2 $\frac{1}{2}$ in. J.B. "Full Vision" dial and drive assembly. SI 4 pole 2 way. 3 B9G valve holders. 2 IO. valve holders. Red "Pilot" indicator bulb holder. 6.3V 0.3A bulb.

speaker and aerial (also earth if used) to appropriate sockets. Insert mains plug and switch on. After a few seconds the heater glow in V5 and V4 will be visible, then advance the volume control to maximum, when a slight breathing sound should be audible from the loudspeaker. Gently touch a screwdriver blade on the centre tag of VR1 and a loud mains hum should emanate from the loudspeaker, indicating that the a.f. stages are functioning. Removing and replacing the aerial lead should produce a loud "click" from the speaker indicating that the r.f. section is also functioning. Rotating the tuning capacitor should locate the local BBC transmitter. Clockwise position of the wavechange switch gives medium wave band coverage, anticlockwise gives long wave band.

As soon as a signal of some sort is heard adjust the trimmers on the appropriate aerial and h.f. coils (long or medium wave band, according to setting of SW1). With SW1 definitely in the m.w. position endeavour to tune in a station at the low wavelength end of the dial such as the BBC Light Programme on 247m or Radio Luxembourg on 208m, then adjust the trimmers (on L2 and L4) for maximum volume consistent with reasonably accurate station indication by the dial pointer. Slight adjustment of the pointer itself is permissible to obtain exact indication of station tuned to. Now swing the tuning capacitor towards the high wavelength end of the dial and the local regional and Third programmes should be received at the correct point on the dial as the J.B. "Full Vision" is designed to match accurately to Wearite "P" type coils. Switch to long wave and, as the only station likely to be required will be the BBC Light


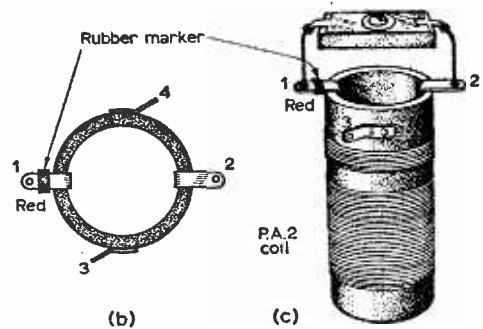


Fig. 4: PA2 coil connections


on 1,500m set the pointer to this mark and adjust the trimmers on L1 and L3 for best results.

The receiver should be found to have more than adequate volume, even when used with a short "picture rail" aerial, within 30-50 miles of BBC regional transmitters and a most pleasing standard of reproduction. Thanks to the employment of infinite impedance detection it will be particularly noticeable that transient sounds such as cymbals and other percussion instruments come through with especially realistic clarity, superior to all but the most expensive superhet or f.m. receivers. One final word: When inserting or removing EF50 valves a firm, straight pull (or push) is desirable. Any effort such as rocking from side to side to assist insertion or removal is liable to crack the glass seals around the valve base pins. ■

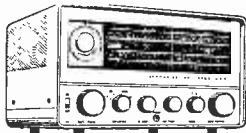


LAFAYETTE HA 63 COMMUNICATION RECEIVER

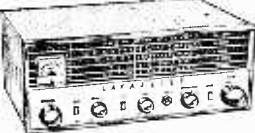7 valves + Rectifier. 4 Bands 550 Kc/s-31 Mc/s. 'S' Meter. BFO-ANL-Bandspread Tuning. 200/250v. A.C. Brand New. 24 Gns. carr. paid.



STAR SR 40 COMMUNICATION RECEIVER

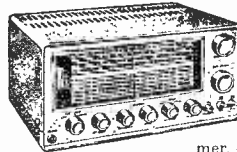4 Bands 550 Kc/s-30 Mc/s. 'S' Meter - BFO - ANL - Bandsread Tuning-Built in speaker. 200/250v. A.C. Brand New. 181 Gns. Carriage 10/-.




NEW MODEL LAFAYETTE HA-230 AMATEUR COMMUNICATIONS RECEIVER

Supersedes model HE-30. 8 valves + rectifier. Continuous coverage on 4 bands. 550 Kc/s-20 Mc/s. Incorporates 1 RF and 2 IF stages. Q Multiplier BFO. ANL. 'S' meter. electrical bandsread. Aerial trimmer, etc. Supplied brand new and guaranteed. 33 Gns. SAE for full details.

Also available in Semi-Kit form 25 Gns.


NEW MODEL LAFAYETTE HA-55 AIRCRAFT RECEIVER

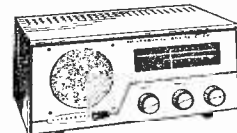108-136 Mc/s. High selectivity and sensitivity. Incorporates 2 RF stages including 6CW4 Nuvistor. 8 tubes for 11 tube performance. solid state power supply, adjustable squelch control, slide rule dial, built in 4in. speaker and front panel phone jack. 220/240v. A.C. Supplied brand new and guaranteed. 19 Gns. Carr. 10/-.



TE-22 SINE SQUARE WAVE AUDIO GENERATORS

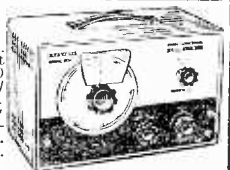Sine: 20 c.p.s. to 200 Kc/s on 4 bands. Square: 20 c.p.s. to 25 Kc/s. Output 5000 ohms. 200/240 v. A.C. Brand new Guaranteed. £15. Carr. 7/6.



LAFAYETTE NUVISTOR GRID DIP METER

Compact true one hand operation. Frequency range 1.7-180Mc/s. 230v. AC operation. Supplied complete with all coils and instructions. £12-10.0, carr. 5/-.

OS/8B/U OSCILLOSCOPES

High quality Portable American Oscilloscope. 3in. c.r.t. T1B 3c/s-50 Kc/s X Amp: 0-500 Kc/s Y Amp: 0-2 Mc/s. Power requirements 105-125v. A.C. Supplied in 'as new' condition. Fully tested. £25. Carr. 10/-. Suitable 230/115v. Transformer. 15/6.



CLEAR PLASTIC PANEL METERS

First grade quality. Moving Coil panel meters available ex-stock. S.A.E. for illustrated reater. Discounts for quantity. Available as follows. Type MR32P 121/32in. square fronts.



2mA	..	22/6	1V. DC.	..	22/6
5mA	..	22/6	10V. DC.	..	22/6
10mA	..	22/6	20V. DC.	..	22/6
20mA	..	22/6	50V. DC.	..	22/6
50mA	..	22/6	100V. DC.	..	22/6
100mA	..	22/6	150V. DC.	..	22/6
150mA	..	22/6	300V. DC.	..	22/6
200mA	..	22/6	500V. DC.	..	22/6
300mA	..	22/6	750V. DC.	..	22/6
500mA	..	22/6	15V. AC.	..	22/6
750mA	..	22/6	50V. AC.	..	22/6
1-0-1mA	..	22/6	15V. AC.	..	22/6
1A. DC.	..	22/6	300V. AC.	..	22/6
2A. DC.	..	22/6	500V. AC.	..	22/6
5A. DC.	..	22/6	'S' Meter 1mA	..	29/6

POST EXTRA. Larger sizes available—send for lists. ILLUMINATED 'P.S.' METER 3in. square front. Cal. in 5 units. SV. lamp. 29/6. P.P. 1/-. Ditto 2 1/2 in. square. 39/6. P.P. 1/-.

AVOMETER MODEL 7



First class condition, fully guaranteed. Complete with leather case and leads. 13 gns. P. & P. 5/-.

TRANSISTORISED TWO-WAY TELEPHONE INTERCOM

Operative over amazing long distances. Separate call and press to talk buttons. 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batts. & wall bracket. 7 gns pair. P. & P. 5/-.



TWO-WAY RADIOS

Superb quality. Complete with all accessories and fully g'd. 3 Transistor £7.19.6 pr. 4 Transistor 11 gns pr. 9 Transistor 19 gns pr. 10 Transistor 25 gns pr. Post extra. (S.A.E. for full details).




VOLTAGE STABILIZER TRANSFORMERS

Will stabilize your mains voltage. Ideal for TV receivers and industrial equipment. Input 80-120 v. and 100-240 v. Constant output 110 v. or 240 v. 250 watts Brand new guaranteed. £10.10.0 Carr. 7/6.




VARIABLE VOLTAGE TRANSFORMERS

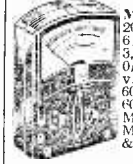
Brand New Guaranteed. Fully Shrouded. Input 230v. 50/60 c/s. Output 0-260 v. 1 Amp £4.10.0 2.5 Amp £5.17.6 5 Amp £8. 0.0 8 Amp £13.10.0 10 Amp £17.10.0 12 Amp £19.15.0 20 Amp £32.10.0 2.5 Amp Portable Metal Case with Meter. Fuses, etc. £9.17.6.



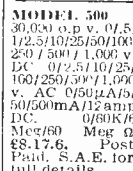MODEL TE-12 20,000 O.P.V. 0/06/6/30/120/600/1,200/3,000/6,000 v. D.C. 0/6/30/120/600/1,200 v. A.C. 0/60uA/6/60/600 mA. 0/6K/600K/6 Meg. 1/60 Meg. 0. P.F. -2 MFD. £5.19.6. P. & P. 2/6.



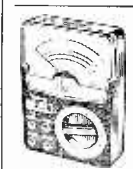MODEL 500 30,000 o.p.v. 0/5/1/2.5/10/25/50/100/250/500/1,000 v. DC 0/2.5/10/25/100/250/500/1,000 v. AC 0/50uA/5/50/500mA/12amp DC. 0/60K/6 Meg/60 Meg/6 Post Paid. S.A.E. for full details.



TE-51 NEW 20,000 OHM VOLT METER 0/6/60/120/1,200 V. A.C. 0/330/60/300/600/3,000 v. DC. 0/60uA/12/200 mA DC. 0/60K/6 Meg. Ohm & pack. 2/6.

OPEN 9 a.m. to 6 p.m. EVERY DAY MONDAY-SATURDAY Trade Supplied.

ERSKINE TYPE 13 DOUBLE BEAM OSCILLOSCOPES



Timebase 2 c/s-750 kc/s. Separate Y1 and Y2 amplifiers. Up to 5.5 Mc/s. calib at 100 kc/s. and 1 Mc/s. 110/230 v. A.C. Guaranteed perfect. £27.10.0. Carr. 20/-.

MINE DETECTOR No. 4A

Will detect all types of metals. Fully portable. Complete with instructions, 3/6 each. Carr. 10/-. Battery 8/6 extra.

MAGNAVOX 363 TAPE DECKS

New 3 speed tape deck, super-sized coil Colloar studio deck. 2 track. £10.10.0. 4 track £13.10.0. Carr. Paid

SILICON RECTIFIERS

200 P.I.V.	..	300mA	2/6
1,000 P.I.V.	..	650mA	7/6
800 P.I.V.	..	500mA	5/6
400 P.I.V.	..	3 amp	7/6
100 P.I.V.	..	500mA	3/6
150 P.I.V.	..	165mA	1/-
70 P.I.V.	..	1 amp	3/6
95 P.I.V.	..	3 amp	5/6

AMERICAN TAPE

First grade quality American tapes. Brand new and guaranteed. Discounts for quantities.

3in. 2525T. T.P. mylar	4/-
5in. 600ft. std. plastic	10/-
5in. 900ft. L.P. acetate	8/6
5in. 1200ft. D.P. mylar	10/-
5in. 1800ft. L.P. acetate	15/-
5in. 1200ft. L.P. mylar	12/6
5in. 1800ft. D.P. mylar	22/6
5in. 2400ft. T.P. mylar	45/-
7in. 1200ft. std. mylar	12/6
7in. 1800ft. L.P. acetate	15/-
7in. 1800ft. L.P. mylar	20/-
7in. 2400ft. D.P. mylar	25/-
7in. 3600ft. T.P. mylar	58/6

Postage 2/- Over £3 post paid.



THE WORD **MAXI-Q** IS THE REGISTERED
REGD. TRADE MARK

OF DENCO (CLACTON) LIMITED
IT IS ALSO A GUARANTEE OF
WORKMANSHIP AND
TECHNICAL PERFORMANCE

OUR RANGE OF PRO-
DUCTS IS SO GREAT THAT
WE NOW HAVE TO
REQUEST THE AMOUNT
OF 2s. 0d. FOR OUR GENER-
AL CATALOGUE AND TO
SAVE YOU POSTAL ORDER
POUNDRAGE CHARGE WE
REQUEST SEND 2s. 0d. IN
STAMPS.

IN RESPONSE TO CONTINUOUS DEMAND WE HAVE COMMENCED PRODUCTION of self Contained Multiplex Decoder Unit, aligned ready for immediate use, that will convert your two receivers—tuner and two amplifiers—tuner and stereo amplifier or stereo receiver without Multiplex provision to a complete B.B.C. Stereo Broadcast Reception Unit. Price £8.0.0 post paid. Technical Publication MD.1. 4s. 0d. post paid.

IFT.11/465 kc/s centre tapped transformer for use in crystal filter circuits. 1-7/8" x 13/16" square. 10s. 6d. plus 8d. post.

IFT.18/465 kc/s and 1.6 Mc/s Double Tuned transistor IF transformer, 1 1/2" x 1/2" square. 10s. 6d. plus 8d. post.

General Catalogue 2s. 0d. post paid. S.A.E. all enquiries please.

DENCO (CLACTON) LTD.

(Dept. P.W.)

357/9 OLD ROAD, CLACTON-ON-SEA, ESSEX

USEFUL GIFTS *for the RADIO AMATEUR* and *SHORT WAVE LISTENER...*

RSGB PUBLICATIONS

Radio Data Reference Book	12/6 (by post 14/-)
Technical Topics for the Radio Amateur	10/- (by post 10/8)
Amateur Radio Circuits Book	7/6 (by post 8/6)
Amateur Radio Call Book (1966 Edition)	6/- (by post 6/6)
Radio Amateurs' Examination Manual...	5/- (by post 5/9)
A Guide to Amateur Radio	5/- (by post 5/7)
Service Valve Equivalents	3/- (by post 3/6)
S.S.B. Equipment... ..	3/- (post free)
Communications Receivers	3/- (post free)
Log Book (RSGB)	6/6 (by post 7/-)

ARRL PUBLICATIONS

Antenna Book (10th Edition)	17/- (by post 18/6)
A Course in Radio Fundamentals	9/6 (by post 10/-)
Hints and Kinks, Volume 6	9/6 (by post 10/-)
Mobile Manual for Radio Amateurs	22/6 (by post 23/6)
Radio Amateur's Handbook	40/- (by post 42/6)
Single Sideband for the Amateur	22/- (by post 23/6)
Understanding Amateur Radio... ..	17/- (by post 18/6)

Write for information about membership of the Radio Society of Great Britain, including a free copy of the monthly RSGB BULLETIN.

CQ PUBLICATIONS

Antenna Roundup	22/- (by post 23/6)
CQ Mobile Handbook	21/6 (by post 23/-)
CQ New Sideband Handbook	22/- (by post 24/-)
Shop and Shacks Shortcuts	28/- (by post 29/6)

73 MAGAZINE PUBLICATIONS

Simplified Maths for the Hamshack	4/- (by post 4/6)
V.H.F. Antenna Handbook	14/6 (by post 15/-)

EDITORS' & ENGINEERS' PUBLICATIONS

Radio Handbook (16th Edition)	75/- (by post 78/-)
Transistor Radio Handbook	40/- (by post 42/-)

AMERICAN MAGAZINE SUBSCRIPTIONS

CQ (Cowan) Monthly—(per ann.)	44/-
QST (ARRL) Monthly—(per ann.)	43/6
73 Magazine Monthly—(per ann.)	30/-

● The above publications are obtainable from leading booksellers or direct from—

RADIO SOCIETY of GREAT BRITAIN

Dept. PW, 28 Little Russell Street, London, W.C.1.

HOLborn 7373, 2444



No. 3 **BASILDON & DISTRICT AMATEUR RADIO SOCIETY**

THE Basildon and District Amateur Radio Society was formed in 1962 by a number of licensed amateurs and short wave listeners living in the new town of Basildon and the surrounding country area. The Club now has over fifty members of whom twenty are licensed with a number of them SWL's studying for the Radio Amateurs' Examination or for the Post Office Morse tests. Club members cover a wide range of ages and professions, teenagers still at school and members in their sixties; firemen and chartered accountants.

Most of the licensed amateurs operate on the frequencies 160, 80 and 40 metres, but there is strong interest in 70 and 144Mc/s and 70 centimetres. G3EDM and G3ORT are keen mobile operators. G3PZZ and G3OIT are active on the DX bands. G3PGN and G3OQT can often be heard at weekends operating on 70Mc/s, while G3ASH and G3IJB are active on 144Mc/s.

The Club is affiliated to the Radio Society of Great Britain and each year enters for National Field Day. In 1963 and 1964 the Club won the Bristol Trophy, awarded for the highest score achieved by a single station entry.

The Club holds meetings twice a month; the first at the Bullseye Hotel, Town Centre, Basildon,

when wives and girl friends are cordially welcomed, and the second meeting, usually held in the third week of the month, is devoted to talks, junksales, lectures and film shows. This latter meeting is held in the Mayflower Restaurant, adjacent to the Van Gogh, Paycocke Road, Basildon. Members are advised of forthcoming activities in a monthly newsletter.

Last year the Club visited the G.P.O. receiving station at Brentwood and later the transmitting station at Ongar, where great interest was shown in the equipment used by the Post Office. Envious eyes were cast on the masts supporting the transmitting and receiving aerials, but all cars were searched before leaving these stations by the chairman, Geoff Mills (G3EDM)!

In recent months visits have been arranged to the Marine Control Centre of Lathol Ltd., which controls the movement of all oil tankers entering or leaving the Thames; to the G.P.O. Telephone Exchange at Grays/Thurrock, and to the Communications Division of the Municipal Airport of Southend-on-Sea. For the winter months the Committee has planned a demonstration of portable and mobile equipment, a lecture on aerials, a film show, junk sales as well as an illustrated lecture on lasers.

The Society endeavours to look after the interests of those concerned with amateur radio, whether members or not, and is at present co-operating with the Company concerned regarding possible interference, from or to, the wired television system being installed in Basildon New Town.

The Club aims to bring the activities of the amateur world to the attention of residents in the district through the local press as well as the National magazines. It welcomes new members, whether licensed or not, and a letter to the Secretaries, B.D.A.R.S., Milestone Cottage, London Road, Wickford, Essex (Telephone: Wickford 2462) will bring full details of membership. The subscription for those over 18 years of age is only 12s. 6d. per year—so come and join a really go-ahead Club. ■



With acknowledgements to the *Southend Standard*


Members of the Club taking part in the R.S.G.B. N.F.D. this year.

26 1/2"gn TAPE RECORDER for ONLY £19.10.

carr 12/6

Bargain of the Year Offer - cancelled Export Contract

Famous manufacturers brand new unused and factory tested 2 speed 31 and 7 1/2 i.p.a. twin track tape recorder 3 Watt output. Tape position Rev-counter. Fast forward and rewind. take 7" reels on 3" and gram input. Straight through amplifier facilities. Output sockets to ext. speaker, monitor or external amplifier. Super-imposed switching magic eye recording level and mains neon indicator. Volume and tone controls 7" x 4" speaker. Attractively styled cabinet with detachable lid mike and reel storage facilities. A.C. 200/250 volts operation. Complete with crystal mike, tape spare reel and screen lead etc.

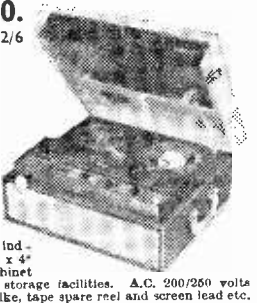

MULLARD "3-3" & "5-10" HI-FI AMPLIFIERS

3 ohm & 15 ohm output



"3-3" Amp. 3 valve, 3 watt hi-fidelity at reasonable cost. Bass Boost and treble control. Quality scotchpan output transformer, 40 ohm-25 kc/s - 1 dB, 100mV for 3W, less than 1% distortion. Iron-on escutcheon panel. Complete Kit only £8.10.0. Carr. 5/- Wired and tested £8.10.0.

MULLARD "5-10" AMPLIFIER. 5 valves 10W 3 and 15 ohm output. Mullard's famous circuit with heavy duty ultra-linear quality output transformer. Basic amplifier kit price **£9.19.6** Carr. and Ins. 7/6.

CONTROL PANEL KIT. Bass, Treble and Volume controls with 4-position selector switch for radio tape and 11in. x 4in. escutcheon panel. **AMPLIFIER KIT AND CONTROL PANEL KIT, £11.19.6.** Ditto, ready wired. £14.19.6.

2-VALUE PRE-AMP UNIT. Based on Mullard's famous 2-valve (2x6F6) circuit with full equalisation. With volume, bass, treble and 5-position selector switch. Size 9 1/2 x 2 1/2in. Ready built £7.19.6. Carriage 3/6.

L.P. RECORDING TAPE BARGAIN

By leading British manufacturers—

PROFESSIONAL GRADE DOUBLE-SIDED OFFER!

(each side coated) 5 1/2" reels only

Special price offer 1,450 feet (2 reels) 20/- post free

Ideal for the experimenter who wishes to record both sides, and a good L.P. Tape for the enthusiast who wishes to record single side only.

Alumin. Chassis. 15g. Plain Undrilled. 4 holes, 2 deep, 8" x 4", 4/8; 8" x 6", 6/8; 10" x 6", 9/8; 12" x 6", 7/8; 12" x 8", 8/-, etc.
Alumin. Sheet. 15g. 6" x 6", 1/-; 6" x 8", 1/6; 6" x 12", 2/-; 12" x 12", 4/8, etc.

Jack Plugs. Standard 2 1/2" Igranite Type, 2/6. Screened Ditto, 3/3. Miniature scr. 1 1/2", 3/3. Sub-mm. 1/3. Soldering Irons. Mains 200/220V or 230/250V. Solenoid 25W Inst., 24/6. Spare Elements, 6/6. Bits, 1/3. 65W, 29/6, etc.

SPECIAL OFFER 3" Message Tape. 150', 3/9; 3" L.P. 225', 4/9; 3" D.P. 300', 6/6. P. & P. per reel 6d.

TAPE REELS. Mintra. surplus 7", 2/3; 5 1/2", 2/-; 5", 3/-; 1 1/8"; spool containers, 3", 1/8; 5", 1/8; 5 1/2", 2/-; 7", 2/3.

DE-LUXE RECORD PLAYER KIT



Incorporating 4 Sp. Garrard Auto-Slim unit and Mullard latest 3 watt printed circuit amplifier (EC8 and EZ 80), vol., bass and treble controls, with 8" x 5" 10,000 Hz speaker. Contemporary styled 2-tone cabinet, charcoal-grey and off-white with matching blue-relief. Size 17 1/2" x 16" x 8". A stylish unit capable of quality reproduction. Circuit and const. details 2/6 (free with kit). **£13.19.6**

COMPLETE KIT Carr. and Ins. 12/6 Ready-wired 30/- extra Illuminated perspex control panel; escutcheon, 7/6 extra. For contemporary mounting legs 6in. 10/6; 9in. 11/6; 12in. 12/6 extra

TRANSISTOR COMPONENTS

Midget I.P.s: 405 Kc/s 9/16in. 1st, 2nd, 3rd, 4th, 5/6 Osc. Coil M. & L.W. 9/16 in. dia. 6/- Midget Driver Trans. 9.1 1/2 6/- Midget Output Trans. Push-Pull—3 ohms 6/- Elect. Condensers—Midget type 1mFd.-50mFd. ea. 1/8, 100 mFd. 2/-, 13V. W.K.G. Condensers 150 v. working: .01 mFd., .02 mFd., .03 mFd., .04mFd. 9d.; .05 mFd., 1mFd., 1/-; .25 mFd., 1/3. 5 mFd., 1/6, etc. Midget Tuning Condensers, J.B. "Dito" 205 pF and 176 pF, 8/6. Dito with trimmers, 9/6. J.B. 220 pF and 105 pF conc. slow motion 10/6. 865pF single 7/6. Sub. min. 1in. Dileman 100 pF, 300pF, 500pF, 7/- each. **FERRITE AERIALS, M. & L.W.** "aerial coil" 9/3.

Midget Vol. Control with edge control knob, 5 K/ohms with switch 4/6; Ditto less switch 3/6. **Speakers:** P.M.: 2in. Plessey 75 ohms 15/6. 2 1/2in. Continental 8 ohms, 13/6. 7 x 4in. Plessey 35 ohms, 23/6. **Ear Plug Phones—Min.** Continental type 3in. lead, jack plug and socket. High imp., 8/-. Low imp., 7/6.

Phono Plugs, 9d. Phono Socket (open) 8d. Ditto (closed), 1/-. Twin Phono Socket (open), 1/3.

6 VALVE AM-FM TUNER UNIT



Med. and VHF 190m-550m. 46 Mc/s-103 Mc/s. 6 valves and metal rectifier. Self-contained power unit. A.C. 200/250V operation. Magic-eye indicator, 3 push-button controls, on/off Med. VHF. Diodes and high output Sockets with gain control. Illuminated 2-colour perspex dial 11 1/2" x 4", chassis size 11 1/2" x 4 1/2".

A recommended Fidelity Unit for use with Mullard "3-3" or "5-10" Amplifiers. Now available as complete kit as illustrated, inc. power unit. Ditto, but less power unit, £9.19.6, carriage 7/6. Circuit and construction details, 4/6, free with kit.

£10.19.6 Carriage 7/6.

Condensers—Silver Mica. All values 2pF to 1,000pF, 6d. each. Ditto Ceramics 9d. Tub. 450V T.C.C. etc. 6,001 mFd to 0.01 and 0.1/350V. 9d. 0.02-0.1/600V. 1/-, 0.25 Hertz 1/8. 0.8 T.C.C. 1/9, etc. etc. Close Tol. S/Micas—10% 5pF-500 pF 8d. 600-5,000pF, 1/-, 1% 2pF-100pF, 9d. 100pF-500pF, 11d. 575pF, 5,000pF, 1/6. Resistors—Full Range 10 ohms-10 meg. ohms 20% 1 and 1/4 W. 3d. 1W 5d. (Midget type modern rating) 1W, 6d., 2W, 9d. Hi-Stab. 5% 1W, 1W, 6d. (100 ohms-1 meg). Other values 9d. 1% 1W, 1/6 etc., etc.

JASON FM TUNER UNITS. Designer-approved kit of parts. P.M.T. 5 mcs. 4 valves, 20/- P.M.T. £7.10.0 5 valves 35/- JTV MERCURY 10 gna. 3 valves, 22/6. JTV £13.19.6 4 valves, 28/6. **NEW JASON FM HANDBOOK, 2/6.** As by Alignment Service, 7/6. P. & P. 2/6.

TRIMMERS. Ceramic (Compression Type)—50pF, 50pF, 70pF 9d.; 100pF/150pF, 1/3; 250pF, 1/6; 400pF, 1/8. **PHILLIPS.** Bee Hive Type (conc. air-spaced)—3-30pF, 1/-; 3-30pF 1/-. **KNOBs—Modern Continental types.** Brown or Ivory with Gold Centre; 1" dia., 9d. each; 1 1/2" each; Conc. knobs Ivory with Gold Centre 1 1/2" dia. 2/6 per pair. Matching ditto 2/6 ea.

LARGE SELECTION AVAILABLE. METAL RECTIFIERS, 5TC Types—RM1, 4/8; RM2, 5/8; RM3, 7/8; RM4, 1/8; RM5, 2/1-; RM11, 17/8; RM16-ELECTROLYTICS—CAN 25/25, 50/12V, 1/8; 3-8/450V, 4/6; 50/50V, 100/125V, 2/-; 32+32/275V, 4/6; 8/450V, 4/850V, 2/3; 50/50/350V, 4/8; 18-18/450V, 5/8; 60/250/275V, 12/8; 32-82/450V, 6/6; 100+200/275V, 12/8

Volume Controls—5K-2 Meg. ohms. 3in. Spindles, Morganite Midget Type 1 1/2in. diam. (near 1 year. 12-way or L.V. ratios less Sw. 3/- DP. Sw. 4/6, Twin Steer less Sw 7/6 100k to 2M ohms with DP Sw. 9/6. **WAVELENGTH SWITCHES.** 1 p. 12-way 2p. 2-way 2 p. 8-way 3 p. 4-way, 4 p. 2-way, 4 p. 3-way, long spindle, 3/6 ea.


EXPANDED ANODISED METAL. Attractive gilt finish 1in. x 1in. diamond mesh 4/6 sq. ft. Multiples of 6in. cut. Max. size 4ft. x 2ft., 47/6, plus cart. Do. finer pattern mesh 6d. sq. ft., multiples of 12in., max. size 3 ft. x 2 ft., 2/76 sheet.

ENAMELLED COPPER WIRE— 1in. reels 14g-20g, 3/-; 22g-26g, 3/6; 28g-30g, 4/8; 32g-40g, 6/-, etc.

7 VALVE AM/FM RADIOGRAM CHASSIS

Valve one-up ECC85, ECH81, EF89. New 1965 Model now available. EAB8C0, EL54, EM81, EZ85.

Three Waveband and Switched Gram. positions. Med. 200-550 na Long. 1,000-2,000 m. VHF/PM 88-95 Mc/s. Philips Continental Tuning Insert with permeability tuning on FM and combined AM/FM IF transformers. 400 Kc/s. and 10.7 Mc/s. Dust core tuning all coils. Latest circuit including AVC and Neg. Feedback. Three watt output. Sensitivity and reproduction of a very high standard. Chassis size 13 1/2 x 6 1/2in. Height 7 1/2in. Edge illuminated glass dial 11 x 3 1/2in. Vertical pointer. Horizontal station names. Gold on brown background. A.C. 200/250V. operation. Magic-eye tuning. Circuit diagram now available. Aligned and tested ready for use £13.19.6. Carr. & Ins. 7/6. Conn. with tape, O/P socket, ext. ap'kr and P/U sockets and indoor FM aerial and 4 knobs—walnut or ivory to choice. 3d P.M. Speaker only required. Recommended Quality Speakers 10" R.A. 27/6, 13 1/2" x 8" E.M.I. Fidelity 37/6, 12" R.A. with conc. Tweeter, 42/6. Carr. 2/6.

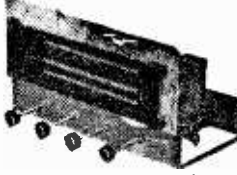

BONDACOUT Speaker Cabinet Acoustic Wadding (1 in. thick approx.) 16-22g. any length cut, 2/3 per ft., 6/- per yard. **TINNED COPPER WIRE,** 18-22g. 4 1/2 lb. **ERIN MULTICORE SOLDER,** 60/40 4d. per yard. **Cartons 6d., 1/-, 2/6 etc.** **TYGAN FRET** or Vynair, 12 x 12in. 2/5; 12 x 18in. 3/4; 12 x 24in. 4/-, etc.

We manufacture all types Radio Mains Transf., Chokes, Quality O/P Trans., etc. Enquiries invited for Specials. Prototypes for small production runs. Quotations by return. Send for detailed bargain list 3d. stamp.

RADIO COMPONENT SPECIALISTS

70 Brigstock Rd., Thornton Heath, Surrey. Hours: 9 a.m.-6 p.m., 1 p.m., Wed. THO 158. Terms C.W.O. or C.O.D. Post and Packing up to 1 lb. 1/-; 1 lb. 1/8; 2 lb. 3/-; 5 lb. 3/8; 8 lb. 4/6.



Est. 1949


YOU ARE ALWAYS AHEAD WITH A SINCLAIR DESIGN

The world's smallest radio

No transistor set has ever yet compared in its class with the Micro-6 for size, power, performance and design. Everything except the lightweight ear piece is contained within the smart minute white, gold and black case which weighs under one ounce complete. Quality of reproduction is so outstandingly good that you will derive enormous pleasure from this fantastic set. Order your Micro-6 now. See why it cannot be too highly recommended to build and to use. You can easily have it working in an evening!



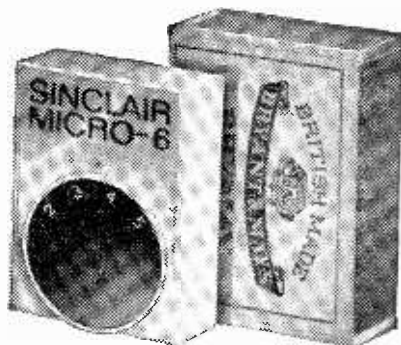- 1 4/5" x 1 3/10" x 1/2"
- PLAYS ANYWHERE
- COMPLETELY SELF-CONTAINED
- EASY TO BUILD




AMAZING CIRCUITRY

The six-stage circuit uses three special transistors to provide two stages of R.F. amplification with double diode detector and high gain 3-stage A.F. amplifier. A.G.C. counteracts fading from distant stations; bandspread brings in Luxembourg like a local station. Plugging in earpiece switches set ON. Tunes over medium waveband by vernier-type dial. Two self-contained batteries give about 70 hours working life.

Complete kit of parts inc. special earpiece and instructions **59/6**

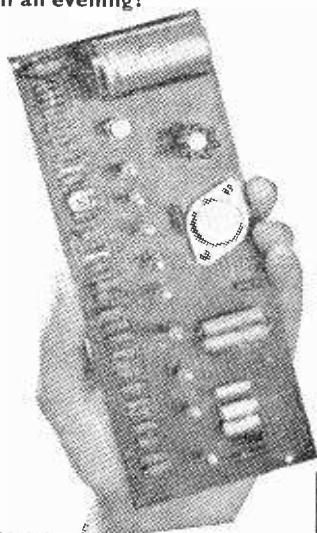MALLORY MERCURY CELL TYPE ZM.312 (2 required) each 1/11d.
Pack of six 10/6d.



The world's most advanced audio amplifier

Size 8 1/4" x 3 1/4" x 1" Output 20 watts

The only audio amplifier in the world to use Pulse Width Modulation which, with circuitry developed specially by Sinclair gives power and quality years ahead of anything in its class. You can feed any signal source into the X-20—modern high quality pick-up, radio tuner, electric guitar, car radio, microphone, tape, etc. The X-20 manual shows a number of circuits by which inputs can be matched to the integrated pre-amplifier of the X-20 both in mono and stereo. When you have built this 12-transistor amplifier you use it in the same way as any other top quality hi-fi unit except that it is smaller, costs less and behaves perfectly.



- 20 WATTS R.M.S. OUTPUT INTO 7.5 ohms
- 20-20,000 o/s ± 1dB
- Constant square wave amplitude
- 95% conversion efficiency at output
- Input sensitivity—1mV into 6K ohms
- Power requirements—36Vd.c. at 700mA

COMPLETE KIT OF PARTS COSTS **£7.19.6**
Built and tested **£9.19.6**
Mains power Unit **£4.19.6**

Weights 4 1/2 oz.

MICRO FM and Z.12
See pages following

● FULL SERVICE FACILITIES AVAILABLE TO ALL SINCLAIR CUSTOMERS



SINCLAIR RADIONICS LTD., COMBERTON, CAMBRIDGE Telephone: COMBERTON 682

A BRILLIANT NEW TUNER

The world's first pocket-size FM Tuner/Receiver



The SINCLAIR MICRO FM is a high quality FM tuner designed for use with hi-fi amplifier or tape recorder and independently as a self-contained pocket FM receiver for personal listening. Barely half the size of a packet of 20 cigarettes, the Micro FM is a fully-fledged 7 transistor-2 diode superhet circuit with unique and original design features to ensure fantastically good standards of performance. Pulse counting detection ensures better linearity than conventional detection methods, and therefore better audio quality. Powerful A.F.C. which locks on to the station tuned in, together with unusually good sensitivity make tuning easy and the set's own telescopic aerial suffices almost everywhere. In styling, this is the most elegant, most professional looking design in miniaturised equipment ever made available to constructors, and is one you will be very proud to possess. **YET WITH ALL THESE WONDERFUL FEATURES, THE SINCLAIR MICRO FM COSTS POUNDS LESS AND MEANS THAT ANYONE CAN AFFORD AND ENJOY THE ADVANTAGES OF FM RADIO NOW.**

SINCLAIR MICRO FM

7 TRANSISTOR SUPERHET FM TUNER/RECEIVER

- ★ SIZE 2½" x 1½" x 2"
- ★ TUNES FROM 88-108 Mc/s.
- ★ A.F.C. FOR EASY TUNING
- ★ NO ALIGNMENT NEEDED
- ★ PULSE COUNTING DETECTION
- ★ EXCEPTIONALLY ELEGANT APPEARANCE

BRIEF TECHNICAL DESCRIPTION



THE SINCLAIR MICRO FM is a seven transistor, two diode FM superhet. The low I.F. dispenses with the need for alignment. A three stage I.F. amplifier limits the signal to produce a square wave of constant voltage which is fed into the pulse counting discriminator. This converts the square wave formation into uniform pulses, the average output from which is directly proportional to the signal frequency, so that the original modulation is reproduced exactly. After equalisation, the signal is fed to the audio output amplifier stage for use as a tuner and also to the receiver's own audio amplifier. A.F.C. locks on each station automatically. THE SINCLAIR MICRO FM is completely self-contained within a neat black plastic case faced by an elegantly designed front panel of brushed and polished aluminium with spur aluminium tuning dial to match. The tuning scale is marked in Mc/s. When built, the Micro FM performs as well as any other good tuner.

THE COMPLETE KIT OF PARTS for building the SINCLAIR MICRO FM including extending aerial, 7 transistors, case, tuning dial, aluminium front panel, lightweight earpiece, plugs and sockets and instructions costs only

- ★ Operates from 9v self-contained standard battery
- ★ Consumption 5mA
- ★ Audio response—10-20,000 dB | 1 dB
- ★ A GUARANTEED SINCLAIR DESIGN

Use it as—

AN F.M. TUNER FOR YOUR TAPE RECORDER.

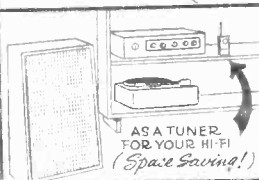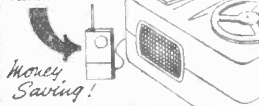

AS A SELF-CONTAINED POCKET FM RECEIVER.

(The only one in the World!)



£5.19.6

Full service facilities available to all Sinclair customers

SINCLAIR RADIONICS LTD.
COMBERTON, CAMBRIDGE


Telephone: COMBERTON 682

sinclair

A BRILLIANT NEW AMPLIFIER



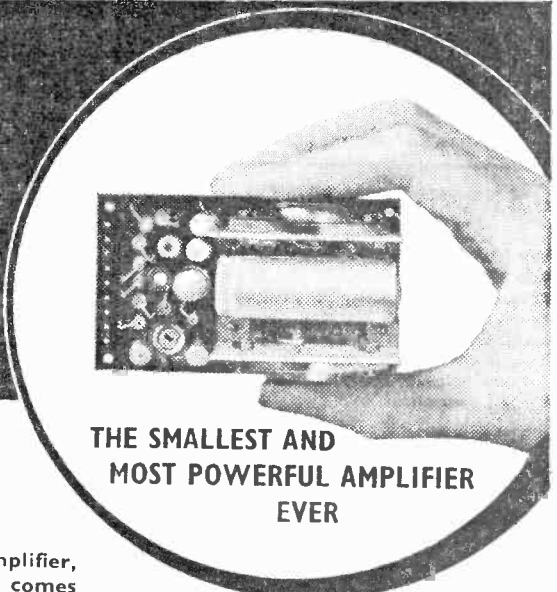**SINCLAIR
Z.12** COMBINED
AMPLIFIER
AND
PRE-AMP



THE SMALLEST AND
MOST POWERFUL AMPLIFIER
EVER

Fantastic power and quality

The Sinclair Z.12 is a universally flexible amplifier, exceptionally powerful, fantastically small. It comes to you ready built, and is very easy to instal and use. The Z.12 can be incorporated into any high quality hi-fi system. Its small size and high efficiency make it equally useful for a guitar, for car radio, P.A. system or any other application where high quality is the first requirement. The Z.12 incorporates its own pre-amplifier to which you add the tone and volume control system of your choice as shown in the Z.12 manual supplied with the amplifier. The size, the performance, and the price of the Sinclair Z.12 all favour the constructor who wants the best in modern transistor equipment; in fact, the Z.12 is unbeatable in every way and is today's finest buy in top grade high fidelity.

USE IT FOR
Hi-fi
Radio
Car Radio
Guitar, etc.

TECHNICAL DETAILS

High fidelity amplifier with pre-amp and ultra-linear class B output. Eight special R.F. transistors are used in original circuitry to achieve laboratory standards of performance. Generous negative feedback ensures extra good quality.

- **FREQUENCY RESPONSE**—15 to 50,000 cps ±1dB
- **OUTPUT**—12 watts RMS continuous sine wave (24 watts peak) 15 watts RMS music power (30 watts) peak
- **OUTPUT IMPEDANCE**—suitable for 3, 7.5 and 15 ohm speakers. Two 3 ohm speakers may be used in parallel if required
- **INPUT**—2mV into 2K ohms
- **SIGNAL to NOISE RATIO**—better than 60dB
- **QUIESCENT CURRENT CONSUMPTION**—15mA
- **POWER SUPPLY**—6 to 20V d.c. from power unit available or batteries

GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, your money will be refunded in full and at once without question. Please quote PW-169 should you prefer to write your order instead of cutting out this coupon.

- 3" × 1 3/4" × 3/4"
- Weighs 3 ozs.
- 12 watts R.M.S.

Supplied ready built, tested and guaranteed, complete with Z.12 Manual **89/6**

SINCLAIR DX-10 Power Supply Unit £2.14.0

GUARANTEE ORDER FORM

To: SINCLAIR RADIONICS LTD.,
COMBERTON, CAMBRIDGE

Please send me

.....
.....
.....
for which I enclose Cash/Cheque/Money Order
value £.....s.....d

NAME

ADDRESS

PW166

SEND COUPON WITHOUT DELAY

SERVICE SHEETS

SERVICE SHEETS for all makes of Radio and TV, 1925-1956. Prices from 1/- with free fault-finding guide. S.A.E. inquiries. Catalogue of 6,000 models 1/6. Valves, modern and obsolete. Radio/TV Books. S.A.E. lists. HAMILTON RADIO, Western Road, St. Leonards, Sussex.

SERVICE SHEETS, Radio and Television. 4/-, post paid. VEST and EMERY, 17 Hallgarth St., Durham.

SERVICE SHEETS, Radio, TV, 5,000 models. List 1/-. S.A.E. inquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS (75,000) 4/- each. Callers welcome. Always open. 5 South Street, Oakenshaw, Bradford.

SERVICE SHEETS

4/- ea., plus postage

We have the largest display of Service Sheets for all makes and type of Radios, Televisions, Tape Recorders, etc., in the country. Speedy service.

To obtain the Service Sheet you require please complete the attached coupon.

From:

Name:

Address:

To: **S.P. DISTRIBUTORS**
44 Old Bond St., London, W.1
Please supply Service Sheets for the following:

Make:

Model No..... Radio/TV

Make:

Model No..... Radio/TV

Make:

Model No..... Radio/TV

I also require list of Service Sheets at 1/6.

(please delete items not applicable)

I enclose remittance of.....

MAIL ORDERS ONLY Jan. PW

RECEIVERS & COMPONENTS

NOISE LIMITERS, new miniature solid-state, for valve and transistor circuits, 21/- each, postage 1/- Most effective limiter known. Send stamp for leaflet. G. ELLIOTT, 3 Sandgate Ave., Tilburst, Reading, Berks.

TREASURE HUNT! Help me to find Certain Types of Relays and Contacts to earn spare cash. Send S.A.E. for details. 112 Groby Rd, Glenfield, Leicester.

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. DIRECT TV REPLACEMENTS LTD, Dept. PW7/9, 295 Hamilton Road, West Norwood, S.W.13. Order 2/6.

RATES: 7/3 per line or part thereof average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager "Practical Wireless," Tower House, Southampton St., London W.C.2.

RECEIVERS & COMPONENTS
(continued)

TRANSISTORS, UNMARKED, UNTESTED, 40 for 10/-, p. and p. 17, 4 packets post free. Relays, thousands of types, special catalogue free. General catalogue of Mechanical and Electrical Gear, Tools, etc., 5,000 items free. K. R. WHISTON (Dept. PRW), New Mills, Stockport.


TRANSMITTER RECEIVER

13 valves, 2 wavebands 2-8 Mc/s. (150-37 metres) R.T. and C.W. operation. Complete with low-drain 12V. D.C. power unit, headset, microphone. Fully tested.

£9.10.0
Carr. 30/-



MARCONI CANADIAN RECEIVER No. 52

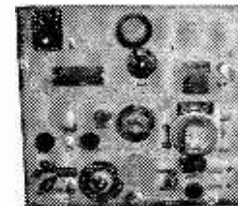

Shipping Amateur, & Broadcast. Magnificent 10-valve receiver in three switched wavebands covering 1.75-16 Mc/s (19 - 170 metres), plus 3 valve crystal call.

brator employing dual crystal to provide marker check at 10-1000-1000 kc/s. One RF and two IF stages. Other refinements: valve, HT, and signal check meter. Internal 3in. speaker and two H/Phone outputs with switched control. RF-AM Gain, Noise Limiter, Filter, BFO, Heterodyne pitch control. Wide and Narrow Bandwidth, Man or AVC on CW & RT. Fast and Slow tuning with lock. Additional OSC Tuning (plus & minus). Power requirements HT 180v, 60mA; LT 12v 1 1/2 amps size 10 x 14 x 1 1/2in. Fully tested and working ONLY £9.19.6. Carr. 15/6 or complete with Power supply unit suitable for 115/230v, AC mains £12.19.6. Carr. 20/-.

No. 58 GROUND-STATION comprising Receiver, Transmitter and 12v. D.C. Power Unit. £27.10.0. Carr. £2.10.0. (Mainland only).

TELESCOPI AERIAL MASTS. Tubular steel copersided, spray finish, ring cam locking on each section provides for full or any height required. Suitable all fixings and base locations. Bottom section 1 1/2in. diameter, 20ft. (4 section) Closed 6ft. 9in. Weight 16lb. 55/-, Carr. 5/-, 34ft. (6 section) Closed 6ft. 6in. Weight 20lb. 75/-, Carr. 5/-. Further height by adding 3-4ft. Whip sections 18/6. Carr. 4/-. Special prices for quantities.

ROTARY TRANSFORMER, 12v. D.C. input, 250 v. D.C. output at 125 mA. Size 3 1/4" x 6 1/2". Brand new 17/6. P. & P. 5/-.

R.F. ANTENNA TUNER (A.T.U.) Calibrated scale, ideal 150/30/40 metres. Limited number only. Brand new with instructions. 17/6. P. & P. 7/6. Complete list of other bargains 1/- S.A.E. all enquiries

A. J. THOMPSON (Dept P.W.)
"ELLING LODGE"
CODICOTE, HITCHIN, HERTS.
Phone: CODICOTE 248

RECEIVERS & COMPONENTS
(continued)

SPEAKER REPAIRS, cones fitted. Satisfaction guaranteed L. S. REPAIRS, Pluckley, Ashford, Kent.

R & R RADIO & T V SERVICE

Dept. P.W.
MARKET STREET, BACUP, LANCS.
Telephone 465

SALVAGE VALVES Tested before despatch
6P13 4/6 U29 5/- PL36 6/- 20P4 6/6
6L18 4/6 10P14 5/- PL82 3/8 30P16 5/-
EF80 1/8 20P5 6/8 U501 7/8 PC984 4/-
ECU82 3/- 30F 7/- 10F1 1/8 PYS1 8/6
ECL80 3/8 6F15 5/- 20F2 5/3 U301 6/-
30F5 5/- EB91 1/- 30FL1 5/- 10P13 5/6
PL38 6/- EF85 5/- PY32 8/- 20D1 2/-
PCF80 4/- 630L2 4/- 6U4GT 8/- 30P12 5/-
PL81 6/- 20P1 6/- 6F1 2/6 FY83 5/-
PZ30 5/- 30P11 4/- EY86 4/-

Speakers. Ex-TV. 5in. round 6 x 4in. 3/8; 8in. round, 6/-; post 2/-.

Line Output Transformers available. State set model No.

Turret Tuners. 8/-, post 2/-.
Scan Coils, etc. Quote set model No. with all enquiries and S.A.E. for prompt reply. All goods subject to satisfaction or money refunded.

V.H.F. RECEIVER. PYE P.T.C. 114

65-100 Mc/s 12 Volt D.C. Supply
This is an 11 valve double superhet receiver, operating on one fixed frequency between 65-100 Mc/s., crystal controlled, speaker output using midget valves throughout. Supplied in first class condition with tuning data, circuit diagram and complete crystal formula. Ideal for the four-metre band (70.2 Mc/s.) offered at only 70/-, post 5/-.

AERIAL MATCHING TUNING UNITS

These well-made tuning units, made for the American I9 Tx-Rx, are housed in a metal case, colour green or brown using a large precision calibrated scale, are an essential piece of equipment for the serious Tx or Rx operator. This unit will match an untuned wire or Whip Aerial to almost any Short Wave Receiver or Transmitter, exceptionally good for Mobile Top Band use. This American version being well noted as far superior to any other. GUARANTEED BRAND NEW, only 20/-, post 7/6. Instructions supplied.

18 Mk. III RECEIVER

This is a 4 valve superhet covering 6-9 Mc/s. Phone or C.W. Set is very compact, size only 9 1/2 x 6 x 5in. Supplied in fair condition with circuit. ONLY 30/-, post 5/-. Sender chassis with 500 microamp meter same size only 20/-, post 5/-.

JOHN'S RADIO
OLD CO-OP, WHITEHALL ROAD
DRIGHLINGTON, BRADFORD



CANADIAN MARCONI 32 RECEIVERS as per previous adverts. £10.10.0. Carriage Paid. Handbooks 5/-. Leaflet S.A.E.
LOUDSPEAKERS 10in. 3 ohm in wood case. Cases soiled, 600 ohm Line Transformer, 25/-, carriage paid. 16 or 22 Set Head and Mike Sets. 10/- Post Paid.
CERAMIC insulated 3 gang variables, 56 x 56 x 35 pf. 3/6, Post 1/6.
V.H.F. FIELD STRENGTH METERS, 100-150 mc/s. Telescopic Aerial, 2" Round, 1 mA Meter, 35/- Post Paid.
PILOT BULBS 6.5v. .06 amp. 5/-, dox. Post Paid. Meters 100 mA 24" Round, 10/- Post Paid. (Carriage charges apply to England and Wales only)

Telephone: Worthing 9097
40/42 PORTLAND ROAD. WORTHING

RECEIVERS & COMPONENTS
(continued)

DIRECT TV REPLACEMENTS LTD., largest stockists of TV Components in the U.K. Line Output Transformers, Frame Output Transformers, Deflector Coils for most makes. Official sole suppliers for many set makers. Same Day Dispatch Service. Terms C.O.D. or C.W.O. Send S.A.E. for quotes. Day and Night Telephone Gipsy Hill 67-66, 126 Hamilton Road, West Norwood, S.E.27.

A.I. POST FREE BARGAINS

Stock clearance of reclaimed values

B36	3/- PCL82	4/- UF42	1/9 10G1	7/-
EB11	1/9 PCL83	3/8 UCH42	5/- 10C2	3/9
JR91	9d. PEN46	1/8 UL46	5/6 10P13	3/9
EBF80	3/6 PL33	2/6 Z63	3/- 10P14	3/9
ECN2	2/6 PL82	3/- Z56	3/6 20D1	1/9
EF89	4/- PL83	2/- OF1	1/- 20P2	4/3
ECL50	1/8 PY31	1/3 6F13	2/9 20L1	3/9
EF42	2/9 PY32	2/6 6F14	2/9 20L1	3/9
EF80	9d. PY80	1/6 6F15	3/- 20P1	2/6
LF95	4/3 PY81	1/9 6K23	3/6 20P3	3/-
EL42	4/3 PY82	1/6 6L14	3/6 30P5	3/8
KT33C	2/8 PY230	1/6 6L18	3/- 30P11	3/9
KT36	3/3 T41	4/6 6L19	12/6 30P11	3/9
L63	1/6 UC1	2/3 6L120	4/3 30P12	3/9
N37	3/- UC24	3/6 6P25	2/9 18B7	7/8
N39	1/- UC29	3/6 6P28	4/6 KTW63	2/8
PCF80	2/- UC34	3/6 6R3L2	2/9 KTZ63	3/6
PF80	5/- doz.	ECL80 12/- doz.	PCF80 18/- doz.	
EB91	5/- doz.	PY82 12/- doz.	PL83 18/- doz.	

A.I. RADIO COMPONENTS

14 The Borough, Canterbury, Kent

FOR SALE

HAMMERITE

HAMMER PATTERN BRUSH PAINT FOR PANELS AND BOXES

★ THE PATTERN IS IN THE TIN ★
ALL YOU DO IS BRUSH IT ON!

24 oz. tins 3/6 1/2 gallon 35/-
1/2 pint 7/6 1 gallon 55/-
1 pint 15/- (*seat by road)

Carriage: Orders up to 5/- 9d.; up to 10/- 1/9; over 10/- 2/9.

Colours: Blue, Silver or Metallic Black. Return of post service. Mon. to Fri. From your component shop or direct from the manufacturer:

FINNISH SPECIALITY PAINTS (PW)
Mickleby Square, Stockfield, Northumberland.
Phone: Stockfield 2250

ARMATURE REWINDS. Hoover Armature Exchange Service. Models 375/119; 224 32/6 inc. post. Fields 15/- Send for lists. JERVIS & TONGE LTD., Ringwood Road, Brimington, Chesterfield, Derbys. Tel: Chest 75267.

ELECTRIC SOLDERING-IRON



FANTASTIC BARGAIN OFFER

Light-weight Pistol Grip handle 40 watt, 240/250v. A.C. Solid copper bit. Detachable handle forms cover for iron when not in use. With 4ft. Safety 3-core flex. Indispensable for every home handyman. A boon to model makers and a necessity for every wireless enthusiast. Offered to you at this new amazing price.

9/6

G. H. SERVICE, (Dept. P.W.)
Lusted Hall Lane, Tatsfield, Kent.

FOR SALE
(continued)

MORSE MADE EASY !

The famous RHYTHM RECORDED COURSE cuts the practice time down to an absolute minimum.

One student, aged 20, took only 13 DAYS, and another, aged 71, took only 6 WEEKS to obtain a G.P.O. pass certificate if you wish to read Morse easily and naturally please enclose 8d. in stamps or two international reply coupons for full explanatory booklet.

To G3CHS.

45 GREEN LANE, PURLEY, SURREY.

240^{WATT} ELECTRIC POWER ANYWHERE

ANYTIME! from 12^{WATT} CAR BATTERY

THE AMERICAN DYNAMOTOR UNIT
Input 12v. output 200/250w. at 150 to 220 volts
Perfect for TELEVISION, POWER TOOLS and all general purpose ELECTRICAL EQUIPMENT (generators) under 1/2 horse power ONLY 58/- per cartridge
Send stamp or cheque for full illustrated details
W. SCIENTIFIC PRODUCTS, CLEVELYD, LANC.

SPECIAL OFFER

GEVAERT TAPE. New, Boxed, 57, 100ft. with Stop and Leader Tapes, 9/- or 8 for 50/-.

GRUNDIG MAL 2 Transistor Pre-amplifier for Tape Monitoring or Microphone Boosters, 57/6.

LIST PRICE 4 GNS.

LEE ELECTRONICS

400 Edgware Road, Paddington 5521

Send for Free Lists details of above

TRANSISTORS

1/- each. Red or White Spots.

2/- each. XA101, XA102, XB103, OA90, XA111, XA112, OC430, V10/15.

3/- each. OC44, OC45, OC70, OC71, OC81, OC81D, XA151, XB104, XC101, XC101A, OC169, OC200.

4/- each. AF114, AF115, AF116, AF117, OC170, OC171, XA103, XA116, XB102, XB105, XC121, XU611.

5/- each. OC139, OC140, OC204, ORP60, XA701, XA703, GET7, GET8, GET9, XC141, BY100, OA211.

10/- each. OC19, OC22, OC25, OC26, OC28, OC35, 25013.

ZENNER DIODES

4.7v. to 30v., 1/4w. 3/6, 1.5w. 5/-, 7w. 6/- each.

Plus many more. Send 6d. in stamps for full list and eq. chart

B. W. CURSONS

78 BROAD STREET
CANTERBURY, KENT

TAPE RECORDERS, TAPES ETC.

TAPE TO DISC - New High-level Cutters, 45 r.p.m., 21/- S.A.E. leaflet. DEROY, 52 Hest Bank Lane, Lancaster.

WANTED

WE BUY New Valves, Second-hand Cameras, Binoculars, Projectors, Amplifiers, Records, Car & Transistor Radios, Components, etc. Send s.a.e. to **EDDY'S (Nottm.) Ltd.**, 116 Alfreton Road, Nottingham.

WE BUY New Valves for cash, large or small quantities, old types or the latest. Send details. Quotations by return. **WALTONS WIRELESS STORES**, 15 Church Street, Wolverhampton.

WANTED VALVES ONLY

Must be new and boxed
Payment by return

WILLIAM CARVIS LTD.

103 North Street, Leeds 7

URGENTLY WANTED: New modern Valves, Transistors, Radios, Cameras, Tape Recorders and Tapes, Watches, Tools, any quantity. **S. N. WILLETTS**, 16 New Street, West Bromwich, Staffs. Tel. 2392.

DAMAGED AVO METERS wanted. Models 7 and 8 Any condition. Any quantity. **HUGGETTS LTD.**, 2-4 Pawns Road, West Croydon.

MISCELLANEOUS

CONVERT ANY TV SET into an Oscilloscope. Diagrams and Instructions, 12/6. **REDMOND**, 42 Dean Close, Portslade, Sussex.

ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write NOW for free leaflet and further details to **C. & S., 20 Maude Street, Darlington, Durham.** Send 3d. stamp.

BUILD YOURSELF A LOW PRICE, HIGH QUALITY RECORD PLAYER AND SAVE 22/- Refined circuit, yet simple to build. **BACKED BY A SERVICE SCHEME**, so even the complete beginner can tackle this job with confidence. Instructions and diagrams 5s. 6d. **HARRIS**, 16 Melrose Avenue, Portslade, Sussex.

TV NOT WORKING 30/-

SETS CALLERS ONLY EACH

OR 20 FOR £20

20 PALMERSTONE ROAD
EARLEY, READING, BERKS.

METAL WORK

METAL WORK. All types cabinets, chassis racks etc., to your specifications, PHILPOTTS METAL WORKS LTD., Chapman St., Loughborough.

SITUATIONS VACANT

TV AND RADIO—A.M.I.E.R.E., City and Guilds, R.T.E.B. Cert., etc., on "Satisfaction or refund of fee" terms. Thousands of passes. For details of Exams, and Home-training Courses (including practical apparatus) in all branches of Radio, TV and Electronics write for 156-page handbook—FREE, B.I.E.T., (Dept. 242G), 29 Wright's Lane, London, W.8.

INSTRUMENT MAKER required in Dept. of Telecommunications and Electronics, Norwood Technical College, Knight's Hill, London, S.E.27. Duties include repair of standard electronic and electrical test equipment, fabrication of chassis for instructional use and building of such other electrical equipment. 40-hour week. £15 ss., rising to £17 ss. Superannuable post. Forms, returnable within 14 days, from Secretary.

A.M.I.Mech.E., A.M.I.E.R.E., City and Guilds, G.C.E., etc. Become a Technician or Technologist for high pay and security. Thousands of passes. For details of Exams, and Courses in all branches of Engineering, Building, Electronics, etc., write for 156-page handbook—FREE, B.I.E.T. (Dept. 242B), London, W.8.

ELECTRONIC ENGINEERS required for maintenance and fault finding on photo-typesetting equipment. Instruction courses can be arranged for suitable applicants. H.M. Forces would qualify for further training. Excellent pay and conditions of employment plus expanding opportunities in progressive printing group. Please write to Works Engineer, SOUTHEARW OFFSET LIMITED, 25 Lavington Street, London, S.E.1.

RADIO AND TV Exam. and Courses by Britain's finest Home-study School. Coaching for Brit.I.R.E., City and Guilds Amateur's Licence, R.T.E.B., P.M.G. Cert., etc. FREE brochure from BRITISH NATIONAL RADIO SCHOOL, Russell Street, Reading.

SMITH'S RADIOMOBILE

Britain's Car Radio Specialists

RADIO SERVICE ENGINEERS

These appointments are progressive and there are prospects of advancement for men with the right experience and ability.

Please apply to:

The Personnel Manager

**S. SMITH & SONS
(RADIOMOBILE) LTD.**

Goodwood Works
North Circular Road
London, N.W.2.
GLAdstone 0171

SITUATIONS VACANT

(continued)

A FULL-TIME TECHNICAL EXPERIENCED SALESMAN required for Retail Sales. Write, giving full details of age, previous experience and salary required, to the Manager, HENRY'S RADIO LTD., 38 Edgware Road, London, W.2.

TWO LABORATORY TECHNICIANS required as soon as possible in Dept. of Telecommunications and Electronics, Norwood Technical College, Knight's Hill, London, S.E.27. Duties include minor maintenance of test equipment and accessories, preparation of students' experiments and upkeep of laboratories and 39-hour week. £220 at 21, rising to £275 at 29. Holders of certain recognised qualifications £260 at 21, rising to £915 at 29. Forms, returnable within 14 days, from Secretary.

BOOKS & PUBLICATIONS

AUDIO, America's foremost journal. Year's subscription 43/-, specimen copy 4/-. All American radio journals supplied — list free, WILLEN (Dept. 40), 61a Broadway, London, E.15.

SURPLUS HANDBOOKS

19 set Instruction Handbook, 3/6, p/p 6d.
1155 Instruction Handbook, 3/6, p/p 6d.
H.R.O. Instruction Handbook, 3/6, p/p 6d.
58 set Instruction Handbook, 3/6, p/p 6d.
48 set walkie talkie Circuit & Notes 3/6, p/p 6d.
88 set walkie talkie Instruction Handbook, 4/6, p/p 6d.
Frequency Meter BC221 Instruction Handbook 3/6 p/p 6d. Wavemeter Class D Handbook Mk. I, II and III, 3/6, p/p 6d. 18 set Circuit Details & Notes, 3/6, p/p 6d. A.R. 85D Instruction Handbook, 15/-, p/p 1/8. R.107 Instruction Handbook, 4/6, p/p 6d. R1116/A Circuit Diagram & Details, 1/9, p/p 6d. R1224/A Circuit Diagram & Details, 1/6, p/p 6d. R1355 Circuit Diagram & Details, 1/6, p/p 6d. RF Unit 24 Circuit Diagram & Details, 1/6, p/p 6d. RF Unit 25 Circuit Diagram & Details, 1/6, p/p 6d. RF Unit 26 Circuit Diagram & Details, 1/6, p/p 6d. Amplifier A1134 Circuit Diagram & Details, 1/9, p/p 6d. Resistor Colour Code indicators. Indicates the value of a resistor at a glance. Price 1/8, p/p 6d. All mail orders to:

Instructional Handbook Supplies (PW)
Talbot House, 28 Talbot Gardens
Roundhay, Leeds, 8

EDUCATIONAL**EDUCATIONAL**

(continued)

CITY AND GUILDS (Electrical, etc.) on "Satisfaction or refund of fee" terms. Thousands of passes. For details of modern courses in all branches of Electrical Engineering, Electronics, Radio, TV, Automation, etc., send for 156-page handbook—FREE, B.I.E.T. (Dept. 242A), 29 Wright's Lane, London, W.8.

RADIO OFFICERS' training courses. Write Principal, Newport and Monmouthshire College of Technology.

**TRAIN FOR SUCCESS
WITH ICS**

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for I.E.R.E., City & Guilds (Telecoms and Radio Amateurs') R.T.E.B., etc. Many unique diploma courses inc. Colour TV, Electronics, Telemetry & Computers. Also self-build kit courses—valve and transistor. Write for FREE prospectus and find out how ICS can help you in your career.

ICS DEPT. 541 PARKGATE ROAD,
LONDON, S.W. 11.

RADIO OFFICERS see the world. Seagoing and shore appointments. Our many recent successes provide additional trainee vacancies during 1966. Grants available. Day and boarding students. Stamp for prospectus. WIRELESS COLLEGE, Colwyn Bay.

THE INCORPORATED PRACTITIONERS IN RADIO AND ELECTRONICS (I.P.R.E.) LTD. Membership conditions booklet 1/-. Sample copy of I.P.R.E. Official Journal 2/- post free. Secretary, Dept. B, 32 Kidmore Road, Caversham, Reading, Berks.

City and County of Bristol Education Committee

**BRISTOL TECHNICAL COLLEGE
CAREERS IN RADIO AND RADAR**

Marine Radio Officers

Licensed Aircraft Radio Engineers

2-year, full-time course for young men aged 16 upwards; leading to 1st and 2nd Class P.M.G. Certificates and B.O.T. Radar Maintenance Certificate.

Conversion Course (2nd Class to 1st Class).
R.T. Courses (for Full or Restricted Licence).

2-year, full-time course for A.R.M.E. Licences, categories A & B, and 6 months' courses for Radar Rating in association with above.

Training given on the latest types of Marine and Aircraft Equipment in the newly equipped Laboratories at


THE SCHOOL OF MARINE RADIO AND RADAR

For details write to:

THE REGISTRAR
BRISTOL TECHNICAL COLLEGE
ASHLEY DOWN, BRISTOL 7

SOUND RECORDINGS

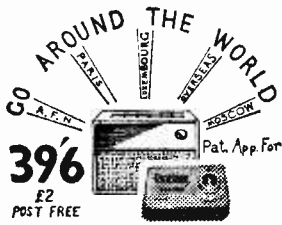A UNIQUE TAPE. Buy top brand 7in. 2.40ft. 25/-, 3 1/2in 15/-. P. and P. 1 at 2/-. 2 at 2/9. 3-6 at 3/6. Bargains in all sizes S.A.E. for list. E. C. KINGSLEY & CO. LTD. 93 Tottenham Court Road, London, W.1. EUSton 8500.



On your OWN TRANSISTOR PORTABLE.

- ★ No Plugs—No Connections! Just place Dewtron Wave Trap near radio! Boosts 'Pirate' and distant stations, reduces 'tadnls'.
- ★ Extends Battery Life!
- ★ Use in car or caravan. Without Aerial!

British-made. Supplied with PP3 batt. (life several months) and instructions. Money refund guarantee.

D.E.W. LTD., Dept. P.W., Ringwood Road, FERNDOWN, Dorset

PADGETTS RADIO STORE
OLD TOWN HALL
LIVERSEDGE, YORKS.

Telephone: Cleckheaton 2866

Special Offer. Brand New Boxed TV Tubes. MW43/69, 65/-, MW36/24, 37/6. 90 Degree Tubes with slight glass fault 37/- each. Carriage on any tube in G.B. 10/- Fully Guaranteed for 12 months.

Reclaimed Tubes, Six months guarantee. AW43/90, 30/-, MW43/90, 30/-, MW43/89, 30/-, CRM172, 30/-, CRM142, 17/-, 12 inch tubes, 10/-, 17 inch tubes perfect but without guarantee, 17/- each. Carriage on any tube in G.B. 10/-.

Scope Tube removed from units, DG7-S, 2.5in., perfect condition, 30/-, Post 4/6.

New JAP earpieces complete with lead and plug, 3 or 5mm., 1/11 post paid or 20/- per dozen.

13 Amp Double Switch Sockets. Brown surface type, 3/-, Post 1/6. 6 for 18/- post paid.

New Diodes, top grade, no duds, 3/- doz., post paid.

New 12in. Speakers with built-in tweeter' 3 or 15 chms, 28/6. Post paid.

Perfect Speakers, ex. equipment, 8in. round, 6/-, Post 3/-, 7 X 4in., 5/-, Post 2/-, 6 X 4in., 3/-, Post 2/-, Six for 20/-, post paid. 6in. round, 3/-, Post 2/-, 20/-, Philips 5in. round, 5/-, Post 2/-.

Motors Single Phase 240v. quarter H.P., 28/-, 1400 Revs. Fully guaranteed, ex. washing machines, carriage 8/6.

Small Switch Motor 24v. will run from 12 or 6v. a.c., 10/-, post paid.

Bush 12in. TV 24 c 13 channel TV. Complete and tested with good tube, only wants cleaning, 75/-, carriage 10/-, G.B.

VALVE LIST

Ex equipment, 3 months' guarantee

EL91	1/6	20P1	4/-	PCC84	4/-
EL90	2/-	20P4	8/6	PCL82	5/-
EL84	5/-	U801	8/6	PCL85	5/-
ECC81	3/-	U281	8/-	PL36	3/-
ECC82	3/-	U282	5/-	12AT7	3/-
EY51	2/6	U329	5/-	6CH6	1/6
EY98	5/-	K730	5/-	R18	3/6
EBP30	4/6	6V8GT	7/-	ARP12	1/6
EB91	9d.	6B3	1/6	50 for £1	5/-
ECC83	4/-	6K25	5/-	807	5/-
EL38	5/-	6P25	3/6	EF50	6/-
EF91	9d.	6U4	5/-	Doz. 6/1	1/6
6F14	5/-	6Y33	6/-	EF90	Doz. 10/-
6F15	5/-	PY80	3/-	6K7	Doz. 10/-
1902	5/-	PY81	3/-	6V6	Doz. 10/-
10F11	1/-	PL81	4/-	6K3	Doz. 18/-
10F13	5/-	PL82	3/-	6K8	Doz. 18/-
12P14	5/-	PL83	3/-	U25	5/-
20D1	2/-	PY82	3/-		
20L1	5/-	PCF90	4/-		
20P3	4/-	PZ30	5/-		

All valves post paid

ANYONE CAN AFFORD THESE NEW JOB TRAINING COURSES

NEW. No. 500 RADIO AND TELEVISION COURSE 75/-

Here at last is your opportunity to own a most complete course at a very modest cost! This expanded course which now includes television as well as radio repair training could get you started on a whole new career!

The Radio Section of the course was ORIGINALLY DEVELOPED BY THE RADIO TECHNICAL INSTITUTE, while the Television Servicing Course has formed the basis of instruction provided by one of the world's largest television and electronics firms!

Compare lesson by lesson with some courses costing ten times as much! You save because you receive all the lessons at one time and are not required to purchase equipment you may not need.

The lessons are crystal clear, practical, easy to master and use. Early lessons make fundamentals clear even to the beginner, while other lessons will give you the practical know-how of an expert!

The new 500 Radio & Television Course consists of 352 large quarto size pages of instruction, hundreds of illustrations. We positively guarantee that you will be delighted or your money refunded!

NEW. No. 600 RADIO-TELEVISION ELECTRONICS COURSE 85/-

This is really big value in home training. Similar in details to the above course excepting that you get an extra 56 pages of instruction making a total of 408 quarto size pages. Hundreds of illustrations. Includes all the usual subjects plus Radio Transmitter Circuits, Electronic Test Equipment, Thyatron Tubes, Inter-Communicators, Sound Level Meters, Servicing Printed Circuits and many more similar items. This course could be your first step into the fascinating world of electronics!

No. 400. ELECTRONICS COURSE 45/-

A complete home-study course of 35 lessons. Consists of 216 large quarto size pages of instruction. Comes complete with instructor's notes and test questions. This is a modern course that teaches without resorting to comic strip methods. Thousands of readers of this magazine have taken this course and enjoyed every minute of it. Why not you? Clip this coupon for your free trial offer now!

No. 19. REFRIGERATION SERVICE MANUAL 27/6

Learn refrigeration! This manual is packed solid with information to enable you to start in refrigeration right away! Used by many leading firms as a standard reference. Features 364 pages, 157 illustrations, bound in cloth. An excellent book now offered for the first time!

UNCONDITIONALLY GUARANTEED TO GIVE COMPLETE SATISFACTION

Any course not satisfactory may be returned within 10 days post-paid for full refund or credit of the purchase price.

IF YOU SEND CASH WITH ORDER WE WILL INCLUDE A FREE BOOK worth 4/6 to 5/- if bought separately. By sending cash you reduce book-keeping and other costs which we pass back to you. But you must include cash at the time of order to get this special offer!

***** FREE TRIAL OFFER *****

PAY ONLY 5/- per week if you wish.

To: SIM-TECH TECHNICAL BOOKS DEPT. G.2. Gate's Mill, West End, Southampton, Hants.

Please send the courses I have circled.

No. 500 No. 600 No. 400 No. 19

If not delighted I may return any book post-paid without further obligation on my part. Otherwise I will pay cash price or 6/- weekly (10/- fortnightly) commencing not later than 10 days after delivery. I am over 21 years of age. (If under 21 parents should place order).

I enclose cash to the sum of £ £ £
I understand you will refund this money if I am not 100% satisfied and I return the book within 10 days.

Please send me the free book(s) I have ticked.

Oscilloscope Book Electronic Gadgets Book
Transistor Book Radio Instrument Book

Name

Address

2 METRES 4

The thrills of VHF Amateur Radio! Complete kit, 70-150 Mc/s, costs only 42/6 (by post, UK, 3/3 extra) also now available. Short-wave kit model TR2 10-180 metres, ideal for beginners to Ham radio via simplified "Easy-Build" step-by-step instruction. From 79/6. Write today enclosing a stamped addressed envelope for literature and full details. Overseas enthusiasts note we despatch to all parts of the world—local stamp OK for literature. "GLOBE-KING" (Heard.) precision standard products tried and trusted by Amateurs everywhere.

JOHNSONS (Radio)
St. Martins Gate, Worcester

EXPRESS ELECTRONICS


32 SOUTH END, CROYDON, SURREY Tel: Croydon 9186
FOR THE FOLLOWING BRAND NEW UNITS

AMPLIFIERS AND TUNERS		
TRIPLETONE HI-FI MAJOR	12 watt	£15.18.6
TRIPLETONE CONVERTIBLE	12 watt	£8.19.8
TRIPLETONE GEMINI STEREO	5 watt	£15.15.0
TRIPLETONE FM TUNER		£15.14.6
LINEAR		£6.6.0
LINEAR DIATONIC	3 watt	£12.12.0
LINEAR CONCHORD	30 watt	£15.18.0
LEAK TL12	14 watt	£18.18.0
LEAK VARISLOPE PRE-AMP		£15.15.0
LEAK TL50	60 watt	£35.12.0
LEAK THROUGH LINE 3 FM TUNER		£31.14.6
QUAD	15 watt	£22.1.0
QUAD STEREO/MONO PRE-AMP		£25.0.0
LOUDSPEAKERS		
GOODMANS AXIETTE 8in.	6 watt	£5.5.0
GOODMANS AXIOM 10in.	25 watt	£8.6.0
GOODMANS AXIOM 20in.	15 watt	£10.15.0
BAKERS 'SELHURST' 3 or 15 ohm		
STALWART 12in.	15 watt	£5.5.0
BASS GUITAR 12in. 'Group 25'	25 watt	£8.5.0
BASS GUITAR 'Group 35'	25 watt	£8.18.0
BASS GUITAR 'Group 50'	50 watt	£8.18.0
STANDARD Heavy Duty 12in.	20 watt	£7.7.0
BASS Heavy Duty 12in.	25 watt	£12.12.0
AUDITORIUM 15.	35 watt	£18.18.0
RECORD PLAYERS		
GARRARD MODEL 1000 4-speed MONO		£6.19.6
GARRARD MODEL 2000 MONO		£7.15.0
GARRARD MODEL 3000 STEREO		£10.10.0
GARRARD MODEL 401		£29.10.0
GARRARD MODEL LAB90		£24.10.0
GARRARD AT8 TRANSCRIPTION MONO		£6.17.6
CARRARD MODEL AT90		£11.15.0
GARRARD MODEL A70		£16.10.0
GARRARD SRP 10		£4.19.8

Delivered free U.K. S.A.E. enquiries.

10/14 WATT HI-FI AMPLIFIER KIT

A stylish finished monaural amplifier with an output of 14 watts from 2 EL84's in push-pull. Super reproduction of both music and speech with negligible hum. Separate inputs for mike and gram, allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15Ω speaker and independent volume controls and separate bass and treble controls are provided giving good lift and cut. Valve line-up 5Z5, 6X4, 6C83, 6E96 and E280 rectifier. Simple instruction booklet 1/6. (Free with parts).

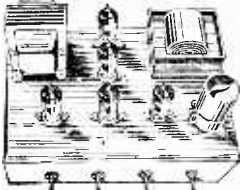


All parts sold separately. **£6.19.6 P. & P.** Also available ready built and tested complete with standard input sockets. **£8.15.0 P. & P. 8/6.** Carrying Case for above **28/6 P. & P. 7/6**

SPECIAL HARVERSON OFFER !!!

BRAND NEW HEAVY DUTY 12in. SPEAKERS Response 45 c/s-13 Kc/s. 1 1/2in. voice coil. Available in 3 to 15 ohms. Guaranteed full 15 watts British rating. Heavy cast aluminium frame. These are current production by world famous maker and as they are offered well below list price we are not permitted to disclose the name. LIMITED NUMBER ONLY. UNREPEATABLE AT 89/6 P. & P. Also 25 watt Guitar Model available at **25.5.0** And 35 watt Guitar Model **28.8.0**.

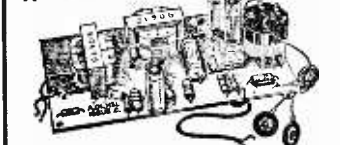
HIGH GAIN 4-TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TAI



● Peak output in excess of 1 1/2 watts. ● All standard British components. ● Built on printed circuit panel size 8 x 3in. ● Output transformer tapped for 3 ohm and 15 ohm speakers. ● Transistors (GT114) or 81 Mullard OC81D and matched pair of OC81/p/s ● 9 volt operation. ● Everything supplied wire cutters, solder, etc. ● Comprehensive easy to follow instructions and circuit diagram 1/6. (Free with Kit). All parts sold separately. **SPECIAL PRICE 45/- P. & P. 3/-.** Also ready built and tested **28/6 P. & P. 3/-.** A pair of TAI's are ideal for stereo.

HARVERSON'S F.M. TUNER Mk. I

● F.M. tuning head by famous maker. ● Guaranteed non-drift ● Permeability tuning ● Frequency coverage 88-100 Mc/s ● Balanced diode output. ● Two I.F. stages and discriminator. ● Attractive maroon and gold dial (7 x 3in. glass). ● Self-powered using a good quality mains transformer and valve rectifier. ● Valves used: 6C83, two 6E96's and E280 (rectifier). ● Fully drilled chassis. ● Size of completed tuner 8 x 5 x 5 1/2in. ● All parts sold separately. Set of parts if purchased at one time, **£5.19.6**, plus 8/6 P. & P. and inc. Circuit diagram and instructions 1/6 post free. Mark II Version as above but complete with magic eye front panel and brackets **£6.12.6 P. & P. 8/6**.

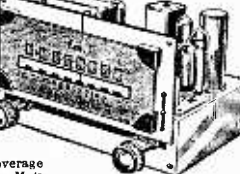

Mark III Version as Mark II but with output stage (ECL82) and tone control **27.7.0 P. & P. 8/6**. Handmade Metal Cabinets. Choice of Black or Green. To fit Mark I, 25/-, P. & P. 3/- To fit Mark II, 17/6, P. & P. 3/-.

SPECIAL PURCHASE TURRET TUNERS

By famous maker. Brand new and unused. Complete with PC84 and PCF80 valves 34-35 Mors I.F. Blocks for Channels 1 to 5 and 9 and 0. Circuit diagram supplied. ONLY 25/- each. P. & P. 3/9.

GORLER F.M. TUNER HEAD


88-100 Mc/s 10.7 Mc/s L.F. 15/-, plus 2/- P. & P. (E0C85 valve, 8/6 extra).

4-SPEED PLAYER UNIT BARGAINS

All Brand New in Maker's Original Packing SINGLE PLAYERS
GARRARD SP25 De Luxe..... £12.10.6, Carr. 5/6
B.S.R. G07 with unit mounted pick-up arm, £4.18.8, Carr. 5/6
LATEST B.S.R. T012..... £3.9.6 Carr. 5/6
E.M.I. with unit mounted pickup arm. £4.9.6, Carr. 5/6
AUTO CHANGERS
LATEST B.S.R. UA25 Super Slim tone. £6.2.6
B.S.R. UA15, £6.19.6, B.S.R. UA16, £6.19.6
LATEST GARRARD 47..... £8.8.0
Standard Garrard Autolink..... £8.10.0
GARRARD AT8..... £10.10.0, Carr. 6/6 on each.
All the above units are complete with t/o mono head and sapphire stylus or can be supplied with compatible stereo head for 12/6 extra.

THE NEW HARVERSON KIT FOR THE HOME CONSTRUCTOR

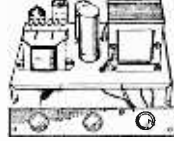A really excellent all purpose A.C. mains 200/240v. AMPLIFIER KIT TYPE HSL 'FOUR' 3 VALVE 4 WATT USING 6C83, EL34, E280 VALVES
Special features include:



● Heavy duty double-wound mains transformer with electro-static screen. ● Separate Bass, Treble and Volume controls, giving fully variable boost and cut with minimum insertion loss. ● Heavy negative feedback loop over 2 stages ensures high control. ● Suitable for use with guitar, microphone or record player. ● Provision for remote mounting of controls or direct on chassis. ● All this builds onto a chassis size only 7 1/2in. wide x 4in. deep. Overall height 4 1/2in. ● All components and valves are brand new. ● Very clear and concise instructions enable even the inexperienced amateur to construct with 100% success. ● Supplied complete with valves, output transformer (3 ohms only), screened lead, wire nuts, bolts, solder etc. (No extras to buy). **PRICE 79/6 P. & P.** Comprehensive circuit diagram, practical layout and parts list 2/6. (Free with kits).

QUALITY RECORD PLAYER AMPLIFIER

A top-quality record player amplifier. Size 7in. w. x 2 1/2in. d. x 5 1/2in. h. This amplifier (was used in a 20 in. record player) employs heavy duty double-wound mains transformer, 6C83, EL34, E280 valves. Separate bass, treble and volume controls. Complete with output transformer matched for 3 ohm speaker Ready built and tested. **PRICE 69/6 P. & P. 4/9.**

ALSO AVAILABLE. Mounted on board with output transformer and 9in. speaker ready to fit into cabinet below. **PRICE 89/8 P. & P. 5/9.**

QUALITY PORTABLE R/PLAYER CABINET

Uncut motor board. Will take above amplifier and B.S.R. or GARRARD Autochanger or single Record Player Unit. Size 18 x 14 x 8 1/2in. **PRICE £3.9.6. Carr. 7/6**

6 TRANSISTOR AND DIODE SUPERHET

A first-class 2 waveband transistor superhet ● Printed circuit panel (size 8 1/2 x 2 1/2in). ● 3 pre-aligned I.F. transformers. ● High-gain Ferrite Rod Aerial. ● All First-grade transistors. ● Car aerial winding. ● Push-pull output. ● All parts supplied with simple instructions. All parts sold separately. Set of parts if purchased at one time ONLY **£4.5.0 P. & P. 2/6**. Circuit diagram 2/- (free with set of parts).

35 OHM SPEAKERS

Suitable for use with above. 2in. Goodmans. Ideal replacement for most pocket portables 8/6, 3 1/2in. 12/6, 7 x 4in., 21/-, P. & P. 2/- per speaker.

Portable CABINET

Size approx. 9 1/2 x 8 1/2 x 3 1/2in. Suitable for above using 3 1/2in. speaker 25/-, P. & P. 2/6.

COIL AND TRANSFORMER SET FOR TRANSISTOR SUPERHET

3 I.F. transformers one oscillator coil one driver transformer and wound Ferrite aerial (med. long and car aerial coupling) 29/6 complete post 2/- 6 transistor printed circuit board to match 8/6. Post 1/- Circuit diagram 1/6 extra.

BARGAIN OF THE YEAR!

A wonderful opportunity for you to build a quality AM/FM TRANSISTOR RADIO TUNER UNIT

for 9v. operation. We offer the essential very high grade specially matched components comprising FM Tuner Head pre aligned (88-108 Mc/s) complete with transistors. Two combined AM/FM I.F. Transformers, one discriminator transformer, one AM last I.F. transformer with diode detector. Most attractive coloured dust-size 8 1/2 x 3 1/2. AM tuning gang, hardware items for tuning mechanism, AM ferrite rod aerial (MW/LW) with coupling winding trimmer bank, tuning drum, pulleys, etc., and suggested circuit diagram giving coil connections etc.

OFFERED AT THE AMAZING PRICE OF **4 Gns. P. & P. 4/6**

Owing to the very high value offered and the limited number we regret that no correspondence can be entered into regarding this item.

SPECIAL PURCHASE!

FROM LEADING HI-FI MANUFACTURERS


7-10 watt OUTPUT TRANSFORMERS to match pair of ECL86's in push-pull to 3 ohm output. ONLY 11/-, P. & P. 2/6.
7-10 watt ULTRA LINEAR OUTPUT TRANSFORMERS to match pair of ECL82's in push-pull to 3 ohm output. ONLY 15/-, P. & P. 2/6.
SPECIAL MAINS TRANSFORMERS to match either of the above. Tapped primary. Secondary 250v. 80mA half wave and 6.3v. 2 amps. ONLY 12/6 P. & P. 3/6.

NEW CARTRIDGE BARGAINS

RONETTE STEREO 105 CARTRIDGE. Stereo/I.P. 78. Complete with 120 supplies. Original list price **67/6. OUR PRICE 24/-, P. & P. 1/-.**
ACOS 71-5 single sided crystal cartridge for Stereo and I.P. records. Complete with diamond stylus and universal mounting bracket. List price **22.8.4**. Our price **18/6 P. & P. 1/-.**
ACOS 947-1 Mono complete. List price **£1.1**. Our price **13/6 P. & P. 1/-.**

STEREO AMPLIFIERS

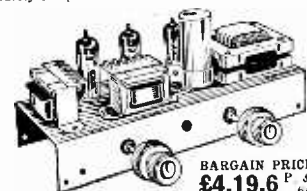Incorporating 2 ECL82's and 1 E280 heavy duty double-wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.



BARGAIN PRICE **£4.19.6 P. & P. 6/6**

SUPER DE LUXE version of above incorporating ECL85 valves separate bass and treble controls and full negative feedback, 8 gns., P. & P. 6/6.

SPECIAL BRAND NEW TRANSISTOR BARGAINS

GET 15 (Matched Pair) 15/-; V15/10p. 10/-; OC71 5/-; OC76 6/-; AF17 7/8; ORP12 10/8. Set of Mullard 6 transistors OC4, 2—OC45 OC81D matched pair OC81 25/-, ORP12 Cadmium Sulphide Cell 10/8.

EDISWAN MAZDA

PXA101 6/8; XA103 8/8.
R.F.I. Pack: 1—PXA102 Mixer; 2—PXA 101 I.F. Amp. (Equiv. OC4 and OC45) 10/8
R.F. 2 Pack: 2—PXA101 I.F. 1—PXA102 Osc. 1—PXA102 Mixer 12/6
L.P. Pack: Consisting of PXE113 Driver Matched pair PX171 mounted complete with heat sinks (Equiv. OC81D and OC81) 12/8
ALL TRANSISTORS POST FREE

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, S.W.19 CHerrywood 3985

Open all day Saturday Early closing Wed. 1 p.m.

A few minutes from South Wimbledon Tube Station (Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. OVERSEAS ITEMS ORDERS CHARGED EXTRA.

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

SEE RIGHT HAND PAGE FOR MORE ITEMS

WEYRAD

TRANSISTOR RECEIVER COILS

Special versions of the P50 Series are now available for the AF.117 or OC.170 Transistors. Details of the simple modifications to our standard receiver are given in the latest edition of the Constructors Booklet which is priced at 2/-.

The new components and their original equivalents are listed below:

	For OC45	For AF117	Price
Oscillator Coil ...	P50/1AC	P50/1AC	5/4
1st I.F. Transformer ...	P50/2CC	P51/1	5/7
2nd I.F. Transformer ...	P50/2CC	P51/2	5/7
3rd I.F. Transformer ...	P50/3CC	P50/3V	6/-
Rod Aerial	RA2W	12/6
Driver Transformer	LFDT4/1	9/6
Output Transformer	OPT1	10/6
Printed Circuit	PCA1	9/6

WEYRAD (ELECTRONICS) LIMITED

School Street, WEYMOUTH, Dorset

SUB-MINIATURE

Set of 3 I.F.'s and oscillator coil, 455-470 Kc/s. Size approximately $1\frac{1}{2} \times \frac{1}{2} \times \frac{1}{16}$ in. Limited quantity available at only 8/- per set. P. & P. 1/6.

Also: Eagle I.F. and osc. coil kit with tuning capacitor and dial, and bar aerial. All complete, miniature and boxed. Supplied with s/ht. cct. at only 24/9 complete. P. & P. 2/6.

SILICON RECTIFIER

Type BY100, 6/- (250v, 500mA) P. & P. 1/6.

TRANSFORMERS

AUTO 50W only 24/- P. & P. 2/6
150W only 45/- P. & P. 3/6

FILAMENT 250-0-25v. 7/8 P. & P. 2/6
TRANSISTOR Complete range of driver and output transformers available.

EARPHONES

New and Boxed
2,000 ohms — 14/3 P. & P. 2/6
4,000 ohms — 17/3 P. & P. 2/6
Also full range of earpieces from 4/11 to 12/8. P. & P. 1/-

VOLUME CONTROLS

Standard, linear and log tracks. All values. Less switch, only ... 2/10 P. & P. 1/6
With d.p. sw. only ... 3/8 P. & P. 1/6
Full range of TEST METERS always in stock—drop in and see for yourself. A fine example is our popular 20Kohms/v. multimeter at only 24.19.6.

We are also stockists of the following items and we will be pleased to furnish you with detailed information and literature on request:
LANDER range of D.I.Y. Burglar Alarm Kits
Philips Electronic Kits
Sinclair Products
Veroboard

REMEMBER



BOTHWELL ELECTRIC SUPPLIES (Glasgow) LTD.
54 EGLINTON STREET
GLASGOW, C.S.

Member of the Lander Group
have all you need for your industrial and domestic electrical applications. See for yourself or telephone 804th 2904 for further information.

TRADE ENQUIRIES WELCOME

LISTEN

AND ENJOY THE
WORLD'S RADIO AMATEUR
AND BROADCAST STATIONS WITH
THE GREATEST OF EASE !!!

WE HAVE SOLVED your aerial problem for
WORLD-WIDE RECEPTION—NO MATTER
WHERE YOU LIVE !!!

World Expert Radio Amateur WIBB
(U.S.A.) claims the "JOYSTICK"
aerial—easier to read stations than with
his massive 520' VEE aerial 70' high.
ZL4GA, who is probably NEW ZEALAND'S
best known Radio Amateur, has
scrapped his outstanding 300' 45'
high aerial and has WORKED ALL
CONTINENTS on the "JOYSTICK" in
under 12 hours !!!

"CO" the Radio Amateur's journal
claims "JOYSTICK" better for reception
than the world popular DIPOLE
(four different receivers used to confirm
this decision).

YOU CAN BE THE PROUD OWNER OF THE
WORLD'S MOST VERSATILE & COMPACT
"JOYSTICK" COMPLETE RECEIVING SYSTEM
FOR AS LITTLE AS
£5.12.6 (DX-MAGNET system), £6.9.0
(Standard system), £7.10.0 (De-luxesystem)
including carriage and packing.

Money Back if not Delighted
Not convinced! Then send for
brochure and showers of testimonials
to:

PARTRIDGE ELECTRONICS LTD

(Dept. P.W.)
CAISTER HOUSE, PROSPECT ROAD
BROADSTAIRS, KENT

MUSICAL INSTRUMENTS AND AUDIO

The performance and frequency range of more than 60 instruments is examined, with a large number of photographs and diagrams. In fact, the book is intended to appeal to both the concert-goer and the audiophile.

by G. A. Briggs.

32/6 Postage 1/-

TRANSISTOR ELECTRONIC ORGANS FOR THE AMATEUR.
by A. Douglas and S. Astley. 18/-.
Postage 1/-.

SERVICING ELECTRONIC ORGANS by C. R. Pittman and E. J. Oliver. 30/-.
Postage 1/-.

ELECTRONIC ORGAN HANDBOOK by H. E. Anderson. 35/-.
Postage 1/-.

AN INTRODUCTION TO COUNTING TECHNIQUES & TRANSISTOR CIRCUIT LOGIC by K. J. Dean. 25/-.
Postage 1/-.

REFERENCE DATA FOR RADIO ENGINEERS by S.T.C. 42/-.
Postage 2/6.

PICK-UPS THE KEY TO HI-FI by J. Walton. 10/-.
Postage 8d.

BRIMAR VALVE AND CATHODE RAY TUBE MANUAL No. 0. 7/6.
Postage 1/-.

COMPLETE CATALOGUE 1/-.

THE MODERN BOOK CO.

19-21 PRAED STREET

LONDON, W.2

Phone: PADdington 4185

Open 6 days 9-6 p.m.


VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS 1R5, 1R5, 1T4, 884, 3V4, DAF91, DF91, DK91, DL92, DL94
Set of 4 for 15/-, DAF96, DF96, DK96, DL96. 4 for 24/6.

1A7GT	7/6 7H7	4/9 B36	4/6 ECF80	7/8 MUT4	4/- TYN6F	10/-
1H5GT	7/3 7Y4	5/- CL33	9/6 ECF82	6/- N1S	5/6 U2S	8/6
1N3GT	7/9 9BW6	6/8 CY1	12/6 ECF86	10/9 PC95	6/3 U26	8/9
1R5	4/9 10C2	11/8 DAC92	7/3 ECH35	6/- PC97	7/- U47	8/6
1R5	4/9 10F	9/9 DAF91	3/3 ECH42	8/3 PCN4	5/6 U52	4/6
1R5	3/9 10L D12	7/6 DAF96	6/- DCH81	9/- POC89	8/6 U54	8/9
1T4	1/9 12AT7	3/9 DCU90	6/6 ECL80	6/3 PCF89	6/6 U78	3/6
3A5	6/9 12A06	4/9 DF33	7/6 ECL82	6/9 PCF82	6/- U191	9/9
3Q4	5/6 12AU7	4/9 DF91	1/9 ECL86	8/6 PCF84	7/9 U281	8/6
3R4	4/9 12AX7	4/9 DF96	6/- EP30	3/6 PDL86	8/3 U301	10/9
3V4	5/6 12K7GT	3/6 DH76	3/6 EP41	6/3 PCF80	9/9 U301	15/-
5Y3GT	4/11 12K8GT	8/6 DH77	4/- EP80	4/9 PCF82	9/9 UAC80	5/9
3Z4GT	6/9 12Q7GT	3/6 DH81	12/6 EP85	5/- PCF85	8/- UAF42	7/9
6Z0L2	8/9 19BG6G	6/6 DK32	7/9 EP86	6/9 PCL82	6/3 UBC41	6/6
6AL5	3/- 20L1	11/9 DK91	4/9 EP89	4/2 PCL83	8/- UBC81	6/3
6AM6	2/6 20P3	10/9 DK92	6/- EP91	2/6 PCL84	8/3 UBS80	6/-
6AQ5	5/9 20P4	13/6 DK96	6/6 EP92	1/9 PCL85	8/- CBF89	5/9
6AT6	4/- 20P5	11/8 DL33	6/9 EP97	7/6 PCL86	8/6 UC84	3/6
6BA6	4/6 25L6GT	4/3 DL35	5/- EP183	6/9 PEN44	6/6 UC85	6/6
6BE9	4/9 25C6TTL1	6/6 DL92	4/9 EL33	6/6 PEN83	9/6 DCF80	8/3
6RH6	5/- 30C18	8/- DL94	6/6 EL38	11/9 PEN305	15/- UCH42	7/6
6BH6	5/6 30F5	8/6 DL96	6/- EL41	7/3 PFL200	17/6 UC181	6/6
6RW6	7/9 30FL1	9/6 DY6	6/9 EL84	4/6 PL26	6/9 UCL82	7/2
6F13	3/6 30L13	10/3 DY7	8/- EL95	5/- PL1	6/9 UCL83	9/3
6F14	9/- 30L17	12/- EAB30	6/- EM34	9/6 PL2	5/6 UFL41	6/9
6K7G	1/6 30P1	13/6 CAF2	7/6 EM9	5/9 PL3	6/- UFL42	4/6
6K8G	4/3 30P12	7/6 EB41	4/- EM81	7/3 PL4	6/3 U85	6/3
6K8GT	7/6 30P19	18/6 EB91	2/- EM84	5/9 PL500	14/- UFL89	6/9
6P28	9/6 30P14	9/6 EBC33	6/- EM87	6/6 PL601	7/6 UL41	7/3
6Q7G	6/9 30P13	10/9 EBC41	6/6 EV51	6/3 PX25	7/9 UL44	15/-
6L7GT	4/9 30P14	11/9 EBF50	6/- FX86	6/- PY32	8/9 UCL46	8/6
4V6G	3/6 35L6GT	9/3 EBF83	7/6 E240	6/6 PY33	8/6 UCL84	6/-
6Y6GT	5/6 35W4	4/6 EBF89	5/9 E241	6/6 PY40	5/3 PY41	4/9
6X4	3/6 35Z4GT	4/6 ECL40	6/9 EZ80	4/- PY81	5/3 UY85	4/9
6X5GT	6/3 35ZKU	8/6 FOC81	3/9 EZ81	4/6 PY82	5/- VP4B	11/-
6Y6	10/8 80	4/6 ECL82	4/9 FV4300	6/3 PY83	5/9 W76	3/6
7B7	7/9 85A2	5/6 EOC28	7/- G233	12/6 PY60	6/6 W77	2/-
7C5	7/9 6063	12/6 EOC54	6/3 G237	3/9 TH91C	6/9 X79	24/6
7C8	5/9 LAZ81	9/3 EOC85	5/6 K701	6/6 TH232	6/6 Z77	2/6

HIGH QUALITY

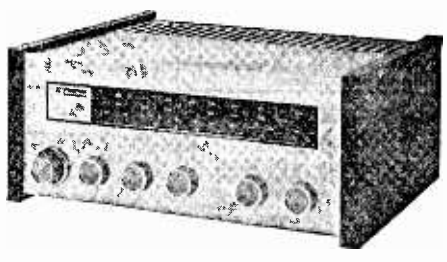

LOWER COST

READERS RADIO

24 COLBERG PLACE, and at 85 TORQUAY GARDENS
STAMFORD HILL REDBRIDGE, ILFORD
LONDON N.16, STA 4587 | ESSEX, CRE 7441

Postage on 1 valve 9d. Extra. On 2 valves or more postage 6d. per valve extra
Any Parcel Insured against Damage in Transit 8d. extra.

BARGAINS FROM BROADWAY ELECTRONICS

GARRARD Latest Model A.T.60, Mono or Stereo £12.0.0. Autoslim £5.5.0. A.T.5 Stereo £6.15.0. Autoslim pick-up arm fitted with Romette Stereo 25 - A.T.6 shells 9/- GC8, GC2, cartridges with brackets 15/- ea.

The "BLAKE" 12in. Heavy Duty Cabinet, Size 24 x 13 x 9in. The 12in. 8 1/2in. Choke. Covered in Rexine and Vynair 85/-. De Luxe model veneered with wood grain Formica and standing on smart fin. legs £5. Please add 10/- for postage.

"HAYDON" Cabinet, 16 1/2 x 15 x 7 1/2in. Fabric covered suitable 12in. speaker 45/-. Postage 7/6. Vynair speaker cloth 50in. wide 14/- yard. Rexine leather cloth 50in. wide 10/8 yard S.A.E. for samples.

The B.M.3. CRYSTAL MIKE 30/-; table stand for same 9/6.

GUITAR PICK-UP complete with clip and screened lead. 12/6. NEON PANEL LIGHTS, 240v A.C. Arcoelectric, 2/6 each.

BARGAINS IN TRANSISTORS
AC127 (NPN) 5/- each. AF114, AF116, AF117, AF118, AF119, OC189, OC170, OC71, OC172 4/6 each. OC81M, OC71 2/6 each. OC72, OC75, OC82 all at 3/- each. RF Packs two OC45, OC4 3/6. AF Packs two OC81, OC81D 6/-; AF Packs two GET119 (OC83 equiv.) GET118 Driver 5/6; OC28, OC29 7/6; ORP12 Light Cell 7/6; Diodes OA81 2/3; OA91 1/6.

TRANSISTOR ELECTROLYTICS: 1, 2, 4, 5, 8, 10, 16, 32, 50, 100 mfd. all at 15 volts, 1/3 each. 100 mfd. 6v, 9d. each special offer. 25 mfd. 50v, 50 mfd. 50v, 50 mfd. 100v, 250 mfd. 25v, 500 mfd. 25v, 100 mfd. 50v, 1.000 mfd. 12v all at 3/- each.

EARPIECES with cord and 3.5 mm plugs, 8 ohm magnetic 3/-; 250 ohm 4/-; 180 ohm magnetic with clip 6/6; Crystal 4/-.

BROADWAY ELECTRONICS

92 MITCHAM ROAD, Tooting, S.W.17

Phone: BALham 3984
(four minutes from Tooting Broadway Underground Station)

Combine an Armstrong Tuner and Amplifier and you have all the advantages of separate units, plus compactness, easier installation, and equivalent performance at a lower price.

Stereo model 127, above, derived from the more expensive model 227, has an identical AM-FM tuner section, with an amplifier section designed for those whose power requirements are more modest.

It has a more modest price too, as does the mono version model 127M.

Each Armstrong Tuner-Amplifier is ideal as the basis of a high fidelity system for radio and record reproduction, tape recording, and playback, and each unit may be built into your own cabinet or used in our optional case, of teak and vinyl hide, as shown.

For full details and technical specifications of all models plus list of over 300 stockists, post coupon or write mentioning I PW 66.

- model 127 STEREO TUNER AMPLIFIER £37.10.0
- model 127M MONO TUNER AMPLIFIER £26.10.0
- optional case £3.10.0



ARMSTRONG AUDIO LTD-WARLTERS ROAD-N.7
Telephone: NORth 3213

Name _____
Address _____
I PW 66

WIRECOMP ELECTRONICS

TRANSISTOR POCKET RADIOS

Ideal Gifts—all supplied complete with personal earpiece, battery and carrying case. Fully guaranteed. Post free.

BOY'S 2 TRANSISTOR MODEL (Illustrated)
In attractive plastic case. Size only 4 x 2 1/2 x 1 1/2 in. 2 1/2 in. speaker. Uses PP3 battery. Tunable over full medium waveband. **39/6**

BOY'S 4 TRANSISTOR MODEL 45/-

6 TRANSISTOR MODELS
In plastic case. 4 x 2 1/2 x 1 1/2 in. with 2 1/2 in. speaker. Uses PP3 type battery Tunable over full medium waveband. **59/6**

2 Waveband (Long and Medium) Model size 5 x 3 1/2 x 1 1/2 in. cream/black plastic case. **89/6**

FAMOUS MAKE TRANSISTOR RADIO THE "STELLA"

7 transistor portable radio. Long, Med. and Short wavebands. Fitted tone switch and sockets for personal earphone and external aerial; chrome telescopic aerial. Uses four 1.5 v. torch batteries. Plastic cabinet in beige and red. size 4 x 7 x 1 1/2 in. Excellent tone. 3in. p.m. speaker. Comp. with shoulder strap and external aerial. Full guarantee. List price 17 Guis. **WIRECOMP'S PRICE £9.19.6** P. & P. 5/-



WONDERFUL BARGAIN FROM RUSSIA THE "SOKOL"

7 transistor radio covering full Medium and Long wavebands with exclusive rechargeable battery which can be recharged from any 110/250 v. A.C. mains supply. Can also operate on PP3 type dry battery. High quality P.M. speaker. Ivory and black Plastic case with metal trim—size 6 x 3 1/2 x 1 1/2 in. Sockets for external aerial and earpiece. Complete with real leather case, dry battery, rechargeable battery and charger, personal earpiece. **WIRECOMP'S PRICE £6.9.6** P. & P. 2/6

WIRECOMP'S BARGAIN STORE
48 Tottenham Court Road, London, W.1
Thousands of bargains: Transistor Radios—Record Players
—Tape Recorders—Radiograms—Rock Bottom Prices

THE "REALISTIC" 7

Transistorised Portable Receiver made to the highest professional standard. Comprises 7 Mullard Trans. plus Crystal Diode. 350 milliwatt output to 4in speaker.—I.F. frequency 470 Kcs—fully tunable over medium and long wavebands. Two-tone plastic cabinet with handle—size 7 x 10 x 3 1/2 in. fitted socket for car aerial. Complete with full instructions.



MADE IN BRITAIN £5.19.6 All parts sold separately FOR Battery 3/9 extra
P. & P. 4/6 extra. (Circuit diagram 2/6, free if all parts bought.)
Also De Luxe Model with superior PVC covered wood cabinet and full view tuning dial. **ONLY £1 EXTRA.** All parts sold separately. Battery 3/9 extra. P. & P. 4/6.

SINCLAIR SUPER MINIATURE POCKET RADIOS
THE MICRO-6. Pocket radio only 1 1/2 x 1 1/2 x 1 1/2 in. Complete with earphone and detailed construction data. Can be built for only **59/6**

THE SLIMLINE. The new 2-transistor pocket radio size only 2 1/2 x 1 1/2 x 1 1/2 in. Can be built for **49/6**

INTERNATIONAL BRAND TAPE—Fully Guaranteed

MYLAR BASE		ACETATE BASE	
3 1/2 in. Triple play, 600ft.	15/-	3 in.—150ft.	3/6
4 in. Triple play, 900ft.	17/6	3 in.—225ft.	4/11
5 in. Double play, 1,200ft.	15/-	3 in.—300ft.	7/6
5 1/2 in. Triple play, 1,800ft.	35/-	5 in. Long play, 900ft.	10/-
5 1/2 in. Double play, 1,800ft.	22/6	5 1/2 in. Long play, 1,200ft.	12/6
5 1/2 in. Triple play, 2,400ft.	45/-	7 in. Stand play, 1,200ft.	10/-
7 in. Stand play, 1,200ft.	12/6	7 in. Long play, 1,800ft.	15/-
7 in. Long play, 1,800ft.	19/6	P.V.C. BASE	
7 in. Double play, 2,400ft.	25/-	5 in. Stand play, 600ft.	8/6
7 in. Triple play, 3,600ft.	58/6	5 1/2 in. Stand play, 840ft.	11/6
P. & P. 1/- extra per reel, 4 reels and over Post Free			

323 EDWARE RD., LONDON, W.2. AMBassador 7115
All Branches open all day Saturday. Early closing Thursdays

378 HARROW RD., LONDON, W.9. CUNningham 9530
Mail Orders to the above address for prompt service

RADIO CLEARANCE LTD.

27 TOTTENHAM COURT ROAD, LONDON W.1. Telephone: MUSEum 9188
Bulk enquiries invited. The oldest component specialists in the trade. Est. 35 yrs.

LOUDSPEAKER BARGAINS STILL AVAILABLE

Enormous purchases of Brand New and Guaranteed Plessey loudspeakers enable us to offer these units at THE LOWEST PRICES EVER! Don't miss this golden opportunity to obtain a first-grade permanent-magnet LOUDSPEAKER at the production line at LESS THAN THE MANUFACTURER'S COST! Read carefully the prepared list below and choose just the right speaker for the job—COMPARE THE PRICES ANYWHERE! SELLING FAST—STOCKS CHANGING RAPIDLY.

Size in inches	Gauss in ohms	Imped. Price	Size in inches	Gauss in ohms	Imped. Price	Size in inches	Gauss in ohms	Imped. Price
2 7000	80	8/-	3 2500	35	10/8	4 9500	25	11/6
2 7000	35	8/6	3 7000	35	8/6	5 7000	3	8/6
2 7000	50	8/6	3 9500	35	10/8	5 7500	3	9/-
2 7000	80	8/-	3 9500	50	10/8	5 9500	3	10/8
3 8500	3	10/-	4 6000	35	10/8	5 9500	15	12/6
3 7000	3	9/-	4 7500	35	9/8	5 8500	25	10/6
3 7000	35	9/-	4 9000	50	11/6	6 7000	3	11/-
3 6500	80	9/8	4 9500	35	11/6			
3 6000	15	10/-	4 9500	15	12/-			
3 7000	3	9/6						
5 x 3 9000	35	12/-	7 x 3 7000	3	9/8	8 x 21 6000	3	8/6
5 x 3 7000	3	8/-	7 x 3 9500	3	10/8	8 x 22 7000	5	9/-
5 x 3 9000	3	8/8	7 x 3 9500	8	11/6	8 x 22 9500	3	10/-
5 x 3 9500	3	9/-	7 x 4 9500	3	11/-	10 x 6 11000	3	22/6
6 x 4 8500	3	10/8	7 x 4 9500	30	12/6	10 x 6 11000	5	22/6
6 x 4 9500	3	10/-	7 x 4 10000	3	12/6	10 x 6 11000	25	23/8
6 x 4 9500	35	12/-	7 x 4 12000	3	15/8			

ALLOW 2/6 each Speaker for postage and packing and handling charge and please specify the exact requirements—the nearest available will be sent.

SELECTED BARGAINS
Beautifully geared AM/FM 2-gang Condensers, 4/8; AM/FM IFT'S 465 Kc/s and 10.7 Mc/s 4/8 pair; Magnavox Crystal Tape Recorder Mikes, 12/6; 3 watt Stereo Amplifiers complete, ready to switch on, 79/8; Sentercel rectifiers R3/2D-D3-2-1-Y, 2/6 each. DIODES—OA79, OA90, CG46H, GD10, 2/- each.
TRANSISTORS: OC35 4/6, PXA101 3/9, AF115 4/6 Sub min. Germanium diode 1/3. **MI diode 6d.** each. Silicon diodes, 400 p.p.m., 330mA, 2/6 each, please send STAMPED complete, ready to switch on, with any enquiry. We regret no catalogue—our stocks move too quickly! Kindly make provision for additional postage and package charge to avoid delay. **Terms: Cash With Order or C.O.D. on Orders over 10/-.**

CHEAPER BY THE DOZEN

RED SPOT TRANSISTORS 9/- Doz.
Audio Similar to OC71
or 1/- each + 4d. postage Post 6d. extra

WHITE SPOT TRANSISTORS 10/6 Doz.
Similar to OC45,
or 1/3 each + 4d. postage Post 6d.


SILICON RECTIFIERS 24/- Doz.
G17M 24V 1/2 Amp
or 2/6 each + 6d. postage Post 1/-

MINIATURE GERMANIUM DIODES 6/- Doz. Postage 6d.

TANK AERIALS 6 Section. Total length 10ft. 10in.
Perfect for Vertical Aerial or Fishing Rod
10/6 each. 1/6 P. & P.

VEROBOARD Now in Stock
2 1/2 x 5 in., 3/8 2 1/2 x 3 1/2 in., 3/8
3 1/2 x 5 in., 5/2 3 1/2 x 3 1/2 in., 3/8
Postage 6d. each extra.

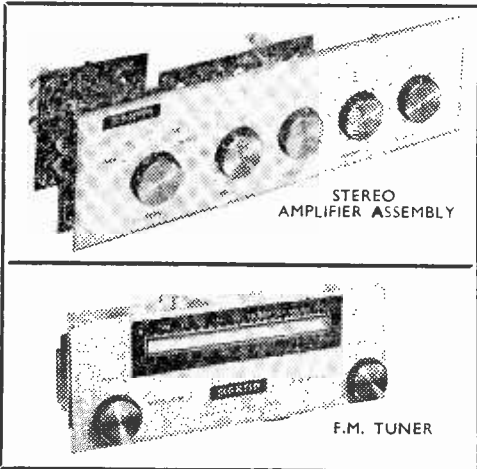PETHERICK'S RADIO SUPPLIES
Dept. P
22 HIGH STREET, BIDEFORD N. DEVON
Tel.: Bideford 3217



KITS WITH A FUTURE

The Martin Audiokit assembly you own today can become part of an even better hi-fi system tomorrow. No other system allows you to enlarge your installation stage by stage in the way Audiokits do. They comprise a wide range of very well made prefabricated units in which the connections are standardised throughout. Each is rigorously tested to stated specification before despatch. **NEW KITS FOR ADDING ON ARE IN COURSE OF PREPARATION NOW**—so by starting with Martin today, you insure yourself for still better listening tomorrow.

Choose Martin for quality

- Build for 3 or 15 ohm system
- Start with Mono and add Stereo or start completely with Stereo
- Power packs available
- Professionally styled escutcheon plates
- Assembly is easy by following the well presented instructions

- 5 stage input Selector £27.6
- Pre-amp. and vol. control £117.6
- Pre-amp. with tone controls £32.6
- 10 watt amp. (3 ohms) £5.12.6
- 10 watt amp. (15 ohms) £6.12.6
- Mains power supply £2.15.0

Send for leaflet describing entire range



Martin Audiokits and Recordakits are obtainable from good stockists everywhere. In cases of difficulty please write direct.

MARTIN ELECTRONICS LTD., 154/155 HIGH ST., BRENTFORD, M'SEX

Phone: ISLeworth 1161/2


MARTIN ELECTRONICS LTD., 154—155 High Street
Brentford Middlesex

Full details of Martin Audiokits please

NAME

ADDRESS

(Block letters) PW1

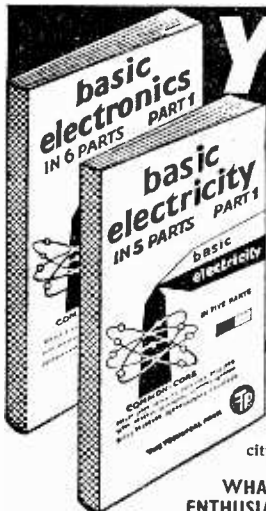

YOURS FREE FOR 7 DAYS

The New 'Picture-Book' way of learning BASIC ELECTRICITY (5 VOLS.) BASIC ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this outstandingly successful new pictorial method—the essential facts are explained in the simplest language, one at a time; and each is illustrated by an accurate cartoon-type drawing.

The books are based on the latest research into simplified learning techniques. This has proved that the **Pictorial Approach** to learning is the quickest and soundest way of gaining mastery over these subjects.

the series will be of exceptional value in training mechanics and technicians in electricity, Radio and Electronics.

WHAT THIS MONTH'S ENTHUSIASTIC READERS SAY

EVERY DAY WE RECEIVE LETTERS PRAISING THESE BOOKS, HERE ARE A FEW FROM THIS MONTH'S POSTBAG.

"Without doubt they are the easiest to follow books I have read, they will be used continuously from now on."
J. W. Fife.

"I may add that these books make the subject of Electronics, very simple to understand."
S. W. Leyton.

To Selray Book Co.
60 Hayes Hill, Hayes, Bromley, Kent

Please send me **Without Obligation to Purchase**, Basic Electricity Basic Electronics on 7 Days Free Trial. I will either return set carriage paid, in good condition within 8 days or send down payment of 15/- (Basic Electricity) followed by 6 fortnightly payments of 10/-, Down payment of 15/- (Basic Electronics) followed by 6 fortnightly payments of 12/6. Alternatively, I will send 68/- (Basic Electricity—5 parts), 81/- (Basic Electronics—6 parts) post free. This offer applies to United Kingdom only. Tick against set required (only one set allowed on free trial).

BASIC ELECTRICITY BASIC ELECTRONICS

Signature

(If under 21, signature of parent or guardian)

NAME

BLOCK LETTERS BELOW

FULL POSTAL ADDRESS

POST NOW FOR THIS OFFER!!

PRACTICAL WIRELESS

blueprints

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London W.C.2.

DOUBLE-FEATURE BLUEPRINTS

The Strand Amplifier	}	5/-
The PW Signal Generator		
The Savoy VHF Tuner	}	5/-
The Mayfair Pre-amplifier		
The Berkeley Loudspeaker Enclosure	}	5/-
The Luxembourg Tuner		
The PW Troubadour	}	7/6
The PW Everest Tuner		
The PW Britannic Two	}	6/-
The PW Mercury Six		
Beginner's Short Wave Two	}	5/-
S.W. Listener's Guide		
Beginner's 10-watt Transmitter	}	5/-
Transmitting and Aerial Data... ..		
PW "Sixteen" Multirange Meter	}	5/-
Test Meter Applications Chart		
The Celeste 7-transistor Portable Radio	}	5/-
The Spinette Record Player		
Transistor Radio Mains Unit	}	5/-
7 Mc/s Transceiver		

SINGLE-FEATURE BLUEPRINTS

The Tutor	3/-
The Citizen	5/-
The PW Pocket Superhet	5/-
The PW 35-watt Guitar Amplifier	5/-
The Mini-amp	5/-
The PT Multimeter	5/-
The Autocrat Car Radio	5/-
The Beginner's Short Wave Superhet	5/-
The Empire 7 Three-band Receiver	5/-
Electronic Hawaiian Guitar	5/-

PLEASE NOTE that we can supply no blueprints other than those shown in the above list. Nor are we able to supply service sheets for commercial radio, TV or audio equipment.

QUERY SERVICE

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

(f) We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.

QUERY COUPON

This coupon is available until 6th January, 1966 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, JANUARY, 1966




NEW 1966 CATALOGUE 140 PAGES

Fully detailed and illustrated components, equipment and Hi-Fi. All types and makes. 5000 Stock lines. The Finest Range available.

Price 6/- post paid.

FREE with Catalogue, 6/- Discount vouchers gives 2/- in pound discount on purchases.

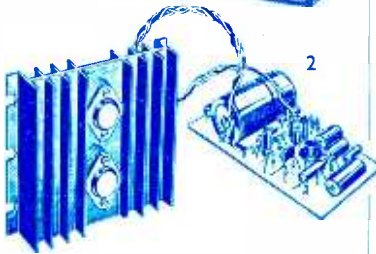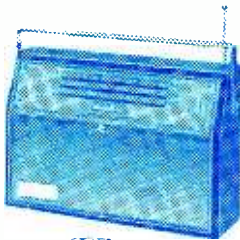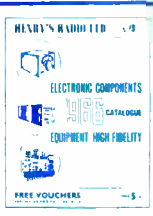CATALOGUE COSTS NOTHING AFTER USING VOUCHERS



(1) GLOBEMASTER MW/LW/SW PORTABLE

Full 3-waveband tuning. Pushbutton waverange. Superhet printed circuit. Black-chromed cabinet 11 x 7½ x 3½ in. (SW 17-50 metres). Ear/Record sockets. **TOTAL COST £8.19.6** P.P. **TO BUILD** 3/6.

(6) VHF FM TUNER

87/105 Mc/s Transistor Superhet. Geared tuning. Terrific quality and sensitivity. For valve or transistor amplifiers. 4 x 3½ x 2½ in. **TOTAL COST £6.19.6** P.P. **TO BUILD** 2/6. (Cabinet Assembly 20 - extra)

10 AND 20 WATT TRANSISTOR MONO AND STEREO HI-FI UNITS

(2) **POWER AMPLIFIERS.** 10 watts RMS output. 100mV input. 30c/s to 20kc/s ±1dB. 6 transistor. Push-pull. Panel size 4 x 2½ x 1 in. H/S 4 x 4 in. **TPA10/3** 3-5 ohms spkr. **£5.10.0**, p.p. 2/6 **TPA10/15** 12-16 ohm spkr., **£5.19.6**, p.p. 2/6 (Mains unit for 1 or 2 amplifiers, 5/6, p.p. 2/6)

(3) **PREAMPLIFIERS.** 8 input selector. Treble, bass, volume, filter controls. 1½mV to 300mV inputs. Battery operated or from Mains Unit. Output up to 150mV RMS.

MP2 Mono 9½ x 2½ x 2 in. **£5.10.0**, p.p. 2/6 (brown or gold front panel 8/6).

SP4 Mono/Stereo, 9 x 3½ x 1½ in., **£10.19.6**, p.p. 3/6 (front panel plate 12/6)

The Finest High Fidelity at Unbeatable Prices

● ALL UNITS BUILT AND TESTED

(4) TRANSMITTER/RECEIVERS

★ Up to ½-mile range **£7.19.6**, p.p. 2/6 per pair
★ Up to 5 mile range **£22.10.0**, p.p. 3/6 per pr.

HI-FI WE CAN NOW SUPPLY FROM STOCK ALL MAKES OF HIGH FIDELITY EQUIPMENT (Hi-Fi Room opening shortly)

(9) MICROPHONES

★ Professional 50K ohms D-301 **79/6**
★ 50k Stick Dyn07, Dynamic **69/6**
★ 100c Xtal Stick with stand **32/6**
★ BM3 Stick M.c. **37/6**

(5) BUILD A TAPE RECORDER

Three speeds—3 watts. Complete kits with new "363" decks. Supplied as preassembled sections. Complete with portable cabinets and Speaker—excellent quality.

★ **TWO TRACK** P.P. **£26** 8/6
★ **FOUR TRACK** P.P. **£30** 8/6

(7) 5 WATT AMPLIFIER

6-Transistor Push-pull, 3 ohms. 6mV into 1K. 12/18V supply. 2½ x 2 x 1½ in. **BUILT AND TESTED 79/6** P.P. (optional mains units 54/- 2/- p.p. 2/-).

New matching Preamplifier, 6 inputs, treble/bass/selector/volume controls. 6-10mV o/p. 9-18V supply. **79/6**, p.p. 2/-

(8) REGENT-6 MW/LW POCKET RADIO

6-transistor superhet. Geared tuning. Push-pull output. Moulded cabinet 5 x 3 x 1½ in. Phone socket.

TOTAL COST 85/- P.P. **TO BUILD** 2/-

MULTI-METERS

PT34 1kV	39/6	TP55 20kV	£5.19.6
M1 2kV	49/6	EP30k 30kV	£6.10.0
TP10 2kV	75/-	EP50k 50kV	£8.15.0
EPI0k 10kV	79/6	500 30kV	£8.17.6
IT1-2 20kV	89/6	EP100k 100kV	£10.10.0
EP20k 10kV	99/6		

FREE Lists on request.

★ 12 page. Transistor, SCR, diode, lightcell, quartz crystal, valve, heat sink, Benier catalogue and 4 page short catalogue of units.

SINCLAIR KITS

Micro FM (VHF) Kit	...	£5.19.6
Micro 6 (MW) Kit	...	£2.19.6
Slimline (MW) Kit	£2.9.6
X10 Built	Mains unit	£6.19.6
X10 Kit		54/-
X20 Built	Mains unit	£5.15.6
X20 Kit		99/6

● KITS IN STOCK

Sinclair, Macgregor and Martin transistorised tuners, radio control, amplifiers, radios, tape recorders, all at advertised prices.

● LET US QUOTE FOR PARTS FOR YOUR CIRCUIT. SEND LIST OF PARTS FOR QUICK REPLY. MOST PARTS IN STOCK FOR ALL PUBLISHED DESIGNS.

HENRY'S RADIO LTD.
303 EDGWARE ROAD, LONDON W2
PADdington 1008/9
Open Mon. to Sat. 9-6. Thurs. 1 p.m.
Open all day Saturday.

***PROVED AND TESTED DESIGNS—
FULLY GUARANTEED**