

# PRACTICAL WIRELESS

NOVEMBER  
1976

40p

## EXTRA INSIDE!

### 8 PAGE SUPPLEMENT

# CAR ELECTRONICS



**CIRTEST'  
PROBE**

**LOW LEVEL  
BATTERY INDICATOR**

**BURGLAR  
ALARM**

**PLUS REGULAR FEATURES**

**ELECTRONIC THERMOSTAT**



# TRANSPLUS ELECTRONICS LTD

58-60 GROVE RD., WINDSOR, BERKS. SL4 1HS. TEL. 54525. TELEX 27950, REF 1617.

ADD 8% VAT TO PRICES MARKED \* ADD 12 1/2% TO ALL OTHER PRICES, OR AS CURRENT VAT LEGISLATION SEND C.W.O. (EXCEPT GOV'T DEPT) POST & PACKING 20p FOR THE UK. BARCLAYCARD & ACCESS BY POST OR 15 MIN ON TELEPHONE ORDERS. CATALOGUE LIST FREE SEND SA MONEY BACK IF NOT SATISFIED.

## A SEMICONDUCTOR POWERHOUSE

### FAST SERVICE

NORMALLY 24 HOURS ON EX STOCK ITEMS.

### QUALITY PRODUCT

ADD VAT TO PRICES

### IC's LOW PRICES

### TRANSISTORS

FULL SPEC. DEVICES

#### OPTO-ELECTRONICS

DISPLAYS  
DL707 0.3" £1\*  
DL704 0.3" £1\*  
DL747 0.6" £1.25\*  
DL727 2x1/2" £1.99\*  
3015F or G £2\*  
ZENON STROBE TUBES  
DISCO/FLASH GUN  
TE606 Tube £7\*  
605 SMALL £4\*

RED POLARISE FILTER 6"x1" £1.50\*

#### RED LEOS 10P.

RED LEOS 209 STYLE 0.125" DIA. OR 0.2" DIA. NO CLIP ONLY 10p.\*  
TIL209 RED LED & CLIP 12p\*  
BIG 0.2" RED LED & CLIP 14p\*  
GREEN LED LARGE OR SMALL 29p\*  
ORANGE LED LARGE OR SMALL 29p\*  
ORP12 60p\* 2N5777 39p\* TEC12 £1\*



#### AUDIBLE WARNING BLEEPER

12VOLT 35mA, SPARKLESS £1\*

#### Technology Toy

ELECTRONIC CONSTRUCTION KITS, 4 in 1 £3.50, 10 in 1 £6. Subject to availability. Send S.A.E. for details.

#### 0-365pf Tuner 99p

SHORT/MED WAVE AIRSPACED  
0-365 pf CAPACITOR 99p  
3 DIGIT & RESET TAPE COUNTER 99p  
SET 3 455KHZ IF CANS 7 or 10 mm £1

#### DALOPEN 75p

ETCH RESIST PEN & 2 TIPS 75p\*  
PEC ETCH PAK 500gm £1.  
6"x4" BOARD, NYLON £1. SRBP 50p\*  
PCB KIT: B ITEMS £2.  
DECON DESOLDER BRAID REEL 60p\*

#### VERO

VERO 0.1" PITCH COPPERCLAD  
2 1/2"x5 1/2" 40p\* 3 1/2"x5 1/2" 45p\*  
2 1/2"x3 1/2" 36p\* 3 1/2"x3 1/2" 40p\*  
3 1/2"x1 1/2" 22FACE CUTTER 65p\*  
DIL BREADBOARD 6"x4" £2.25\*  
VERO PINS: 36 30p, 200 £1.16\*  
5 MIN CLEAR EPOXY GLUE 75p\*

TRADE SUPPLIED

703 RF/IF 29p	LM381 2xpreA £2
709 T099 25p*	LM1808 radio £3
709 DIL 14 25p*	LM3900 4xOPA 60p*
710 DIL 14 35p*	MC1503 2x Pre £2*
723 Regulator 49p*	MC1310 stereo £2
741 DIL 8 PIN 22p*	MC1312 sig £2*
741 DIL 14 35p*	MC1318 £2.50
741 T099 33p*	MC1330 75p*
747 Dual 741 69p*	MC1339 2xPre £2
748 DIL 8 PIN 33p*	MC1350/1/2 £1*
4195 15-0-15 £3*	MC1468/1469 £4*
7805 5V 1A+ £1.50*	MFC4000 iW AF 75p
7812 or 15 £1.69*	NE536 FET OPA £2*
7905/12 & 15 £3**	NE540 Buffer £2*
76013 6W AF £1	NE550 2V ref £2*
CA3046 65p	NE555 TIMER 35p*
CA3048 £2.20	NE556 Dual1555 99p*
CA3054 £2.20	NE560 PhaseLL £4*
CA3130 OPA 84p*	NE561 PLLoop £4*
ICL8038 Siggen £3*	NE562 PLLoop £4*
LM300 OPA £1.50*	NE565 £3*
LM301 OPA 38p*	NE567 £3*
LM304 0-40V £3*	SN7271 as 741
LM308 Hi Bo £1*	SN76660 IF £1
LM309K 5V Reg. £2*	SN76611 IF £1
LM318 70Vus £3*	TBA 800 AF 80p
LM372 IF £2	TBA 810 AF 7W 85p
LM377 2x2W AF £3	TBA 820 AF 80p
LM380(60745) 89p	ZN414 Radio £1.20

PRICE EACH:-	MATCHING 25p
AC127/8 176 20p*	TIP29 & 30 ea 64p*
AC187/8 20p*	TIP29C & 30C 85p*
AD149 49p*	TIP31 & 32 ea 74p*
AD161/162 ea50p*	TIP31C & 32C £1*
BC107 10p*	TIP41 74p*
BC107B 13p*	TIP41C £1.35*
BC108 9p*	TIP42 85p*
BC108B 13p*	TIP42C £1.50*
BC109 9p*	TIP2955 99p*
BC109B 14p*	TIP3055 69p*
BC109C 15p*	TIS43 UniJunc 27p*
BC147/8/9 9p	2N706 & 8 16p*
BC157/8/9 12p	2N2646 UJT 49p*
BC177/8/9 12p	2N2904 & 5 pnp29p*
BC182/3/4a4112p	2N2926Brovys 11p
BC212/3/4a4112p	2N3053 48p*
BCY70/1/2 18p*	2N3055 115W 45p*
BD131 & 132ea39p	2N3055 RCA 89p*
BFR39/88250V39p	2N3614 TO3 £1.50*
BFY50 15p*	2N3702/3/4/5 10p
BFY51 15p*	2N3706/7/8/9 12p
BFY52 & 53 15p*	2N3710/11 £2.25*
BSX19/20/21 20p*	2N3819e & 23e 16p
MJ2955 TO3 95p*	2N3820 FET 40p
MJE3055 64p*	2N3904/5/6 17p
MPU131 PUT 49p	2N5457 FET 29p
INS BUSH SETS sp, DATA LIST 15p.	

**741 22p**  
**8pin**  
**555 35p**  
**BC109 9p**  
**2N3055 45p**  
**FET3819 16p**  
**MC1310 £2**

#### CMOS TTL

SAFE MOTOROLA	7400N	15p*
CD4000	15p*	7401 16p*
CD4001	19p*	7402/3 16p*
CD4002	19p*	7404 19p*
CD4006	£1*	7405/6/7 36p*
CD4007	19p*	7408/9/10 19p*
CD4008	87p*	7411/12 22p*
CD4009	50p*	7413 28p*
CD4010	50p*	7417 28p*
CD4011	18p*	7420/27 23p*
CD4012	15p*	7430/32 22p*
CD4013	50p*	7440 16p*
CD4015	94p*	7441 75p*
CD4016	50p*	7442 65p*
CD4017	94p*	7445 78p*
CD4020	£1*	7447 79p*
CD4022	87p*	7450/3/4 16p*
CD4023	19p*	7470 29p*
CD4024	72p*	7472 25p*
CD4025	19p*	7473 31p*
CD4027	50p*	7474 31p*
CD4028	87p*	7475 49p*
CD4040	94p*	7476 36p*
CD4042	78p*	7480 45p*
CD4046	£1.25p*	7481 99p*
CD4049	50p*	7482 69p*
CD4050	50p*	7483 82p*
14501	26p*	7485 51p*
14502	99p*	7486 33p*
14507	69p*	7490 42p*
14510	£1.64*	7491 75p*
14511	£1.65*	7492 45p*
14512	£1.20*	7493 45p*
14516	£1.70*	7495 68p*
14518	£1.40*	7496 68p*
14519	£1.69*	74100 £1.10*
14520	£1.40*	74107 33p*
14527	£1.99*	74121 32p*
14528	£1.00*	74122 42p*
14541	£2.16*	74123 65p*
14543	£1.99*	74141 82p*
14553	£3.85*	74145 72p*
14566	£1.59*	74147 £2*
14583	99p*	74151 68p*
14585	£1.25*	74154 £1.20*

#### DIGITAL CLOCK IC

AY51224 4DIGIT £3.49

#### SWITCHES

SPST 18p\* DPDT 24p\*  
SUBMIN SPST 65p\*  
WAVECHANGE SWITCHES ALL 40p\*  
1POLE 12 WAY, 2P6W, 3P4W, 4P3W.  
COIL FORMERS 0.2 or 0.3" 10p.

#### GAS DETECTOR TGS

TGS308 £4+ MAINS KIT £6:

#### POTENTIOMETERS AB EGIN

2 NEG LIN OR LOG ONLY 10p. ea  
2.2K 5K & 10K 100K 20p ea  
ALL OTHER VALUES ONLY 16p ea  
PRESETS 6p. RESISTORS iW 1p ea.  
HEATSINKS TO5 & 18 7p\* TO3 16p\*  
TV4 PLASTIC POWER 17p\*  
TO3 EXTRUDED 4" FINNED 45p\*

#### DIN PLUGS ALL 15p ea.

DIN SOCKETS all 10p ea.

#### LARGE RANGE OF OTHER PLUGS ETC

ALSO CASES, SOLDER, METERS, ....  
MANY VERO CASES AVAILABLE PLUS:-  
2518 £1.90\* 2520 £2.15\*etc.  
BLACK PLASTIC CASES IN ABS x42mm  
80x60 50p\*100x75 75p\*  
120x100 89p\* MATCHBOX 40p\*

#### CAPACITORS

CERAMIC 22pf to 0.1 uf 50V .50p  
ELECTROLYTIC, IN 10, 25 & 50V.  
2UF/10V, 10, 50, & 100uf 25V  
& 10V 7p ea. 50VOLT 10p ea.  
1000 uf 25V 18p. 200/500uf 9p.

#### ALUMINIUM BOXES

AB7 50p\* AB8 47p\* AB12 44p\*  
AB13 85p\* AB5 50p\* AB10 50p\*

#### DIL RELAY 1A 250V SPCO £1

TRANSFORMERS 100mA 6, 9 or 12 £1.  
1A/1A 6/12 or 12/24 £2 each.



TRANSISTOR DATA LEAFLET 15p  
TTL TABLES . . . LEAFLET 15p  
OPTO LED & DISPLAYS 40p  
CMOS BOOK £2.50- CLOCK 15p  
ALL OTHER PRODUCTS 40p

#### DIODES

0A81 & 0A91 Germanium 5p  
1N4001 1A50V & 1N4002 5p  
1N4004 6p 1N4007 9p\*  
1N4148 & 1N414 SILICON 4p  
ZENERS BZY88 400mV 10p  
BRIDGE RECTIFIERS 1A50V 22p\*  
1A 400V 30p\* 6AMP 100V 55p\*

#### SCR'S TRIACS

SCR's TAG1/400 1A 400V 50p\*  
1A 50V 39p\* 1A 600V 69p\*  
C10E 4A 400V THYRISTOR 55p\*  
TRIACS: SC146 10A 400V £1\*  
15A 400V DISCO TRIAC £1.50\*  
DIACS: BR100 & MV2 25p ea.

#### BULK OFFERS PER 100 off

1N4001 £3.50  
1N4007 £5  
BC108 £7.50  
2N3055 £33  
741C(8)18  
1A 50V BRIDGE £16.

#### BARGAIN PAKS £1 ea. Full spec.

PAK A: 11 RED LEADS full spec £1\*  
PAK B: 5 741C 8 PIN OP AMP £1\*  
PAK C: 4 2N3055 11.5D 12 BC109 £1\*  
PAK E: 11 BC182 £1.1F 11 2N3704 £1\*  
PAK G: 7 BFY51 £1.8 \* 2N3819 £1\*  
PAK J: 6 2N3053 £1.1 \* K 1N914x40 £1\*  
PAK M: 3 T099 3055 £1.25 \* 2N4011

#### cassettes

LOW NOISE NOT REJECTS.  
C60 33p ea TEN FOR £2.70  
C90 42p ea TEN FOR £3.65

# PRACTICAL WIRELESS

VOL. 52 NO. 7

ISSUE 837

NOVEMBER 1976

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

## EDITOR

Lionel E. Howes, G3AYA

## ASSISTANT EDITOR

Eric Dowdeswell, G4AR

## ART EDITOR

Peter Metalli

## TECHNICAL EDITOR

Terry Carter

## PRODUCTION & NEWS EDITOR

Bill Tull

## TECHNICAL ARTIST

Alan Martin

## SECRETARIAL

Linda Robinson

Jill Austin

## ADVERTS MANAGER

01-634 4444

Roy Smith

## CLASSIFIED ADVERTS

01-261 5762

Colin R. Brown

Advertisement correspondence and enquiries to the Advertisement Manager, Roy Smith, Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD

Published by IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. Tel. 01-634 4444

## BINDERS

Binders £2.10 and indexes 45p (inc. VAT) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London, SE1 0PF.

## ● NEWS & COMMENT

- 568 LEADER ARTICLE—Big Brother Watches
- 569 NEWS . . . NEWS . . . NEWS . . .
- 576 PW READERS' PCB SERVICE
- 581 LETTERS—Comments from PW Readers
- 585 TELEVISION—What's in next month's issue
- 586 PRODUCTION LINES
- 588 NEXT MONTH IN PRACTICAL WIRELESS
- 591 HOTLINES—Recent Developments—*Ginsberg*
- 609 ON THE AIR—Amateur Bands—*Eric Dowdeswell, G4AR*  
Broadcast Bands SW—*Derek Bell*  
Broadcast Bands MW—*Charles Molloy*

## ● CONSTRUCTIONAL

- 589 DFM PRESCALER & MODIFIED DISPLAY BOARDS—  
*T. J. Johnson*
- 592 VIDEO WRITER, part 4—*M. J. Hughes, MA, C.Eng., MIERE*

**EXTRA WITH THIS ISSUE—8-PAGE  
CAR ELECTRONICS SUPPLEMENT**

## ● OTHER FEATURES

- 570 DISCOS AND ASSOCIATED AUDIO EQUIPMENT—  
*Ben Duncan*
- 577 VAGARIES OF VHF—*Ron Ham, F.R.A.S.*
- 602 IC OF THE MONTH (Number 61)—*Motorola MC1339P*  
Stereo Pre-amp
- 606 TECHNICROSS—Puzzle Number 16

## COPYRIGHT AND QUERIES

© IPC Magazines Limited 1976. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press. We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.



# Technical Training in Radio, Television and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or are already working in the industry, ICS can provide you with the specialised training so essential to success.

## Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

## City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, TV Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

## Diploma Courses

- Colour TV Servicing
- Electronic Engineering and Maintenance
- Computer Engineering and Programming
- Radio, TV and Audio Engineering and Servicing
- Electrical Engineering, Installations and Contracting

## Qualify for a New Career

Home study courses for leading professional examinations and diploma courses for business and technical subjects:-

G.C.E.	Engineering	Purchasing
60 subjects at "O" & "A" levels	Farming	Sales
Accountancy	Heating	Storekeeping
Air Conditioning	Industrial Management	Work Study
Building	Mechanical	

**POST OR PHONE TODAY FOR FREE BOOKLET.**

# ICS

**To: International Correspondence Schools**

Dept 7772 Intertext House, London SW8 4UJ or telephone 622 9911

Subject of Interest

Name

Address

Telephone Number

**YES SIR 1st class post TONIGHT!**  
We specialise in high spec components with express service for phone customers



**HIGH SPEC components FAST!**

Agents for VERO - ANTEX -

**BIB MULTICORE SOLDER**

- OPEN 9am-5pm, 6 days—Phone orders 9am-4pm.
- S.A.E. for stock list including pots, presets, I.C.'s 7400 & CMOS, capacitors, plugs, sockets, switches, cable, etc.
- Post free envelope included for your next order.
- SUPER EXPRESS phone service—ask for details.
- Shop at keen prices 6 days per week. Late night—Fri. 7-10pm.

**TRANSISTORS + 200 OTHER TYPES IN STOCK**

AC125 20p	BC109 11p	BC262A 15p	BFX29 26p	TIP41A 67p
126 20p	109B 12p	287 20p	84 22p	42A 80p
127 20p	109C 13p	300 27p	88 22p	TIS43 35p
128 20p	117 18p*	301 26p	BFY50 17p	ZTX300 15p*
151 35p	142 22p	303 30p	51 16p	302 18p*
153 35p	143 24p	338 16p*	52 18p	500 15p*
176 20p	147A 9p*	557 9p*	BY164 40p	502 18p*
187 20p	147B 10p*	BCY71 18p	ME0401 18p*	1N914 5p
188 20p	148 9p*	72 14p	0411 18p*	1N4001 5p
AD149 60p	148B 10p*	BD123 90p	ME4001 10p*	4002 6p
161 42p	149B 11p*	124 60p	4101 11p*	4005 9p
162 42p	149C 11p*	131 36p	MPF102 32p*	4006 10p
MCH/PR 1.04	154 18p*	132 35p	OA47 8p	4148 5p
	157B 12p*	139 54p*	90 5p	2N2219 20p
AF116 24p	177 17p	155 75p*	91 4p	2646 40p
117 24p	178B 18p	BF158 20p*	200 6p*	29250 13p*
124 30p	179B 19p	184 25p	OC28 90p	2928G 15p*
239 37p	184B 12p*	185 28p	29 58p	3053 18p
AU113 1.50*	184L 11p*	194 10p*	35 80p	3055 60p
BC107 11p	187 26p	196 12p*	44 30p	3702 11p*
107A 12p	212A 13p*	197 12p*	71 25p	3703 10p*
108 10p	212L 15p*	199 15p*	ORP12 57p	3704 13p*
CIL108 6p	213B 12p*	200 38p	TIP29A 47p*	3705 10p*
BC108B 11p	214 15p*	338 34p	30A 56p*	3707 12p*
108C 12p	214L 17p*	BFW11 68p	31A 57p	3819E 25p*

<b>DIODES</b>	<b>BRIDGES</b>	<b>RESISTORS 1p* each</b>	<b>LINEAR I/C's</b>
50V 3A 13p	100V 1A 24p	WATT E12 (5%)	741 33p
100V 3A 15p	200V 1A 25p	1 ohm - 10m ohm	LM380 SL60745 1.25*
200V 3A 18p	400V 1A 26p	<b>ZENERS (400mw) BZX 83</b>	LM390N 69p
400V 3A 21p		3V, 3V3, 5V1, 5V6, 7V5,	NE555 60p
		9V1, 10V, 12V, 18V, 22V,	SN76103ND 1.60*
		30V. All at 12p* each.	SN76013N 1.75*
<b>THYRISTORS</b>		<b>LED T11 209/0 125 0.2"</b>	SN76023N 1.75*
60V 1A 20p		Red 20p	TBA800 1.35*
600V 1A 60p	TAG 1 600	Green 29p	TBA810S 1.49*
700V 1A 1.20	BT105	Clips for above 1p.	TBA820 1.20*
400V 4A 58p	CT10ED1		ZN414 1.35*
500V 6½A 1.25	BT109		


Post & Packing 25p per order. VAT please add to total \* 12½%, rest 8%

**ORCHARD ELECTRONICS**

FLINT HOUSE, HIGH STREET, WALLINGFORD, OXON, OX10 0DE  
Telephone 0491 35529.

# Test Equipment

## Multimeters

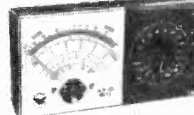

The Eagle range of multimeters covers every possible need of the electrical or electronic engineer. They cost from about £6 to £58 (inc V.A.T.). There's at least one which suits your job precisely.

We have a lot of other test equipment too. Send the coupon and we'll send you our complete catalogue.



Please send me details of all your test equipment.

NAME

ADDRESS

Eagle International, Precision Centre, Heather Park Drive, Wembley HA0 1SU Tel: (01)-902 8832





# RSC 200 WATT DISCO SYSTEM

100 plus 100 WATT OUTPUT

AT A FANTASTIC LOW PRICE!



Consisting of  
(1) Twin T/table Console with Pre-Amp and P.U. Cartridges  
(2) 100 + 100 watt Power Amplifier.  
(3) & (4) Pair 100 Watt Loudspeakers including 12" Units Console complete with lid

Rec. Mic. UD150 Cardioid £9.95 extra with system only

**40W SYSTEM £99.95. 100W SYSTEM inc. Mic. & H'phones £169.95**  
OTHERS UP TO 300 WATTS AT UNBEATABLE PRICES. Send stamp for Free catalogue.

## DISCOMAJOR TWIN TURNTABLE POWER CONSOLE £119.95



Twin Full size BSR turntables, Sonotone or Accus Cartridges with Diamond Stylis. Facilities as TD1 Console but with built-in 100 watt Power Amplifier complete with lid. Terms: Deposit £13.95 and 18 fortnightly payments. £8.78 (Total £135.99)

**STEREO VERSION £155 Carr. £3**  
or Deposit £25 and 18 fortnightly payments £8.30 (Total £174.40)

## ALL RSC PRICES INCLUDE VAT

### RSC PHANTOM 50 COMBO AMP. £59.95


Rating 50 watts, 3 inputs, 2 vol. controls—Bass, Treble Presence. Carr. £1.50 Suitable for Lead or Rhythm Guitar, mic., Radio, Tape etc. Inc. High Flux 12" 50w Speaker. Dep. £7.95 & 8 monthly payments £7.48 (Total £87.79).

## POWER (SLAVE) AMPLIFIER 100 WATT



Suitable for use with DISCO-Consoles. Also for increasing output of lower-powered Amplifiers. Terms: Dep. £9.00 and 8 mthly payments of £5.75 (Total £55.00) **£49.95** carr. £1

## TITAN TA/50A 50W AMPLIFIER

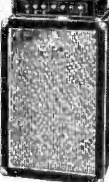

Solid state, 3 sep. controlled inputs plus Master control, Bass & Treble Controls. Vinylite covered cab. with corner protectives. List price £60 Terms: Dep. £9 & 12 mthly pymts **£49.95** £4 (Tot. £57)



## TITAN TA/50A WITH 70W TWIN SPEAKER UNIT

Vinylite covered. Fitted protective corner pieces. Terms: Dep. £11 & 12 mthly pymts £7.67 (Tot. £103.04). **£89.95** Carr. £2.50

## TITAN TA50A WITH 100W TWIN SPEAKER UNIT

For all purposes inc. Bass Guitar. Terms: Dep. £14.80 & 18 fortnightly payments £5.15 (Tot. £107.20) **£94.50** Carr. £2.50

## RSC TRANSFORMERS, L.F. CHOKES FULLY GUARANTEED. Impreg. and interleaved where necessary.

**MIDGET CLAMPED TYPE 200-250v 50 Hz**  
60mA 6.3v. 2a. £1.75  
250-0-250v. 60mA 6.3v. 2a. £1.85  
**STD. UPRIGHT MOUNTING OR DROP-THERO**  
250-0-250v. 100mA 6.3v. 4a. 0.5-6.3v. 3a. £4.85  
300-0-300v. 130mA 6.3v. 4a. C.T. 6.3v. £5.20  
1a. for Mullard 510 Amplifier  
350-0-350v. 100mA 6.3v. 4a. 0.5-6.3v. 3a. £4.85  
350-0-350v. 150mA 6.3v. 4a. 0.5-6.3v. 3a. £5.20  
425-0-425v. 200mA 6.3v. 4a. C.T. 5v. 3a. £9.85  
200mA 6.3v. 4a. 6.3v. 4a. 6v. 3a. £10.00  
450-0-450v. 250mA 6.3v. 4a. C.T. 5v. 3a. £10.45  
250-0-250v. 70mA 6.3v. 2a. 0.5-6.3v. 2a. £2.60  
250-0-250v. 100mA 6.3v. 3.5a. £2.90  
250-0-250v. 100mA 6.3v. 2a. 6.3v. 1a. £3.20  
350-0-350v. 80mA 6.3v. 2a. 0.5-6.3v. 2a. £3.20  
350-0-350v. 100mA 6.3v. 4a. 0.5-6.3v. 3a. £4.35  
**FILAMENT OR TRANSISTOR POWER PACK**  
12v. 1a. £1.10, 6.3v. 1.5a. £1.06, 6.3v. 2a. £1.10, 6.3v. 3a. £1.70, 6.3v. 5a. £2.60, 12v. 3a. or 24v. 1.5a. £2.80 0.9-18v. 1a. £2.26, 0.12-25-42v. 2a. £2.19  
**CHARGER TRANSFORMERS 0.9-15v. 1a. £2.03**  
2a. £2.26; 3a. £2.32; 5a. £2.84. 6a. £3.19; 8a. £3.48.

## New Branches at YORK CARLISLE, DEWSBURY LIVERPOOL, PRESTON



OPEN ALL DAY SATURDAYS (5 Day Week)  
**BRADFORD** 10 North Parade (Closed Wed.). Tel. 25349  
**BOLTON** 23 Deansgate. (Closed Wed.). Tel. 33512  
**BIRMINGHAM** 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.).  
**CARLISLE** 8 English Street. (Closed Thurs.). Tel. 38744  
**COVENTRY** 17 Shelton Sq., The Precinct. Tel. 25983  
**DURBY** 67 St. Peter's Street. (Closed Wed.). Tel. 41361  
**DARLINGTON** 19 Northgate (Cl. Wed.). Tel. 68043  
**DEWSBURY** 9/11 Kingway (Closed Tues). Tel. 460558  
**DONCASTER** 3 Queensgate, Waterdale Centre. (Closed Thurs.). Tel. 63069

All items subject to availability. Prices correct at 13.9.76 E. & O.E.  
**EDINBURGH** 101 Lothian Rd. (Cl. Wed.). Tel. £29 9501  
**GLASGOW** 328 Argyll St. (Cl. Wed. Tues.). Tel. 248 4158  
**HULL** 7 Whitefriargate (Closed Thurs.). Tel. 20505  
**LEICESTER** 32 High Street (Closed Thurs.). Tel. 56420  
**LEEDS** 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 458252  
**LIVERPOOL** 35 Dawson's Way, St. John's Shopping Centre Tel: 708 9380 (Cl. Wed.).  
**LONDON** 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629  
**MANCHESTER** 60A Oldham Street (Closed Wed.). Tel. 938 2778  
**MIDDLESBROUGH** 103 Linthorpe Rd. Tel. 210585 (Closed Wed.)

Barclaycard and Access accepted  
MAIL ORDERS & EXPORT ENQUIRIES TO:—  
AUDIO HOUSE, HENONNER LANE, LEEDS, 18. Tel: 0532 577631.  
MAIL ORDERS MUST NOT BE SENT TO SHOPS  
TERMS C.W.O. or O.O.D. No O.O.D. under £1.  
POSTAGE 40p PER ORDER OR AS QUOTED.  
PLEASE SEND STAMP FOR FREE CATALOGUE.  
**NEWCASTLE UPON TYNE** 24 Newgate Shopping Centre, 59 Grainger St. (Closed Wed.). Tel. 21489  
**NOTTINGHAM** 10/19A Market Street (Closed Thurs.). Tel. 48068  
**PRESTON** 41 Friargate Walk, St. George's Shopp Prec. Tel. 61078  
**SHEFFIELD** 13 Exchange Street (Castle Mkt. Bldg.). (Closed Thurs.). Tel. 20710  
**STOCKPORT** 8 Little Underbank (Closed Thurs.). Tel. 480-0777  
**SUNDERLAND** 5 Market Sq. (Closed Wed.). Tel. 70573  
**YORK** 5 CHURCH ST. (Wed.) Tel. 34355

# £199.95 carr. £7.50

Terms: Dep. £40.00 and 12 monthly payments £15.80 (Total £227.20)

- ★ ILLUMINATED P.U. ARMS
- ★ FULL SIZE B.S.R. Turntables
- ★ SEPARATE MAINS SWITCHES for L. & R. Turntables
- ★ NEON MAINS INDICATORS for all three switches
- ★ INPUTS (Each with its own SLIDER Control) for Mic & Tape
- ★ MASTER BASS, TREBLE and VOLUME CONTROLS
- ★ FADE IN/FADE OUT SLIDER MIXER Controls for each T/table

## TDIM DISCO CONSOLE

Incorporating twin BSR MP80 type turntables and Sonotone or Accus Cartridges with diamond stylis. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mixe' with vol. control. Black Vinylite covered Cabinet with lid. Or DEP. £14.95 and 18 fortnightly payments. £5.47 (Total £113.41) Carr. £1.50 **£99.95**

## TD2S STEREO VERSION OF ABOVE

Terms DEPOSIT £20 and 18 fortnightly payments £8.71 (Total £140.78) Carr. £2.00 **£125.00**

## TITAN 100W BASS BINS £99.95

High quality 15" high flux Bass Unit and J104 Horn Tweeter in folded horn type enclosure to provide amazing level of sound output. List price £144 Terms Dep. £14.95 and 18 fortnightly payments £5.47 (Total £113.41) Carr. £3.

## FANE HIGH POWER L'SPEAKERS

Power ratings R.M.S. Cont. 2 YRR GUARANTEE \*Gauss 14000 Imp 8-15 ohms. CARR FREE.  
**POP 33T 12" 33w £13.95 Dual conc. Full range.**  
**\*POP 50/2 12"-50w £15.99 Dep for Pair £5.95 and 8 monthly pymts £3.81 (Total £36.43)**  
**\*POP 60 15" 60w £25.95 Dep £5.99 & 8 monthly pymts £2.90 (Total £29.19)**  
**\*POP 100 18" 100w £39.95 Dep £8.95 & 8 monthly pymts £4.38 (Total £43.99)**

## TITAN GROUP/DISCO SPEAKERS

GUARANTEED FOR 5 YEARS	List RSC Price	MONTHLY PAYMENTS DEPOSIT	TOTAL
T12/35 12" 35w	£15.00	£4.90 & 8 at £2.62	£27.86
T12/60A 12" 60w	£21.00	£5.90 & 8 at £3.37	£33.86
T12/100 12" 100w	£36.00	£9.90 & 8 at £3.00	£39.90
T15/60 15" 60w	£28.00	£4.99 & 8 at £2.25	£22.99
T15/70 15" 70w	£30.00	£4.95 & 8 at £2.37	£23.91
T15/100 15" 100w	£40.00	£7.00 & 8 at £3.37	£33.96
T18/100 18" 100w	£44.00	£9.95 & 8 at £3.37	£36.91


## FANE CRESCENDO SPEAKERS

FULL RANGE AVAILABLE AT ALL BRANCHES

## CABINETS FOR ABOVE SPKRS £10.95

Heavy duty. Beautifully finished FROM 18 fortnightly payments. In black Vinylite with Vynair fronts fitted protective corner pieces. Various sizes and cut-outs.

## TITAN H.F. UNITS

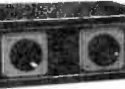

Incorporating a pair of Highly Sensitive Horns. Frequency range 3.5 to 15KHz. Rating 70/100 watts. For 8 or 15Ω. Or Dep. £2.95 & 8 monthly payments £3.38 (Total £23.90) **£27.95**

## HI-POWER TWEETER

Response 3KHz-20KHz with 2 mid. Non elect. filter available 55p. Rating 50 Watt Imp 8 Ω **£6.95**

## 'SOUND TO LITE' SYSTEM PULSAR

Special price **£106.95** Dep. £14.95 and complete kit 18 fortnightly payments £5.95

Super 8L Unit. 1000 watt (Total £121.69) per channel. Manual override buttons, 2 spotbanks with 6 bulbs (3 sep. colours) 5 yd. and 10 yd. leads, fitted plugs. Units sold sep.  
**FAL SOUND-TO-LITE UNIT £21.60**  
**3-WAY SPOT BANK Exc. Bulbs £16.20**  
**COMPLETE SYSTEM £55**  
Incl. 2 Spotbanks and bulbs

**JINGLE MACHINES from £37.95**  
**ECHO CHAMBERS from £49.95**  
**COLUMN SPEAKERS from £29.95**  
**GROUP/DISCO SPKRS in CABS from £11.95**

# BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX

All prices inclusive of V.A.T. at 12½%

Telephone 6743

OB2	40	6BR8G	35	6K7G	35	12B7H	55	30PL13	1.00	DC90	-70	
OZ4	55	6BA6	40	6K8G	50	12B7Y	55	30PL14	1.50	DF91	-80	
1A3	60	6BC8	40	6K9GT	55	12E1	3.50	30PL15	1.00	DF96	-80	
1A5GT	55	6BE6	40	6LI	2.50	12F6GT	40	35A3	-75	DK40	-70	
1A7GT	60	6BE6	70	6L6G	70	12J7GT	70	35C5	-80	DK92	1.00	
1B3GT	55	6B7E	65	6L7	-60	12K5	1.50	35D5	-95	DK96	-70	
1B5GT	60	6BK7A	65	6L18	-60	12K7GT	50	35L6GT	-80	DL96	-80	
1L4	25	6BQ7A	60	6L19	2.00	12K8	-75	35W4	-55	DM70	-80	
1N6GT	75	6BR7	1.00	6LD20	-80	12Q7GT	50	35Z3	-70	DY717	85	
1R5	50	6BR8	1.25	6N7GT	-70	12RGT	-70	35Z4GT	-80	DY80Z	45	
1R4	40	6BR7	1.75	6O	6L1	2.50	12SQT	40	42	1.50	E80CC	2.50
1U4	-70	6BW6	1.00	6Q7G	-50	12R7	-50	42	1.85	E80F	2.80	
1U5	-85	6BW7	-65	6Q7(M)	-65	12S7	-60	43	1.85	E80F	2.80	
2D21	55	6BZ6	60	6R7G	60	12R7	-80	50B5	-95	E80F	2.80	
2GK5	-75	6C4	-48	6SA7	-55	12R7	-75	50C5	-70	E88CC	1.20	
2X2	-70	6C5G	-60	6SC7GT	-75	14H7	-75	50CD6G	-80	E92CC	-70	
3A4	55	6C6	45	6RG7	-50	14S7	1.00	50REH5	-85	E182CC	-70	
3D6	40	6C9	2.00	6RH7	-55	15A5	-55	50L6GT	3.00	E180F	1.15	
3Q4	-80	6CB6A	-50	6S17	-65	19G6	6.50	50L6GT	3.00	E180CC	-70	
3Q5GT	-70	6CDB	-60	6R7GT	-55	19H1	4.00	1.00	E180CC	-70		
3B4	-45	6CDBA	-55	6R7GT	-55	20D1	-70	85A2	-75	E1148	-80	
3V4	80	6CL6	-75	6V6G	-60	20P2	-85	85A3	-75	E1148	-80	
4CB6	-75	6CL8A	-95	6V6GT	-55	20L1	1.20	90A9	3.00	EAS9	-40	
5C8	-75	6CM7	1.00	6X4	-45	20P1	1.00	10B2B	1.00	EABC	1.30	
6E4GY 1.00	6C6U	9.00	6B7GT	-60	20P3	1.00	807	1.10	EAC91	-55		
6U4G	-60	6D3	-75	7B7	-80	20P4	-80	1.10	EAC91	-55		
6V4G	-60	6D6G	1.50	7H7	-80	20P5	1.50	1625	8.50	EAF42	-70	
6Y3GT	-55	6DT6A	-65	7H7	-80	20A6G	-70	5782	1.20	EAF801	-75	
5Z3	1.00	6E6W6	-85	7R7	2.00	20L6G	-70	5783	1.85	EB34	-30	
5Z4G	48	6E5	1.00	7Y4	-80	20Y5G	-80	6057	1.00	EB91	-77	
6J80GT	-55	6P1	-80	7Z4	-80	25Z2	-80	6060	1.00	EB81	-45	
6J80GT	-70	6P8G	-80	8D2	-75	25Z5	-75	6067	1.00	EB41	-45	
6A8G	1.40	6P13	90	9D7	-70	25Z6G	-80	7193	-80	EBP80	-40	
6A7	55	6P14	90	10C2	-70	28D7	2.00	9002	-55	EBP83	-45	
6AG5	-35	6P15	-75	10DE7	-80	30A6	-75	9006	-45	EBP89	-40	
6A7	-60	6P18	-60	10P1	-67	30C16	-77	ACPEN	-80	EBL21	2.00	
6A16	-70	6P23	-65	10P9	-85	30C17	-77	AOFPEN	-60	EC86	-84	
6A15	-70	6P24	-80	10P19	-65	30C13	1.00	AL50	1.20	EC92	-55	
6AK5	-45	6P25	1.00	10LD11	-75	30P5	-70	ABP3	-60	EC92	-55	
6AK6	-70	6P25	-70	10P13	-80	30FL1	1.07	ATP4	5.00	EC93	2.00	
6AN8A	-70	6P32	-70	10P14	-85	30FL2	1.07	AZ1	-50	EC93	2.00	
6AN8	-70	6G6G	-60	12A6	-80	30FL13	-70	AZ31	-60	ECC40	-90	
6AQ5	-47	6GH8A	-80	12AC6	-80	30FL14	1.00	AZ41	-60	ECC81	-84	
6AR5	-80	6GK5	-75	12AD6	-80	30L15	-75	B36	-75	ECC82	-84	
6A87	1.00	6GU7	-80	12AE6	-80	30L17	-70	B63	9.00	ECC83	-84	
6AT6	-80	6H6GT	-30	12AT6	-45	30P4MR	-85	CL33	1.75	ECC84	-35	
6A16	-40	6J8GT	50	12AU6	-50	30P12	-74	CY1C	1.00	ECC85	-39	
6AV6	-80	6J6	-85	12AV6	-60	30P19	-70	CY31	-70	ECC88	1.25	
6AW8A	-84	6J7G	-35	12BA6	-60	30P4	-80	DAF91	-35	ECC88	-51	
6AX4	-75	6J78A	-80	12BE6	-55	30PL1	1.00	DAF96	-80	ECC189	-80	

Special offer of 2F50 valves. Boiled but unused and tested. £1 each.

All goods are unused, tested, and guaranteed. Despatch charges:—25p on all orders below £10 in value. Orders over £10 post free. Orders despatched same day as received. Any parcel insured against damage in transit for 5p per parcel extra. Terms of business available on request. Many others in stock too numerous to list. Please enclose S.A.E. for reply to any correspondence.

## NOW HEAR THIS! 50p

### TAPE HEADS FROM ONLY

Fit a brand new head and transform the quality of your tape player. Large production runs of Standard cassette and cartridge heads for European and U.S. manufacturers enable us to offer single items at bulk-order discount prices.

50p Mono Cassette	Qty	<b>SAVE MONEY &amp; IMPROVE PERFORMANCE!</b> Fantastic value—they fit most tape players Data sheets on full range
60p Stereo 8 Cartridge	Qty	
£1.25 Stereo Cassette	Qty	

I enclose cheque/P.O. in full payment for Qty. marked above + 15p P & P per order

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

Money back if not satisfied

MONOLITH ELECTRONICS LTD., 5/7 Church St., Crewkerne, Som.

## CJL C.J.L. LTD. P.O. BOX 34, CANTERBURY, CT11 1YT

### ALL PRICES INCLUSIVE P&P AND V.A.T.

<b>AUDIO MODULES</b>		<b>SOLDERING IRONS (ANTEX)</b>	
<b>AMPLIFIERS</b>		15W 'C' Miniature Irons	£3.30
5W RMS	£3.15	15W 'CCN' Low leakage Irons	£3.50
10W RMS	£3.50	18W 'G' Miniature Irons	£3.50
25W RMS	£4.60	25W 'X25' Low leakage Irons	£3.25
35W RMS	£14.75	'SK1' Soldering Kits	£5.20
125W RMS	£17.40	'MLX' 12V Kits	£4.10
<b>PRE-AMPLIFIERS</b>		Elements. 'C' £1.50 'CCN' £1.85	
Microphone pre-amplifiers	£2.75	'G' £1.85 'X25' £1.60	
Stereo pre-amp for 5W, 10W	£7.50	Bits. 3/32", 1/8", 3/16"—each £0.50	
Stereo pre-amp for 25W, P.B. selector	£15.35	(N.B. State Type of Iron)	
<b>STEREO FM TUNER Decoder, P.B. selector</b>	£22.70	'ST3' Stands for all models	£1.50
<b>POWER SUPPLIES</b> for 5W, 10W	£1.50	<b>SOLDER</b> in handy dispenser	£0.45
<b>TRANSFORMERS</b> for 5W, 10W	£2.95	<b>WIRE STRIPPER &amp; CUTTER</b>	£0.85
<b>POWER SUPPLIES</b> for 25W	£3.55	WELLER Dual Heat Gun	£7.75
<b>TRANSFORMERS</b> for 25W	£3.35	(Spotlight, Pistol Trigger)	
		WELLER Dual Heat Gun Kit	£10.55

# THE OPEN DOOR TO QUALITY

This 144 page catalogue—Electrovalue Catalogue No. 8 (Issue 2, up-dated) offers items from advanced opto-electronic components to humble (but essential) washers. Many things listed are very difficult to obtain elsewhere. The Company's own computer is programmed to expedite delivery and maintain customer satisfaction. Attractive discounts are allowed on many purchases; Access and Barclaycard orders are accepted.

## 40p

POST PAID inc. 40p Refund Voucher

+ FREE POSTAGE on all C.W.O. mail orders in U.K. over £2.00 list value (excluding V.A.T.) if under, add 15p handling charge.

All communications to Dept. PW10  
 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY  
 TW20 0HE. Tel Egham 3803. Telex 264476 Shop 9-5-30, 9-1 pm Sat  
 NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester  
 M19 1NA. Tel: (061) 432 4945. Shop 9-5-30pm, 1 pm Sat.

# BI-PAK **NEW** Order yours NOW!

## OUR 1977 ILLUSTRATED CATALOGUE

The most comprehensive range of products and technical information ever, including **OVER 800 ADDITIONS** to our list of Semiconductors and Electronic Components. Fully illustrated and designed to be updated as we increase our range. This is **A MUST FOR ALL**: Order NOW—every copy carries a **Special Discount Order Form**.

### GP300

115 WATT SILICON TO3 METAL  
V<sub>ceo</sub> 100V. V<sub>ceo</sub> 80V. IC 15A.  
replacement for 2N3055, BDY11  
1-24 25-99  
\*58p \*48p

### GP Switching

TO3 SIM. TO 2N706 & BSY27/28/30  
All usable devices. No open and  
AVAILABLE IN PNP similar to 2N706  
20 for \*58p, 50 for \*61. 100 for \*61.80  
1,000 for \*64.  
When ordering please state NPN or PNP

**WORLD SCOOP!**

## BI-PAK SEMICONDUCTORS

### ELECTRONIC COMPONENTS

Catalogue

## TRANSISTORS

AND NEW FULLY GUARANTEED

Type	Price	Type	Price	Type	Price
BF117	*0.46	BFY53	*0.13	OC75	*0.16
BF118	*0.71	BSY19	*0.16	OC76	*0.16
BF119	*0.71	BSX20	*0.16	OC77	*0.28
BF152	*0.58	BSY25	*0.16	OC81	*0.16
BF153	*0.46	BSY26	*0.16	OC81D	*0.16
BF154	*0.46	BSY27	*0.16	OC82	*0.16
BF155	*0.71	BSY28	*0.16	OC82D	*0.16
BF156	*0.49	BSY29	*0.16	OC83	*0.29
BF157	*0.58	BSY38	*0.16	OC139	*0.29
BF158	*0.58	BSY39	*0.16	OC140	*0.23
BF159	*0.81	BSY40	*0.29	OC189	*0.28
BF173	*0.15	BSY41	*0.28	OC170	*0.26
BF176	*0.36	BSY95	*0.13	OC171	*0.26
BF179	*0.31	BSY95A	*0.13	OC200	*0.26
BU180	*0.31	BU105	*1.90	OC201	*0.29
BF181	*0.31	MJE521	*0.58	OC202	*0.28
BF184	*0.10	MJE2955	*0.58	OC203	*0.28
BF195	*0.10	MJE3055	*0.57	OC204	*0.28
BF196	*0.82	MJE3440	*0.51	OC205	*0.38
3F197	*0.12	MPP102	*0.28	OCP71	*0.44
1F198	*0.12	MPP104	*0.28	ORP12/	
F199	*0.12	MPP105	*0.28	NSL4931	*0.48
F257	*0.28	OC19	*0.38	ORP50	*0.41
2558	*0.38	OC20	*0.60	ORP61	*0.41
2559	*0.46	OC22	*0.47	TIP29	*0.40
262	*0.56	OC23	*0.49	TIP30	*0.45
263	*0.56	OC24	*0.57	TIP31A	*0.52
270	*0.36	OC25	*0.39	TIP32A	*0.60
171	*0.31	OC28	*0.38	TIP41A	*0.65
72	*0.81	OC28	*0.60	TIP42A	*0.72
73	*0.36	OC29	*0.60	TIS43	*0.25
1	*0.36	OC35	*0.45	UT46	*0.20
2	*0.25	OC36	*0.51	ZTX107	*0.67
3	*0.19	OC41	*0.29	ZTX108	*0.67
4	*0.19	OC42	*0.25	ZTX109	*0.67
5	*0.19	OC44	*0.18	ZTX300	*0.67
6	*0.19	OC45	*0.13	ZTX500	*0.66
7	*0.19	OC70	*0.10	2N696	*0.16
8	*0.19	OC71	*0.10	2N697	*0.11
9	*0.19	OC72	*0.15	2N698	*0.26
10	*0.19	OC74	*0.15	2N699	*0.34

APPROX. 200 PAGES  
Assorted full-out integrated circuits  
Logic, 74 series, Linear, Audio etc.  
Many coded devices but some unmarked  
to identify.

**OUR SPECIAL PRICE**

**P&P**  
Postage and Packing add 25p unless  
otherwise shown. Add extra  
airmail. Minimum order £1.

### ★ Indicators

3015F Miniltron 7 Segment Indicator £1.16

### L.E.D. DISPLAYS

DL707 Common anode 0.3" 85p. DL767  
common anode 0.8" £1.76. DL727 Double  
Display, common anode 0.5" £2.98

### L.E.D.'s

Available in 0.125" and 0.2" dia lenses  
RED 19p. GREEN 17p. YELLOW 17p.

### ★ 74 Series

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURES

Type	1	25	100+	Type	1	25	100+	Type	1	25	100+
7400	0.09	0.09	0.08	7448	0.80	0.78	0.76	74122	0.50	0.48	0.46
7401	0.10	0.09	0.08	7450	0.12	0.11	0.10	74123	0.58	0.56	0.54
7402	0.11	0.10	0.09	7451	0.12	0.11	0.10	74141	0.00	0.58	0.56
7403	0.11	0.10	0.09	7453	0.12	0.11	0.10	74145	0.00	0.84	0.82
7404	0.13	0.12	0.11	7454	0.12	0.11	0.10	74150	£1.30	£1.25	£1.20
7405	0.13	0.12	0.11	7460	0.12	0.11	0.10	74151	0.78	0.74	0.72
7406	0.25	0.24	0.23	7470	0.25	0.24	0.23	74153	0.85	0.83	0.81
7407	0.25	0.24	0.23	7472	0.22	0.21	0.20	74154	£1.50	£1.45	£1.40
7408	0.15	0.14	0.13	7473	0.29	0.26	0.22	74155	0.80	0.78	0.76
7409	0.15	0.14	0.13	7484	0.27	0.25	0.23	74156	0.80	0.78	0.76
7410	0.09	0.09	0.08	7475	0.48	0.46	0.44	74157	0.85	0.83	0.81
7411	0.23	0.22	0.21	7476	0.25	0.24	0.23	74160	£1.00	0.98	0.96
7412	0.26	0.25	0.24	7480	0.50	0.48	0.46	74161	£1.00	0.98	0.96
7413	0.26	0.26	0.25	7481	£1.02	£1.00	0.98	74162	£1.00	0.98	0.96
7416	0.28	0.27	0.26	7482	0.83	0.81	0.79	74163	£1.00	0.98	0.96
7417	0.28	0.27	0.26	7483	0.98	0.96	0.94	74164	£1.25	£1.20	£1.15
7420	0.12	0.11	0.10	7494	0.27	0.25	0.23	74165	£1.25	£1.20	£1.15
7422	0.28	0.27	0.26	7485	£1.25	£1.20	£1.15	74166	£1.48	£1.44	£1.39
7423	0.30	0.28	0.26	7486	0.32	0.30	0.29	74174	£1.00	0.95	0.90
7425	0.30	0.28	0.26	7489	£2.90	£2.90	£2.70	74175	0.85	0.83	0.81
7426	0.30	0.28	0.26	7490	0.37	0.35	0.33	74176	£1.16	£1.11	£1.06
7427	0.30	0.28	0.26	7491	0.80	0.80	0.80	74977	£1.16	£1.11	£1.06
7428	0.42	0.38	0.36	7492	0.43	0.42	0.41	74180	£1.16	£1.11	£1.06
7430	0.12	0.11	0.10	7483	0.43	0.42	0.41	74181	£2.00	£1.90	£1.85
7432	0.30	0.28	0.26	7494	0.43	0.42	0.41	74182	0.90	0.88	0.86
7433	0.39	0.37	0.35	7495	0.70	0.68	0.66	74184	£1.87	£1.82	£1.77
7437	0.30	0.28	0.26	7496	0.68	0.66	0.64	74190	£1.50	£1.45	£1.40
7438	0.30	0.28	0.26	74100	£1.00	0.98	0.96	74191	£1.50	£1.45	£1.40
7440	0.12	0.11	0.10	74104	0.40	0.38	0.36	74192	£1.15	£1.10	£1.05

ONLY 50p 15p P+P

WORLD SCOOP!!

JUMBO SEMICONDUCTOR PAK  
Transistors-Germ. and Silicon.  
Rectifiers-Diodes. Triacs-Thyristors-I.C.'s and  
Zener. ALL NEW AND CODED.  
Approx. 100 pieces only \*1.85p.

**VAT CHAT**

Please add 12½% to prices marked\*. Remainder add 8%

**ZENER DIODES**

FULL RANGE IN STOCK. 2-33 Volts  
400mW 8p 1.5W 17p 10W \*30p

**REGULATORS**

TO3 Plastic Encapsulation  
µA.7805/L129 5V (equiv. to MVR5V) £1.23  
µA.7812/L130 12V (equiv. to MVR12V) £1.23

# BI-PAK

P.O. BOX 6, WARE, HERTS

SHOP AT 18, BALDOCK ST, WARE, HERTS.  
OPEN 9 to 5.30 Mon/Sat. Tel: 61593



# Sparkrite Mk2

## Capacitive discharge electronic ignition kit

**VOTED BEST OF 8 SYSTEMS TESTED BY 'POPULAR MOTORING' MAGAZINE**



- \* Smoother running
- \* Instant all-weather starting
- \* Continual peak performance
- \* Longer coil/battery/plug life
- \* Improved acceleration/top speeds
- \* Up to 20% better fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

### THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

### OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes: switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

**CALLERS WELCOME.** For Crypton tuning and fitting service - 'phone (0922) 33008.

**PRICES INCLUDE VAT, POST AND PACKING.**

**Improve performance & economy NOW**

**POST TODAY!**

**Quick installation**  
No engine modification required

Electronics Design Associates, Dept., PW.11  
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name .....

Address .....

Mk. 2 DIY Ass. Kit @ £11.80	QUANTITY REQUIRED	I enclose cheque/PO's for <b>£</b>
Mk. 2 Ready Built Negative Earth @ £14.97		
Mk. 2 Ready Built Positive Earth @ £14.97		Cheque No.
Ignition Changeover switches @ £4.30		Send SAE if brochure only required.
R.P.M. Limit systems in above units @ £2.42		

**THESE**

**PLUS THIS**

**EQUALS**

The easiest, fastest way of constructing your electronic circuits. 0.1" x 0.1" or 0.15" x 0.15" Matrix, 15 sizes.

**VEROBOARD<sup>®</sup>**

New catalogue available (price 10p + S.A.E. at least 7" x 9")  
Vero Electronics Limited, Retail Dept.,  
Industrial Estate, Chandler's Ford, Hants. SO5 3ZR  
Telephone: Chandler's Ford 2956 (STD 04215)

## J. BIRKETT

### Radio Component Suppliers

25 The Strait, Lincoln, LN2 1JF

Telephone: 20767

**20 SILICON PHOTO TRANSISTORS AND PHOTO DARLINGTONS** Untested for £1.

**GERMANIUM TRANSISTORS** AC 141K, AC 142K, AC 153K, AC 176K, AC 187K, AC 188K. All at 20p each.

**SILICON SOLAR CELLS** -5 Volt 5mA @ 35p, -5 Volt 50mA @ 50p, -5 Volt 100mA @ 60p, -5 Volt 500mA @ £2.20.

**ST C CRYSTAL FILTERS** 10-7MHz B.V. ± 6KHz @ £4.

**ST 12 VOLT DOUBLE POLE CHANGE OVER RELAYS** @ 50p.

**MULTI-TURN CERMET 20 TURN TRIMPOTS** 10, 20, 50, 100, 200, 500 ohms, 1K, 2K, 5K, 10K, 20K, 50K, 100K, 200K, 500K, 1 Meg, 2 Meg. All at 30p each.

**MULTI-TURN WIRE WOUND 20 TURN TRIMPOTS** 10, 20, 50, 100, 200, 500 ohm, 1K, 2K, 5K, 10K, 20K, All at 20p each.

**20 ASSORTED TUNING VARACTOR DIODES** Untested @ 45p.

**NEW BOOKS** "Constructing Simple Short Wave Receivers" @ 60p, "Building Simple Transistor Test Gear" @ 75p.

**50 ASSORTED TRANSISTOR ELECTROLYTICS** @ 57p.

**PLASTIC POWER TRANSISTORS** MP 8112 NPN @ 15p, MP 8512 PNP @ 15p.

**HIGH CAPACITY TUNING VARACTOR DIODES** 180 to 300pf. Untested 3 for 30p.

**VHF DUAL GATE MOS FET** Like 40673 @ 33p, 4 for £1.10.

**OP-AMPS** 8 Lead Round with circuit for Audio Pre-Amp. Untested 5 for 57p.

**COMPRESSION TRIMMERS** 10pf, 30pf, 50pf, 150pf, 750pf, 1000pf. All 6p each.

**MULLARD SEMI AIR-SPACED TRIMMERS** 5 to 60pf at 8p each.

**F.M. I.C.'s** Like TAA 570 Untested with data @ 5 for 57p.

**TEXAS PNP DARLINGTON POWER TRANSISTORS TIP 117.** @ 35p.

**SPECIAL OFFER OF RESISTORS 5% CARBON FILM** 1/2, 1, 1/2 watt assorted. 20 different odd values in Lots of 200 @ 80p.

**JACKSON 10pf TUNING CAPACITOR C802** @ 75p.

**60 ASSORTED WIRE WOUND RESISTORS** 1 to 10 Watt for 57p.

**200 TUBULAR CERAMICS** Assorted @ 57p.

**TEXAS 800 PIV 2 Amp PLASTIC TO3 NPN TRANSISTORS** 50p each. 3 for £1.10.

Please add 20p post and packing on U.K. orders under £2.

# barclay

ELECTRONICS

## TECHNOLOGICAL PRECISION PRODUCTS

### CBM

- SR7919D ● 8-digit or 6-digit+2 Exp.
- Full trig and log functions ● Sq. root
- Reciprocals  $Yx, X^x, \pi$
- Register exchange
- Memory plus
- Store recall
- Sign change
- Algebraic logic.



£11.70\*

4148R—10-digits, 2 exponents, Full log and trig functions.  $X^3$ , Reciprocal,  $\pi$ , X root of Y. Polar rectangular coordinates. 2-store memory. Rechargeable. Mean and Standard deviation.

(R) £28.50

SR4190R—10-digit, 2 Exp. 90 function pre-programmed, metric conversions. Extra functions to the 4148R—Perms and combinations. Gamma. Poisson and Binomial distributions, factorial, complex numbers, hyperbolic functions, linear regression and integration of  $Y=f(x)$ .

(R) £39.95

SR1800—Similar to the 4148R. Green display. Battery operated. £19.40\*

### SINCLAIR

- CAMBRIDGE SCIENTIFIC
- 5-digit ● 2 Exp.
- C & CE key ● sin ● cos ● tan ● arcsin ● arccos and tan ● reciprocal ● E to the X ● natural log
- antilog ● memory + ● memory — ● memory exchange ● memory cancel ● EE exponent ● change notation ● LUS a degree radian switch.



£10.54

OXFORD 300—Larger version of above.

£12.49\*

### DECIMO

- VATMAN—SCIENTIFIC
- Large green display, 8-digits, 2 exponents, 4 trig log functions  $10^{--}$ .
- Radian degrees. Exchange, Memory,  $\pi$ , Reciprocal,  $X^x$  etc.
- Single Function keyboard. 20 hr battery life. £23.50



SUPER-VATMAN—Similar to above but with full-function memory,  $X^x$  Reciprocal,  $\pi$ ,  $\sqrt{\quad}$  etc. £11.50

### ROCKWELL

- 44RD. 9-digit or 5-digit + 2 Exp. Green display. Store. Similar to the 53R less factorial.
- £17.55\*
- 64RD. 12-digit or 8-digit+2 Exp. Additional to 44RD: Polar rec., coordinates, log, rad or grad.
- £22.20\*
- 83R—8-digit, 2 exponent.  $10^{--}$ . Memory. 2-level parentheses. All trig and log functions. Degree radian. Factorial. Reciprocal.  $\pi$ ,  $\sqrt{\quad}$  etc. Rechargeable.
- (R) £23.95



Including recharger. 61R—Green display. 8-digits. All trig and log functions. (R) £20.42

## The ZYCON range of Quality Electronic Watches

### L.C.D.

KLC3 L.C.D. Constant display Shows Hrs, Mins & pulsating secs. Chrome finish with Stainless Steel back and FREE Adjustable S/Steel bracelet. £22.68

KLC5 5-Functions. Shows Hrs, Mins, pulsating secs. Press button once for Mth & Date. Twice for Secs readout. Auto-set back to time! Plus 'Nite Lite' for viewing in dark. Stylish Chrome finish. S/Steel back. FREE matching S/Steel bracelet. £32.68

KLC6 SWISS MADE—Solid S/Steel throughout. Constant disp., shows Hrs, Mins, pulsating Secs. Single Command Button—Press once for Mth & Date, twice for Mins & Secs. Auto-reset back to time. 'Nite-Lite'. FREE matching S/Steel bracelet. £36.98

Or in Heavy Gold Plate on Solid S/Steel with Gold Plated bracelet. £41.61

All come in FREE Presentation Box. All Zycron watches carry our 'NO QUIBBLE' 1 Year Guarantee!



### L.E.D.

KED5 5-Functions. Shows Hrs, Mins, Secs, Mth & Date. 4-Yr calendar. Beautifully finished with S/Steel back & FREE Leatherette Strap. £18.47

KED6 A fantastic 6-Functions—window display shows Hrs, Mins, Secs, Mth & Date. Day of week in letters. Single button. Auto-hold & Fade-out. 4 Yr calendar. Case in Heavy Rhodium on Brass + S/Steel back. FREE matching S/Steel adjustable bracelet. £27.33

KED6 PLUS Month & Day of the Week in Letters! Shows Hrs, Mins, Secs, Date, Mth & Date, Day of Week, Auto 4-Yr calendar, A.M./P.M. Set/Indicate. One of the most sophisticated watches at this price. Accurate to within a few secs a year. Finished in Satin Stainless Steel with FREE matching Steel bracelet. £34.62 ONLY



### NOVUS

4525—8-digit, 2 Exp. 100 step programmable. R.P.N. Full log, & trig functions. X Y Exchange, exponent key, change sign, memory, 4 roll atack, skip, delete, accessible additional programmes within the 100 step. (R) £39.55

4526—Non-programmable version of the 4525 incl. mem +  $x^2$ , deg. & Rad. (R) £21.20

4510—8-digits. 3 level stack. All trig and log functions.  $\sqrt{\quad}$ ,  $\pi$ , Reciprocal. Memory etc. £13.50\*



NEW 4640. 10-digit, 2 Exponent, 54 functions. 4-level Roll Stack. 3 fully addressable memories. Logs, Trigs, Stat & Metric Conversions etc. (R) £47.10

4600—Same but (R) £47.10

Algebra IC (R) £33.10

4515—100-step programmable version. (R) £17.80\*

6010—Metric £16.65\*

6020—Financier. £16.65\*

6025—Rechargeable. Financier 100-step programmable. (R) £39.50\*

6030—Statistician. £16.50\*

6035—100-step programmable Statistician. Rechargeable. (R) £39.50

### CASIO

FX-20—Full trig and log functions. 8-digit mantissa or 6-digit mantissa and 2-digit exponent  $10^{--}$  to  $10^{--}$ . Bright green display. Full sin, cos, tan, inverse sin, inverse cos, inverse tan. Log X and  $\ln x$ ,  $e^x$ ,  $X^x$ ,  $\sqrt{\quad}$ , Reciprocal Degree Radian conversion. Memory and exponent key. ONLY

£15.65\*

FX-15—As above but larger and including a larger display,  $x^2$  key,  $\pi$  key, Reciprocal key. ONLY £19.25\*

FX-101—De Luxe model with similar functions to the FX-15 but 8-digits + 2 exponent  $10^{--}$  to  $10^{--}$ . OUR PRICE £23.50\*



### DECIMO DIGITAL CLOCK/RADIO

£32.95 OUR PRICE

Incl. VAT plus £1 p&p



### LARGE DIGITAL READOUT

This is the most unique clock/radio in the country today having a soft 11" high orange-glow digital readout which is completely silent and non-pulsating. In a beautiful teak style cabinet with up-to-date VHF/MVW radio. You can awake to soft music or alarm—and if you want up to 10 minutes more—just press the 'Drowse' button. Automatic 80 minute 'sleep' button in case you drop off while the radio's on

## ORDER FORM

PHONE CALLS AND PERSONAL CALLERS WELCOME MONS TO THURS BETWEEN 2 & 5 p.m. 01-458 4755. SUNDAYS 10 a.m. to 1 p.m. To: BARCLAY ELECTRONICS Dept. 10PW, 1115 FINCHLEY ROAD, TEMPLE FORTUNE, LONDON N.W.11


Please send me.....  
with/without optional mains adaptor. I enclose cheque/money order for a value £.....Please add 55p to all items to cover p. & p.

NAME .....


ADDRESS .....

barclay

# Bring 'scope' to your interest.

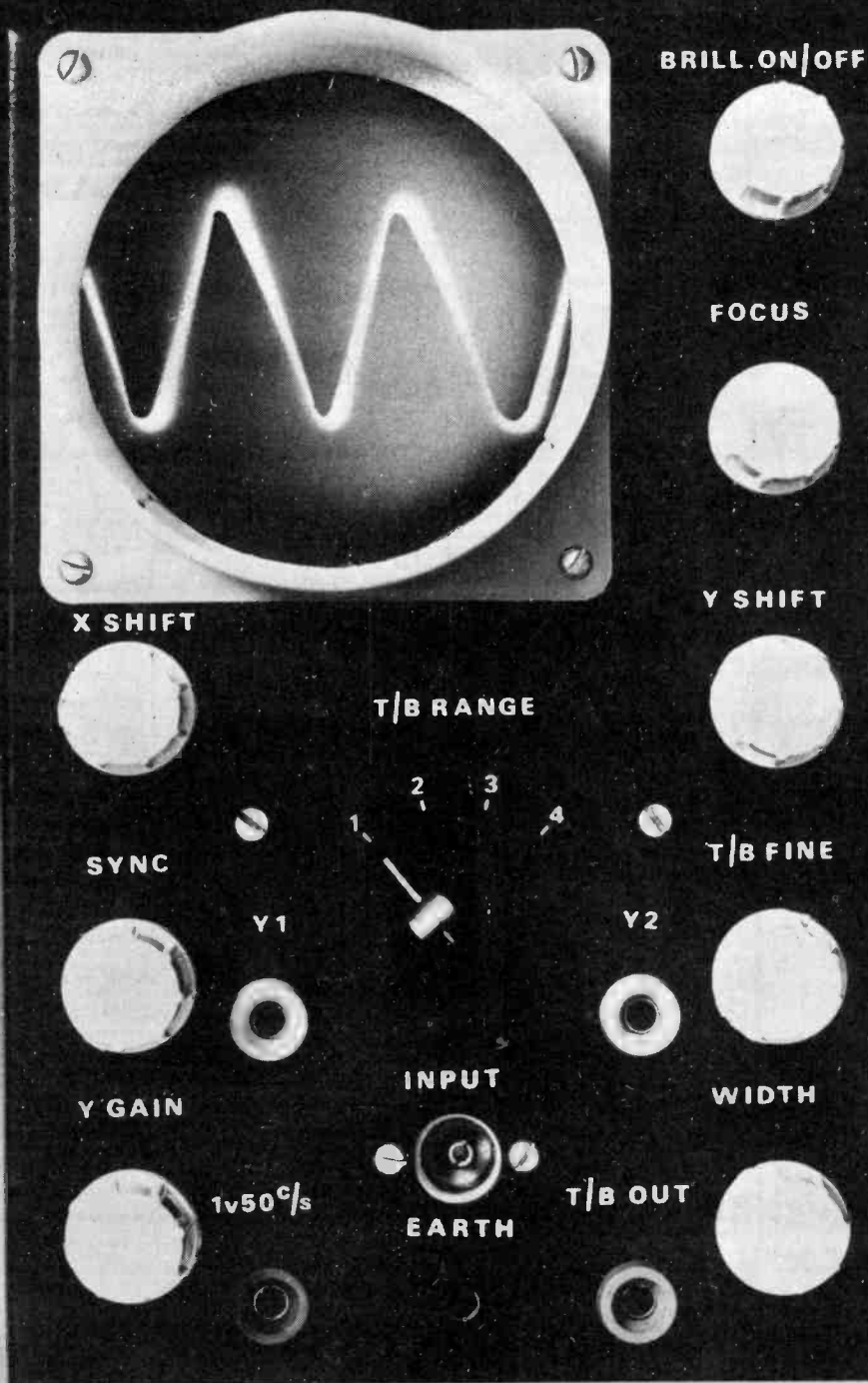




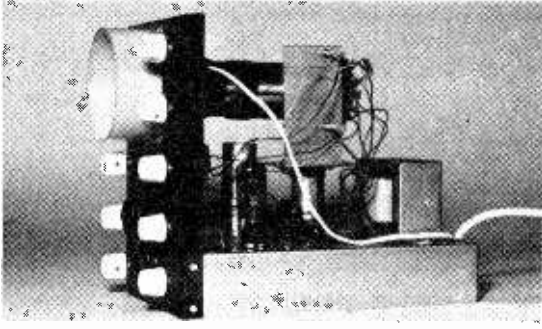

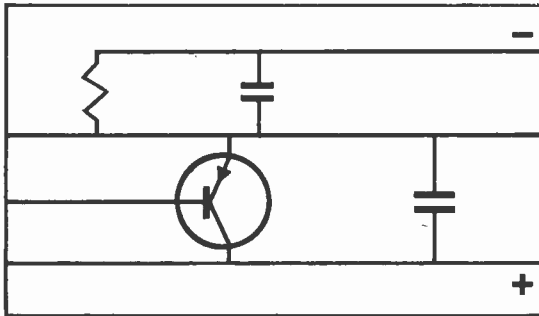
## 1 Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.


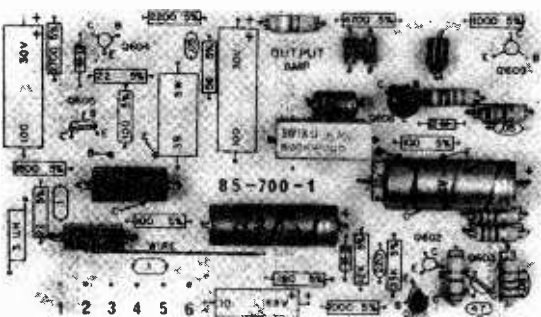
## 2 Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.



## 3 Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

# 'There's only one way to master electronics... to see what is going on and learn by doing.'

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

Write to:- British National Radio & Electronic School  
P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

WI 116

# FANE 'SPECIALIST RANGE' LOUDSPEAKERS

OF OUTSTANDING QUALITY FOR THE DISCRIMINATING PROFESSIONAL  
Features include ROBUST CAST ALUMINIUM CHASSIS and 2" EXTRA HIGH POWER VOICE COILS  
All models available in impedances of 8 ohm or 15 ohm. Guarantee: 2 years. Recommended Prices Inc. VAT



Illust.  
12"  
'DISCO 80'

## 12" 'DISCO 80' 80 watts R.M.S.

Linen Cone Surround. Fitted extra large Tweeter Cone. Frequency Range 50-15,000 Hz. Rec. Retail Price **£25-95**

## 12" 'GUITAR 80L' 80 watts R.M.S.

Plastiflex Cone Surround. Alluminium Centre Dome. Frequency Range 50-9,000 Hz. Rec. Retail Price **£24-75**  
DESIGNED FOR LEAD GUITAR

## 12" 'GUITAR 80B' 80 watts R.M.S.

Linen Cone Surround. Frequency Range 45-9,000 Hz. Rec. Retail Price **£24-95**  
FOR USE IN MULTIPLES FOR BASS GUITAR

## 12" 'PA 80' 80 watts R.M.S.

Plastiflex Cone Surround. Fitted Tweeter Cone. Frequency Range 50-15,000 Hz. Rec. Retail Price **£24-75**  
FOR GENERAL PURPOSE PUBLIC ADDRESS

## 15" 'BASS 85' 85 watts R.M.S.

Linen Cone Surround. Frequency Range 40-7,000 Hz. Can be used singly but ideally TWO UNITS IN A SINGLE CABINET. Rec. Retail Price **£37-75**  
RECOMMENDED FOR ALL BASS INSTRUMENTS

## HIGH FREQUENCY HORNS

**MODEL J44**  
Range: 2.5KHz-15KHz  
Power: 50 watts with HPX2  
Power: 30 watts with HPX1  
Impedance: 8 ohms  
Size: 3-437" Sq. 3-099" Deep  
Smooth response. Extra high sensitivity

Rec.  
Ret.  
Price  
**£7-95**



**MODEL J104**  
Range: 2KHz-15KHz  
Power: 70 watts with HPX2  
Power: 50 watts with HPX1  
Impedance: 8 ohms  
Size: 10-563" x 3-5" x 7-717" Deep  
high sensitivity Level response Rec. Ret Price **£16-95**

Ultra



**MODEL 920 Mk II**  
Range: 1000Hz-18000Hz

**MODEL 910 Mk II**  
Range: 2KHz-15KHz  
Power: 50 watts with HPX1  
Imp: 8-16 ohms  
Size: 16-8cm x 9-1cm  
Depth 16-5cm  
Rec. Retail Price **£17-75**

**£59-95**

Power: 100 watts with HPX1  
Impedance: 8 ohms  
Size: 35-6cm x 22-5cm  
Depth 38-1cm  
Rec. Retail Price

**HIGH POWER 'CROSS-OVERS'**  
Employing reliable low leakage components wired on printed circuit board. Rating 200 watts Rec. Retail HPX1 'Cross-over' frequency 3-5KHz, HPX2 'Cross-over' frequency 5KHz. **£2-75**

Rec. Retail Price

## 'POP' RANGE

FAST SELLING and RELIABLE UNITS

POP 33T 12" 33w £13-95

POP 50/2 12" 50w £15-99

POP 55/2 12" 60w £22-95

POP 60 15" 60w £25-95

POP 70 15" 70w £28-95

POP 100 18" 100w £44-95

Available in impedances of either 8Ω or 15Ω

AND for those who can afford the very best there is our range of 'CRESCENDO' MODELS

Nine models for specific purposes

12" UNITS from **£56-95**

15" UNITS from **£72-95**

18" UNITS from **£89-95**



Distributors (Wholesale & Retail Trade): LINEAR PRODUCTS LTD., ELECTRON WORKS, ARMLEY, LEEDS  
Manufacturers enquiries to: FANE ACOUSTICS LTD., 286 BRADFORD ROAD, BATLEY, YORKS.

Please send S.A.E. for leaflets on any of the above ranges  
Prices correct at 16-9-76.

## H.A.C. SHORT-WAVE KITS

### WORLD-WIDE RECEPTION



Famous for over 35 years for Short-Wave Equipment of quality. "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Special offer Air8 valves—70p each.

### 1976 "DX" RECEIVER

Complete kit—Price £8-60 (incl. p. & p. & V.A.T.). Customer writes: "I think the performance is astonishing for such an inexpensive and foolproof kit. I would wholeheartedly recommend this kit to anyone, however inexperienced, as an antidote to TV-titis, and as an entry into a fascinating hobby".

This kit is ready to assemble and contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched within 7 days. Send now for free descriptive catalogue of kits and components.  
Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS  
P.O. BOX No. 16, EAST GRINSTEAD,  
SUSSEX RH19 3SN

## 'GREENWAY'

Capacitors E12 Values I.T.W. Polyesters  
10% 100V Radial\* .001; .0012; .0015; .0018; .0022mfd 3p each. .0027; .0033; .0039; .0047mfd 3p. .0056; .0068; .0082; .01mfd 3-5p each. .012; .015mfd 4p. .018; .022mfd 3-5p. .027; .033; .039mfd 4p. .047; .056; .068mfd 4-5p. .082mfd 5p. .1mfd 5-5p. .12; .15mfd 6p. .18mfd 6-5p. .22mfd 7p. .27; .33mfd 9p. .39mfd 10-5p. .47mfd 12p. Dipped Tantalum .1; .15; .22; .33; .47; .68; 1; 1-5; 2-2; 3-3 35V 10p each. 4-7; 6-8 10mfd 25V 11p. 4-7 10mfd 10V 10p. 15 22mfd 16V 15p. 33 10V 15p. 47 6V; 68 3V 15p. Electrolytic Capacitors\* Axial 1000 40V 25p. 470 16V 15p. 220 25V 12p. 4-7 63V 5p. 2-2 63V 5p. 1mfd 63V 5p. Radial 2200 40V (Tag) 50p. 1000 16V 25p. 470 25V 19p. 220 25V 12p. 100 25V 6p. 47 16V 5p. 33 16V 5p. 10 16V 4p. 5mfd 16V 3p. 4-7 16V 3p. 2-2 50V 4p. 1mfd 50V 4p. ½Watt Carbon Resistors\* 1R-10Meg 1-5p each. BARGAINS Transformer Toroidal (Plessey) £1-25 + 42p p&p. 500mA 20V Capacitors 16mfd £1-25 + 42p P&P. Edge Connectors .15 pitch 18/13/10/7 Way with Polarising Key 10p each. \*Slider Pots 47K Log Stereo 20p—single 10p. \*½ Open Fuse Holders 5p. \*Phono Panel with 4 sockets 10p.

SEND FOR FULL LIST—Industrial Distributors. Terms C.W.O. V.A.T. (\*) add 12½%, others 8%. P&p on orders under £3 (25p).

**Greenway Electronic Components**  
(East Grinstead), Ltd.

62 Maypole Rd., Ashurst Wood,  
East Grinstead, Sx. RH19-3RB.  
Tel: Forest Row 3782 (STD 034-282) 3713

## Camera Kits and Ready Built Modules



Please send 10/- 12/5p stamp addressed envelope

Whether professional student, teacher or amateur a CROFTON module is the answer



CROFTON don't just sell kits, we offer you a technical back up service to ensure your success

Apart from our popular C.C.T.V. Camera Kits we are launching a range of ready built, tested, and guaranteed electronic modules both for trade and end user. The ultimate range will be extensive. Some of the existing modules available are:—

E.T.I. Master Mixer  
E.T.I. Electronic Ignition  
Wide range R.F. Wobulator  
E.T.I. Digital Voltmeter  
E.T.I. Frequency Meter  
Video Amplifier  
Video Mixer  
Sound/Video Modulator  
Guitar Amplifier  
As well as all E.T.I. P.C.B.'s.  
V.L.F. Transmitters & Receivers  
Send S.A.E. for information.

Secondhand cameras and monitors always available

NOTE: PCBs for most published projects available to order

**CROFTON ELECTRONICS LTD**

Dept. B, 35 Grosvenor Road, Twickenham, Middx. Tele. 01-891 1923

# CALCULATOR DISPLAYS

1" digit height, bright red LED 7 segment displays for calculators, digital watches, miniature clocks, DVMs, timers etc.

- \* Fairchild FND-10, single digit common cathode £1.00 (+vat 8p) 6 for £5.00 (+vat 40p)
- \* HP 7414 4 digit, common cathode 12 pin d.i.l. pin out 99p (+vat 8p) 6 for £5.00 (+vat 40p)
- \* Bowmar 81 digit, common cathode with pc connector, and red bezel £1.85 (+vat 15p) 6 for £10 (+vat 80p)
- \* Texas 3 digit common cathode 12 pin d.i.l. pin out 85p (+vat 7p) 6 for £4.00 (+vat 32p)
- \* Texas 4+5 digit, common cathode 2x14 pin d.i.l. £1.85 pair (+vat 15p)
- \* 30 pin termination board for all types except FND-10 20p (+vat 2p)


Texas calculator keyboards, 19 gold plated "snap" type key contacts on gold plated pcb. 75p (+vat 6p) p & p on all the above 25p.



7414



BOWMAR

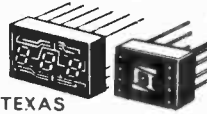

TEXAS 3 DIGIT FNDIO

## TAPE HEADS

**BX12E343 TRACK ERASE HEAD** - £1.25 (+vat 15p)  
**BX12RP63 WITH BX12E343** - £2.95 (+vat 36p)  
**STEREO CASSETTE R/RP HEAD (200 ohm)** - £2.25 (+vat 28p)  
**TWIN STAGGERED MARRIOTT HEADS R/RP** - £1.50 (+vat 18p)  
**MARRIOTT RECORD/REPLAY & ERASE HEAD** - £1.75 (+vat 21p)  
**MINIFLUX RSN ERASE** - £2.25 (+vat 28p)  
**GX11 E388 ERASE 675 ohms 2 mA** - £0.88 (+vat 11p)  
**GX12 E387 ERASE 675 ohms 2 mA** - £0.88 (+vat 11p)  
**GX20 E362 ERASE 90 ohms 90 mA** - £0.88 (+vat 11p)  
**R/RP1/3 TAPE HEAD** - £2.00 (+vat 15p)  
**TRACK** - £0.65 (+vat 8p)

## MULLARD TUNER MODULES

LP1171 combined AM/FM IF strip - £4.29 (+vat 53p) \* LP1179 FM front end with AM tuning gang, used with LP1171 - £4.29 (+vat 53p) \* LP1171 & 79 pair - £8.00 (+vat £1.00) \* LP1157 complete AM strip - £2.05 (+vat 26p) \* Ferrite Aerial - 95p (+vat 7p)  
 p & p all modules 25p each

HR-RP TAPE HEAD SINGLE TRACK £0.55 (+vat 6p)  
 XRPS17; TRACK - £3.25 (+vat 40p)  
 XRPS18; TRACK RED - £3.25 (+vat 40p)  
 XRPS36; TRACK - £6.75 (+vat 79p)  
 XES11; TRACK ERASE - £1.25 (+vat 15p)  
 BX/RP/63; TRACK - £2.25 (+vat 28p)

**BULK PURCHASE - EXCLUSIVE TO HENRY'S**  
**ALLOWS US TO SELL AT SUCH FANTASTIC PRICES!**

**QUALITY ITEMS**  
 Compare performance and specification with units costing 3 times as much!




AS USED IN BRAUN DIGITAL CLOCKS

**DIGITAL 24 HOUR CLOCK**  
 WITH BUILT-IN ALARM

- SILENT RUNNING
- LARGE ILLUMINATED NUMERALS
- AC MAINS • SIZE 6 3/8 x 2 3/8 x 2 1/2


NORMALLY £24 WITH CASE

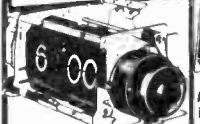

**MECHANISM ONLY**  
 £6.00 + VAT 48p P&P 25p



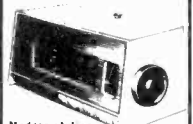**MECHANISM AND CASE** inc. assembly instructions  
 £7.99 + VAT 64p P&P 25p



**COMPLETE UNIT**  
 £8.99 + VAT 72p P&P 25p

THREE FOR £16.50 + VAT £1.32 POST FREE

THREE FOR £22.00 + VAT £1.76 POST FREE

THREE FOR £25.00 + VAT £2.00 POST FREE

## HENELEC RADIO CONTROL SYSTEM



Specially designed to provide aircraft and boat model-makers with a low-cost, easy-to-use radio control, the Henelec system gives you everything from single channel, up to sophisticated 7-channel Digital Proportional System! Buy the components you want. Ideal for any radio control application.  
 - Simple transmitter - £2.95



\* INCLUDING PROPORTIONALLY CONTROLLED SWITCH \* FEATURING COSMOS DIGITAL LOGIC to minimise power consumption and extend battery life.

(+vat 37p) - Single-ch. add-on for receiver - £11.75 (+vat £1.47p)  
 - PC board for above - 75p (+vat 6p) - Case for transmitter - £1.25 (+vat 18p) - Basic receiver - £6.95 (+vat 87p) Send now for leaflet No. 8 (35p) for full details. Post etc. 50p each

## TEXAN AMPLIFIER

featured by PRACTICAL WIRELESS  
 still the best selling amp in the UK

Build it yourself

£29.95 - VAT £3.74  
 P&P £1 Built £39.95 VAT £4.93


Build the Texan stereo amplifier, and be doubly proud! You'll own a superb home entertainment unit. And the pleasure of doing it yourself. Look at the Texan specification Fully integrated stereo preamp and power amp, 6 IC's, 10 transistors, 6 rectifiers and zener diodes. Plus stabilised, protected circuitry, glass fibre pcb, Gardners low-field low-line mains transformer; all facilities and controls. Slim design, chassis 14 1/2" x 6" x 2" overall. 20 watts per channel RMS.
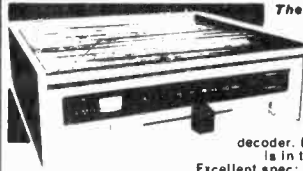
## DESIGNED BY TEXAS

30,000 ALREADY SOLD!



\* Can be built Stage by stage. Ask for leaflets 5.  
 \* Everything necessary supplied. Full after sales service and guarantees.



**TEXAN FM TUNER KIT** £20.95 + VAT £2.62  
 Built and tested £25.95 + VAT £3.24

Build the matching Texan stereo tuner! Features advanced varicap tuning. Phase lock loop decoder. Professionally designed circuit. Everything you need is in the kit. From the glass fibre pcb to the cabinet itself. Excellent spec: 2.5 uV aerial sensitivity, 500 mV output (adjustable). Tuning range 87-102 MHz. Mains powered.



£21.95 + VAT £2.74

## NEW HENELEC AM/FM TUNER MODULE

MAY BE ASSEMBLED IN AN EVENING. FEATURES \* Built-in AM Ferrite aerial \* LW coverage 150KHz-250KHz \* MW coverage 530KHz-1.6MHz \* FM coverage 87-102MHz \* 75 Ohm aerial for FM \* 150mV output \* Size 8(L) x 6(W) x 2(H)  
 Price £21.95 + VAT £2.74 p&p £1.00

This new AM/FM tuner kit incorporates 2 Mullard modules. Supplied as a pre-aligned and tested printed circuit, the constructor only has to build the PCB into the chassis, connect the power, aerial and output loads. Styled to match the Texan amp, mains operated.

Easily adapted for stereo, using the Henelec IC stereo decoder kit, high performance modular design, phase lock loop principle. Low pass filters for optimum performance. Price £8.75 + VAT £1.02 p&p 50p.

We will be pleased to quote for parts for circuits in this magazine. Send your list for quotation in S.A.E. Ask for FREE leaflets and lists on our kits projects.

# HENRY'S GREAT NEW CATALOGUE

For this latest edition, we have made hundreds of changes and additions. Containing virtually everything for amateurs and professionals, Henry's Radio Catalogue is also a "must" for manufacturers.

Again, we have included a complete alphabetical index, as well as a sectional index, so that you'll have no trouble at all in finding what you need.



IT'S THE BEST EVER!

Henry's Radio 76 ONLY 85p PLUS 14p p&p

- \* OVER 5,000 ITEMS
- \* OVER 200 PAGES
- \* DISCOUNT VOUCHERS
- \* QUANTITY DISCOUNTS ON MOST ITEMS

FREE - to educational establishments and manufacturers when ordered on official headed notepaper.

# HENRY'S RADIO

All mail to: Henry's Radio 303 Edgware Rd. London W2

LONDON W2: 404/6 Edgware Road. Tel: 01-402 8381  
 LONDON W1: 231 Tottenham Ct Rd. (lower sales floor) Tel: 01-636 6681



**SCOPES.** General purpose bench scopes 3" screen for use on 200/250v 50c/s. Vertical amp 10c/s to 100Kc or 5c/s to 300Kc at 3Db down, Sensitivity 10 Mill/V to 100v per Cm.T.B. 10c/s to 5Kc in 3 ranges. Sync int or ext with free running T.B. Controls. Focus, Brill, X & Y Shift, X amp, Y atten, Y amp, Sync Amp & polarity, T.B. coarse & fine freq, Y amp cal. Provision for direct Y plate I/P & Z mod. Contained in case 10 1/2 x 8 x 20" supplied with copy of manual & mains lead tested. Very well made unit made for A.M. ideal for Radio & Audio servicing, **£25. V.H.F. Rx A.M.** type 1392 single channel Rx crystal controlled Rx covering 100 to 150Mc/s normally used as ground station Rx, uses 13 valves as 2 RF & 3 IF stages, BFO, O/P for phones, Tuning meter etc. Contained in 19" case reqs ext 250v HT & 6-3v supplied with copy of manual & suggested mods to make Rx tunable. These Rx are in good cond having been fully reconditioned by A.M. **£18-50. SIGNAL GENERATORS.** Marconi type TF144G for use on 200/250v O/P 85Kc to 25Mc/s in 8 bands, as fine & coarse atten with O/P var luv to 1 Volt, fitted meter to read RF & Modulation levels, int mod at 400c/s. Supplied with circ & inst book & connectors, in good cond tested **£26. AIRPORT TAPE RECORDERS** 10 channel units complete with amplifier, bias osc, monitor & P.U. panels. These have two 5 track Rec & Two 5 track replay heads for use with 1/4" tape on 14" spools, tape deck & all panels contained in 19" frame rack for use on 230v 50c/s **£86.40.** We have a few tape decks only at **£35. LOW BAND R.T. UNITS** Storno for use in 70/90Mc/s range F.M. 10w O/P for use on 12v less crystals but complete with control box, mike etc. Note the accessories are complete but soiled condition, with circs & notes **£12. CRYSTALS** 2 pin 10X & 10XJ types in range 2 to 10Mc/s 20 different for **£2. TAPE DECKS & AMPS** with BSR TD2 decks two chan units with twin amps, bias erase osc, mixer O/P stage etc all transistor mounted on base 23 x 14" reqs 24vDC smoothed & 240v with circs, can be used for stereo **£10-50**, also similar unit with valves reqs ext HT & LT with circ **£7-50. CRYSTAL CALIBRATORS** type CT432 for use on 200/250v general purpose unit with O/Ps at 100kc, 1 & 10Mc/s these O/Ps are provided by 3 separate crystals, with harmonics up to 50th. Unit as mixer & O/P for phones also provision for selecting ext crystals of various types, neat unit in case 7 x 14 x 11" tested with manual **£19. HELIPOTS** 5K 10t new small type by Bournes **£1-70. HEAD & MIKE SET** for use with 19 set new boxed **£3-40. SPEAKER UNIT** small horn spk. 3 ohm for use with M/C RT size 5 x 3" with mt brk & cable new **£3-50. CRYSTAL FILTERS** 10-7Mc/s size 28 x 16 x 18mm 12Kc b.w. **£2-20**, 30Kc b.w. **£1-50**, both new. **R1155 Rx** we have a few of these in stock B L&N models tested in price range **£26 to £36** depending on condition & model, enquire.

Above prices inc carr/postage & V.A.T. Goods ex equip unless stated otherwise. SAE for 11st 16 or enquiry. Shop open Tues to Sat.

## A. H. SUPPLIES

122, HANDSWORTH ROAD, SHEFFIELD S9 4AE  
Phone 444278 (0742)

## complete DIGITAL CLOCK KITS TEAK CASES



prompt order  
despatch  
**NON-ALARM**  
**£10-65**  
+ VAT £0-85  
**ALARM**  
**£12-43**  
+ VAT £1-07  
Including P & P

### "DELTA"

GENUINE TEAK OR PERSPEX CASE

**DELTA DATA:** 4 Radiant Red 1/4 inch high LEDs. 12hr display with AM/PM indication. Beautiful Burma Teak Case or Pretty Perspex In White, Black, Blue, Red, Green. Power failure is indicated by flashing display.

**MODULES:** Kits can be bought without case: Non Alarm £9-00 Alarm £12-50 inclusive.

**READY BUILT:** Buy a working tested module and fit your own case. Non Alarm £9-50. Alarm £13-00. Or put it with our case parts @ £4-32 and save on complete clock price.

**ALARM FEATURES:** Complete Clock ready built. 2 yr guarantee. Non Alarm £13-50 Alarm £16-50. Pulsed tone. Tilt operated 10 minute 'Snooze' period. Single switch setting Optional extra mercury switch (45p) allows Alarm reset by tilting clock. Digit brightness is automatically controlled to suit lighting level.

### "ALPHA" CHRISTMAS OFFER

4 Glowing Green 1/4" high digits 12 or 24 hour. Non Alarm. **£11-00 inc.**  
Built & Tested module plus perspex case.

**NOVUS CALCULATORS:** 650: £5-40 4510: £16-20  
850: £6-75 6030: £21-60

Send payment with order. SAE for complete range of clocks, calculators and components.

## PULSE ELECTRONICS LTD

DEPT. PW4, 202 SHEFFORD ROAD,  
CLIFTON, SHEFFORD, BEDS.  
Telephone Hitchin (0462) 814477

## poly-planar

20-Watt Full Range Speaker

Completely replaces the  
conventional cone speaker  
Super-thin construction  
permits new installation ideas.



Power capability: 40 watts peak. Frequency range: 40 Hz-20 KHz  
Sensitivity: 85 dB/M for 1 watt electrical input. Input Impedance:  
8 ohms. Operating temperature range: -20°F to +175°F. Size  
(WxDxL): 1-7/16" x 11-3/4" x 14-11/16". Weight: 19 ounces.

£8-50 each Stereo pair £16-50

INCLUSIVE OF VAT AND POSTAGE

## web europa

P.O. Box 9, Ruthin Clwyd

OVER 2,000 ELECTRONIC COMPONENTS IN A

# BIG NEW FREE

## 100 PAGE CATALOGUE



**YOURS BY  
POSTING  
TODAY**

Please send me  
the 100 page  
Tandy catalogue

Name \_\_\_\_\_


Address \_\_\_\_\_

# TANDY

Nationwide supermarket of sound!

PW3  
Tandy Corporation (Branch UK), Bilston Road,  
Wednesbury, W. Midlands WS10 7JN

PHOTO COURTESY PULSE

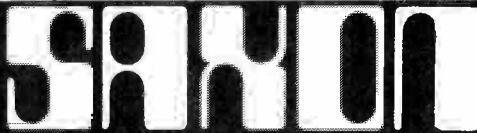

# for professional sound

## BREAK THE SOUND PRICE BARRIER!

- 100W output
- 4-channel sound/light converter, variable speed and chaser
- X-fade and P.F.L.
- Tape & mic. Inputs
- Strong wood cabinets, Vynid-covered

With sound-light converter, synchronous motor twin turntables, and features that give you professional levels of operation. Full range of heavy duty speakers.



Delivered U.K. + 8% VAT



with CENTAUR  
100W STEREO  
sound-light  
mobile disco  
**£199.00**

INCLUDES CONDENSER MIC AND HEADPHONES  
**ABSOLUTELY NO MORE TO BUY !!**

## Magnificent MINOTAUR 100 Professional 100 watt Amplifier



Compatible with all Saxon System 7000 units, this is a superb amplifier readily adaptable to a wide range of applications:

- 100W r.m.s. into 8Ω
- Two mixed inputs, wide range bass and treble controls
- May be operated as a slave amplifier
- Extremely compact (27cm x 16cm x 10cm)
- Fully protected against all in correct loads and short circuits
- Plug isolated terminals
- Silver anodised fascia

**£49.50**

## PUT SYSTEM 7000 IN CONTROL NOW!

AUTOMATIC MIC OVER-RIDE




- Ready to plug in—no soldering at all
- Stainless steel front panel
- Inputs for 2 ceramic cartridges/tape/microphone
- Individual deck controls AND left/right fader
- Low noise (−80dB) 20 Hz −50kHz ± 1dB
- 1 watt headphone monitor
- CONTROLS—Master, Monitor, Volume, Selector X-fade, etc.

READY BUILT  
MONO £37.50  
STEREO £53.50

MODULAR PCB with all electronics  
Mono £18.50  
Stereo £27.50  
Front panel £3.50
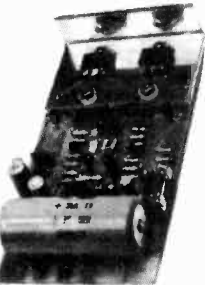
## HIGH IN POWER—LOW IN COST! (120 watts from £14.50) POWER AMPS 30-120 W.R.M.S.



- Only 4 connections
- Distortion typically 0.4%
- Single supply rail
- Input—240mV
- Size—6" x 3" x 1"
- Individually tested & grntd.

SA1208 120 watt R.M.S./8 ohms	£21.00
PM1201/8 supply for one module	£11.60
PM1202/8 supply for two modules	£15.30
*SA1204 120 watt R.M.S./4 ohms	£19.50
PM1201/4 supply for one module	£11.60
PM1202/4 supply for two modules	£15.30
SA608 60 watt R.M.S./8 ohms	£12.50
PM601/8 supply for one or two modules	£11.60
*SA604 60 watt R.M.S./4 ohms	£10.50
PM601/4 supply for one or two modules	£11.60
SA308 30 watt R.M.S./8 ohms	£9.50
PM301 supply for one or two modules	£9.90

## STROBE AND LIQUID WHEELS



SUPERSTROBE AT NEW LOW PRICE

- 1 flash/2 secs.—up to 20/sec.
- Compact black Bondene case
- Ideal for mobile disco or smaller club

NOW ONLY £19.75

PRO-STROBE

- Giant 80 watt tube
- Discharge energy up to 6 Joules
- External trigger—audio up to 240w

NOW ONLY £31.50

## NEW! NEW! NEW! SYSTEM 7000 LIGHTING CONTROL MKII

Successor to the LIGHTING CONTROL UNIT this new SYSTEM 7000 controller offers increased facilities and effects. Note these features:

- FOUR channels—up to 1000 watts each
- Twin sequencer—1 flash/2secs—20 flashes/sec
- Independent Dimmers on each channel
- IC LOGIC circuitry PLUS RCA 8 A Trics
- Stainless Steel steel panel to match other System 7000 units.

NOTE: Sound/Lite plus Sequencer plus Dimmers all in the same unit £42.50



QUADRAEFFECT MODULE—same features as above but pcb only. Ready to connect and use £29

SYSTEM 7000 SOUNDLITE THE tried and tested soundlite now in module form and complete on front panel. THREE CHANNELS—THREE KW—INDIVIDUAL CONTROLS PLUS MASTER. COMPLETE ON PANEL MODULE ONLY £24.75 £16.50

## Mix it perfectly with modular SYSTEM 7000 MIXERS

- Automatic mic over-ride
- Inputs for all sources inc. mag. cartridge
  - Wide range bass and treble controls
  - 1W monitor power outlet
  - Echo send/return facility
  - Feeds most amplifiers
  - With front panels, ready to use
  - Individual monitor buttons




INPUT Mono	£8.50	MIXER Mono	£8.50
Stereo	£12.00	Stereo	£12.00
PCB Modules only Mono	£5.50	PCB Modules only Mono	£5.50
Stereo	£9.00	Stereo	£9.00

NOW ALSO AT WALLINGFORD (Between Reading and Oxford) with sales 7 service 6 days a week

FLINT HOUSE HIGH ST WALLINGFORD OXON OX10 0DE Phone (0491) 35529

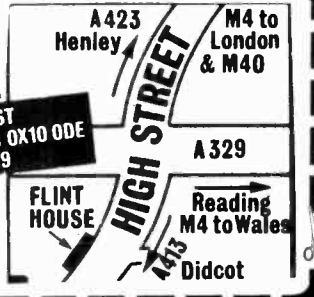Saxon equipment is designed and made in our own Croydon factory



PRICES include carriage and packing. VAT must be added to all orders at 8%. C.O.D. 65p extra. S.A.E. with all enquiries please.

Send or phone your ACCESS or BARCLAY CARD No. for prompt attention. After 4.0 p.m. leave your message on our answerphone 01-684 6385.

Orders by post—Please make cheques or crossed P.O.'s payable to  
**SAXON ENTERTAINMENTS LTD.**  
327-333 WHITEHORSE ROAD, CROYDON, SURREY CR0 2HS  
Telephone: 01-684 0098/6385  
Shop Hours 9 am-5 pm (Lunch 12.30-1.30); Sat. 9.30 am-5 pm  
Subject to alteration without notice

TRADE ENQUIRIES NORMAN ROSE (ELECTRICAL) LTD. London 01-837 9111 Birmingham 021-236 4710 Manchester 061-273 1498 Bradford, Yorks. 0274 26104  
VAT NO. 218 6921 49

Get a great deal from

# Marshall's

A. Marshall (London) Ltd Dept: PW

40/42 Cricklewood Broadway London NW2 3ET Tel: 01-452 0161/2 Telex: 21492

& 85 West Regent St Glasgow G2 2QD Tel: 041-332 4133

& 1 Straits Parade Fishponds Bristol BS16 2LX Tel: 0272-654201/2

& 27 Rue Danton Issy Les Moulineaux Paris 92

Catalogue price 40p post paid

(30p to callers)

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat

Our range covers over 7,000 items. The largest selection in Britain

## Top 200 IC's TTL, CMOS & Linears

CA3020A	£1.45	CD4049	56p	NE555V	48p	SN7446	86p	SN74153	73p
CA3028A	£1.85	CD4050	56p	NE556	£1.30	SN7447	81p	SN74154	£1.29
CA3035	£1.35	CD4510	£1.54	NE560	£4.48	SN7448	85p	SN74160	£1.20
CA3046	73p	CD4511	70p	NE555	£1.30	SN7450	16p	SN74161	£1.20
CA3048	£2.15	CD4516	£1.54	SL14E	£3.35	SN7451	16p	SN74162	£1.20
CA3052	£1.62	CD4518	£1.38	SL610C	£2.35	SN7453	16p	SN74163	£1.20
CA3089E	£2.00	CD4520	£1.38	SL11C	£2.35	SN7454	16p	SN74164	93p
CA3090Q	£4.25	LM301AH	47p	SL612C	£2.35	SN7460	16p	SN74165	93p
CA3130	88p	LM308N	£1.17	SL620C	£3.50	SN7470	32p	SN74167	£3.70
CD4000	20p	LM309K	£1.80	SL621C	£3.50	SN7472	26p	SN74174	£1.06
CD4001	20p	LM380	98p	SL623C	£3.75	SN7473	30p	SN74175	94p
CD4002	20p	LM381AN	£2.07	SL640C	£4.00	SN7474	30p	SN74176	86p
CD4006	£1.16	LM702C	75p	SN7400	16p	SN7475	40p	SN74180	£1.23
CD4007	20p	LM709	SN7401	16p	SN7476	36p	SN74181	£1.58	
CD4008	97p	TO99	40p	SN7402	16p	SN7480	45p	SN74190	£1.23
CD4009	57p	8D1L	40p	SN7403	16p	SN7481	£1.10	SN74191	£1.33
CD4010	57p	14D1L	40p	SN7404	18p	SN7482	67p	SN74192	£1.33
CD4011	20p	LM710	45p	SN7405	18p	SN7483	92p	SN74193	£1.13
CD4012	20p	LM723C	60p	SN7406	51p	SN7484	85p	SN74196	£1.81
CD4013	59p	LM741C	60p	SN7407	18p	SN7485	£1.25	SN74197	£1.81
CD4014	£1.01	TO99	38p	SN7408	18p	SN7486	29p	SN74198	£2.04
CD4015	£1.01	8D1L	38p	SN7409	18p	SN7490	43p	SN74199	£2.04
CD4016	56p	14D1L	40p	SN7410	16p	SN7491	68p	SN76003N2	36
CD4017	£1.01	LM747	78p	SN7411	20p	SN7492	43p	SN76013N1	50
CD4018	£1.01	LM748	SN7412	25p	SN7493	43p	SN76023N1	50	
CD4019	57p	8D1L	44p	SN7413	40p	SN7494	74p	SN76033N2	50
CD4020	£1.12	14D1L	41p	SN7416	43p	SN7495	59p	TAA263	£1.25
CD4021	£1.01	LM3900N	55p	SN7417	43p	SN7496	78p	TAA300	£2.67
CD4022	97p	LM7805P	£1.39	SN7420	16p	SN74100	£1.15	TAA350A	£2.48
CD4023	20p	LM7812P	£1.39	SN7423	26p	SN74107	30p	TAA550	40p
CD4024	79p	LM7815P	£1.39	SN7425	27p	SN74118	90p	TAA611C	£2.25
CD4025	20p	LM7824P	£1.39	SN7427	27p	SN74119	£1.80	TAA621	£2.15
CD4027	56p	MC1303L	£1.44	SN7430	16p	SN74121	34p	TAA661B	£1.32
CD4028	91p	MC1310P	£1.91	SN7432	27p	SN74122	45p	TAA641B	£2.50
CD4029	£1.17	MC1330P	£1.35	SN7437	35p	SN74123	40p	TBA651	£1.80
CD4030	57p	MC1351P	£1.87	SN7438	35p	SN74141	72p	TBA800	89p
CD4031	£2.26	MC14553	£4.07	SN7440	16p	SN74145	74p	TBA810	98p
CD4037	97p	MC1466L	£3.95	SN7441	76p	SN74150	£1.20	TBA820	85p
CD4041	83p	MC1469R	£2.50	SN7442	55p	SN74151	77p	TBA920	£1.79

## POPULAR SEMICONDUCTORS

2N696	25p	2N3906	22p	AF139	69p	BD139	42p	MPSA56	20p
2N697	16p	2N4058	20p	AF239	74p	BF115	36p	OC28	£2.00
2N699	55p	2N4062	18p	AF279	80p	BF117	70p	OC42	50p
2N706	12p	2N4921	60p	AF280	85p	BF154	25p	TIP29A	50p
2N708	21p	2N4923	70p	AL102	£1.50	BF180	36p	TIP31A	62p
2N916	43p	2N5245	29p	BC107	14p	BF181	36p	TIP32A	75p
2N918	34p	2N5294	35p	BC109	15p	BF184	35p	TIP34A	£1.20
2N1302	37p	2N5296	36p	BC147	10p	BF194	12p	TIP35A	£2.50
2N1306	45p	2N5458	26p	BC149	13p	BF196	13p	TIP36A	£3.55
2N1308	60p	2N5459	29p	BC157	12p	BF197	14p	TIP41A	70p
2N1711	27p	2N6027	45p	BC158	11p	BF198	15p	TIP42A	70p
2N2102	60p	3N128	80p	BC167	12p	BF244	35p	TIP2955E1	00
2N2148	£1.65	3N140	£1.00	BC168	12p	BF258	49p	TIP3055	50p
2N2218A	47p	3N141	85p	BC169	12p	BF259	49p	TIS43	30p
2N2219A	52p	3N200	£2.60	BC182	11p	BF598	27p	ZTX300	15p
2N2220	35p	40361	45p	BC182L	14p	BF839	24p	ZTX301	15p
2N2221	22p	40362	48p	BC183	11p	BF879	24p	ZTX501	15p
2N2222	25p	40406	48p	BC183L	14p	BF829	36p	ZTX502	18p
40407	30p	BC184	12p	BF884	38p	IN914916	7p		
40408	50p	BC184L	14p	BF885	41p	IN4007	18p		
40409	55p	BC212L	14p	BF888	32p	IN4148	7p		
40410	55p	BC212L	14p	BF950	30p	IN5404	18p		
40411	£2.30	BC213L	16p	BF951	38p	IN5408	40p		
2N2926G	13p	40594	75p	BC214L	19p	BFY52	36p	AA119	14p
2N3053	25p	40595	88p	BC237	14p	BF939	50p	BA102	15p
2N3054	50p	40636	£1.15	BC239	16p	ME0412	20p	BA145	19p
2N3055	65p	40673	73p	BC257	17p	ME4102	10p	BA155	12p
2N3391	29p	AC126	37p	BC259	18p	MJ480	£1.05	BB103B	20p
2N3393	15p	AC127	44p	BC301	45p	MJ481	£1.30	BB104B	34p
2N3440	57p	AC128	37p	BC307	20p	MJ490	£1.05	BY126	27p
2N3442	£1.20	AC132	50p	BC309	25p	MJ491	£1.55	BY211	70p
2N3638	16p	AC133	40p	BC327	20p	MJ2955	£1.21	BYZ12	70p
2N3702	17p	AC176	40p	BC328	19p	MJ370	68p	OA47	10p
2N3703	15p	AC187K	40p	BCY70	25p	ME371	81p	OA90	6p
2N3706	14p	AC188K	45p	BCY72	24p	ME520	65p	OA91	6p
2N3708	14p	AD161	75p	BD121	£2.00	ME521	75p	OA200	8p
2N3716	£2.60	AD162	75p	BD124	£2.00	ME2955E1	25p	BY164	57p
2N3771	£1.60	AF106	45p	BD131	51p	ME3055	75p	ST2disc	20p
2N3773	£2.65	AF109	45p	BD132	54p	MPB113	45p	40669	£1.00
2N3789	£2.60	AF115	65p	BD136	36p	MPSA05	20p	TIC47	38p
2N3819	26p	AF116	65p	BD137	36p	MPSA06	20p	CI06D	65p
2N3904	21p	AF118	65p	BD138	39p	MPSA55	20p	ORP12	70p

**VIDEO-WRITER PROJECT IN THIS ISSUE—WE CAN SUPPLY MOST COMPONENTS AT DISCOUNTED KIT PRICES**

Call in or send S.A.E. for details

Prices correct at 1st. Sept., 1976, but all exclusive of VAT. P. & P. 30p

## Dolby™ Noise Reducer Kit



PRICE: £37.90 + VAT

'Wireless World'  
May, June, July '75

Trademark of Dolby Laboratories Inc.

The latest addition to our exclusive range of matching high fidelity units.

The Dolby Noise Reduction System is designed to reduce background noise on open reel or cassette tape recorders. Used in the signal path to and from the tape recorder, the unit will encode (Dolbyise) signals during recording, and, during playback, may be used to decode either your own encoded material, or commercially available Dolby encoded cassettes.

Featuring:

- switching for both encoding (low-level h.f. compression) and decoding
- a switchable f.m. stereo multiplex and bias filter
- provision for decoding Dolby f.m. radio transmissions (as in USA)
- no equipment needed for alignment
- suitability for both open-reel and cassette tape machines
- check tape switch for encoded monitoring in three-head machines

The kit includes:

- complete set of components for stereo processor
- regulated power supply components
- board-mounted DIN sockets and push-button switches
- fibreglass board designed for minimum wiring
- solid mahogany cabinet, chassis, twin meters, front panel, knobs, mounting screws and nuts

Calibration tapes are available for open-reel use and for cassette (specify which) PRICE £2.00 + VAT\*

## S-2020TA STEREO TUNER/AMPLIFIER KIT

PRICE: £53.95 + VAT

SOLID MAHOGANY CABINET

A high-quality push-button FM Varicap Stereo Tuner with Interstation mute combined with a 20W r.f.m.s. per channel Stereo Amplifier.



THD < 0.1% @ 20W  
Tuner S/N 30dB @ 1.2µV (mono)  
Toroidal Transformer


Please add VAT at 12½% unless marked thus \* when 8% applies  
We guarantee full after sales technical and servicing facilities on all our kits

Please send SAE for complete lists and specifications  
Portwood Industrial Estate, Church Gresley,  
Burton-on-Trent, Staffs DE11 9PT  
Tel. Burton-on-Trent (0283) 215432. Telex 377106

Access  
Barclaycard

## INTEGREX LTD.



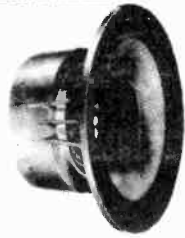

# WILMSLOW AUDIO

## THE Firm for speakers!

### SPEAKERS

Baker Group 25, 3, 8 or 15 ohms	£9.00
Baker Group 35, 3, 8 or 15 ohms	£10.75
Baker Group 50/12 8 or 15 ohms	£14.00
Baker Group 50/15 8 or 15 ohms	£18.82
Baker Deluxe 12" 8 or 15 ohms	£12.38
Baker Regent 12" 8 or 15 ohms	£12.65
Baker Major 3, 8 or 15 ohms	£16.31
Baker Superb 8 or 15 ohms	£9.00
Baker Auditorium 12" 8 or 15 ohms	£14.65
Baker Auditorium 15" 8 or 15 ohms	£19.41
Celestion G12M 8 or 15 ohms	£13.50
Celestion G12M 8 or 15 ohms	£16.75
Celestion G12/50 8 or 15 ohms	£19.50
Celestion G15C 8 or 15 ohms	£18.00
Celestion G18C 8 or 15 ohms	£26.95
Celestion G18C 8 or 15 ohms	£34.50
Celestion HF1300 8 or 15 ohms	£6.98
Celestion HF2000 8 ohms	£8.55
Celestion MH1000 8 or 15 ohms	£13.50
Decca London ribbon horn	£4.46
Decca London CO/1000/8 Xover	£29.95
Decca DK30 ribbon horn	£6.95
Decca CO/1/8 Xover (DK30)	£19.95
EMI 14 x 9 Bass 8 ohms 14A770	£4.75
EMI 8 x 5, 10 watt, d/cone, roll surr.	£11.92
EMI 8" d/cone, roll surr. 8 ohms	£3.56
EMI 8" roll surr. bass	£3.93
EMI 5" mid range	£5.73
Elac 59RM109 (15) 59RM114 (8)	£3.15
Elac 61" d/cone, roll surr. 8 ohms	£3.38
Elac 10" 10RM239 8 ohms	£3.83
Eagle Crossover 3000hz 3, 8 or 15 ohm	£1.57
Eagle FR4	£5.51
Eagle FR65	£8.95
Eagle FR8	£11.95
Eagle FR10	£14.00
Eagle HT15	£3.96
Eagle HT21	£4.95
Eagle MHT10	£4.00
Eagle FF28 multicell. horn	£6.50
Fane Pop 15, 8 or 16 ohm	£5.50
Fane Pop 33T, 8 or 16 ohm	£9.75
Fane Pop 50, 8 or 16 ohm	£12.50
Fane Pop 35, 8 or 16 ohm	£15.50
Fane Pop 60, 8 or 16 ohm	£17.95
Fane Pop 70, 8 or 16 ohm	£18.75
Fane Pop 100, 8 or 16 ohm	£27.95
Fane Crescendo 12A, 8 or 16 ohms	£37.95
Fane Crescendo 12BL, 8 or 16 ohms	£39.95
Fane Crescendo 15/100A, 8 or 16 ohms	£49.95
Fane Crescendo 15/125, 8 or 16 ohms	£59.95
Fane Crescendo 18, 8 or 16 ohms	£67.95
Fane 910 Mk II horn	£15.75
Fane 920 Mk I horn	£39.95
Fane HPX1 crossover 200 watt	£2.80
Fane 13 x 8, 15 watt dual cone	£3.50
Fane 801T 8" d/c, roll surr.	£8.96
Goodmans Axent 100	£7.00
Goodmans Audiom 200 8 ohm	£13.48
Goodmans Axlom 402 8 or 15 ohm	£18.80
Goodmans Twinaxiom 8, 8 or 15 ohm	£5.50
Goodmans Twinaxiom 10, 8 or 15 ohm	£9.88
Goodmans 8P 8 or 15 ohm	£6.20
Goodmans 10P 8 or 15 ohm	£6.50
Goodmans 12P 8 or 15 ohm	£14.95
Goodmans 12PG 8 or 15 ohm	£16.95
Goodmans 12PD 8 or 15 ohm	£18.95
Goodmans 12AX 8 or 15 ohm	£39.00
Goodmans 15AX 8 or 15 ohm	£45.00

### SPEAKERS

Goodmans 15P 8 or 15 ohm	£22.50
Goodmans 18P 8 or 15 ohm	£39.00
Goodmans Hifax 750P	£16.00
Goodmans 5" midrange 8 ohm	£4.05
Gauss 12"	£95.00
Gauss 15"	£110.00
Gauss 18"	£121.00
Jordan Watts Module 4, 8 or 15 ohm	£15.36
Kef T27	£5.18
Kef T15	£6.25
Kef B110	£6.75
Kef B200	£7.85
Kef B139	£15.08
Kef DN8	£2.08
Kef DN12	£5.39
Kef DN13 SP1015 or SP1017	£4.05
Lowther PM6	£30.50
Lowther PM6 Mk 1	£32.95
Peerless KO10DT 4 or 8 ohms	£48.60
Peerless DT10HFC 8 ohms	£7.25
Peerless KO40MRF 8 ohms	£8.26
Peerless MT225HFC 8 ohms	£9.28
Richard Allan CA12 12" bass	£2.95
Richard Allan HP8B	£11.80
Richard Allan LP8B	£8.33
Richard Allan DT20	£6.08
Richard Allan CN820	£16.20
Richard Allan CN820	£3.15
Richard Allan Super disco 60W 12"	£16.95
Richard Allen CG15 15" bass	£27.45
Richard Allen Super Disco 10" 50 watt	£13.25
Richard Allen Super Disco 8" 50 watt	£12.95
Radford MD9	£10.50
Radford MD6 dome mid range	£12.50
Radford TD 3	£7.25
Radford Crossover network	£13.00
BD25 Mk II	£22.00
STC 4001 G	£5.90
STC 4001 K	£5.90
Tannoy 10" HPD	£78.00
Tannoy 12" HPD	£86.00
Tannoy 15" HPD	£99.95
Wharfedale Super 10 RS/DD 8 ohms	£13.50
Castle 8 RS/DD	£9.28

### SPEAKER KITS

Richard Allan Twin assembly	each	£13.46
Richard Allan Triple 8	each	£20.25
Richard Allan Triple 12	each	£25.16
Richard Allan Super Triple	each	£28.25
Richard Allan RA8 Kit	pair	£37.80
Richard Allan RA82 Kit	pair	£59.40
Richard Allan RA82L Kit	pair	£65.70
Fane Mode One Mk2	each	£10.35
Wharfedale Linton II kit	pair	£21.50
Wharfedale Glendale 3XP kit	pair	£47.70
Wharfedale Dovedale III kit	pair	£59.40
Wharfedale Denton 2XP Kit	pair	£23.25

### HI-FI

## ON DEMONSTRATION in our showrooms

Akai, Armstrong, Bowers and Wilkins, Castle, Celestion, Dual, Goodmans, Kef, Leak, Pioneer, Radford, Richard Allan, Rotel, Tandberg, Trio, Videotone, Wharfedale, etc. Ask for our Hi-Fi Discount Price List.

**THIS MONTH'S SPECIALS!** Carr. £2.00. Pioneer SX737 £179.00. Rotel RD20 £135.00. Rotel RA312 £56.00. Videotone Saphir 1 pr £52.00. Videotone Minimax 2 pr £43.00.

We stock the complete Radford range of amplifiers, preamplifiers, power amplifiers, tuners, etc., and also Radford Audio Laboratory equipment, low distortion oscillator, distortion measuring set, audio noise meter, etc.

All Prices include VAT (Prices correct at 2.9.76)

Send stamp for Free 32 page booklet 'Choosing a Speaker'.

All units guaranteed New and Perfect. Carriage and Insurance: Speakers 55p each, 12" and up 85p each. Kits £1.00 each (£2.00 per pair). Tweeters and crossovers 33p each.

### SPEAKER KITS

Baker Major Module 3, 8 or 15 ohms	each	£13.28
Goodmans DIN 20 4 or 8 ohms	each	£13.28
Goodmans Mezzo Twin Kit	pair	£48.50
Halme XLK 20	pair	£17.80
Halme XLK 30	pair	£21.95
Halme XLK 35	pair	£28.75
Halme XLK 40	pair	£38.50
KEF kit 1	pair	£51.00
KEF kit III	each	£48.00
Peerless 1060	pair	£54.00
Peerless 1070	each	£46.50
Peerless 1120	each	£54.00
Peerless 2050	pair	£39.50
Peerless 2060	pair	£53.00

Complete kits in stock for Radford Studio 90, Radford Monitor 180, Radford Studio 270, Radford Studio 360, HiFi Answers Monitor (Rogers), HiFi News No Compromise (Frisby), HiFi News State of the Art, Wireless World Transmission Line (Bailey), Practical HiFi and Audio Monitor (Giles), Practical HiFi and Audio Triangle (Giles), Popular HiFi (Colloms), etc.

Construction leaflets for Radford, Kef, Jordan Watts, Tannoy, Hi-Fi On dem. Answers Monitor, State of Art, Free on Request.

P.A. Amplifiers, microphones etc. by Shure, Linear, Eagle, Beyer, AKG etc.

FREE with orders over £10—"HiFi Loudspeaker Enclosures" Book

# WILMSLOW AUDIO

Dept. PW

Loudspeakers, Mail Order and Export: Swan Works, Bank Square, Wilmslow.


Hi-Fi, Radio & TV: Swift of Wilmslow 5 Swan Street, Wilmslow, Cheshire.

PA, Hi-Fi & Accessories: Wilmslow Audio, 10 Swan Street, Wilmslow, Cheshire.

Telephone:

Loudspeakers, Mail Order and Export Wilmslow 29599

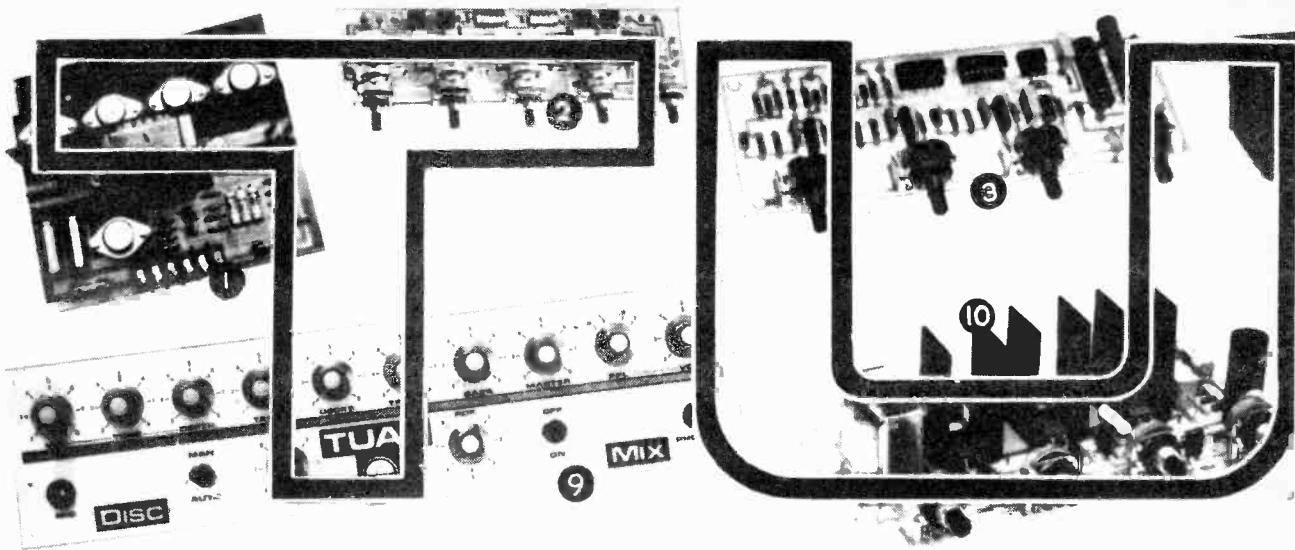Hi-Fi, Radio, etc., Wilmslow 26213 (Access and Barclay Card orders accepted by phone).



TRANSISTOR UNIVERSAL AMPLIFICATION Co. Ltd.

PHONE 01-672 3137 / 672 9080

## 9 MONO DISCO MIXER WITH AUTO FADE

Designed for the discerning D. J. of professional standard. Offering a vast variety of functions. Controls; Mic Vol; Tone, over-ride depth, auto/manual sw; Tape Vol; L & R Deck Faders; Deck Volume; Treble and Bass; H. Phon Vol Selector; Master Vol On/Off sw. Max output 3V RMS.

Specification: Deck inputs—50mV into 1M $\Omega$ ; Deck Tone Controls—treble total range 36dB at 15kHz—Bass total range 36dB at 50Hz. Mic input—200 ohms upwards 2mV into 22k. Mic Tone Control—Total range 40dB at 15kHz. Tape input—100mV into 200 ohms. Power requirements 20-50 volts d.c. at 50mA. R.I.A.A. comp mag inputs available 75p extra.

PANEL SIZE 18 x 4½ in. DEPTH 3in.

**£39-75**

## 4 TUAC AMPLIFICATION

Loline 125 watt with sustain .....	£81
Loline 60-watt with sustain .....	£65
Combo twin 60 reverb .....	£140
Combo 30 .....	£75
4 x 12 200-watt cabs .....	£135
2 x 12 100-watt cabs .....	£80
Mini/PA Bin .....	£125
Disco Reflex Cab .....	£95

### STOCKISTS—CALLERS ONLY

Geo Mathews, 85 87 Hurst Street, Birmingham (Tel. 021-622 1941).  
 Arthur Sallis Ltd., 28 Gardner Street (Tel. Brighton 658066).  
 Bristol Disco Centre, 26 The Promenade, Gloucester Road (Tel. Bristol 41666).  
 SocoDi, 9 The Friars (Tel. Canterbury 60948).  
 Cookies Disco Centre, 132 West Street (Tel. Crewe 4739).  
 H. B. Electronics, 54 Montagu Street (Tel. Kettering 83922).  
 Leighton Electronics Centre, 59 North Street (Tel. Leighton Buzzard 2316).  
 Garland Bros. Ltd., Depford Broadway London 01-682 4412  
 At Music Centre, 88 Oxford Street, Manchester (Tel. 061-236 0240).  
 Damon Electronics, 99 Carrington Street (Tel. Nottingham 53880).  
 Electra Centre, 58 Lancaster Road (Tel. Preston 58488).  
 Luton Disco Centre, 88 Wellington Street, Luton (Tel. Luton 411733).  
 Mitchell Electronics, 7 Queen Street (Tel. Salisbury 23689).  
 TUAC Sound Centre 163 Mitcham Road Tooting (Tel. 01-672 3413)  
 Mon—Sat, 9.30 a.m.—5.30 p.m.  
 Half Day Wed. 9.30 a.m.—1 p.m.

SOLE  
 AGENCY'S  
 NOW  
 AVAIL-  
 ABLE  
 IN  
 LEEDS  
 NORWICH  
 and  
 SWANSEA  
 Reader  
 intros  
 appreciated

## PRE AMPLIFIERS

### VA08

Designed for use with TUAC power amplifier modules. Extensive research has gone into various wide range tone control circuits produces superb sound quality. Thousands are already in use in high quality professional amplification systems.

VA08 Vol. Treb. Mid and Bass controls. HI. IMP. FET. I/P suitable Mid. Guitar, Radio, Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz Mid +20 -15dB at 1kHz Bass +20 -10dB at 40Hz. **£8-50**

VA06 Vol. Treb. and Bass controls. Sensitivity 8mV. Treb. +28 -15dB at 12kHz. Bass  $\pm$  18dB and 40Hz. **£7-50**

2 SVA08 STEREO PRE AMP Vol. Treb. Mid and Bass controls. I/P suitable, Guitar, Radio, Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +20 -15dB at 4kHz. Bass +20-10dB at 40Hz. Plus Full Balance Control. Fully I/C operation supply voltage  $\pm$ 15VDC **£15-00**

## AMPLIFIER MODULES

### 7 TL30 D.C. COUPLED POWER AMPLIFIER MODULE

- Output power 30 watt R.M.S. continuous sine wave into 8 Ohms
- T.H.D. at full power 0.5%
- Signal to noise ratio—85dB
- Input sensitivity 60mV into 50k ohms
- Frequency response 25Hz-50kHz
- 8 transistors 4 diodes

**£12-50**

### 11 TL60 5 x 5 x 3in

- 60 watt R.M.S. continuous sine wave output
- 2 R.C.A. 110 watt 15 amp transistors

**£16-75**

### 11 TL100 5 x 5 x 3in

- 100 watt R.M.S. continuous sine wave output
- 2 R.C.A. 150 watt 15 amp transistors

**£18-75**

### 1 TP125 7 x 6½ x 3in

- 125 watt R.M.S. continuous sine wave output
- 4 R.C.A. 150 watt 15 amp output transistors


**£23-25**

Specification on power modules: ● Rugged layer wound driver transformer ● Short—Open—and Thermal overload protection ● Only 6 connections. All output power ratings  $\pm$  0.5dB. Output impedance 8-15 ohms; THD at full power 2% typically 1%; Input sensitivity 60mV into 10k  $\Omega$ ; Frequency response 20Hz-20kHz  $\pm$  2dB. Hum and noise better than -70dB.

ALL PRICES INCLUDE V.A.T. POSTAGE AND PACKING FREE

TECHNICAL INFORMATION: TEL 01-672 3137

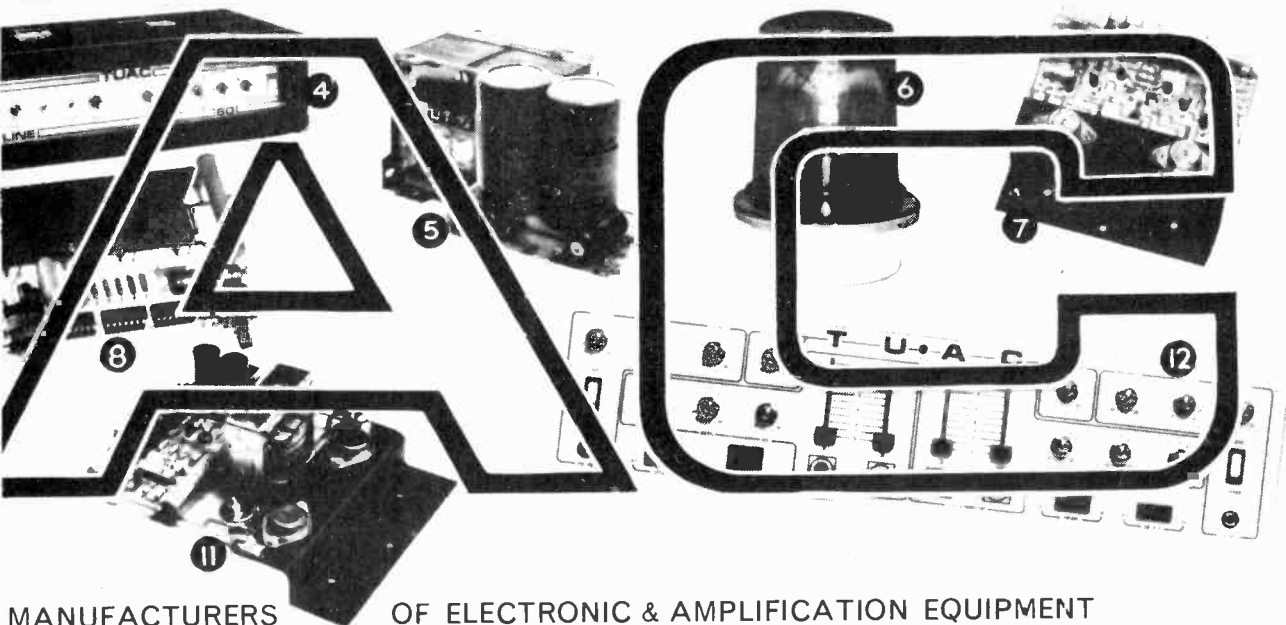TRADE AND EXPORT ENQUIRIES. TEL: 01-672 9080



MANUFACTURERS OF ELECTRONIC & AMPLIFICATION EQUIPMENT

## 9 POWER SUPPLIES

Vacuum varnish impregnated. Transformers with supply board incorporating pre-amp supply:

<b>PS250</b> for supplying 2 TP125s	<b>£28-00</b>
<b>PS 60/60</b> for supplying 2 TL60s	<b>£25-50</b>
<b>PS 125</b> ± 45 volts for TP125	<b>£16-75</b>
<b>PS100</b> ± 43 volts for TL100	<b>£15-50</b>
<b>PS 60</b> ± 38 volts for TL60	<b>£14-50</b>
<b>PS 30</b> ± 25 volts for TL30	<b>£9-75</b>
<b>PSU 2</b> for supplying disco mixer	<b>£6-50</b>

## 4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER—4LSMI 10

- RCA 8A Triacs
  - 1000W per channel
  - Fully suppressed and fused
  - Switched master control for sound operation from 1/2W to 125W
  - Speed control for fixed rate sequence from 8 per minute to 50 per second
  - Full logic integrated circuitry with optical isolation for amplifier protection
  - Full wave control
  - 13 easy connections
- Patents applied for **£18-75**
- Model 501500W per channel as above without sound triggering **£12-25**

## 10 3 CHANNEL LIGHT MODULATOR

- RCA 8A Triacs
  - 1000W per channel
  - Each channel fully suppressed and fused
  - Master control to operate from 1W to 100W
  - Full wave control
  - 12 easy connections
- £18-00**
- (Single Channel Version 1500 Watts **£9-50**)

## 3 ADD SEQUENCE CHASING AND DIMMING EFFECTS TO YOUR TUAC 3 CHANNEL LIGHT MODULATOR

- Speed Control 3 per min. to 10 per sec.
  - Full logic integrated circuitry
  - Dimmer control to each channel
  - 9 easy connections
- SEQUENCE DIMMER MODULE—3SDM1 £13-00**

**Factory reorganisation now completed. Assembly line capacity available for long and short runs to clients specification with Quality control.**

## 12 STEREO DISCO MIXER

With touch sensitive switching and auto fade

**INPUTS:** Four identical stereo inputs available with any equalisation. Two magnetic and two flat supplied as standard. High quality slider control on each channel. Volume, treble, and bass controls for each pair of sliders. Sensitivity mag., 3mV (R.I.A. comp.). Flat 50mV at 1kHz. Bass controls ±18dB at 60Hz. Treble controls ±18dB at 15kHz.

**OUTPUT:** Up to 3 volts (+12dB) available. Attenuated output for TUAC Power Modules. Rotary master and balance controls. Band width 15Hz-25kHz ±1dB. P.F.L.: Output 250mV into 8 ohms. Rotary volume control. Monitoring facility for all 4 channels. Selection via touch sensitive illuminated switches. Switched visual cue indicator.

**Miscellaneous Facilities:** Two illuminated deck on/off switches. Mains illuminated on/off switches. Auto fade illuminated on/off switch. Mains powered with integral screen and back cover. Complete with full instructions.

Size: 25in long x 6in high x 3in deep

**£115**

## FRONT PANELS FOR LIGHTING EFFECT MODULES

(complete with switches, neons and knobs) as illustrated



Size: 8" x 4 1/2"



Size: 6 1/2" x 4 1/2"



Size 9" x 4 1/2"

◀ For S1LMB  
**£6-50**

▲ For 4SLM1  
**£5-50**

◀ For S1LMB combined with 3SDM1  
**£7-50**

## 6 FUZZ LIGHTS

**RED GREEN BLUE AMBER**

240 volt a.c. Long Life Candle Bulb, Revolving Reflector, adds a new dimension to disco lighting effects.

**£19-50**

Suppliers to H. M. Govt. Depts. Manufactured and assembled in Gt. Britain fully tested and guaranteed

### TO ORDER BY POST

Make cheques/P.O.s payable to **TUAC LTD. PW/11** or quote Access Barclay Card No. and post to **TUAC LTD. (PW11)119** Chalfont Road, London, **SW17 9AB**. We accept phone orders from Access Barclay Card Holders. Phone 01-672 3137, 9080.

Send large stamped addressed envelope with all enquiries for fully illustrated 12 page catalogue

# CRESCENT RADIO LTD.

164-166 HIGH ROAD, LONDON N22 6EJ  
(also) 13 SOUTH MALL, EDMONTON, N.9  
MAIL ORDER DEPT.  
1 ST. MICHAELS TERRACE, WOOD GREEN,  
LONDON N22 4SJ Phone 888-4474

## CLEAR PLASTIC PANEL METERS

Size 59mm x 46mm x 36mm these meters require a 38mm hole for mounting.  
ME8 = 0 to 50 micro amp Full Scale  
ME7 = 0 to 100 micro amp Full Scale  
ME8 = 0 to 500 micro amp Full Scale  
ME9 = 0 to 1 m/a Full Scale  
ME10 = 0 to 5 m/a Full Scale  
ME11 = 0 to 15 m/a Full Scale  
ME12 = 0 to 50 m/a Full Scale  
ME13 = 0 to 100 m/a Full Scale  
ME14 = 0 to 500 m/a Full Scale  
ME15 = 0 to 1 amp Full Scale  
ME16 = 0 to 50 volts  
ME17 = 0 to 300 volts  
A.C. Full Scale  
ME18 = "8" Meter  
ME19 = "VU" Meter



OUR PRICE £3-50 + 8%

## MULTI-METER MM12

50,000 o.p.v.  
If you need a good instrument for your work/hobby and you're not prepared to settle for a small scale and poor ranges, then read the specifications for the MM12, and send for one!



AC volts: 0 to 1.5, 0 to 5000 in 10 ranges. DC volts: 0 to 0.5, 0 to 500 in 12 ranges. DC current: 0 to 25  $\mu$ A, 0 to 10 amps 10 ranges. Resistance: 0 to 100 ohms, 0 to 16 meg ohms in 4 ranges. Decibels: -20 to +62 db in 10 ranges. Size: 6 1/2 x 4 x 2 1/2 inch.  
Price £19-50 + 8% VAT.

**BARGAIN PROJECT BOX**  
A plastic box with moulded extrusion rails for PC or chassis panels with metal front plate fitted with four screws (all supplied).  
OUR PRICE 50p. + 8%

## "C100" 100 WATT AMPLIFIER

All built and tested, mounted on a plain aluminium chassis which measures 18" x 9 1/2" x 4" and which you can mount into a cabinet of your choice. Four controlled inputs, master volume, treble, middle and bass controls. S/c protected output. 100 watts clean into 8ohm L/S. Ideal for disco, music groups, P.A. and clubs. A bargain at £42 + £1 carr. + 8% VAT.

## AIRCRAFT BAND CONVERTER

A most popular unit providing instant conversion of any medium wave radio to cover the fascinating V.H.F. aircraft band. Spec: 9 volts. Used with any AM or FM radio without need to be connected. Tunes: 110-135 MHz. Size: 100 x 70 x 40mm. Our price £5-50 + 8% VAT.



## POWER SUPPLY UNITS

+ 8%  
FP1 switched 3, 4, 6, 7, 9 and 12 volts at 500 mA, with on/off switch and pilot light. Size: 130mm x 55mm x 75mm.  
ONLY £4-50



FP1 switched 3, 4, 6, 7, 9 and 12 volts at 500 mA, with on/off switch and pilot light. Size: 130mm x 55mm x 75mm.  
ONLY £4-50

## CARELESS SOLDERING IRON WAIL. "ISO-TIP"

★ Completely Portable  
★ Heats in 5 seconds  
★ Solders up to 150 joints or more per charge  
★ Recharges automatically in its own stand  
★ No AC leakage or induced current to damage delicate components.  
★ Heats to 700 deg. F  
★ Fine Tip for delicate and general purpose soldering  
★ Only 8" long and weighs just 6 ozs.  
OUR PRICE £9-75 + 8% (spare bits are available)

**FERRIC CHLORIDE**  
Anhydrous ferric chloride in double sealed one pound poly packs. Our Price 65p + P/P + VAT @ 8% per lb.

## 3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel Bass, Middle, Treble, Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.)  
£18-50 plus 75p P. & P. + 8%



## BARGAIN TRANSFORMERS

12-0-12 volt 500mA

240 volt primary transformer bargain.  
approx size 60mm x 40mm x 50mm  
fixing centres 75mm  
Our Price £1-20 + 8%



## 3 WAY MULTIPLE AC ADAPTOR

This compact adaptor enables a large range of battery powered radios, and calculators to be more economically operated off the mains (220-240V A.C.) Instantly switchable for 6, 7.5 or 9 Volts, current rating is 250mA. A polarity reversing coupler is incorporated into the 2 metre lead which is terminated by a unique 4 way plug offering connections by 2.1 and 2.5mm sockets, 2.5 and 3.5mm plug. The sealed moulded unit is fitted with a 2 pin 5 amp mains plug and measures 47 x 35 x 63mm. Nominal weight: 0.22 kg.  
ONLY £2-50 + 8%.

## GOODMANS CROSSOVER

Bargain Price Crossovers manufactured by Goodmans for the "Havant" Loudspeaker System. 3 way, 8 ohm. £1 each + 12 1/2% VAT.

**LOW NOISE LOW PRICE CASSETTES** + 8%  
Good quality tape in well made screw type cassettes. Presented in single plastic cases.  
C50 = 33p C90 = 45p C120 = 60p  
10% Discount on ten or more cassettes of one type

## LOUDSPEAKERS + 12 1/2%

2 1/2" 8 ohm 60p  
2 1/2" 40 ohm 60p  
2 1/2" 80 ohm 60p  
5" 8 ohm ceramic £1-25



## A19 STEREO PRE-AMPLIFIER

Using standard phono plug connections. Input impedance: 50,000 ohms. Maximum input: 30 mv. Maximum output: 1.8v (at 1% distortion). Gain: 10mv input, 0.5v output. Frequency response: 30-20,000 Hz. B/N ratio: over 60 dB. Power supply: 240v a.c. Dimensions: 101 x 43 x 40mm.  
Our Price £5-50 + 12 1/2% VAT.

U.K. CARRIAGE 50p UNLESS OTHERWISE STATED

VAT—All prices are excluding VAT. Please add to each item the VAT rate indicated.

# NEWMART for all your hi-fi needs.

Stockists of: Amstrad · Teleton · Akai · Sansui · Wharfedale · Pioneer · Rotel · Garrard · Connoisseur

**BATTERY ELIMINATORS P&P 25p**  
240v input 6, 7.5 or 9v .. .. £2-55  
output .. .. £2-20  
12v d.c. input (specify output 6, 7.5 or 9 d.c.) at 300mA .. .. £4-20

**CARTRIDGES & STYLI P&P 25p**

Acos GP91/25C or 3CS (ster. comp)	Cart.	D/D	Styl
GP93/1 or 95/1 ster. cryst	£1-60	£1-20	
GP94/1 or 96/1 ster. ceram.	£2-00	£1-20	
GP101 cryst. comp.	£1-00	—	
GP104 ster. ceram	£2-75	£1-20	
BSR X5M or X5H cryst. comp.	£1-65	£1-20	
SX6M or SX6H cryst. ster.	£2-25	£1-20	
SC5M ster. ceram.	£2-75	£1-20	
Sonotone 9T AHC or 9T AHC/G (Diam.)	£2-45	£1-20	
3509 Magnetic	£2-45	£1-20	
Audio Technica AT55	£2-25	—	
Goldring G850	£3-50	£1-75	
G800	£5-25	£1-75	
G800H	£5-25	£1-75	
G800E	£3-00	£3-50	
Shure Cartridges & Styl			
M44E	£6-00	£4-95	
M55E	£8-40	£6-30	
M75E Type 2	£15-30	£11-70	
MJ5E Type 2	£12-00	£8-25	

**MICROPHONES P&P 45p**  
UD 130 50K/800 ohm uni-dir. ball metal .. .. £7-45  
Condenser Mic 600 ohm ECM77 omni-dir .. .. £8-00  
Cassette Stick Mic. with R/Control .. .. £1-50  
Cass. Stick Mic. with R. Control (Phillips type) .. .. £1-03

**CASSETTES P&P 25p**

Low Noise	C60	C90	C120
Philips	£9-37	£9-48	£9-59
Memorex	£9-01	£1-16	£1-67
Cassette Head Cleaner			£8-48
Bib Head Cleaner			De-
magnetiser .. ..			£1-99
GARRARD SP25 Mk IV ..			£29-70
GARRARD SP25 Mk IV/G800 with Plinth & Cover ..			£33-20
BSR MP60 .. ..			£17-35
Plinth & Cover for Garrard, BSR .. ..			£4-77

These Prices Apply to Mail Order Only. V.A.T. INCLUSIVE. All items subject to availability & manufacturers increase

Callers Welcome at Manchester 30-32 Shudehill Tel. 061-832 7710. Leeds 4 New Market St. Tel. 0532 42708. Liverpool 15 Whitechapel. Tel. 051-238 0738

**NEWMART ELECTRONICS**  
Mail Order Dept PW/11  
Belmont St, Monton,  
Eccles, Manchester.  
Tel 061-789 5268

# A hobby that pays big salaries.

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, WD11

P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

(Block caps please)



## SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz 30KHz  $\pm$  3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-16 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/240V. PRICE £19.75. P. & P. £1.00.

## DE LUXE STEREO AMPLIFIER



A.C. mains 200-240 V. U.S. 110 V. Heavy duty fully insulated mains transformer or with full wave rectification giving adequate smoothing with negligible hum. Valve line up: 2 x ECL86 Triode Pentodes, 1 x EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" x 4 1/2". Overall height including valves 5". Ready built & tested to a high standard. £19.40. P. & P. £1.30.

## HARVERSONIC STEREO 44



A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din sockets & 5 pin din tape rec./play socket are mounted on the printed circuit panel size approx. 9 1/2" x 2 1/2" x 1 1/2" max. depth. Supplied brand new & tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only £7.50 plus 50p P. & P. Mains transformer with an output of 17V a/c at 500mA can be supplied at £1.50 + 40p P. & P. if required. Full connection details supplied.

**VIYNAR & REKINE SPEAKERS & CABINET FABRICS** spp. 54 in. yd. Our price £1.50 yd. length. P. & P. 50p per yd. (min. 1 yd.). S.A.E. for samples.

**BRAND NEW MULTI-RATIO MAINS TRANSFORMERS.** Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations 0-5-10-15-20-25-30-35-40-45-50-55-60-65-70-75-80-85-90-95-100-105-110-115-120-125-130-135-140-145-150-155-160-165-170-175-180-185-190-195-200-205-210-215-220-225-230-235-240V. P. & P. 60p. Pri. 200/240V. Sec. 9-0-9 at 600 mA. £1.50. P. & P. 60p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. £1.65. P. & P. 60p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £2.35. P. & P. 80p. Pri. 200/240V. Sec. 23V at 1.5amp, 49V at 1.6 amp, 8V at 60mA. £2.90 + 65p P. & P.

**ALL-PURPOSE POWER SUPPLY UNIT 200/240V.** A.C. input. Four switched fully smoothed D.C. outputs giving 6v, and 7 1/2v, and 9v, and 12v. at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Ready built and tested Price £5.75. P. & P. 85p.

**STEREO-DECODER** SIZE 2" x 3" x 1/2" ready built. Pre-aligned and tested. Sens. 20-500 mV for 9-16V neg. earth operation. Can be fitted to almost any FM V.H.F. radio or tuner. Stereo beacon light can also be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £5.69 plus 20p. P. & P. Stereo beacon light if required 40p extra.

**QUALITY RECORD PLAYER AMPLIFIER MK. II** A top quality record player amplifier employing heavy duty double wound mains transformer, EOC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 8 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE £6.20. P. & P. 90p. ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £7.30. P. & P. £1.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday Closed Wednesday. All prices and specifications correct at time of press and subject to alteration without notice.

## HARVERSONIC MAINS OPERATED SOLID STATE STEREO FM TUNER




Enjoy fabulous stereo radio at this low introductory price!

Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-gain, low noise IF stages. Automatic frequency control to "lock-on" station and prevent drift. IC stereo decoder for maximum stereo separation. L.E.D. for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12 1/2" wide x 4 1/2" deep by 2 1/2" high. Supplied ready built, fully tested and fully guaranteed. A/C Mains 200/240V (not available in kit form). SPECIAL OFFER £22.50 + £1.40 p. & p.
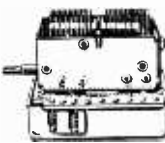
## SPECIAL OFFERS

Multitrad LP1159 R.F.-I.F. Double Tuned Amplifier Module for nominal 470 KHz. Size approx. 2 1/2" x 1 1/2" x 7/8 Volt + earth. Brand new pre-aligned. Full specification and connection details supplied. £3.25. P. & P. 12p

Pye VHF/FM Tuner Head covering 89-108 M/Hz. 10.7 M/Kz I.F. output, 7.8 Volt + earth. Supplied pre-aligned, with full circuit diagram. Connection details supplied. Beautifully made with precision-gear FM gang and 323Pf + 323Pf A.M. Tuning gang only £3.15 + P. & P. 35p.



**PRECISION MAKE** Push Button Switch bank. 8 Buttons giving 16 S/P C/O Interlocked switches plus 1 Cancel Button Plus 3 d/p c/o. Overall size 5" x 2 1/2" x 1". Supplied complete with chrome finished switch buttons. £2 for £1.50 + 20p P. & P.

## HI-FI LOUDSPEAKER SYSTEM MK II

Beautifully made, simulated teak finish enclosure with attractive slatted front. Size 16 1/2" high x 10 1/2" wide x 9" deep (approx.). Fitted with E.M.I. Ceramic Magnet 18" x 8" bass unit, H.P. tweeter unit and crossover. AVAILABLE IN NOMINAL 4 Ohm, 8 Ohm or 16 Ohm impedance (state which). OUR PRICE £12.00 each Carr. £1.90. Cabinet Available Separately £7.25, Carr. £1.40. Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £10.25, Carr. £1.90.

**LOUDSPEAKERS BARGAINS** 5in 3 ohm £1.45. P. & P. 35p. 7 x 4in. 3 ohm £1.69. P. & P. 48p. 10 x 6in. 3 or 15 ohm £3.50. P. & P. 75p. E.M.I. 8 x 6in. 3 ohm with high flux magnet £2.08. P. & P. 60p. E.M.I. tweeter. Approx. 3 1/2". Available 3 or 8 or 16 ohms, £2.90 + 25p. P. & P.

**"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER** Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £7.25 each + p. & p. (one 75p, two 90p). Now also available 8" - 8 ohm 10 watts, r.m.s. 20 watt peak 40 Hz-20,000 Hz. Overall depth 1 1/2". Ideal for Hi Fi or for use in cars £4.90 + p. & p. (one 35p, two 55p).

## SPECIAL LINES OFFERED SUBJECT TO STOCK AVAILABILITY


Hi-Fidelity stereo cassette tape deck transport mechanism as used in Hi-Fi Music Centres. Electronically speed controlled motor, belt-driven flywheel capstan, three digit re-settable counter. Record/Play pre-amps. Bias oscillator. Record/Play and erase heads etc. Power supply required 12V D.C. Circuit diagram, etc. supplied. These units are brand new, but untested and are only offered to the more advanced constructor enthusiasts. PRICE £18.97 + £1.25 P. & P.

WE REGRET THAT WE ARE UNABLE TO ENTER INTO CORRESPONDENCE ON THESE UNITS. New but very slightly marked 'GLENBURN' B8R automatic record changer decks fitted with cueing lever, lightweight arm and ceramic Hi-Fi stereo/compatible cartridge. Can be used for automatic or manual play. PRICE £9.56 + £1.20 P. & P.

Latest model GARRARD 6300 auto/manual changer de-luxe with cueing lever, bias compensator, counter-balanced low resonance arm and fitted with AC08 104 diamond ceramic stereo cartridge. PRICE ONLY £14.50 + £1.50 P. & P.

Limited number of the latest B8R C141R1 auto/manual changer de-luxe. Lightweight tubular arm cueing lever, bias compensator. PRICE £12.80 + £1.40 P. & P. Also similar but without cueing lever or bias compensator. ONLY £11.00 + £1.40 P. & P.
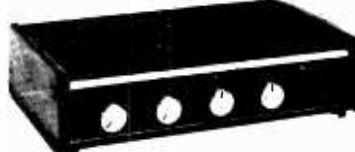
## HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including 8 Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 16 ohms. Compact design, all parts supplied including drilled metalwork high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification; Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response  $\pm$  3dB 12-30,000 Hz. Sensitivity: better than 80mV into 1M $\Omega$ . Full power bandwidth:  $\pm$  3dB 12-15,000 Hz. Bass boost approx. to  $\pm$  12dB. Treble cut approx. to  $\pm$  16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.

AMPLIFIER KIT . . . . . £13.50 P. & P. 65p (Magnetic input components 33p extra)  
POWER PACK KIT . . . . . £4.85 P. & P. 85p  
CABINET . . . . . £4.85 P. & P. 85p

**SPECIAL OFFER—only £22.50 if all 3 items ordered at one time plus £1 p. & p.**

Full after sales service

Also available ready built and tested £29.25. P. & P. £1.




## 3-VALVE AUDIO AMPLIFIER MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" x 4 1/2" x 4 1/2". Incorporates EOC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £7.80. P. & P. £1.00.

**HSL "FOUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc £7.00 P. & P. £1.00.
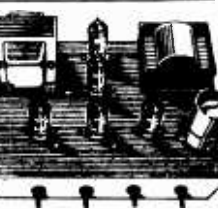
## 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished non-aerial amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other.



Fully shrouded section wound output transformer to match 3-16  $\Omega$  speaker and 2 independent volume controls, and separate Bass and Treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, EOC83, EF86 and EZ80 rectifier. Simple instruction booklet 25p + 8AE (Free with parts) All parts sold separately. ONLY £11.25 P. & P. £1.35. Also available ready built and tested £15.20 P. & P. £1.35.

## GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18V battery or from H.T. line 200/300V. Frequency response 15Hz-28KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 3". Brand new complete with instructions. Price £1.60 P. & P. 15p.

Prices include VAT at Current Rate

# HARVERSONIC SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station. SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly) PLEASE NOTE: P. & F. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.



#### PLASTIC BOXES IN 5 SIZES

Easily drilled or punched, grey ABS boxes incorporate slots for 1.5mm pcb's with lid fixing screws running into integral brass bushes

100x50x25mm	51p	(1-9)	49p	(10+)
112x62x31mm	59p	(1-9)	52p	(10+)
120x65x40mm	68p	(1-9)	62p	(10+)
150x80x50mm	77p	(1-9)	74p	(10+)
190x110x60mm	£1.33	(1-9)	£1.30	(10+)

#### Polystyrene version

Plain inside, no integral bushes				
112x61x31mm	35p	(1-9)	32p	(10+)

Add 25p per £1 order value for Post & Packing

#### TYPE A NEDN INDICATORS

Held in 8mm hole by plastic bezel  
150mm wire leads



Red, Amber, Clear, Opal	19p each
Green	28p each

#### TYPE MP NEDN INDICATOR


150mm leads, held in 6.4mm hole by nut



Red, Amber, Clear, Opal	20p each
-------------------------	----------

On all orders quote reference PW/11/76

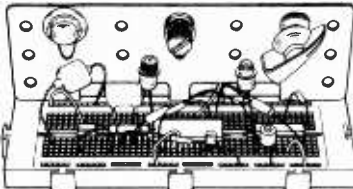
Stop wasting time soldering  
The **NEW MW BREADBOARD** accepts  
Transistors, LED's, Diodes, Resistors, Capacitors  
and all DIL packages with 6 to 40 pins



Includes slot-in Component Support Bracket and has over  
400 individual sockets, plus Vec & Ground Bus Strips  
Price £9.72 (includes VAT & P.P.)
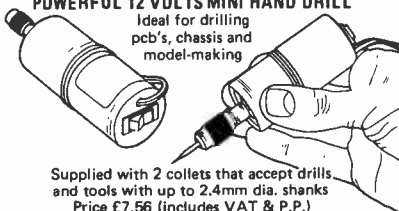
#### POWERFUL 12 VOLTS MINI HAND DRILL

Ideal for drilling  
pcb's, chassis and  
model-making



Supplied with 2 collets that accept drills  
and tools with up to 2.4mm dia. shanks  
Price £7.56 (includes VAT & P.P.)

#### SEVEN SEGMENT DISPLAYS


Economy Quality — Only 66p  
0.3" — Red  
Common Anode — Left Decimal

Full specification displays also available  
Red, Green and Yellow  
£1.35 each inc. data



P.P. Note. Unless included in price add 25p post & packing  
for orders totalling under £10. Prices include VAT and are  
valid in UK only for 2 months from journal issue date.

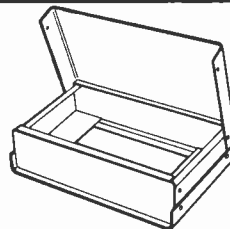**Michael Williams Electronics**  
47 Vicarage Av., Cheadle Hulme, Cheshire SK8 6JP



#### EYE CATCHING INSTRUMENT CASE

Removable Red, Orange or Grey covers  
Black chassis with support brackets  
Overall size 250x167x68mm  
Price £11.86 (includes VAT & P.P.)

#### ECONOMY QUALITY LED'S

50 for only £5  
100 for only £9

Mixed bags, all sizes, various colours



#### FULL SPEC. INDIVIDUAL LED'S

Red (any size) £0.75/pack  
Green, Yellow, Orange (any size) £1.20/pack  
Packs contain 5 LED'S, clips and data



#### DH LAMPHOLDER

For LES or Midget flange lamps  
13mm hole fixing, lamp not included  
Red, Blue, Green, Amber, Clear, Opal, Orange  
Price 25p each (See P.P. Note below)

Quantity quotations on request.



## Are you only **HALF** a Constructor?



For a year or two I was only half a constructor—struggling along trying to find the right components by tramping from shop to shop. Then I discovered Home Radio and their marvellous Components Catalogue! It's made life so much simpler for me—I can soon locate just what I need and then order by phone. I really feel that now I can claim to be a *complete* constructor.

The Home Radio Components Catalogue consists of 200 pages containing some 5,000 items, nearly 2,000 of them illustrated. Everything is set out so clearly the catalogue is a pleasure to use. When you buy one you also receive *free* a mini catalogue filled with super bargains. The saving on some of your purchases from this bargain list alone can more than pay for your catalogue. The catalogue costs 90 pence plus 35p for postage and packing. Why hesitate? Send off your cheque or P.O. for £1.25 now, and discover the satisfaction of being a *complete* constructor.

Please write your Name and Address in block capitals

NAME .....

ADDRESS .....

HOME RADIO (Components) LTD. Dept. PW  
234-240 London Road, Mitcham, Surrey CR4 3HD



(Regn. No  
London 912966)

**POST THIS COUPON**  
with cheque  
or P.O. for  
**£1.25**



## "Manta"

THE **CAPACITIVE DISCHARGE ELECTRONIC IGNITION UNIT**

### IMPORTANT NEWS!

WE ARE PLEASED TO ANNOUNCE THAT THE "MANTA" — ONE OF THE HIGHEST QUALITY IGNITION UNITS AVAILABLE — IS NOW SUPPLIED IN KIT FORM

CONSTRUCT THIS TOP PERFORMANCE IGNITION UNIT AND BENEFIT FROM IMPROVED PETROL CONSUMPTION, SMOOTHER RUNNING AND INSTANT STARTING FOR YOUR VEHICLE.

KIT PRICE (INCLUDING POSTAGE AND PACKING, V.A.T., FULL ASSEMBLY AND INSTALLATION INSTRUCTIONS)

**ONLY £16.50**

(Ready made unit available at £19.85, including V.A.T., postage and packing)

Send S.A.E. today for full details of this top quality unit to:—

## **ELECTRO SPARES**

Dept. P.W., 187a SHEFFIELD RD., CHESTERFIELD DERBYSHIRE S41 7JQ TELEPHONE (0246) 36638

## **CHROMASONIC electronics**

From Denco Coils, through TTL, C'Mos, Quartz Crystals, Vero, DVM Chips, Clock chips, LED's; LCD's; Displays, Transformers, Boxes, Cases, Knobs and millions of R's and C's, Transistors and Diodes.

It's all in our **BRAND NEW** illustrated **CATALOGUE. FREE** with every copy are 36p worth of vouchers.

Send 35p, inc. Free p & p to

Dept. 1 Chromasonic Electronics, 56, Fortis Green Road, London, N10 3HN.

**MAGENTA** PW10, 61 Newton Leys, Burton on Trent, Staffs. DE15 0DW electronics Ltd.

for professional components and service

### **COMPONENTS & HARDWARE**

Applications. Inclusive prices. No minimum order. Speedy despatch by first class post.

SHEET METALS; CAPACITORS; ENAMELLED & TINNED COPPER WIRES; RESISTORS; CABLE; IC's; TOOLS; SWITCHES; SCREWS, CASES, DIODES; PCB SUPPLIES; TRANSISTORS; PLUGS & SOCKETS; LED's; DRILLS; VEROBOARD ETC.

### **FREE CATALOGUE**

INCLUDES SAMPLES & TRANSISTOR TESTER DATA OFFER.

Please send 2 x 6p stamps to cover postage etc.

# Ham re-born with Record-breaking Antenna!

The JOYSTICK VFA (Variable Frequency Antenna—a six band, patented omni-directional antenna of extreme flexibility) is a **MUST** for confined locations —at the worst it can stand in the corner of the shack and still do its stuff! But space problem or no... what you need most is **EFFICIENCY**.

Ex-G3IYQ is making a come-back after nearly 16 years off the air. He has a "System A" Joystick and tuner and describes himself, at present, as a "receiver-designing SWL". In his rather unfavourable QTH, the System A. gives up to 4 S-points over any other antenna and he looks forward to getting his ticket back to test the JOYSTICK on transmission. (You won't be disappointed, OM!)

Alan also enthuses about recently hearing, courtesy of the Joystick, a GC working all over G, G1, GM & GW. The GC was coming in like a bomb and in almost all cases both sides of the SSB QSO's were logged Q5., and this on Top Band in late afternoon!

**ALREADY IN USE BY AMATEUR TRANSMITTING AND SWL STATIONS WORLD-WIDE AND IN GOVERNMENT COMMUNICATION.**

**SYSTEM 'A' £32.40**  
250 w.p.e.p. OR for the SWL.

**SYSTEM 'J' £38.60**  
500 w.p.e.p. (improved 'Q' on receive).


## **PARTRIDGE SUPER PACKAGE**

**COMPLETE RADIO STATION FOR ANY LOCATION**, comprising: the NEW R.300 RX (with Xtal Marker), Gen. Cov. RX., Headphones, VFA, System "A", all connecting cables, Deliv. Securicor (our risk). **ASSEMBLED IN SECONDS!** **£189.00**  
BIG CASH SAVINGS! OR R.300 ONLY £168.75 incl. deliv.

Prices include VAT., insurance and delivery by post or carrier



Just telephone your card number

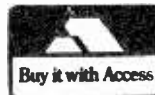

Phone 0843 62535 (or 62839 after office hours)

IF YOU CAN'T HEAR THEM, YOU WON'T BE ABLE TO WORK THEM. LET US GIVE YOU FREE ADVICE ON YOUR ANTENNA PROBLEMS. GIVE US A RING OR WRITE, WITH SAE.

BOX 5



G3CED

G3VFA

# FABULOUS NEW KITS

EASY TO CONSTRUCT

DORAM  
KITS  
CONTAIN  
EVERYTHING  
DOWN TO  
THE LAST  
NUT!



## SOUND TRIGGERED FLASH

Triggers flashgun when microphone picks up sound. Sensitivity may be varied over a wide range enabling a multitude of action photographs to be obtained. Triggers most popular flashguns.

£6.50 + H

## De-luxe FM TUNER

BY LARSHOLT

£89.95 + H

- ★ illum. tuning scale and sig. meter. ★ 5 pre-set tune and scan tune
- ★ Mute control and MPX ★ Sensitivity of 1µV For 26dB quieting.
- ★ No alignment required.

## TIMER

Switch time intervals control changover relay 1 to 1000 seconds. Fitted with reset controls. Ideal for use in photography or any application requiring delayed switching. Incorporates NE555 I.C. Timer

£8.75 + S

**Available NOW!**

## ELECTRONIC COIN TOSS

A simple heads/tails game-random result when activated. Red and green L.E.D. display.

£2.75 + S

See coupon on next page

## ELECTRONIC CAR IGNITION

GIVE YOUR CAR NEW LIFE!

Will give your car greater performance and help to reduce fuel consumption. 12V Neg. operation. Includes changover switch with immobilize position.

£9.95 + S

HERE'S JUST A FEW OF THE MANY NEW AND INTERESTING KITS AVAILABLE

- ★ 'INTERNATIONAL 25' AMP. £29.95 + H
- ★ MOTORISTS DWELL METER £5.70 + S
- ★ TEST BENCH AMP. £4.95 + S
- ★ TV SOUND ONLY TUNER £36.95 + H

S = 8% V.A.T.  
H = 12½% V.A.T.

- ★ CASSETTE POWER SUPPLY £3.20 + S
- ★ DARKROOM EXPOSURE METER £4.75 + H
- ★ 6V ACCUMULATOR CHARGER £9.95 + S
- ★ 60W GUITAR AMP. £29.95 + H

FULL BUILDING INSTRUCTION DETAILS OF KITS IS AVAILABLE ON REQUEST PRICE 25p EACH REFUNDABLE IF KIT SPECIFICALLY APPLIED FOR IS PURCHASED



# DORAM

A PROFESSIONAL DEAL  
FOR AMATEURS

Over 50,000 customers  
REGULARLY SERVICED

## LOOK WHAT'S IN IT FOR YOU

\* SEMI CONDUCTORS \* CAPACITORS \* IC's \* MINI CERAMICS \* RESISTORS \*  
 POTENTIOMETERS \* THERMISTORS \* BRIDGE RECTIFIERS \* REGULATORS \*  
 RADIO MODULES \* AUDIO AMPS \* TIMERS \* CABLE \* TRANSFORMERS \* FET's \*  
 SUPPRESSION FILTERS \* CRYSTALS \* RELAYS \* CONNECTORS \* PLUGS & SOCKETS \*  
 CASES \* KNOBS & DIALS \* HEAT SINKS \* SCREWS, NUTS, TAGS, GROMMETS \*  
 ADHESIVES & CLEANERS \* DIODES & INDICATORS \* PANEL METERS & BULBS \*  
 ILLUM. PUSH BUTTON, TOGGLE, ROCKER & PROXIMITY SWITCHES \* SOLDERING IRONS \*  
 NI CADS \* DRILLS \* REPLACEMENT STYLI \* SPEAKERS \* BLANK CASSETTES \*  
 MICROPHONES \* CABINETS \* MULTIMETERS \* LOGIC PROBES  
 AND MUCH, MUCH MORE !

**NEW**  
**CATALOGUE**  
**Edition 3**

DORAM'S NEW CATALOGUE HAS BEEN SPECIFICALLY DESIGNED FOR THE AMATEUR RADIO, ELECTRONICS & HI-FI ENTHUSIAST.

DORAM'S SERVICE ALSO INCLUDES-

- ★ MANY PRICE REDUCTIONS - QUANTITY DISCOUNTS ON CAPACITOR, RESISTOR OR SEMI-CONDUCTOR ORDERS
- ★ **FREE** - UP-DATE PRODUCT INFORMATION SERVICE DURING LIFE SPAN OF CATALOGUE
- ★ ALL ORDERS SENT BY RETURN-OF-POST
- ★ NO-QUIBBLE REPLACEMENT PART SERVICE
- ★ **POST & PACKING FREE FOR ORDERS OVER £1** (Only applies for Great Britain N.Ireland and B.F.P.O. Nos.- Overseas orders F.O.B.)



SEND FOR YOUR NEW CATALOGUE AND/OR KIT BROCHURE NOW!



## Special Offer

If catalogue ordered (priced 60p) you will receive a refund voucher of 25p.

If catalogue and kit brochure ordered together, price 70p plus 2 x 25p refund vouchers.

DORAM ELECTRONICS LTD.  
P.O. Box TR8,  
Leeds, LS12 2UF.

PW10/76

PLEASE PRINT BLOCK CAPITALS

NAME: .....

ADDRESS: .....

..... POST CODE.....

An Electrocomponents Group Company.

I enclose ..... Please send me by return my new catalogue and/or kit brochure. (Over seas orders except for N.Ireland please add 30p for post and packing surface only.

---

# Big Brother watches

---

SOME years ago, the BBC broadcast an intriguing play called, "Rossum's Universal Robots". These creatures had been designed by man, manufactured by man, for the service of man. They did all the menial tasks; house-keeping, cooking, cleaning, shopping etc.

But after a while, one robot said to another, "There's more of us now than there are of them." And so, like all good revolutionaries before them, the robots took over. Once in command, they became superior species and all mere humans were reduced to second-class citizen status.

The computer is an equipment, a kind of robot; designed by man, manufactured by man, for the service of man. There are lots of them about. Certainly not "more of them than there are of us" but . . .

In their electronic, unailing, frighteningly accurate and detailed memories, data about you, me, him, she, them—everybody, is building up.

"Prefers blondes, likes golf, interests—photography and electronics, police conviction dangerous driving 1967, failed 'O' levels . . . etc. etc."

All your idiosyncrasies, traits, past personal history available instantly. And, of course, it needn't stop there.

Many people, both in the computer industry itself and outside it are asking just how far things are likely to go. Is there really a danger that, like Rossum's Universal Robots, the computers could take over?

Computer programmers (amongst others) often counter this suggestion by observing that the computer is the servant. Man provides the input and receives the output. It also requires man to interpret the output.

The argument has a certain truth and validity. Yet it is also true that the computer will play a major role (if not *the* major role) in the future development and, perhaps, in the ultimate destiny of the human race.

It is being used increasingly to "advise action" for many problems having first devised a solution. The "robot" offers its logical conclusions from the input data. The output is seldom questioned and decisions are based on this logical output—an output devoid of all human feeling and reduced to some cold, algebraic hypothesis.

The computer can store colossal amounts of information. In a police state this would prove useful or disturbing depending upon where you stood in the scheme of things.

Is there not an indication, too, that we could become so dependent upon the computer that to all intents and purposes we will be a slave to it and not the reverse?

Have we not seen this indication already in the

field of electronic calculators? These are now commonly appearing in schools. The danger is that we no longer bother to add, subtract, multiply or divide, the "robot" in our pocket does all that for us. Ask anyone who uses an electronic calculator regularly, and they will admit that they use it even for the simplest of calculations. We are already a slave to one form of robot.

With the advent of microprocessors, desktop computers, new technologies and techniques developing all the time, there must surely be a case for caution or at least for a rethink and appraisal.

At Baglan Bay, in Wales, computers control and virtually run a gigantic chemical plant. Not only does the computer control individual valves, chemical processes etc, but it also operates an alarm system. If anything goes wrong the computer will immediately and automatically effect the best means to keep as much of the equipment working as possible and will shut down only the minimum of plant so avoiding hindrance of production as much as possible.

In between its millions of individual tasks of monitoring and instructing, the computer will fire a series of special signals round all its sensors and circuits to automatically check that it—the computer itself—is functioning correctly at all times. It is self-diagnostic.

Now imagine suddenly removing the computer from Baglan Bay and making man work the plant. The result would be chaos and probably failure because the whole complex is run and has been designed to run from a computer.

In the future our way of life is moving more and more towards dependence upon the computer. All the computers need do is to simply stop working—and we're dead.

The more reliance we place on computers, the more we use them, then by definition, the more we are dependent upon them. It is the slow, unsuspecting, tender trap and we're walking right into it.

Remember, too, that the "thing" (whatever it is) that controls need not assume human form just to please our visual satisfaction. The power behind the throne could just as well be a black box—possibly drawing its power from light and/or radio activity thus making sabotage impossible.

What about those UFO's or anyone else who wanted to take us over. All they need do is conquer our computers and they've got us!

What man does with the computer is now a major consideration. A crossroads has been reached. The computer is destined to be developed far beyond most people's wildest imagination. The final outcome will dominate our entire way of life.

Think about it—while you're still able!

LIONEL E. HOWES—Editor.

## Mail Order Protection Scheme

THE attention of all readers is drawn to the details of the Mail Order Protection Scheme published on page 606 of this issue. We shall publish it again from time to time.

Please note that for the purposes of this scheme, mail order advertising is defined as:—"Direct response advertisements, display or postal bargains where cash had to be sent in advance of goods being delivered". Classified and catalogue mail order advertising are excluded.

## Super Service

VERO ELECTRONICS LIMITED have announced the inauguration of their Verospeed Service Division. They undertake to despatch all written orders on the day they are received and a telephoned order before 3 p.m. will still get the goods in the post that evening.

The products in this service have been carefully selected from the most popular ones in the Vero Electronics range to enable R & D prototyping to be carried out with the same products which can be obtained in production quantities at production prices from Vero Electronics Limited themselves. The prices for components are quoted in the catalogue and there is no extra charge for postage and packing. Vero also state, that there is no minimum order surcharge. Vero Electronics Ltd, Industrial Estate, Chendles Ford, Hants. Tel: 04215 2956.

## Solar on show

JUST a short note for those who enjoy a good exhibition, albeit one that has little to do with wireless. It appears that the Midlands is slowly overtaking London, when it comes to staging

spectacular shows, and the latest, The International Ideal Home Exhibition, promises to be no exception.

To be held at the prestigious National Exhibition Centre, Birmingham, the theme of the show will be the "Family". On show will be three fully-furnished homes, a solar energy house, a theatre with cookery, Hi-Fi, TV, photography, fashion shows and personal appearances by stars of the entertainment world.

The Solar House being shown is equipped with solar panels to heat domestic water, is fully insulated to the latest standards, and equipped with the latest energy saving devices. To back up this new form of energy, researchers claim that for the average family, 50 per cent of the total energy used is for hot water and the sun can provide 70 per cent of this.

For those wishing to attend the Exhibition will be open for two weeks from Thursday, 14th October to Saturday, 30th October.

## Catalogues for all

DORAM ELECTRONICS LIMITED, one of Britain's leading mail-order distributors of electronic components, construction kits and accessories have published a new 'Edition 3' catalogue priced at 60p and a new construction kit brochure priced 25p. Should customers order both publications together, Doram are offering a special price reduction of 15p so customers only pay a total of 70p. In addition each customer will receive two 25p vouchers which may be used at any time, as a refund, when placing orders with Doram.

A special feature of the main catalogue is that during the life span of the catalogue customers will receive, absolutely free, update amendment leaflets giving information on new lines and price changes.

Many new products have been added at the request of customers

which include an extension to Doram's range of NPN, PNP, Unijunction and Field Effect Transistors; a Constant Current Charger and Rhythm Generator IC and 2m mobile aeriels. In addition to the main catalogue Doram have published a fully illustrated brochure containing information on no less than 26 new "easy-to-construct" kits. Doram Electronics Ltd., PO Box TR8, Wellington Rd, Industrial Estate, Wellington Bridge, Leeds LS12 2UF.

## Quad from the Beeb

ACCORDING to a BBC statement, no commercial quadrasonic matrix system so far broadcast has achieved international acceptance. The statement continues by saying that not only is the present array of quadrasonic techniques unacceptable, but by and large, they don't match up to the standard achieved by BBC VHF radio.

Further to these findings, the BBC Research Department has developed a new matrix system which has already undergone rigorous tests and comparisons with other systems already known. The tests are claimed to have been judged by panels of engineers, acoustic experts, musicians, and producers of all types of radio programmes. The findings of these tests on this new type of transmission, known as "Matrix H" are said to be very favourable and that the system is far superior to anything yet tried. "Matrix H" has also been found to combine excellent compatibility with very good quadrasonic reproduction.

The present BBC stereo distribution network it is claimed is capable, without modification, of carrying "Matrix H". However, the extension of BBC VHF radio services and stereo throughout the UK remains the first technical priority and unfortunately, no regular quadrasonic service is envisaged at present.

# DISCOS



# AND ASSOCIATED AUDIO SYSTEMS

BEN DUNCAN

**T**HIS article is intended to help the amateur design and build good high powered audio equipment for discos, groups and PA applications. (Abbreviated to D. G. and PA throughout this article.) Two basic factors predominate:

1) Good reliability. Most group, disco and PA, (G. D. and PA) equipment is used publicly, and breakdowns can be embarrassing at the very least. Also, such equipment is generally under infinitely greater stress than domestic equipment, which is rarely, if ever, run flat out for any length of time.

2) Inherent robustness. G. D. and PA equipment is generally subject to poor physical treatment.

Unfortunately, I know from experience that some constructors and manufacturers use domestic design philosophy for this class of equipment. Reliable equipment is based on good, simple designs, built of top quality components, using generous overratings at points of stress. Such excellence is expensive, but repays the owner a thousandfold in the long run. **IT IS ABSOLUTELY FALSE ECONOMY TO SKIMP.** The fundamentally commercial aspect of the uses of G. D. and PA equipment eases the higher expenditure involved, and in any case, sheer enthusiasm for loud music make it a worthy sacrifice to many.

In the past, G. D. and PA equipment has lacked sound quality, but there is no longer any technical reason why fundamentally Hi-Fi reproduction should not be possible.

Another factor is versatility. For G. D. and PA applications are broadly similar and it is logical to

design a system that will either serve all three purposes and/or is readily convertible for alternative applications (Fig. 1). Consistent with this aim, nothing specific is described in the following text.

## Power amplifier

High power amplifiers, until recently, had been a very acceptable stronghold of valves. However, second generation power transistors make all valve equipment technically obsolete. Only the elusive **valve sound**, beloved of some guitarists, makes the valve a must for a dedicated few.

The relationship between power output and actual loudness is commonly misunderstood. Reference to Fig. 2 shows that for a given volume of space, the output wattage must be multiplied by ten to double the loudness. Thus 100W is only three times louder than one watt. Careful consideration of this graph, and the cost of loudspeakers, shows the optimum power to be around 70/100W. Outdoor PA and (noisy) groups may need higher powers, and 300W would be needed for any worthwhile (50%) increase in loudness. Note that 300W is half as loud as 1,000W and **NOT** 500W as is commonly supposed.

Heatsinking and ventilation must be superlative for the sake of reliability, even if the output transistors run coolly on music and voice signals. The rough sine and square wave inputs derived from synthesisers, guitars and organs can cause rapid overheating and dissipation may well exceed peak

SPECIFICATION	DISCOTHEQUE	GROUP	PUBLIC ADDRESS
Power output (watts RMS)	25-100	25-1000*	50-1000*
Distortion (THD at max. rated output, 1kHz)	10%	10%	10%
Hum and noise—suggested level.	-100dB	-100dB	-100dB (min)
Phono input Tape input/output Microphone input Other inputs	Ceramic (Two) Pre-recorded effects and jingles Dynamic —	— Reverb & pre-recorded effects Dynamic (several) Guitar (several) Synthesiser, Organ	Ceramic Pre-recorded speech & music Dynamic, Crystal —
Specialities	Monitoring, stereo, autofader	—	—

\* The wider range is accounted for by indoor v. outdoor usage.

Fig. 1: Typical specifications for G.D. and PA applications with suggested standards to aim for. From these a composite specification may be obtained.



output power. Apart from overheated output stages, the transformer may overheat unless conservatively rated, due to the heavy load these signals will impose upon it. In order to effect cooling, heat is dissipated in three ways: (1) Conduction, the heat spreading out through the chassis, if of metal. (2) Convection, whereby cool air, in cooling a heatsink, becomes warm, and in rising, draws a fresh supply of cool air in, from underneath it. (3) Radiation. Heat is emitted directly from a heatsink. Matt black surfaces emit (and absorb) heat best. Heatsinks are best mounted inside an amplifier, as there is always the danger in externally mounted heatsinks that the live transistor casing may be shorted to chassis; a sure recipe for disaster.

## Thermal resistance

Where the transistors are in contact with the mica washer and heatsink, these joints should be smeared with thermal conductivity compound. Silicon grease is an inferior substitute. All metal from which heat must be able to radiate freely should be painted matt black. The capacity, or thermal resistance of a heatsink is measured in °C/W and is determined as follows: There are generally three thermal resistances ( $\phi$ ) to be taken into account. These, when added, together with the ambient (room) temperature give the actual transistor junction temperature, the maximum value of which, ( $T_j$  Max) is ascertained from data books. Dissipation is always assumed to be 100 per cent of the transistor's power output, though in reality it is usually closer to 50 per cent, thus giving an overload safety factor of 100 per cent.

Typically,  $\phi_1$  (junction to casing) ..... is 1.0°C/W  
 $\phi_2$  Across mica washer) ..... is 0.5°C/W  
 $\phi_3$  (Heatsink; Area and mass of sink  
 are the basic factors) is (say) 1.5°C/W  
 Then  $\phi_1 + \phi_2 + \phi_3 = 3°C/W$ . Thus the junction temperature of a transistor, driven at 25W, mounted on a 1.5°C/W heatsink with a mica washer, would be  $(3 \times 25) 75°C$ , plus ambient temperature ( $T_{amb}$ ) (say 25°C) = 100°C. Similarly, to calculate the required capacity of a heatsink,

$$\phi_3 = \frac{(T_j \text{max} - T_{amb})}{W} - (\phi_1 + \phi_2)$$

W being the dissipation in watts of the transistor.

## Lead lengths

It is highly inadvisable to mount preamp circuitry within the casing of a power amplifier. Apart from reducing versatility, it makes high frequency instability almost certain in many cases. Any oscillation in these circumstances is likely to be of a very high order and pass unnoticed, the only symptoms being overheated components. Any input level above 200mV is satisfactory, but in any case, input wires must be kept well away from the output stages and under no circumstances should input and output wires be run parallel at less than 60mm distance. If it is necessary for input and output wiring to cross over, minimal interaction is achieved by placing the wires mutually at right angles.

A low input impedance (600Ω) allows long input cables to be used without undue signal loss. However, high impedance inputs are more versatile as all lower impedances may be fed in without loss of quality. Thus provision of both low and high impedance inputs is suggested. The latter is tapped off a low impedance input by addition of a series resistor of a value corresponding to the impedance required. Naturally, there is some signal loss.

Electronic overload protection circuitry is ideal for G. D. and PA equipment, but is necessarily complex to be effective. Therefore low tolerance fuses are the most common form of protection, and are relatively satisfactory. These fuses are simply rated at just above the average peak current, whether in the speaker or power lines. A double throw switch, wired to two fuses allows rapid changeover to a reserve fuse in the event of an exceptional peak blowing the first. If, however, there is a genuine fault, the reserve fuse will blow, and in so doing, confirm this.

## Loudspeakers

Good bass response is essential in this type of equipment, with 70Hz being a maximum satisfactory frequency. Bass response below 30Hz however, due to turntable rumble and LF acoustic feedback, and treble response above 10kHz, due to inevitable scratch and hiss on disco records is unnecessary. Most high power speakers tend in any case to be bass heavy and few extend beyond 10kHz.

It is essential when choosing speakers, to match both speaker and amplifier powers in RMS or peak ratings, and never to compare music ratings, as these vary from 20 per cent to 100 per cent above RMS, depending on the method of measurement. 100W RMS = 200W peak = 200W USA = 120-200W music

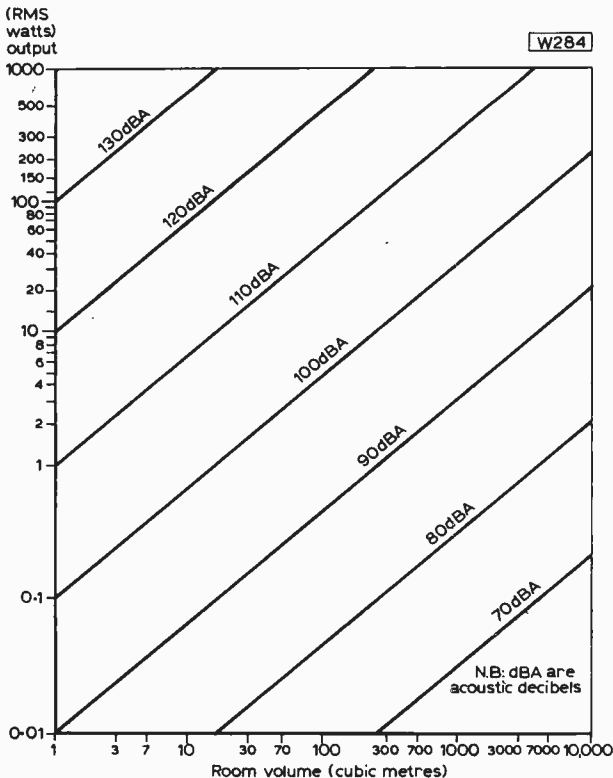


Fig. 2: Straight line graphs showing the relationship between loudness, wattage and room volume. An increase of 10dB represents a doubling of the loudness. Also one acoustic watt is approx. 120dB @ 1 metre, and 10W is approx. 130dB @ 1 metre.

power=150W IHFM! If a speaker is to be used exclusively with voice and music signals, a 20 per cent overload factor is recommended for the speakers. That is, for a 100W system, the speaker rating(s) should total 120W. Some speaker manufacturers significantly underrate their speakers and this possibility should be checked with the manufacturer. For example, a speaker with a nominal 100W rating, could be safely fed using a 100W amplifier with all types of signal input. If the roughly sine and square wave signals from synthesisers, organs and guitars are to be handled, a 50 per cent overload factor is considered mandatory. A significantly lower overload factor may result in premature speaker failure or burnt out voice coils. It is not unknown for speaker cabinets to catch fire!

## Multiple speakers

In high power systems, it is rare to use a single speaker, and units over 100W are not commonly available. With 100W say, two 60W speakers could be used, giving a 20 per cent overload factor. Whether they are wired in series or parallel depends on the required impedance. The wattage rating of each speaker being simply added, provided they are of the same impedance, or if they are of differing impedances, they share the power according to the inverse ratio of their impedances, given that the total impedance matches the amplifier. This applies only to second generation (Constant current source) power amplifiers, the power dissipated being inversely proportional to the loudspeaker impedance, due to the ultra-low source impedance. Use of several speaker cabinets, instead of mounting several speakers in one cabinet allows sound to be evenly distributed with greater ease.

## Cabinet design

Designs specifically for G. D. and PA applications are rarely met, but sensible uprating of a HiFi enclosure design is satisfactory. Here is a summary of cabinet design points: High density chipboard is suitable, and the thicker the better is an ideal maxim as long as it is not carried to extremes. A thickness of 18mm is suitable for most enclosures. Chipboard is easily damaged as are most materials if on the road. A solution is to build a framework of angle-iriders around the cabinet, joined together with wing nuts. Its effect is to make enclosures virtually indestructable. Cabinet dimensions should be rectangular and as large as possible.

Bass reflex cabinets should have both their height and width greater than the speaker cone diameter, with a depth which is greater than a third of the width. Infinite baffle cabinets should be totally filled with tightly packed acoustic wadding. Bass reflex cabinets require lagging of some 6mm thickness on any three non-parallel walls, and only proper (acoustically transparent) speaker cloth should be used, eg "Tygan".

Bass reflex cabinets have a reputation of being difficult to get good results from. In my own experience however, no particularly arduous calculations or long hours spent tuning the reflex vent were engaged upon. The mere cutting of a correctly sized vent, obtained from tables, gave vastly improved and eminently satisfactory response. In the

bibliography, books (2) and (6) give details of bass reflex cabinet design.

## Speaker efficiency

The efficiency of a speaker is simply how many acoustic watts output compared to how many electrical watts input and is expressed as a percentage. At about one metre, one acoustic watt is about 120dBA, ten acoustic watts are 130dBA, and so on. Thus, if 10W drove 10 per cent efficient speakers, the loudness at one metre would be 120dBA, or a power of one acoustic watt would be emitted from the speaker. Efficiencies of reflex systems are generally between 5 and 15 per cent, and infinite baffle enclosures, between 4 and 8 per cent. These efficiencies are far higher than those normally encountered in domestic audio, and are due to the physical size of the speaker units.

If cabinets carrying the same signal face basically similar directions, the speaker cones must move in phase for good results, and vice versa for cabinets facing basically in opposing directions. Speaker terminals are usually marked with relative polarity and it is wise to see that all connectors in the loud-speaker line are coherently encoded for like polarity. For parallel connections, like terminals should be joined, and for series, oppositely marked terminals should be connected.

## Cable types

The use of 1mm<sup>2</sup> cable, as used for domestic permanent wiring, is recommended for speaker systems employing lengths below ten metres. The current capacity of this cable is 10A, and applying

$$I = \frac{W}{R}$$

Where I is average current, W is RMS output wattage, R is speaker impedance, it can be calculated that this cable is suitably overrated for most systems, up to, say, 150W (depending on the speaker impedance). This unused capacity is not wasted. Boomy bass, if not caused by poor acoustic damping can be attributed to poor electrical damping, due to too high a source impedance. For this reason, always run individual wires back to the amplifier for speakers in parallel and always use parallel connections in preference to series ones to keep the resistance between each speaker and the amplifier as low as possible. Long runs of fairly thin cable, exhibiting a relatively high impedance are also responsible for this. Use of the specified heavy cable will avoid serious loss of damping for lengths up to 20 metres, but PA often requires greater lengths. The usual solution is to use a line transformer to step up the impedance and voltage (typically to 25 or 100V), hence reducing the current and allowing long runs of thinner cable to be used, with minimal power loss. Special high impedance speakers are then required, or a second transformer to step down. Good line transformers are expensive and frequency response is bound to suffer, especially at the bass end. This is not unduly serious in PA work, but to say the least, bass is desirable for group concerts! The solution is to use 2.5mm<sup>2</sup> cable, of 20A rating, which is suitable for ultra high power systems, and exhibits extremely low impedance; thus long cable

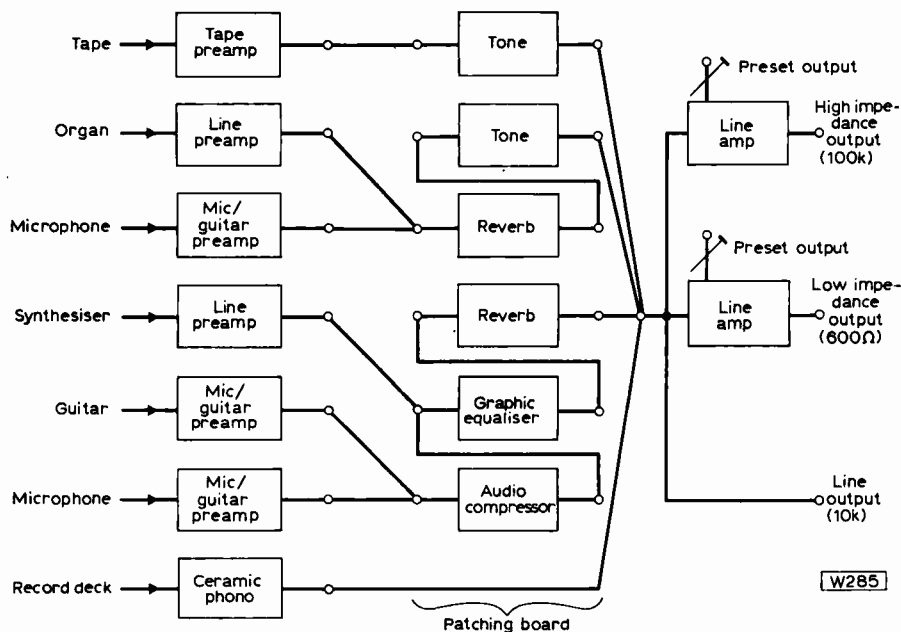


Fig. 3: Block diagram of a versatile group pre-amplifier, shown here with a typical arrangement patched in.

runs up to several hundred metres are practical. The cost of this cable, given that all cable is expensive today, is relatively low, and compared with the cost of line transformers, is trivial! 2.5mm<sup>2</sup> is of the order of £12 per 100 metres, and the smaller sizes, suitable for medium power systems, are correspondingly cheaper.

## The pre-amplifier

The preamp determines the overall versatility of a system of this nature. Maximum versatility is obtained by providing preamps to handle all likely signal inputs, and for these to have a common output voltage and impedance (Termed "line level"). Tone controls and any effects units required can be simply inserted in series with the line, provided they have unity gain and match the line level. F. C. Judd described a system utilising this principle in *PW* some years ago, using a line level of 100mV at 10kΩ. The article is highly recommended, as it contains preamp circuitry for all common signals, though it would not be difficult to design circuitry using IC's.

The line level is raised after mixing to a suitable voltage for feeding power amps, generally between 100 and 1000mV. A preset output of one volt at 600Ω will feed satisfactorily into most amplifiers. Several of these are useful for feeding additional amplifiers, driving sound/light convertors, etc. The preset allows the line to be matched to the power amplifier, thus preventing damage and distortion from overloading. Fig. 3 shows a block diagram preamplifier employing patching, for group and PA use. A patch board is easily made, as only single pole connectors are necessary, there being no need to patch the earthy side.

Fig. 4 shows a preamplifier in block form for a disco. Line inputs can provide additional signals, from say, tape or phono sources. Note that the cross fader must be ganged log/antilog. The monitor signal is derived before the mic signal is mixed in, to avoid acoustic feedback via the headphones. The monitoring allows accurate cueing and control of the music signal sources, and thus the mic signal is

superfluous. A 2W amplifier may seem extravagant for headphones, but power of this order is necessary when surrounded by, say, 110dBA of ambient noise. However, the resistor 'R' is determined so that at maximum volume, the level is safe for short term listening, though not necessarily comfortable! The autofader is an attenuator that reduces the music signal at a preset speed to a preset level when the microphone is used. "Fader on/off" shorts the autofader, allowing normal mixing of music and microphone signals. The line interceptor allows audio effects to be added, and when in the 'off' position (input and output terminals shorted), provides two extra line outputs, which are available for taping, monitoring or linking with another preamp.

Ceramic cartridges are ideal for disco use, in that they are robust and free from hum pickup problems, yet give good quality and can be safely used on high tracking weights (5g) to prevent the tone arm jumping.

Dynamic (moving coil) microphones are tough and relatively unidirectional, thus reducing the probability of acoustic feedback. They are eminently suited to all G. D. and PA applications.

Don't use vintage autochangers with tracking weights measured in ounces. These damage both records and styli, and lack the all essential cueing devices.

## Interference

The potential for troublesome levels of noise and hum is high in these applications. Amplification levels are very high, and bass heavy speaker systems are bound to emphasise hum. The use of quality components throughout is a basic step towards noise reduction. Carbon film, or better still, metal oxide resistors are recommended. Wrongly polarised or leaky electrolytics can be noisy while occasional cleaning of slider tracks and audio connectors with switch cleaning fluid is helpful. Freezer aerosols aid location of noisy components.

Hum is usually capacitatively picked up from stray AC fields. The solution is to totally screen all

internal wires carrying any AC currents, whether they be signal or mains currents. Directly radiated RFI will also be eliminated by these measures. Be extremely careful not to create more hum with earth loops. Earth connections should be made once only so that a common earthing point is made using a 'spider' arrangement of solder tags, to prevent earth currents interacting and causing instability.

## Hum pick-up

Inductive hum pickup is caused when two inductors interact magnetically, commonly a mains transformer and microphone transformer. This type of hum can be difficult to eradicate, and for this reason, magnetic cartridges and microphone transformers are best avoided for these applications—the latter is easily substituted for with a transistor matching preamp. If this is not possible, rotation of both inductors to find a point of minimal hum and maximum separation are helpful.

Instability, mains-borne RFI and RF pickup are all similarly dealt with by connecting a 100nF 1000V capacitor across the AC mains entry point and across the secondary transformer terminals. If the DC power line is longer than 150mm, connect 1000 $\mu$ F and 10nF capacitors in parallel. Add a series resistor of value 1-33k $\Omega$  as close as is practical to the base lead of all low-level silicon common emitter/collector configuration transistors only. Connect also a capacitor of 250-1000pF from base to emitter, again as closely as possible. Keep all wiring short, sliding

extra earthed braiding stripped from coax TV cable over low-level screened input cables in difficult cases. All metal within a unit must be earthed, but once only, to avoid hum loops and instability.

## Power supplies

Stabilised supplies are strictly unnecessary for use with a well designed power amplifier, especially when used with music and voice signals only. It is desirable to use an overrated transformer and large value smoothing capacitors (over 10,000 $\mu$ F), the former for reliability under overload conditions and the latter to eliminate hum and prevent HF instability. If the output of an amplifier drops excessively on the heavy signals previously outlined, then proper electronic stabilisation is advised, though large value smoothing capacitors and overrated transformers should also be used as a matter of course.

Bear in mind that for safety, all smoothing capacitors should be rated at 1.5 times the RMS value of the transformer winding, whatever the nominal voltage may be to which they are subjected. Also, large value capacitors can damage rectifiers with their initial charging current. In any case, the rectifiers should be overrated, more than the transformer, for they are less tolerant to overloading. If the transformer is 100 per cent overrated, and the rectifiers 200 per cent overrated, the power supply will survive most disasters!

Chokes can cure extreme cases of power supply

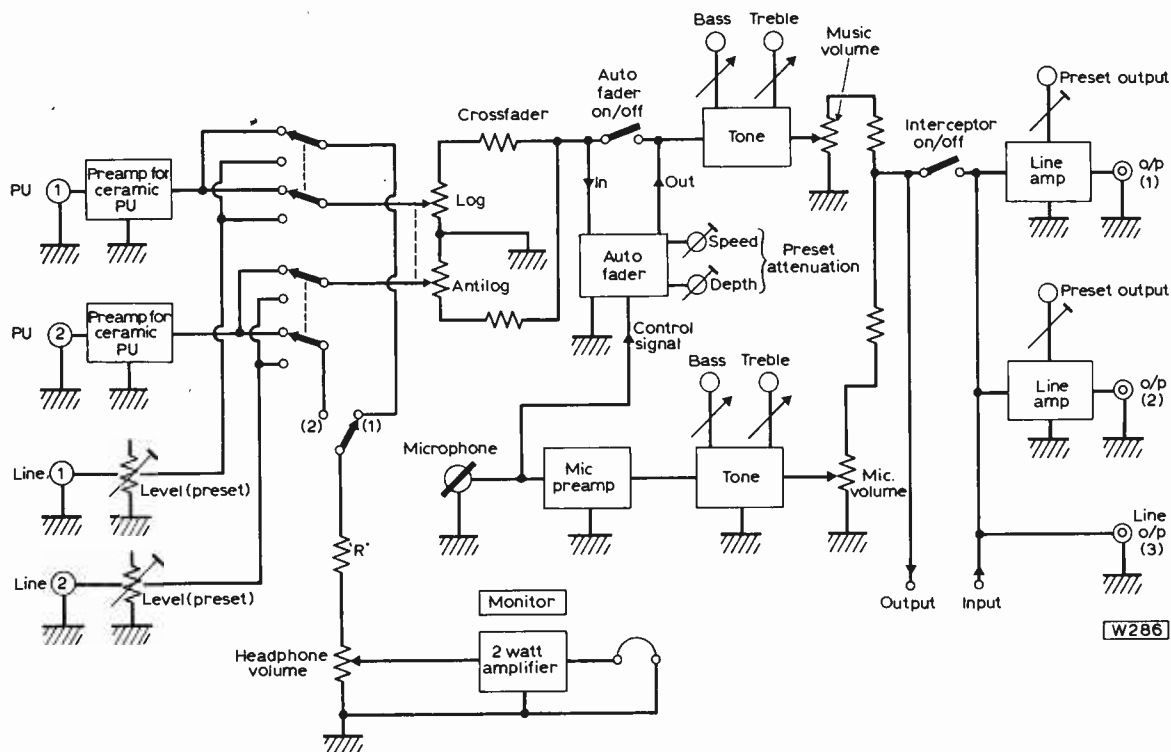


Fig. 4: Basic Disco pre-amplifier shown in block form. The Line inputs provide for additional input signals such as tape or phono.



hum, but should be screened and sited at least 150mm from other inductors to avoid transmitting inductively coupled hum along the power lines. The transformer must be well ventilated, and electrolytics should be mounted so as to remain as cool as possible. Ventilation slots in screening should not be in line with any non-screened circuitry, to avoid pickup of the leaking hum field.

## Lighting

Between them, discos and groups use four types of lighting: Music modulated (Sound/light), random, strobed and gimmickry (Oil wheel, light pipes, etc.). It is worth noting here that it is dangerous to use strobed light for more than a couple of minutes and it must never be the dominant lighting. 9Hz or thereabouts is the most dangerous frequency and can cause epileptic convulsions, even in normally healthy persons.

Any design utilising external signal inputs must incorporate a quality isolating transformer for safety. For RFI suppression, chokes of the same current rating as the control devices should be close wired in series with the live terminal of these. These can be made of about twenty turns of suitable heavy wire wound on an insulated ferrite rod. Connect a 100nF capacitor across the mains supply, and keep all mains and audio wiring short and screened. Triacs are generally better than thyristor control devices, as they give full wave control, thus twice the lighting output of the latter. They may be directly substituted into many designs, though a diac must be added in series with the gate connection.

Bear in mind the massive current surge when lots of cold lamps, exhibiting a very low resistance, have mains current initially applied via the control devices. Rather than overrate these, an alternative solution is to connect a switch across them. Before using the unit, the switch is turned 'on', so as to short the devices, and allow the lamps to warm up and attain normal resistance. This switch can also be used to switch in full lighting.

## Cable and bulbs

Electrical goods suitable for these applications can be obtained cheaply from wholesalers. 1mm<sup>2</sup> (10A) cable is suitable for most connections and is relatively cheap while rubber plugs and sockets, virtually indestructible, are essential for trailing connectors and extension leads. Low wattage bulbs (25-60W) are best for sound-to-light displays, where rapid response is essential, while the slower response rate of 100/150W spot bulbs is suited to strobe and random displays. Gelatine (Coloured, heat-resistant, plastic sheet, used for stage lighting) is indispensable, considering the astronomic cost and limited power of coloured bulbs. Though initially expensive its versatility is infinite, given a creative imagination, and it rapidly works out to be cheaper than coloured bulbs.

## Miscellaneous

Though standard jack connectors are universally used in G. D. & PA applications, DIN connectors are useful for multiple connections, and provision of

these and Cannon connectors would ensure compatibility with Hi-fi and studio professional audio equipment, if desired. Jacks should not be used for speaker connections, as they cause a momentary short circuit on insertion, which may well be sufficient to blow a fuse. It also increases the likelihood of a microphone, for instance, being plugged accidentally into the speaker socket! 4mm connectors (Banana) are ideal for speaker connections, though care is needed to avoid shorting, they are cheap, extremely tough, of low impedance, and unlike DIN loudspeaker connectors, are single pole, thus reversible if necessary.

Stereo is strictly unnecessary for disco systems, as apart from costing nearly twice as much as a mono counterpart, stereo separation on modern day singles is fairly poor, and few people at a disco would hear stereo separation anyway. On the other hand, discos are a lot to do with psychological impact, and effective multi-channel sound would be a welcome step.

Finally, I cannot overstress the goals of reliability, robustness and versatility, in that order. Bear in mind Murphy's law "If anything can possibly go wrong, it will"—and in the worst possible situation.

## Bibliography

Vibrasonic 25/50 Guitar amplifier Sept./Oct. 70 PW. (25/50W).

IC50 guitar amplifier Dec. 75/Jan. 76. PE. (50W).

### Loudspeakers

- (1) Sound and loudspeaker manual, No. BP.8. (Babani).
- (2) Hi-Fi loudspeaker enclosures, No. 146. (Babani).
- (3) Pickups and loudspeakers, John Earl (Fountain Press).
- (4) Hi-Fi loudspeakers and enclosures, A. Cohen (Newnes-Butterworths).

### Preamplification

Modular audio mixing system. Oct./Nov./Dec. 71. PW.

Reverb. unit (matches above system) Dec. 72/Jan. 73. PW.

Auto-fader. Nov. 73. PE.

I.C. Mixer. Oct. 74. PW.

### Lighting

"Tricolour". April/May/June. 73. PW. (Three channel Triac). June 74. PW. (Three channel thyristor). Dec. 75. PW. (Three channel Triac). Oct. 75. PE. (Two channel Triac).

Lighting effects unit. July 73. PE.

Party strobe. Nov. 73. PE.

Random lighting display. July 74. PE.

"Light pipe". Jan. 75. PE.

### General

(5) The audio handbook, G. J. King (Butterworths).

(6) Public address handbook, V. Capel (Fountain Press).

PW. stereo disco system. Dec./Jan. 75/76. PW.

(7) The use of microphones. A. Nesbitt (Focal Press).

(8) HiFi. PA, guitar and disco. amp design handbook, No. BP. 12. (Babani).

# PCB SERVICE FOR READERS

AM 0397

All boards, except SRBP, are glassfibre, drilled and roller-tinned

To:- READERS PCB SERVICES LTD, PO BOX 11, WORKSOP, NOTTS

Please supply PCB/s as indicated by tick/s in box/es

Issue	Project	Ref	Price P/P	
Mar 75	Electronic Organ (set of two)	AM0315 AM0318	7.56+25	<input type="checkbox"/>
Sep 75	Electronic Clock (set of three)	DN0795 DN0796 DN0797	2.40+15	<input type="checkbox"/>
Dec 75	Random Number Selector	DN0793A	0.98+12	<input type="checkbox"/>
Dec 75	Sound-To-Light Display	DN0798	1.15+12	<input type="checkbox"/>
Dec 75	12V PA System	DN2/JM	0.98+12	<input type="checkbox"/>
Dec 75	Disco System, Amplifier (2 required)	each AM0421	3.40+18	<input type="checkbox"/>
Dec 75	Disco System, Light Modulator	AM0423	2.70+18	<input type="checkbox"/>
Jan 76	Music Box	SRBP DN1/JM	2.25+18	<input type="checkbox"/>
		glassfibre DN1/JM	3.00+18	<input type="checkbox"/>
Jan 76	Emergency Light Unit	AM0419	3.50+18	<input type="checkbox"/>
Mar 76	CMOS Crystal Calibrator	AM0438	1.19+12	<input type="checkbox"/>
Apr 76	DF Receiver (set of two)	DN4/JM DN5/JM	1.92+15	<input type="checkbox"/>
Apr 76	Wobulator	AM0443	1.08+12	<input type="checkbox"/>
Apr 76	Auto. Slide Synchroniser	AM0441	2.33+15	<input type="checkbox"/>
June 76	Dig. Freq. Meter (set of 4)	4X A004	3.17+15	<input type="checkbox"/>
Jul 76	Transistor Tester	A002	2.08+15	<input type="checkbox"/>
Jul 76	Disco Pre-amplifier	A003	0.65+12	<input type="checkbox"/>
Aug 76	Cassette Player Power Supply	A001	0.65+12	<input type="checkbox"/>
Sep 76	Jingle Machine	A005	2.30+12	<input type="checkbox"/>
Sep 76	Capacitance Meter	A009	2.59+14	<input type="checkbox"/>
Sep 76	Octavia AF Source	A010	1.30+12	<input type="checkbox"/>
Oct 76	Jingle Machine, Mains Unit	A006	2.08+12	<input type="checkbox"/>
Oct 76	Digital Car Clock (set)	A001/2/3	2.08+12	<input type="checkbox"/>
Oct 76	Interwipe	DN8JM	0.80+12	<input type="checkbox"/>
Oct 76	Video-Writer (set)	D002/3/4/6 A007	19.44+35	<input type="checkbox"/>
Oct 76	Hazard Flasher	D005	0.76+12	<input type="checkbox"/>
Nov 76	Low Level Battery Indicator	A016	0.40+12	<input type="checkbox"/>
Nov 76	Electronic Thermostat	A017	1.30+12	<input type="checkbox"/>
Nov 76	Cirtest Probe	A018	0.48+12	<input type="checkbox"/>
Nov 76	Burglar Alarm	A019	0.50+12	<input type="checkbox"/>
Nov 76	DFM Pre-scaler PCB AO15 will be added to set of four DFM boards at no extra cost.			

Post and packing is for one board or set of boards. Prices include VAT  
Remittances with overseas orders must be sufficient to cover despatch  
by sea or air mail as required.

I enclose Postal Order/Cheque



ACCESS welcome.

No.....

Send card number only.



for £..... made payable to READERS PCB SERVICES LTD.

NAME.....

ADDRESS.....

Post Code.....

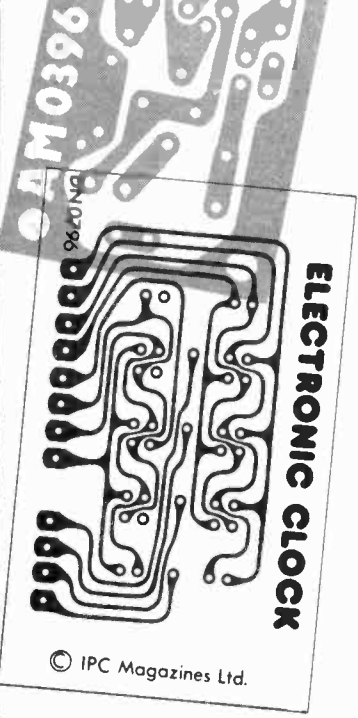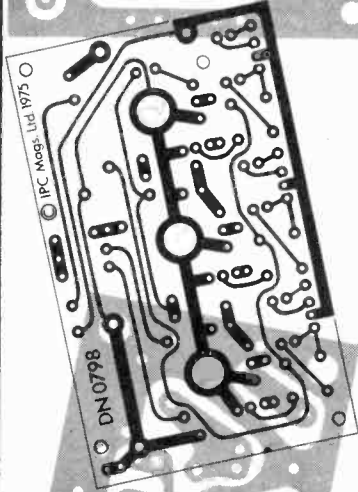Any correspondence concerning this service must be addressed to READERS  
PCB SERVICES and not to the Editorial offices.



# Vagaries of VHF (Contd.)

Ron HAM F.R.A.S.\*

WHEN it comes to propagation, June is a most unpredictable month; the only real certainty is that it is well into the sporadic-E "season" and that there will be disturbances to radio signals in the four to six metre bands. There is always a good chance (like this year) of fine hot weather, so, in June there should be days when the troposphere is "open", to answer the prayers of the 2m and 70cm DXers.

## SOLAR ACTIVITY

At midday on June 16th, 1976, the writer recorded a small burst of radio noise from the "active" sun, and that was the first for a month and more evidence of the sunspot minimum. Maybe it was a good thing that it was "quiet" in June because there were enough other upsets to orderly radio communication without the sun stirring the pot up a bit more.

## SPORADIC-E

It is convenient for the students of sporadic-E that so many east-European countries use parts of the four and six metre bands for their national broadcasting, while those same wavelengths are relatively quiet in the United Kingdom. This situation means that home receivers can be tuned to the frequencies used by these broadcasters with little risk of "local" station interference. It's tough luck for the amateur who uses the four metre band because when sporadic-E is present his tiny bit (70 to 70.7MHz) is blotted out with strong broadcast signals, mainly from Poland.

An average of 14 broadcast signals were heard for varying periods on June 12, 19, 20 and 28th. During the early evening of the 29th, an extensive sporadic-E manifestation enabled very strong signals from 39

of these stations to be heard with ease between 65 and 73MHz. At the same time a host of continental radio-telephone signals plus sundry automatic transmissions (beacons, printers, tones etc) were heard between 40 and 50MHz, causing interference to Band I television pictures, which, before the advent of UHF television, was a real pest around Wimbledon time.

The effects of sporadic-E manifestations were observed by the writer on nine days of the month (Fig. 1) and on each occasion strong pulses were received on the R1 vision channel (49.75MHz) and frequently, programme material was heard on the sound channel (56.25MHz). From experience the writer has found that the 50MHz region is most vulnerable to sporadic-E disturbances (even the minor ones not listed in Fig. 1) therefore the R1 vision signal is a most useful indicator as to the presence and extent of sporadic-E.

## TEN METRE BAND

The most persistent early warning for the short skip conditions which prevailed on the ten metre band (Fig. 1) was, and still is, the signals from the German beacon DLOIGI which was frequently heard at 599, and those from the beacon in Cyprus 5B4CY, which was heard less often, but it told the UK listener that the path was open between "G" and the Middle East. DLOIGI was heard on all of the 18 days indicated in Fig. 1 (12 early morning, 7 at midday and 9 early evening) while the signal from 5B4CY was heard 5 times (5, 7, 19, 22, 28th) in the early evening and once (29th) during the early morning. Both of these beacons are part of the International Beacon Project co-ordinated by the RSGB and reports of these signals are welcomed by the Society because these are the rewards that they,

June 76	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25	26	27	28	29	30
Solar																■														
Sporadic-E												■	■	■		■	■	■	■	■	■	■	■	■	■	■	■	■	■	■
10M beacons					■		■			■		■	■	■	■	■	■	■	■	■	■	■	■	■	■	■	■	■	■	■
Short skip				■					■		■	■	■	■	■	■	■	■	■	■	■	■	■	■	■	■	■	■	■	■
Tropo						■	■	■	■	■	■	■	■	■	■	■	■	■	■	■	■	■	■	■	■	■	■	■	■	■



W299

Fig. 1: The black squares show the days in June 76 when unusual atmospheric conditions were recorded by the writer at his home in Sussex. The various types of activity concerned are shown at the left.

and the beacon keepers, get for all of the voluntary work which they put into running the beacon service.

It is worth remembering that these beacon signals are also very good for checking the sensitivity and calibration of the home receiver, as well as for testing that new ten metre aerial.

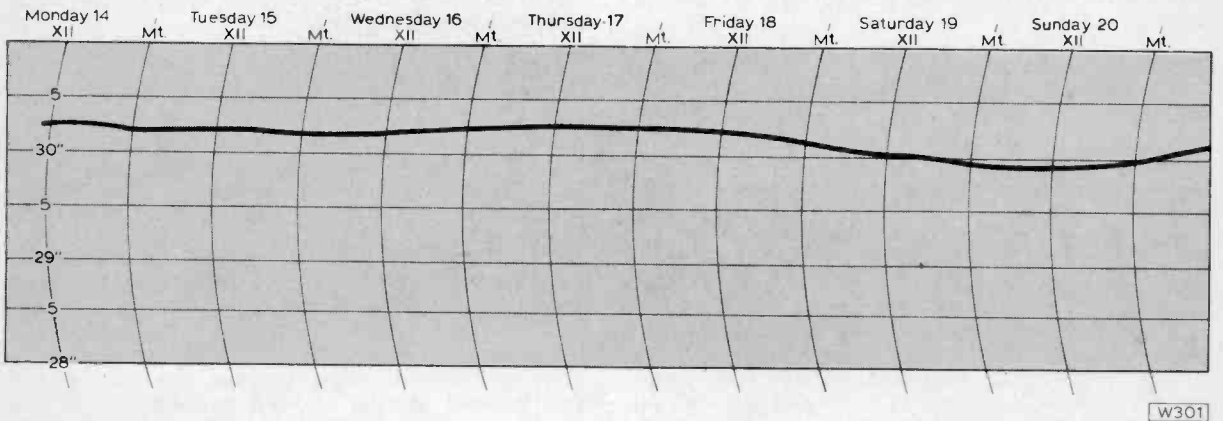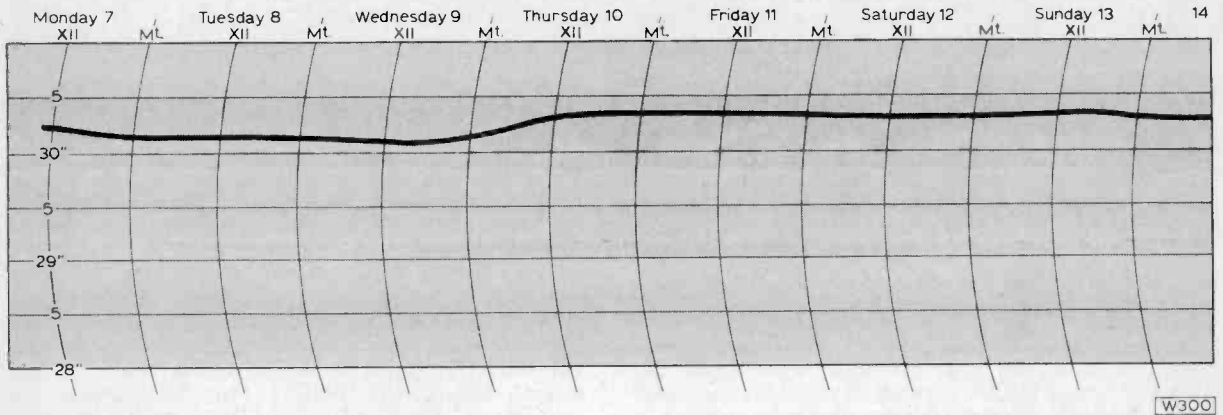*Figs. 2 and 3: The barograph charts for June 7 to 14 and 14 to 20 showing the changes in barometric pressure over that period. What may appear to be small changes in pressure can have a profound effect on the transmission properties of the troposphere. For example, the drop occurring on the 18th was responsible for an opening to the Continent on part of the VHF broadcast band.*



## TROPOSPHERIC

The atmospheric pressure recorded on the writer's barograph throughout June remained consistently high and only fell below 30in. (1016 mb) for about 24 hours during the week-end of June 19/20th. There were several slight changes lasting for a few hours at a time which were enough to "open" up parts of the VHF/UHF spectrum for short periods over a limited frequency range. A good example of this can be seen in Fig. 2. Note the slightly falling pressure early on the 12th; at 0635 GMT the writer logged strong signals from eight continental FM broadcast stations between 89 and 100MHz. A similar fall occurred during the evening of the 13th and at 1838 the writer heard nine continental broadcast signals in Band II. The pressure continued a slight decline and at 0735 on 14th, nine continental broadcast stations were again heard. None of these "extra" stations was heard while the atmospheric pressure was rising.

Reference to Fig. 3 will show a sharp pressure fall during the afternoon and evening of the 18th; at 1239 five continentals were logged between 95 and 100MHz and at 1800 13 continental broadcast signals

were heard between 89 and 100MHz. Band II was open periodically on 6, 7th and again during the early mornings of 12, 14, 15, 23, 24, 25, 26 and 29th and the evenings of 13, 18, 24 and 29th.

A good picture was received in Sussex on Channel 8 from the IBA transmitter in Lichfield, Staffs (with only a dipole) around 0800 on both 26 and 28th showing a path to the north on 189MHz. A UHF opening occurred early on the 26th when a very strong signal was received by the writer from the 70cm beacon at Sutton Coldfield (GB3SC), again with only a dipole feeding the receiver.

*\*Faraday, Greyfriars, Storrington, Sussex RH20 4HE.*

*Readers experiencing unusual reception of stations on the VHF/UHF bands of the nature described by Ron Ham in the first two articles are invited to send brief reports to him at the above address. NOT to the Editorial offices!*

*If there is sufficient response a regular feature could be compiled for inclusion in PW—Editor.*




**JOSTY KIT**  
**THE QUALITY KIT**  
 FOR THE AMATEUR AND PROFESSIONAL ALIKE  
**NEW KITS**  
 AT NEW LOW PRICES

JOSTY KITS ARE GUARANTEED FOR 12 MONTHS.


SEND FOR FREE CATALOGUE NOW AND ENJOY A NEW DIMENSION IN ELECTRONICS.

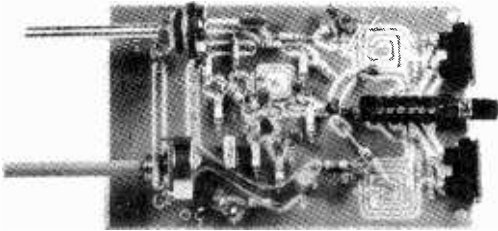**HF 305**      **\* NEW \***  
 VHF RADIO CONVERTER.




£ 6 · 70

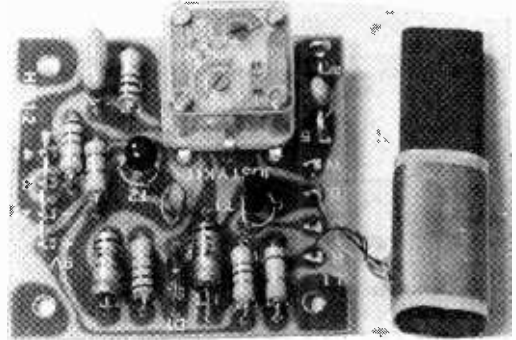**HF 61-2**      **\* NEW \***  
 TRANSISTORISED DIODE RECEIVER.




£ 4 · 30

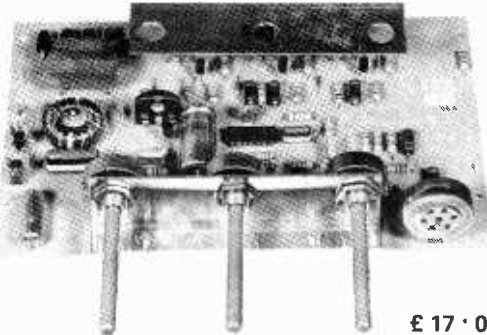**AT 365**      **\* NEW \***  
 3 CHANNEL PSYCHEDELIC LIGHT.



£ 17 · 00

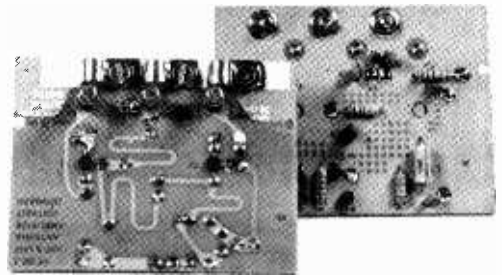**HF 385-2**      **\* NEW \***  
 VHF/UHF AERIAL AMPLIFIER.



£ 5 · 80

ALL PRICES INCLUDE V.A.T. — PLEASE ADD 25<sup>p</sup> P & P

POST THIS COUPON TO MAIL ORDER DEPT. :

JOSTYKIT UK LTD.  
 P.O. BOX 68.  
 MIDDLESBROUGH,  
 CLEVELAND, TS 1 4 BR.

NAME : .....

ADDRESS : .....

.....  
 .....  
 .....





Dear Sir,



## HF losses

I was surprised to see an old hand such as G2BCX advocating the use of Paxolin, PVC tape and even Sealastic for formers and sealants at frequencies of 144MHz. Being very lossy at frequencies well below 144MHz they could introduce a power loss of up to 3dB when used in combination. PTFE is ideal but Nylon 66 would be preferable to Paxolin for formers. For protection of the loading coil and open ends of co-ax, Polystyrene cement is a very much better material than Polyurethane varnish and sealastic is almost worse than nothing.

As to his statement that the standard 0dB reference radiator is a dipole, I would refer him to Antennas by Krauss, F. E. Terman and others. The standard reference for gain and field strength effective radiated power, etc., is the unipole, i.e., the common quarter wave radiator.

J. Bradbury G3AVR (Hayes).

## The young idea

I have been a DXer of the SW broadcast bands ever since I was just 14 (I am now almost 16). I would like to add my views to your mail concerning the subject of CB radio.

If carefully controlled, CB radio could provide a great boon for example, to house-bound people and unlike the USA, I consider that full power operation on CB should be made available to young people if a UK citizens band comes about. Perhaps even putting aside several channels exclusively for people under 18, to prevent the entire band being

totally jammed up by us or adults.

I too feel that SSB is essential, in these days of crowded frequencies, also if we are starting at the beginning then we may as well make the best possible use of the space. Perhaps though, one channel could be set aside for use by low power AM walkie-talkies.

To all the Hams—in particular Mr. Dowdeswell in his August "On the Air" column, who appears to be against CB, I would like to say something. What about the people who just are not interested in technical matters? Some people just want it for company—especially the elderly and infirm. All they want is somebody to talk to—which is in my opinion what CB is about—just pure communication, nothing technical.

If as I hope we get CB then there is one thing we must have. Strict control. We must not learn too late as the Americans did, but control it from the beginning. We must get the "pirates" before they start, not when they are in full swing. **Simon Hicks** (Swindon).

## More amateur gear

I am in agreement with your Editorial completely as the education of the young is a most important feature of your task. The PCB service which you have introduced is really excellent in its concept, I have used it, the service is very good and I will continue to use it.

I have been a Licensed Radio Amateur for many years and very much regret the changes that have taken place. The use of so much foreign made apparatus is a matter to be very much deprecated. The reasons are:

(1) Self training, the spring-board of Amateur Radio is grossly diminished.

(2) Foreign imports are increased.

You have a public duty to form opinion and direct it the right way, it is important to satisfy the reader of course, but I suggest that to lead and direct in the right direction, to increase the quality and number of persons who are concerned about Electronics, Telecommunications, etc, is a fine ideal.

Naturally my interest is in

Amateur Radio, and to this end I would welcome in the space allotted in your magazine more sophisticated PCB apparatus to suit my tastes.

It was a pleasure to see in your Editorial excellent concepts with fine ideals. **David Foster G3KQR** (Tolworth).

## Please repeat

I read, with interest, the comments by E. Watt (Kidsgrove) (September 1976 issue *PW*) with regards to "channelised/mobilised debris" found occupying 2m today.

His vast knowledge concerning the take over of the band by FM repeaters seems devoid of the true reasoning behind the use of repeaters.

Their prime purpose is to ensure a reliable communication link between MOBILES. Granted, there often appears more fixed stations using them, but let us not forget the true objective.

No doubt his idea of true mobile communication is 100 AM QSO's on 145 (the good?, old days).

His remarks about the frequencies being used by the repeaters.

Let us consider: 5 repeater channels are at present in use (R<sub>3</sub>, R<sub>4</sub>, R<sub>5</sub>, R<sub>6</sub>, R<sub>7</sub>) with, say, 12½kHz frequency "windows" for input and output,

Total  $5 \times 12\frac{1}{2} \times 2 = 125\text{kHz}$  in a band 1.35MHz wide (excludes CW, SSB and Oscar bands).

If he cannot find room in the 1.225MHz remaining (over half allocated band) what a poor system he must have.

Please do not think I am all for repeaters and repeater working, I very rarely use them, but I would not remove the chances of those who do and enjoy doing so.

As regards 4m, has he seen the new CHANNELISED band plan, which after the World Radio Conference in 1979 may be meaningless anyway? **P. Salisbury G78KSF** (Wrexham).

## Entranced by a frog!

Since time immemorial, I have been going to suggest that a feature be included, dealing with

the various problems encountered in servicing and construction, but have never done so, because I realise that very few of these have anything like universal interest. To say "since time immemorial" may be a slight exaggeration, but when I had made the Scott-Taggart Four in nineteen hundred and—when was it?—I had already two three-valve receivers "under my belt". What a marvellous set that was; at 4 a.m. I once received Pittsburgh on MW, using a very queer aerial erected in our back yard, in the shape, I suppose, of an irregular trapezohedron, in a youthful attempt to get out as much wire as possible.

In passing, I should like to reply to your correspondent Alexander Dodd (letters, September 1976), who so eloquently laments the passing of the thermionic valve. I think he is right to do so, but Wireless Telephony is Wireless Telephony, whatever apparatus it employs. Much as I like the valve, I have to admit that in almost every respect solid state devices are far superior. It would be absurd for Practical Wireless to dwell in the past, and become a journal for antiquarians.

However, one problem that I do have, is the removal of the enamel insulation from copper wire of 30 SWG or thinner. I have tried burning it off, but the wretched wire itself disappears. I have tried careful scraping with a knife, but the result is a number of tiny lengths of wire, an interesting result, but unproductive. There must be some chemical dip which could be used, if only one knew. Then there is fine Litz wire. It is essential, we are told, to solder every strand. This means that each one must have its covering removed. I have tried, but have little skill in this subminiature kind of knitting. Can anyone give me the answer? In spite of my terrible problems, I must say how much I have enjoyed fifty years of radioactivity, and Practical Wireless.

In the winter of 1924, my sister and I came home from school to find Dad bending over a strange contraption in a corner, on which were two brightly-glowing lamps. Without a word, he separated a pair of headphones, and gave us one each. I was entranced. I heard a woman singing "A Frog he would awoing go", and my father said it was from Man-

chester, fifty miles away. I have never forgotten the magic of that moment. What a wonder that was—and still is.

In many ways sound radio is more remarkable than TV, though less complicated. One has only to look up at the night sky to realise that the unaided human eye can see distances millions of times greater than the human ear can encompass by itself. It is indeed a great wonder, and modern inventions are daily making it more so.

My thanks to Practical Wireless for playing such an important part in my electronic education, and helping me on my way. Long may it flourish. **Howard Padmore** (Blackpool).

### Low-down on peaks

It was disappointing to read Lionel Howe's Editorial (August issue) "Hear Hear?" *Practical Wireless* does not pretend to be in the Hi-Fi bracket, but your Editor does betray some ignorance of what is true High Fidelity. Part of the reason for high output concerns headroom (never heard of it?).

It is well known that a typical domestic set up delivering an average programme level of 1W would be required to deliver 50W in order to avoid clipping at transient peaks. Most of the rubbish which appears at £26.25 is cramped at best, is highly selective about loads and inputs, and very high on distortion! If the editor is happy with that state of affairs—he ought not to inflict the paucity of his hearing on others. There's nothing wrong with aspiring to heights, providing one knows to what one is aspiring!

Just listening is a fair test, but the difference between poorly designed equipment and the best is incredible. If the Editor would care to compare any reasonable amplifier (at £26.25) with say the Naim 160, I'm sure he will appreciate the difference in "musicality".

I am sure the time has come when specifications are virtually meaningless to the majority, but they do have their uses! I am all for a little education, but your Editorial is very backward looking.—**J. C. Nuttall** (Worthing)

### Disgusted

Perhaps I may be allowed to say a few words about your comments concerning the letter "You've Been Warned" by T. W. Hillyard.


As a citizen in a supposedly free society I found it extremely distressing that you should condone what amounts to legalised theft and attempted theft by a government department. Please let me state now that I agree that Mr. Hillyard should have been fined and his "transmitting" equipment confiscated, but the taking of other domestic electronic equipment is a gross infringement of civil liberties.

The state is far too fond of exceeding its authority in respect of individual liberties and for a person such as yourself in a most responsible position to condone this action leaves me with a feeling of disgust. One cannot be expected to respect the law unless one manifestly sees it as open, fair and just. **R. Morgan Lloyd** (Spalding).
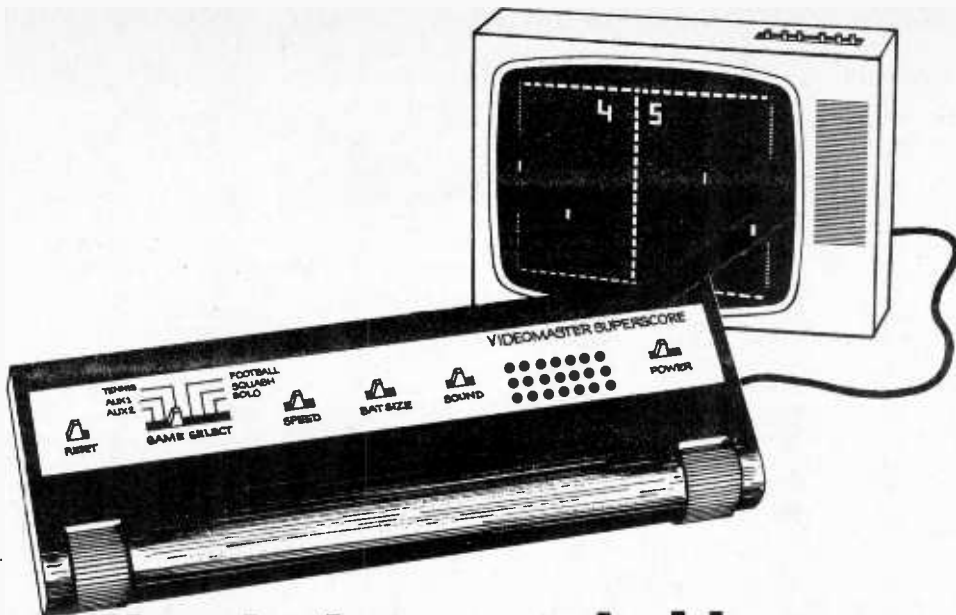
### Err-well!

I refer to the report published in the September issue of *PW* on the Exhibition of Civilian and Military Radio. It stated on page 429 that BBC approval for a piece of radio equipment had to be obtained first, before a constructors licence could be issued in 1923. This is not so. The true facts are that this rare licence covered the home construction of any apparatus, but theoretically one was not supposed to listen to BBC broadcasts with it. It covered experiments under the Wireless Telegraphy Act 1904.

An ordinary BBC stamped licence was issued for listening to BBC and other programmes with a receiver purchased with a BBC transfer on, and made by firms who were members of the British Broadcasting Co. Ltd. However, most enthusiasts listened to anything on the air, from the true transmitting Hams on 10W to KDKA and WJX. The air at this time was reasonably clear, apart from reaction whistles for long distance reception. **C. E. Largent** (Worthing) ("Old Timer" — 40 years Hon. Sec. Ilford and District Radio Soc. Ex. 20T, 20U, 30U).



# Here's the remarkable new **VIDEOMASTER™** Superscore Home TV Game Get it together for only **£24.95**

Available to you in kit form at the same moment as its national launch, the brilliant new Videomaster Superscore contains the latest product of MOS technology: a TV game chip.

The logic contained in it had previously to be generated by 100 TTL devices. Now it is condensed into one 28-pin chip.

This all-new Videomaster plugs into your 625-line UHF TV set (for overseas customers having VHF sets we can supply the necessary VHF modulator) to give you four exciting games (including tennis and football) and two future game options. It features on-screen digital scoring, realistic hit sounds, two bat sizes, two

ball speeds, automatic serving and much more. It runs on six 1½ volt SP11 type batteries (not supplied).

The Videomaster Superscore kit costs only £24.95 including VAT (recommended retail price of the ready built model is over £40.00) and comes complete with ready-tuned UHF or VHF modulator, circuit board with printed legend, all resistors, transistors and diodes, built-in loudspeaker, socket for mains adaptor, and, of course, the TV game chip itself.

Easy to put together the Superscore has full assembly instructions, circuit diagram and circuit description. Don't miss this chance to own the newest electronic game at such low cost.

**POST TODAY TO:**

**Videomaster Ltd** 14/20 Headfort Place, London SW1X 7HN



Please send me (insert No. requ'd).....Videomaster Superscore Kits at £24.95 (inc. VAT & P&P in UK) or £23.10+£4.00 for P&P overseas)

I enclose my cheque/money order\* for £.....

VHF modulator required YES/NO\*

PWT7


NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

ALLOW 21 DAYS FOR DELIVERY

\* delete as necessary

## INVERTORS

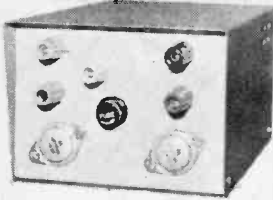

240v-50Hz from your 12v car battery  
 25 watt-£4.75      300 watt (12v)-£33.08  
 40 watt-£8.27      400 watt (24v)-£39.05  
 75 watt-£12.03      500 watt (24v)-£48.18  
 150 watt-£21.27      1 Kw (50v)-£127.00  
 300 watt (24v)-£28.45      1.5 Kw (110v)-£140.80

All above Invertors are in kit form but may be purchased built up in metal case and ready for use. Price list sent on receipt of s.a.e. Prices include p. and p.

### P.W. AUTOMATIC EMERGENCY SUPPLY

240v-50Hz-150 watt inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 72 P.V. Complete kit of parts (excluding meter) £24.50 plus £1.70p.p.


### FLUORESCENT LIGHT INVERTER KIT

8 watt-12v-Fluorescent light, suitable for tents, caravans, houses, boats and secondary lighting for factories, hotels, etc.  
 12"-3 watt £3.90 + 35p p. & p. Built up £4.90 + 35p p. & p.  
 21"-13 watt £4.20 + 52p p. & p. Built up £5.80 + 52p p. & p.

### TRANSFORMERS AND COILS

Both high volume and small order capacity available.  
 Special offer. Miniature mains transformer 6-0-6v-6VA. 85p + 10p p. & p.

## P.E. ORION STEREO AMPLIFIER

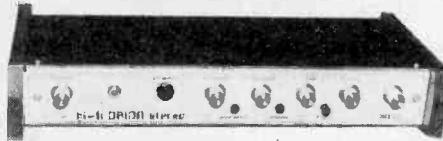

20 + 20 Watts r.m.s. into 8 ohm load. Distortion less than 0.01% 100Hz-10kHz. Frequency response  $\pm$  1dB 20 Hz to 20kHz. Hum level virtually nil with volume full on.

This is a power amplifier of superb quality incorporating the very latest design features. Professional hi-fi enthusiasts have classed it as fantastic and real value for money. The CCT incorporates a low flux transformer and inputs for disc, tape, tuner, etc.


Complete kit of parts including slim line bookend case, silk screened front panel and knobs £47.30 inc. VAT and p. & p.

The bookend case, I.C.'s and semiconductors, P.C. board, Transformer, etc. may be purchased separately if desired. Send S.A.E. for further information.

### INSTRUMENT CASES

Bookend Amplifier and attractive styled Instrument Cases available. Send S. and A. envelope for Price List.

## ASTRO IGNITION

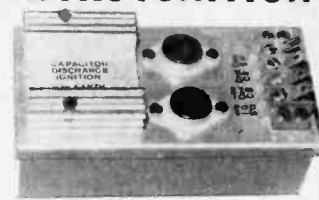

**ASTRO IGNITION SYSTEM**  
 Complete kit of parts for this proven and tested system £10.45 inc. VAT  
 Ready built with only two connections to alter £13.75 inc. VAT.  
 Thousands have used this system both home and abroad. Consider these advantages—more power, faster acceleration, fuel economy, excellent cold starting, smoother running, no contact breaker burning. Also because of the high energy spark the fuel mixture can be made weaker giving further economy and fewer plug problems. Fitting time when built 5 minutes approx. Please state whether positive or negative earth.

TRADE AND EXPORT ENQUIRIES WELCOMED ON ALL PRODUCTS

**ASTRO ELECTRONICS**  
 Springbank Road, West Park  
 CHESTERFIELD. 31475

# B. BAMBER ELECTRONICS

Dept PW, 5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE  
 Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

### PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

**FREE WELLS 25W (SP25) SOLDERING IRON** (worth £3.24 inc. VAT) with all orders over £25. Limited period only. Send now.

**VARIABLE STABILISED POWER SUPPLY**, mains input, 0-24V output, stabilised and current limiting at 500mA + 32V at 50mA. Brand new by British manufacturer. Size approx. 7 1/2 x 2 1/2 x 4 in. complete with external 5A/3-turn pot for voltage control. Connection data supplied. £7.  
 50µA (25-75µA) **EDGEWISE METERS**, modern type by Sangamo Western, display area 1/2 x 1 1/2 in with 2 mounting lugs. (Can be zeroed left or right hand) £1.50 each, while stocks last.

**MAINS ISOLATION TRANSFORMERS**, Tapped mains input, 240V at 3A + 12V at 500mA output. New, boxed, made by Gardners, £12.

**FLEXIBLE HEATER STRIP**, 240V a.c., 150W, approx. 1 metre long (insulated with fibreglass) with mains connector block. Many, many uses. 60p each.

**HEAVY DUTY RELAYS**, 24V d.c. operated (will work on 18V) 3 heavy duty make contacts (around 10A rating) + 4 change over contacts + 1 break contact. New, complete with mounting bracket (ideal for switching HT on Linears.) Many uses for this high quality unit. £1.50 each.

Good Quality Pressure Gauges, 2 1/2 in dia. flange mounting, 3 models avail, 0-60 lb/sq. in, 0-100 lb sq. in, 0-200 lb/sq. in. state which £1.25 each.  
 2N3555 type Transistors, O.K., but unmarked, 5 for £1.

**110V NEONS, SCREW-IN-TYPE**, 4 for 50p.  
**SLOW MOTION MOTORS** (suitable for programmers, displays, etc.) 230-240V a.c. input, rotation between 1 and 2 revs per minute. £1.25 each.

**MINIATURE PLIERS** High quality "Crescent" made in USA. £4.35 + VAT (35p).  
**SIDE CUTTERS**, high quality "Crescent", made in USA. £4.45 + VAT (46p).

**MIXED COMPONENT PACKS**, containing resistors, capacitors, switches, pots, etc. All new (random sample bag revealed approx. 700 items). £2 per pack, while stocks last.

**TUNED COILS**, 2 section coils, around 1MHz, with a black smart tuning knob, which moves an internal core to vary the inductance, many uses, easily rewound, 3 for 50p.

**HIGH QUALITY SPEAKERS**, 8 in x 6 in elliptical, only 2in deep, inverse magnet, 4 ohms, rated up to 10W. £1.50 each or 2 for £2.75 (qty. discount available - 12 1/2% VAT).

TO3 transistor insulator sets, 10 for 50p.

**MINIATURE 2 PIN PLUGS AND SOCKETS** (fit into pin hole, pins enclosed, with covers for chassis mounting, or can be used for in-line connectors). Bargain pack of 3 plugs + 3 sockets + 2 covers, 50p.

**PROGRAMMERS** (magnetic devices). Contain 9 microswitches (suitable for mains operation) with 9 rotating cams, all individually adjustable, ideal for switching disco lights, displays, etc., or industrial machine programming. (Need slow motion motor to drive cams, not supplied) 9 switch version £1.50.

**HEAVY DUTY HEAT-SINK BLOCKS**, undrilled, base area 2 1/2 in x 2 in, with 6 fins, total height 2 1/2 in 50p each.

**SPERRY 7-SEGMENT P.G.D. DISPLAYS**, digit height 0.3 in red, with decimal points, 150V to 200V (nominal 180V) operation. These are high-volt industrial type and therefore brighter than normal displays. All brand new. AT THE BARGAIN PRICE OF 50p PER DIGIT. TYPE 332 (two digits in one mount) £1 each. TYPE 333 (three digits on one mount) £1.50. (Sorry, no single digit available!) Data Supplied.

BSX20 (VHF Osc/Multi), 3 for 50p.

BC108 (metal can), 4 for 50p.

PBC 108 (plastic BC108), 5 for 50p.

BFY51 Transistors, 4 for 60p.

BCY2 Transistors, 4 for 50p.

PNP audio type TO3 Transistors, 12 for 25p.

BF152 (UHF amp/mixer), 3 for 50p.

2N3819 Fet., 3 for 60p.

BA121 Varicap Diodes, 4 for 50p.

1N514 diodes, 10 for 25p.

**SMALL MAINS SUPPRESSORS** (small chokes, ideal for radio, Hi-Fi inputs, etc.) approx. 1/2 in x 1 1/2 in, 3 for 50p.

**PERSEUS TUNER PANELS** (for FM Band 2 tuners) marked 88-108 MHz and Channels 6-70, clear numbers, rest blacked out, smart modern appearance, size approx. 8 1/2 in x 1 1/2 in, 2 for 35p.

Lead suppressors (10k ohm) for mobile plug leads, 4 for 50p.

**ALU-SOL ALUMINIUM SOLDER** (made by Multicore). Solders aluminium to itself or copper, brass, steel, nickel or tinplate, 16 a.w.g., with multicore flux, with instructions. Approx. 1 metre coil 50p pack. Large reel (approx. 12 metres) £2.75.

1 1/2 in polythene chassis mounting fuseholders, 6 for 30p.  
 I.C.'s, some coded, 14 DIL type, untested, mixed, 20 for 25p.

Mobile Converters, 24V DC input 13.8V at approx 3-4A DC output, fully stabilised, £3.50 each (ideal for running 12V car radio from 24V lorry battery).  
 R/S Midget 3 pole 4 way, rotary switches, 40p each.

We now stock Spralux Tools for the electronic enthusiast: Screwdrivers, Nut Spanners, SA and Metric sizes, pop rivet guns, etc. S.A.E. for list.

I.F. Cans, 1/2 in square, suitable for rewind, 6 for 30p + 12 1/2% VAT.  
 Miniature earphones with min. jack plug, 2 for 50p + 12 1/2% VAT.

**TWIN I.F. CAMS**, approx. 1 in x 1/2 in x 1 in high, around 3-5 MHz, 2 separate transformers in 1 can, internally screened, 5 for 50p + 12 1/2% VAT.

Dubilier Electrolytics, 50µF, 450V, 2 for 50p.  
 Dubilier Electrolytics, 100µF, 275V, 2 for 50p.  
 Plessey Electrolytics, 470µF, 63V, 3 for 50p.

TCC Electrolytics, 1000µF, 30V, 3 for 60p.  
 Plessey Electrolytics, 1000µF, 180V, 40p each (3 for £1).

Dubilier Electrolytics, 5000µF, 35V, 50p each.  
 Dubilier Electrolytics, 5000µF, 50V, 60p each.  
 ITT Electrolytics, 8800µF, 25V, high grade, screw terminals, with mounting clips, 50p each.

Plessey Electrolytics, 10,000µF at 63V, 50p each.  
 Plessey Cathodray Capacitors, 0-0-4µF at 12-15k DC. Screw terminals, £1-50 each.

**PLEASE ADD 12 1/2% VAT TO ALL CAPACITORS**

**A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES, S.A.E. FOR LIST.**

### PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

**TV PLUGS AND SOCKETS**  
 TV Plugs (metal type), 5 for 50p.  
 TV Sockets (metal type), 4 for 50p.  
 TV Line Connectors (back-to-back sockets), 4 for 50p. Please add 12 1/2% VAT.

**PLUGS AND SOCKETS**  
 N-Type Plugs 50 ohm, 60p each, 3 for £1-50.  
 N-Type Sockets (4-hole chassis mounting), 50 ohms (a small coax lead type), 50p each.  
 PL259 Plugs (P.T.F.E.), brand new, packed with reducers, 85p or 5 for £3.  
 SO238 Sockets (P.T.F.E.), brand new (4-hole fixing type), 50p each or 5 for £2-25.  
 25-way 15EP Plugs and Sockets, 40p set (1 plug + 1 socket).  
 Plugs and sockets sold separately at 25p each. Bulgin Round Free Skis, 3 pin, for mains input on test equipment, etc., 25p each.

**WELLS SOLDERING IRONS**  
**EXPERT**, Built-in spotlight illuminates work. Pistol grip with fingertip trigger. High efficiency copper soldering tip.  
**EXPERT SOLDER GUN**, £8.90 + VAT (54p).  
**EXPERT SOLDER GUN KIT** (spare bits case, etc.), £8.90 + VAT (78p).  
**SPARE BITS**, PATENT + VAT (2p).  
**MARKSMAN SOLDERING IRONS**  
 SP15D 15W £3 + VAT (24p)  
 SP25D 25W £3 + VAT (24p)  
 SP25DK 25W + bits, etc. kit £3.85 + VAT (31p)  
 SP40D 40W £3.44 + VAT (28p)  
**BENCH STAND** with spring for Marksmans Irons, £2.22 + VAT (18p).

**SPARE BITS**  
 MT8 for 15W, 48p + VAT (4p).  
 MT4 for 25W, 38p + VAT (3p).  
 MT10 for 40W, 42p + VAT (3p).  
**TCP1 TEMPERATURE CONTROLLED IRON**, Temperature controlled iron + PSU, £20 + VAT (£1.60).

**SPARE TIPS**  
 Type CC single flat. Type K double flat fine tip. Type P, very fine tip, £1 each + VAT (6p).  
**ALL SPARES AVAILABLE**

**MULTICORE SOLDER**  
 Size 5 Savbit 18 s.w.g. in alloy dispenser, 32p + VAT (3p).  
 Size 12 SAVBIT 18s w.g. in plastic reel £1-80 + VAT (15p).

Terms of Business: CASH WITH ORDER. MINIMUM ORDER £1. ALL PRICES INCLUDE POST & PACKING (UK ONLY). SAE with ALL ENQUIRIES Please. PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN. CALLERS SATURDAYS ONLY 9.30-12.00, 1.30-5.00.



# in this month's issue

# TELEVISION

## ● REMOTE CONTROL UNIT

The latest development by Alan Willcox in his series of remote channel change control units is a version requiring minimum connections and modifications to the TV set. In consequence the receiver section can either be built into or stood on top of the set. A new simple ultrasonic transmitter makes use of a timer i.c. while LEDs give channel indication.



## ● VIDEO CIRCUITS FOR THE EXPERIMENTER

Since building a solid-state monochrome receiver four years ago Luke Theodossiou has tried out in it a number of different video output circuits. The course of this development is traced and the advantages of the various circuits described.

## ● SERVICING FEATURES

John Law describes the Indesit T12LGB portable and its faults, Dewi James describes some interesting faults recently encountered on a variety of models and there's more from Les Lawry-Johns on the Philips K70 colour chassis.

## ● GRUNDIG COLOUR RECEIVERS

Andy Denham relates his experiences in servicing the first Grundig solid-state chassis – the 5010/5011 series. This is the first time we've looked at faults on a chassis using a thyristor line output stage.

## ● THE SONY U-MATIC VCR

Start of a detailed look at the signal and servo techniques used in this well known VCR.

**PLUS ALL THE REGULAR FEATURES**

*on sale OCTOBER 18th,*

# PRODUCTION LINES

bill tull

## NEW RANGE FOR LEAK

New from Rank HiFi is a range of Leak equipment called the 3000 Range. There are four loudspeakers featuring time delay compensation, 35 and 25 watt tuner amplifiers, an 80 watt amplifier, a belt driven turntable and a pair of head-phones using an improved form of the isodynamic principle. The 2075 loudspeaker continues having established itself at the top of the loudspeaker market.

Holography has been used extensively in the development of this new range of loudspeakers and in particular in the design of the treble unit, which is common to all four loudspeakers.

Rank HiFi has aimed this new range at the knowledgeable enthusiast, one who is capable of appreciating technical excellence coupled to a good appearance design and who expects reliability.

## Leak 3000 Range of Loudspeakers

Embodying the latest research and production techniques of the engineering team at Bradford, these



four 8-ohm designs mark a radical departure from previous Leak acoustic products for the following reasons:—

The subjective effect of such a time delay compensated system is subtle, but nevertheless demonstrable. When listening to a single loudspeaker an improvement occurs in perceptual depth and transparency of the sound image, adding a further degree of realism. The effect in stereo is a greater spatial effect and feeling of depth, where one listens through the loudspeakers instead of to them. This gives a more accurate construction of stereo images in the sound field.

A far greater design effort has been applied to the appearance of this range than to previous Leak ranges.

All the new drive units have plastic cones or diaphragms and the physical relationship between the drive units

in space is accurately preserved by the use of a moulded polyurethane foam front baffle.

Due to a greater understanding of Doppler distortion, intermodulation distortion, delayed resonance and the design of crossovers it has been possible to extend the operating frequency range of the bass units into mid frequency areas. The engineering team has been particularly successful in measuring these distortions, especially with regard to their audibility.

The four designs in the Leak 3000 Range of loudspeakers will be offered in teak with black grill covers. The estimated selling prices are expected to be in the region of (per pair):

3020	£90
3030	£125
3050	£175
3080	£262

Rank HiFi, P.O. Box 70, Great West Road, Brentford, Middlesex, TW8 9HR.

## AIR BLAST CLEANER

Available from importers Pelling & Cross Ltd., is a very useful cleaning device for the hi-fi and electronics enthusiast. Dust-Off is a 14oz. can containing a liquified gas (freon) which emerges as a pressurized, super dry but inert gas, capable of dislodging even well ingrained dust and oxide from delicate tape recorder mechanisms, tape heads, and record styli without the danger of creating static by conventional forms of wiping or brushing.


The cost of the initial Dust-Off can and trigger nozzle is £8.57 inclusive of VAT, plus post and packing at 65p. Flexible extension nozzle £1.49 plus post and packing 35p. For further information please contact *Peter Recklin, Pelling & Cross Ltd., 104 Baker Street, London W1. Tel: 01-487 5411.*

## EAGLE ALARMS

A new range of fire and burglar alarms introduced by Eagle International of Wembley, Middlesex meets the need for moderately priced automatic security systems in homes, schools and offices.

For the detection of intruders Eagle market two alternative alarms AB10 and AFB15. The AB10 is a door or window alarm with key and magnetic sensor switch. It is very simple to install and incorporates an instant/delay action switch which allows setting of the alarm without triggering siren. The AB10 is also suitable for use on car doors.

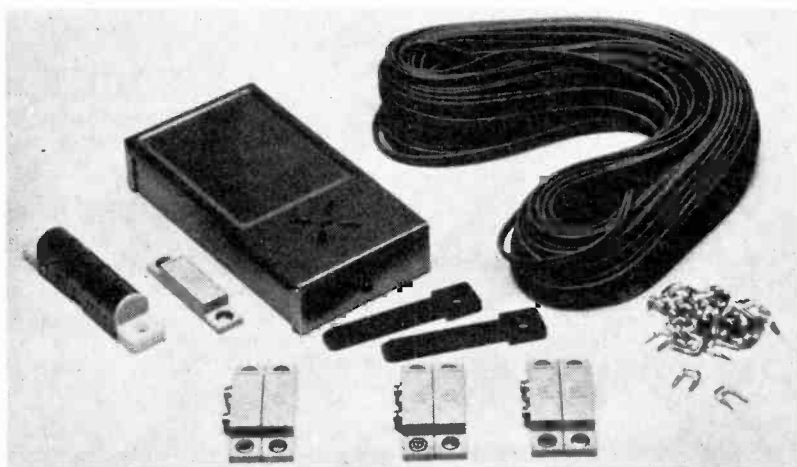The AFB15 (illustrated) burglar/fire alarm employs the same master unit as the AB10, but has three remote detectors, one fire detector, plus plenty of cable, staples and self adhesive pads. *Eagle International, Precision Centre, Heather Park Drive, Wembley, HA0 1SU.*



## NEW HEATHKIT CAT.



Shown for the first time in the new Heathkit catalogue are: an AC voltmeter, X-Y chart recorder, IM distortion analyser, harmonic distortion analyser, amateur radio receiver, triple-output power supply and digital electronic floor and shelf clocks. Also included are details of a 'Big Ben' electronic chimes. Free catalogues may be obtained from *Heath (Gloucester) Limited, Gloucester, GL2 6EE.*

## BIB KIT

Four useful accessories have been put together to make up a new Bib kit ref. 104. They are: cassette storage tray which holds ten cassettes and includes self-adhesive pads for wall-fixing, a Bib Fast Hand Winder, a cassette head tape cleaner, a pack of 20 cassette and 10 library case replacement labels. Price is £2.81 including VAT and this kit is ideal for owners of cassette machines. *Bib HiFi Accessories Ltd., P.O. Box 78, Hemel Hempstead, Herts., HP2 4RH.*



## DECIMO WATCH

With their digital watch Decimo have gone 100% for liquid crystal display. Not only are the digits large enough for all ages to read, but they are constantly displayed and a battery lasts about 18 months as opposed to about six months for the LED electronic type watch.

"The Blue Max is the name they have chosen for their watch. It was of course the name of the famous medal given for extraordinary acts of bravery and achievement in the First World War. Only officers were eligible to receive it. Later it was extended as an award for the highest achievement in the arts and sciences." Price is £49.95. Further information from: *Douglas A. Dorsett—Managing Director, Decimo Limited, Park House, Chobham Street, Luton LU1 3BS, Bedfordshire. Tel: Luton 38881.*



## PERIPHERAL

A peripheral printer which broadens the usage of TI handheld programmable calculators has been announced by Texas Instruments. The new PC-100 print cradle now allows any TI hand-held programmable calculator to become a desktop printing calculator.


When the calculator is locked into the cradle, the user is able to print anything shown in the display or print the step-by-step execution of a program. Programming the calculator becomes simplified, because the "list" feature of the PC-100 will print out program lists for editing, and the "trace" mode provides a complete audit of every step in program execution.

The PC-100, has a suggested retail price of £199.00 inc. VAT.

Since it expands the usefulness of TI programmable calculators, the PC-100 will be available from all retailers which carry either of the recently announced SR-52 and SR-56 calculators. *European Calculator Division, Texas Instruments Ltd., 165 Bath Road, Slough, SL1 4AD. Tel: 35544*

## SONUS CARTRIDGES

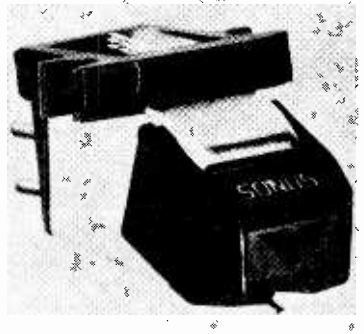
C. E. Hammond & Co. Ltd. announce the availability of the Sonus line of cartridges:



**Blue Label cartridge:** This unit is fitted with a micro-miniature multi-radial diamond tip, ground and polished to a precise contour in order to trace extremely high frequencies while maintaining a relatively large groove contact area. Although originally developed for use with discrete quadrasonic records, these characteristics considerably improve groove tracing in general, with a consequent reduction in distortion in all forms of micro groove records, particularly in the inner grooves. The stylus mounting, although very small, has extremely high mechanical strength and precise orientation. This diamond, combined with a moving system of exceptional lightness and strength definitely represents a 'state of the art' system. Price: £59 plus VAT.

**Red Label cartridge:** This has a conventional elliptical (bi-radial) diamond tip. Except where an extended frequency range is essential, this tip provides most of the precise tracing virtues of the Blue Label, although the stylus groove bearing area is considerably smaller. Again, the stylus mounting and general characteristics provide high mechanical strength and precise orientation in a moving system of exceptional lightness and strength. Price: £46 plus VAT.

**Green Label cartridge:** This unit is fitted with a micro-miniature spherical tip for general purpose use, where minimum stylus and record wear is desired under day to day conditions such as transcription or radio station work. It is also optimum for records compensated for inner groove distortion. Price: £39 plus VAT. *C. E. Hammond & Co. Ltd., Revox: 105-109 Oyster Lane, Byfleet, Surrey KT14 7LA. All other products: 111 Chertsey Road, Byfleet, Surrey KT14 7LA. Tel: Byfleet 41131.*

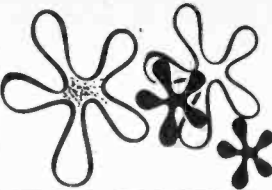The **PW**  **4** IN NEXT MONTH'S  
**'CHROMACHASE'** **PRACTICAL WIRELESS**


**Drive it from your Disco or Hi-Fi**  
**— PLUS —**  
**Selectable Programming of**  
**Coloured Light Display**  
**— PLUS —**  
**full dimming facilities**




**ALSO:**  
**SIMPLE VHF CONVERTER**  
**S-DEC PROJECTS (NEW SERIES)**  
**MORE ON CAR ELECTRONICS**  
**ON SALE IN NOVEMBER**

**P  
W****PROJECT  
SERIES**

# CAR ELECTRONICS

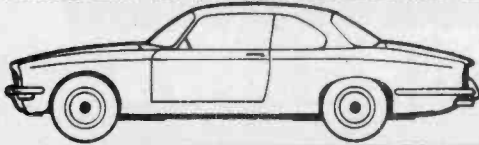

# LOW LEVEL BATTERY INDICATOR

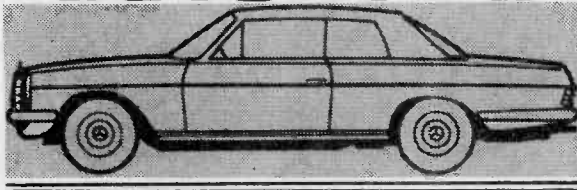


BATTERIES in equipment and cars are often prone to failure at inconvenient moments because no-one remembered to check the battery. More often than not, with the exception of cassette recorders, a monitoring meter is not fitted.

This circuit is designed to monitor the battery voltage and light an LED when it falls below a precisely set level. It is cheap, small and more rugged than a meter. Moreover, a meter has to be looked at and can be mis-read, whereas a light is reasonably eye-catching. The unit consumes very little current (about 2mA), and can be permanently wired across the battery.

# Practical Wireless 8-Page Supplement Nov. 1976
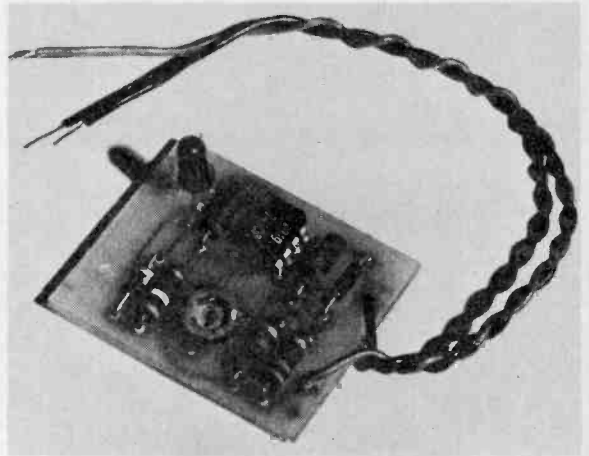
## CIRCUIT


A 741 operational amplifier is used to compare a proportion of the supply voltage,  $V_m$ , at one input, with a fixed reference voltage at the other input Fig. 1.



Photograph showing the prototype printed circuit board with the LED mounted on the board. In practice however, the LED would probably be mounted remotely.

As  $V_m$  falls slowly with use, the voltage at pin 2 drops below that at pin 3 which is fixed by the Zener diode, and the 741 changes state. The 2.2M $\Omega$  resistor supplies positive feedback to ensure sharp switching action.

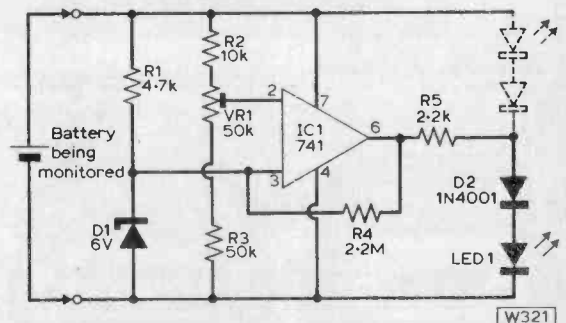The output at pin 6 goes from about 2V when 'off' to just below  $V_m$  when 'on'. In order to prevent the LED emitting



W321

Fig. 1: Circuit diagram showing LED1 and D2 in the two positions enabling either a normally ON or normally OFF display.



slightly when supposedly off, a 1N4001 diode, D2, in series with it drops this 2V to about 1.4V, at which the LED definitely remains in the 'off' state.

The preset enables triggering levels to be set from the Zener voltage to just below the line voltage. With a 9V battery the trigger level would probably be about 8.0V. The value of the Zener should be about half to two-thirds of the battery voltage when new. Circuit values are given for a 9V monitor, but no component is critical.

Should it be desired that the LED is normally 'on', and

switches 'off' when the voltage falls, then just reverse the polarity of the 1N4001 and the LED and take the LED to the positive line instead of the negative. (Shown dotted in Fig. 1).

## CONSTRUCTION

A PCB layout is shown in Fig. 2, and makes for a neat, compact unit. Construction and component layout is very straight-forward, but ensure the LED is inserted with the correct polarity. The LED's the author used had the negative lead indicated by a flat on the body.

To set up, adjust the preset to cause the LED to light at what is considered to be the voltage of a near dud battery. The circuit may be used with batteries up to about 30V but R1 may need to be increased to keep the current drain low at the higher voltages.

## ★ components list

### Resistors

R1 4.7k $\Omega$  R4 2.2M $\Omega$   
 R2 10k $\Omega$  R5 2.2k $\Omega$   
 R3 50k $\Omega$  VR1 50k $\Omega$  Horz. preset  
 All  $\frac{1}{2}$ W, 10%

### Semiconductors

IC1 741 D2 1N4001  
 D1 BZY88 6.2V 400mW zener LED1 0.2in Red

### Miscellaneous

PCB, 45 x 35mm (see readers PCB Service, page 576).



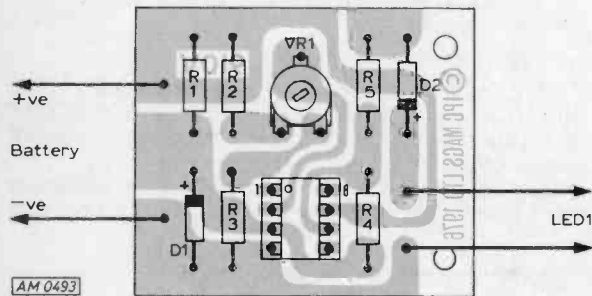
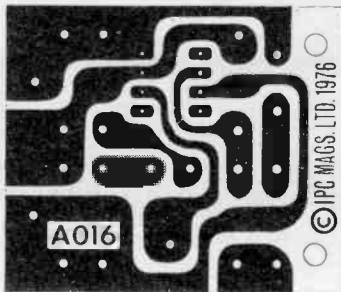


Fig. 2: Actual size PCB showing the foil side above and the component overlay below.


# ELECTRONIC THERMOSTAT

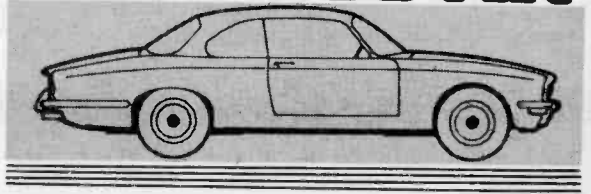

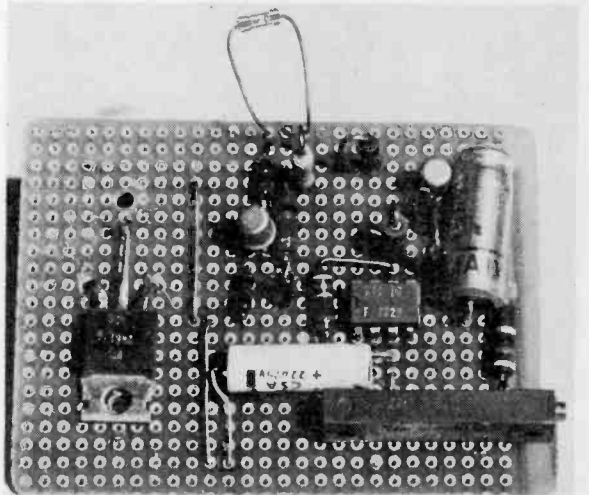THE mechanically operated fan fitted to most cars is an unnecessary waste of power, causing overcooling and increasing warm-up time. If the engine is operating below its optimal operating temperature, the petrol/air mixture



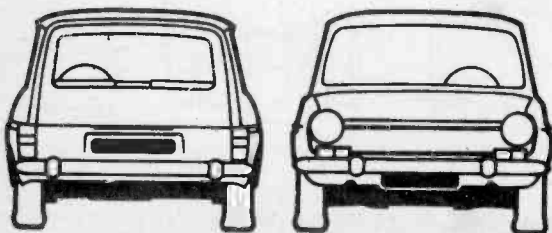The prototype shown here was constructed on Veroboard and used a transistor for switching (see Fig. 2.) The design shown in Fig. 3 is the modified PCB and uses a relay for switching purposes.



will be weakened due to premature condensation causing a reduction in power output. The fan also absorbs actual power from the engine, and on some cars can absorb up to 5%. The fitting of an electronically controlled fan driven

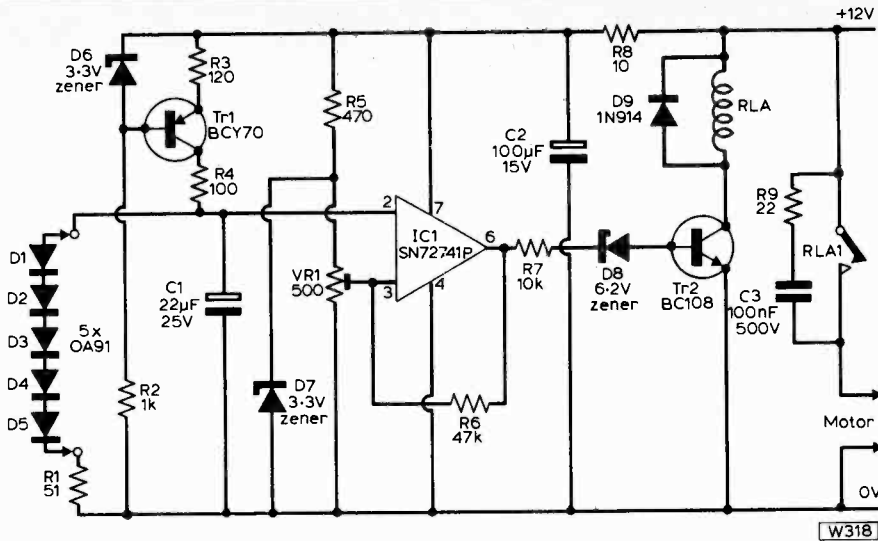


Fig. 1: Circuit diagram of the Electronic Thermostat, showing the string of five OA91 diodes which form the sensing device on the radiator.

by a small heater type electric motor can stop most of these unnecessary power losses.

Fan cooling is only required when the coolant in the radiator rises above about 5 deg. centigrade above the opening temperature of the coolant thermostat. Under normal motoring conditions the ram effect of the air forced into the radiator by the forward motion of the car is adequate to cool the engine, but if, for example, the car engine is left idling in a traffic jam, then some artificial airflow is required, and this is provided by the electric fan. The electronic thermostat described here controls the operation of the electric fan.

The temperature of the radiator coolant is "measured"

## ★ components list

### Resistors

R1 51Ω	R7 10kΩ
R2 1kΩ	R8 10Ω
R3 120Ω	R9 22Ω
R4 100Ω	R10 220Ω
R5 470Ω	R11 47Ω
R6 47kΩ	VR1 500Ω preset
All ½W 10%	

### Capacitors

C1 22μF 25V	C4 22μF 15V
C2 100μF 15V	C5 500μF 25V
C3 100nF 500V	C6 500μF 25V

### Semiconductors

Tr1 BCY70, 2N3906 or equiv.	D8 BZY88 6.2V 400mW zener
Tr2 BC108, 2N3904 or equiv.	D9 1N914
IC1 SN72741P	D10 1N4001
D1-D5 5 x OA91	D11 BZX61 12V 1.3W zener
D6 BZY88 3.3V 400mW zener	
D7 BZY88 3.3V 400mW zener	

### Miscellaneous

RLA, 12V relay with contacts rated at 4A and coil resistance or more than 200Ω i.e. Doram no. 348-131.  
 T1, mains transformer with 12V secondary and rated at 6VA, i.e. Doram 207-201. PCB 125 x 50mm (see page 576 for readers PCB Service)

by a string of germanium diodes D1-D5, which are secured in thermal contact with the top of the radiator at the opposite end from the inlet pipe (this is to ensure that the radiator is allowed to fill completely with hot coolant before any assistance is given to the cooling airflow). The forward voltage drop of germanium diodes changes by  $-10\text{mV}$  per deg. centigrade approximately. Therefore the combined forward voltage drop of five series connected diodes will change by  $-50\text{mV}$  per deg. centigrade and if this voltage change is compared with a reference voltage, then a fairly simple, but effective thermostat can be made.


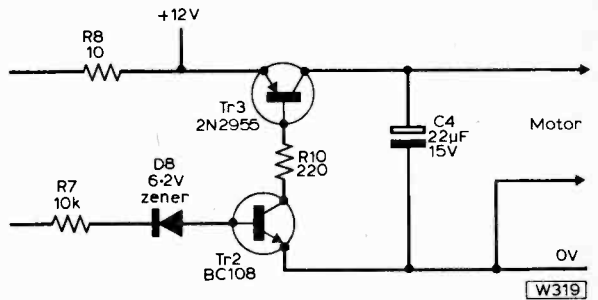


Fig. 2: Alternative switching is achieved by the use of a power transistor instead of a relay as shown above.

## REFERENCE VOLTAGE

As the battery voltage changes considerably with engine speed, state of charge, etc., some form of stabiliser is required to provide the reference voltage and also to supply the forward current for the diodes which are thermally

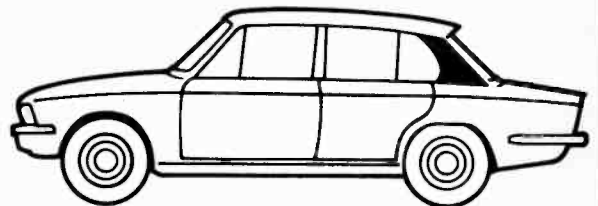


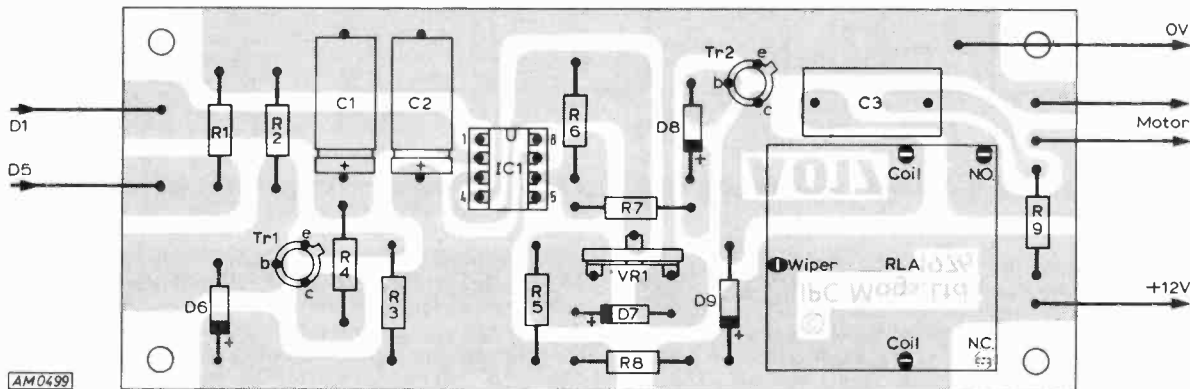
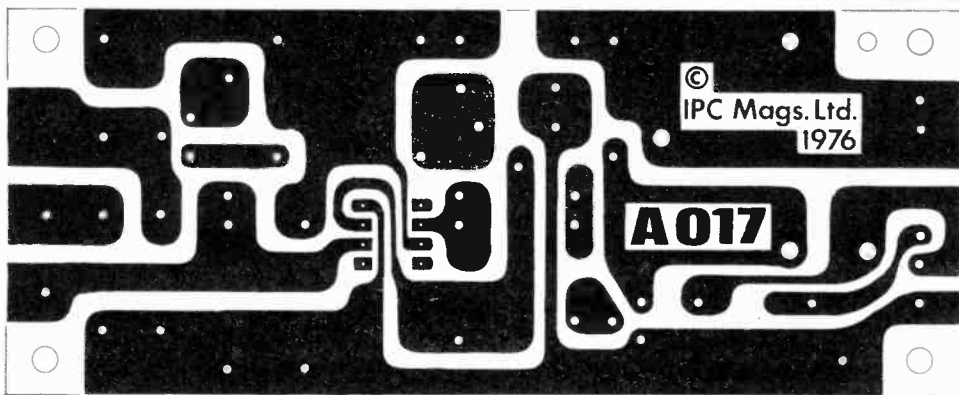


Fig. 3. The PCB shown above is full size and is designed to use the Doram 12V relay, number 349 131.

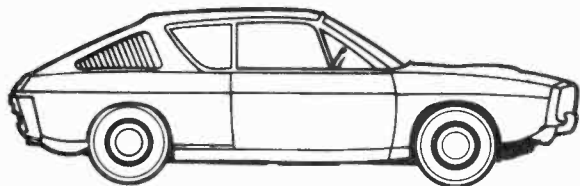connected to the radiator. A regulated current to supply VR1 and the diodes D1/5 is provided by constant current generator Tr1. If the voltage across the diode chain and R1 is greater than that set on the slider of VR1 (threshold temperature) then the output from the voltage comparator



IC1 will be low (about 2V), but if the radiator coolant temperature rises high enough, then the voltage across the diode chain will drop sufficiently for the voltage on VR1 slider to be the larger and in this condition the output of the comparator will go high (about 10V). To prevent "chattering" and to provide some hysteresis for the thermostat, R6 is included to give the voltage comparator some positive feedback—Fig. 1.

When the output of IC1 is at 10V, then D8 conducts providing base drive for Tr2 which switches on and energises the relay, thus starting the fan motor. When the output of IC1 is at 2V, i.e. the radiator coolant is at a lower temperature than requires artificial cooling, D8 does not conduct, Tr2 is not switched on and the relay is not energised. Components C1, C2, and R8 are essential to eliminate the high energy spikes present in most automobile electrical systems which can damage some of the components (notably IC1 and Tr2).

The circuit will work equally well with any negative temperature coefficient device, such as a thermistor; the only proviso being that the device has a resistance of between 20 and 1000 ohms at the desired switching temperature. A power transistor can also be used to switch the supply to the fan motor, and if this is desired, then the circuit should be modified as shown in Fig. 2

The circuit can also be used as a central heating controller, but in this case it is necessary to switch something off, normally the mains powered circulating pump. One of two solutions to this problem is to use the normally closed contacts of the relay instead of the normally open ones in the case of the fan motor. This solution has one disadvantage in that it is not fail safe, so a better way of reversing the function of the thermostat is to reverse pins 2 and 3 of

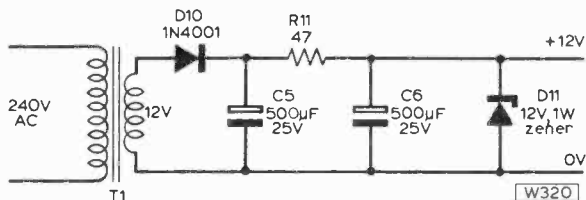


Fig. 4: If this device is to be used for any purpose other than a car thermostat, the power supply shown here is recommended.

IC1 and use the normally open contacts of the relay. For the domestic situation of a central heating controller, a mains power supply will normally be necessary, a suitable unit is shown in Fig. 4. The circuit has various other possibilities

such as a fish tank heater controller, or if the diode chain is replaced by a photocell, the unit can be used to automatically switch on parking lights on a car.

## ★ components list

### Resistors

R1	1k $\Omega$	R3	680 $\Omega$
R2	1k $\Omega$	R4	150 $\Omega$
All $\frac{1}{2}$ W, 10%			


### Semiconductors

Tr1	ZTX500	D5	BZY88 6.2V 400mW
D1	BZY88 12V 400mW		zener
	zener	D6	1N4001
D2	1N4001	D7	1N4001
D3	1N4001	LED1	0.2in. Red
D4	1N4001	LED2	0.2in. Green

### Miscellaneous

S1, single pole slide switch. Crocodile clip. Diecast box 89 x 30 x 35mm (Doram 509-923) PP3 battery and connectors. Material for probe i.e. knitting needle. Grommet, nuts and bolts. PCB 75 x 25mm available from the PW PCB Service (see page 576).

# 'CIRTEST' PROBE

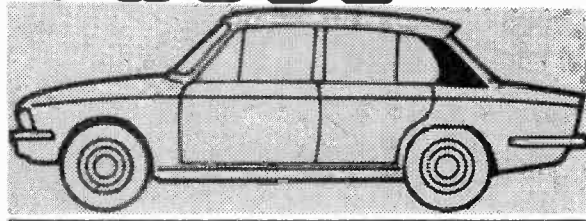

TRACING faults in a car's electrical system, one often requires to know whether a certain point is at earth potential or a live supply point, irrespective of the polarity of the vehicle's electrical system. This device indicates by means of coloured LED's, the state of any such point. The device

## CIRCUIT DETAILS

The circuit is shown in Fig. 1. Point B in the circuit is connected via the crocodile clip, to any conducting part of the car's chassis, and point A is connected to the probe.

If the probe contacts a point at chassis potential, there is no voltage across the bridge rectifier D3, D4, D6 & D7, and LED2, which is supplied by the bridge, fails to light. With the probe at chassis potential however, current from the battery B1 flows in the circuit formed by LED1, R2 and D2, and LED1 lights, indicating a point at chassis potential. No current flows in the circuit D1, R1, since the supply voltage of 9V is below the zener voltage of D1, and Tr1 remains biased off.

If the probe contacts a point at +12V with respect to earth, this voltage appears across the bridge rectifier which


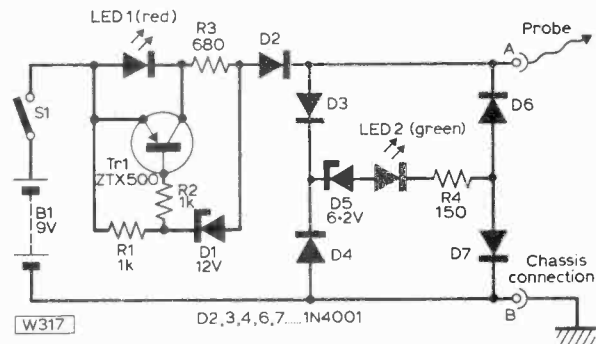



Fig. 1: The above circuit of the Cirtest Probe enables the user to determine the state of any electrical point on a car, whether the car is positive or negative earth.

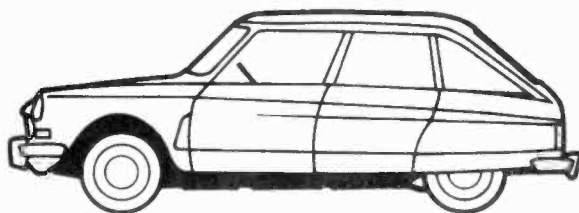is completely self contained and works on both positive and negative earth vehicles with a 12V battery. Only one connection, to any chassis point on the vehicle is required plus a probe contact to the point to be tested.



supplies a voltage of the correct polarity to the series circuit D5, LED2 and R4. This voltage being higher than the zener voltage of D5, current flows in LED2 causing it to light and indicate a supply point. LED1 remains off, since with the probe at +12V with respect to earth, D2 is reverse biased, and no current flows in LED1.

A small box, such as the Doram model shown here, is most convenient for housing the electronics, and for ease of handling.

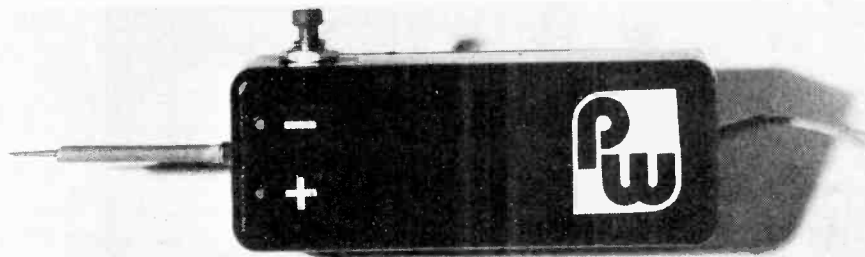

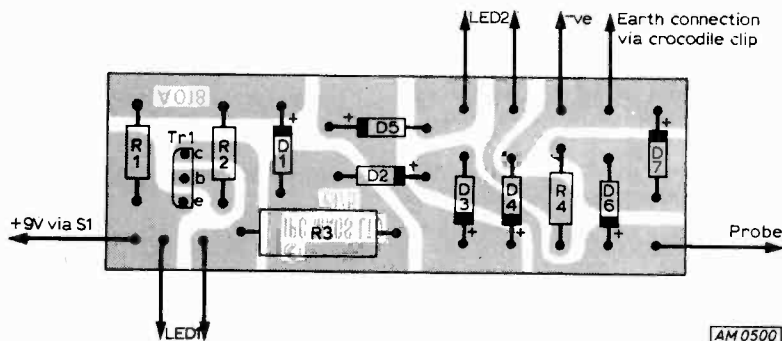


Fig. 2: Designed for fitting in a small diecast box with the battery, the above PCB is reproduced full size with foil side above and component overlay below.

If the probe contacts a point at  $-12V$  with respect to earth potential, this voltage appears across the bridge rectifier as before, and LED2 lights as before, indicating a point at supply potential. Simultaneously, a voltage of  $21V$  appears across the circuit LED1, R2, D2. In order to prevent LED1 from illuminating, D1 conducts as the voltage has exceeded its zener voltage. The voltage developed across R1 due to this current flow appears via R2 at the base of Tr1 which as a result conducts. This prevents LED1 from lighting, since the saturated collector-emitter voltage of Tr1 is below the voltage required to forward bias LED1.

D5 is included in the circuit to prevent current from B1 flowing through LED1 to earth, via R3, D2, D3, D5, LED2, R4, and D7. The zener voltage of D5, plus the forward voltage drop of the other diodes in the path, prevents this from happening with a 9V battery for B1.

## PROTOTYPE HOUSING


The printed circuit board, Fig. 2., was housed in a small diecast box as shown in the photograph. A PP3 battery was used to keep the overall dimensions small, and the components mounted neatly on the PCB for the same reason. In the author's prototype, a small slide switch was used for S1, but a spring return push-button switch could be fitted if so desired. Two bolts with spacers support the circuit board, and a small right angle piece of aluminium, bolted to the box, serves as a battery clip. The two LEDs fix into holes in the end of the box, using the fixing clips supplied with them. A red LED was used for LED1, and a green one for LED2.

The probe consists of a steel knitting needle, cut to the appropriate length, with a piece of plastic sleeving (the plastic covering from screened lead was found to be ideal) slipped tightly over the end. This was fixed into a hole in the end of the box, using an epoxy resin adhesive. If desired, the fixed probe could, of course, be replaced with a probe on a flexible lead. The earth lead was formed from a suitable length of wire, with a crocodile clip fitted on the end.

## IN USE

To check any point in a car's electrical system, of either polarity, the crocodile clip is affixed to any conducting point on the car's chassis, and the probe applied to the point to be tested. If the point is at chassis potential, the red LED will light, if the point is at supply potential, the green LED will light. The device will be found to be of use in checking lighting, ignition, and auxiliary circuits in any 12 volt electrical system.

# BURGLAR ALARM

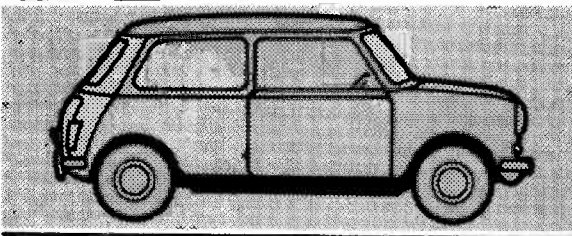


THE alarm unit described here is suitable for use in the home, car or shop display, and will supply an alarm requiring up to 6A.


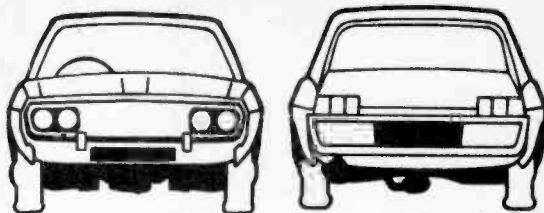
## CIRCUIT OPERATION

The circuit of the complete unit is shown in Fig. 1. The Thyristor or Silicon controlled-rectifier, SCR1, is triggered by a voltage from Tr1 collector. If the alarm loop is kept closed i.e. Tr1 base is connected to ground, the voltage at this point will be zero, and the voltage across resistor R2 will also be below the trigger voltage needed to fire SCR1. When the circuit is broken by the intruder the base of Tr1 will become negative with respect to ground. This will alter



the voltage across R2 to the state of trigger on the gate of the thyristor, and will supply power to the alarm.

The resistor R4 is to make sure that the holding current

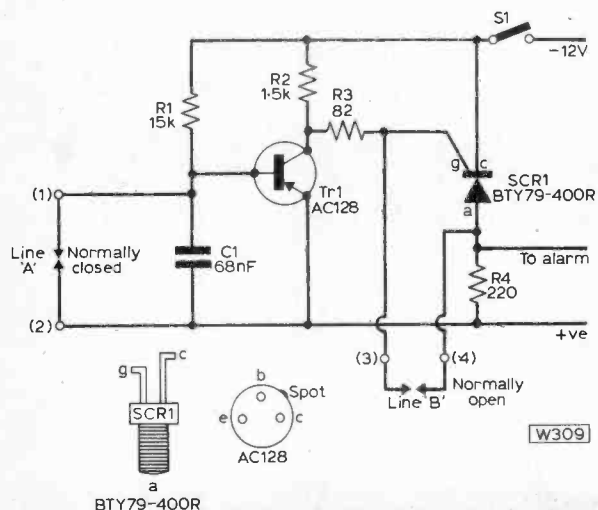


Fig. 1: Complete circuit of the Burglar Alarm, showing just two contact points. The Thyristor SCR1, should be mounted on a small heatsink if current in the order of 6A is to be drawn.

## ★ components list

### Resistors

R1	15k $\Omega$	R3	82 $\Omega$
R2	1.5k $\Omega$	R4	220 $\Omega$
R1, 2, 3 $\frac{1}{2}$ W 5%. R4 1W 10%			

### Capacitor


C1 68nF 400V Polyester.

### Semiconductors

Tr1 AC128 or OC81 or equivalent.  
SCR1 BTY79-400R

### Miscellaneous

Alarm, Audible Warning Device, Doram number 248-808. 4-way terminal block. S1, SPST switch. 75 x 30mm PCB. HP1 12V battery. Aluminium box 114 x 55 x 89mm, Doram 509-945. Aluminium mounting bracket for SCR1.

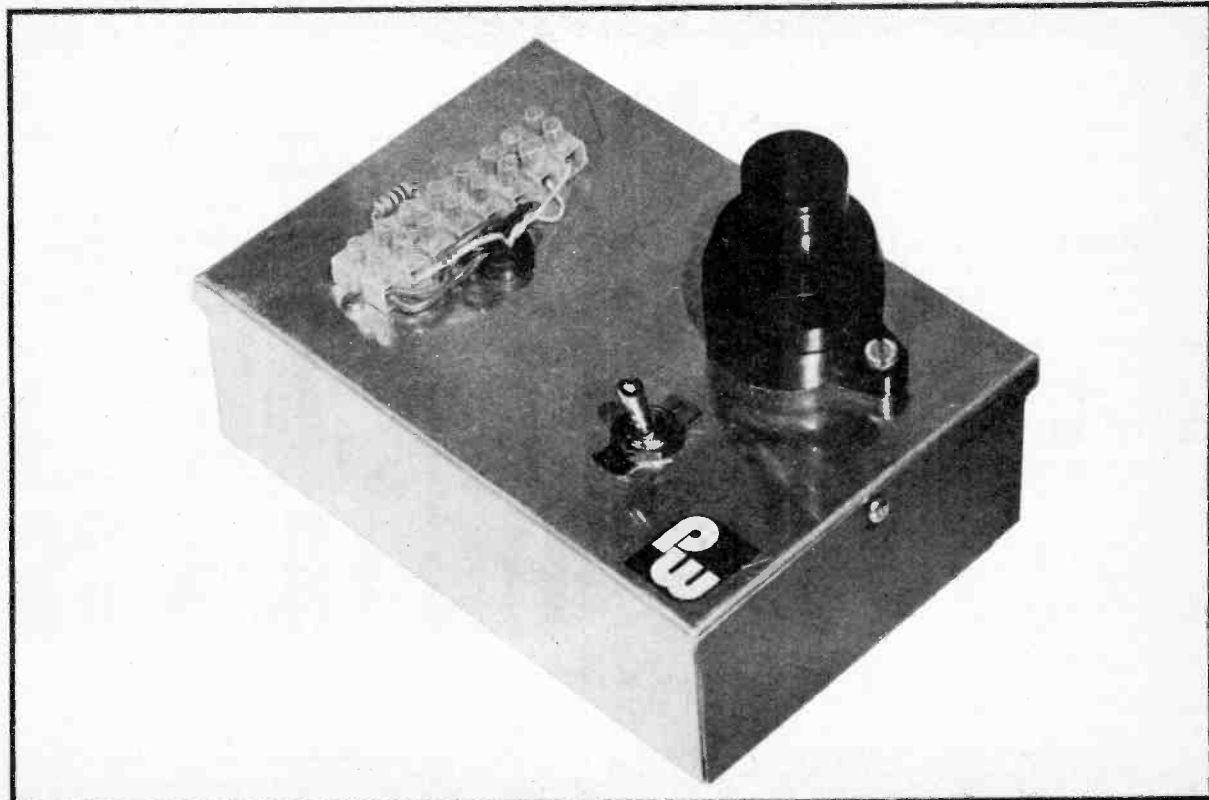

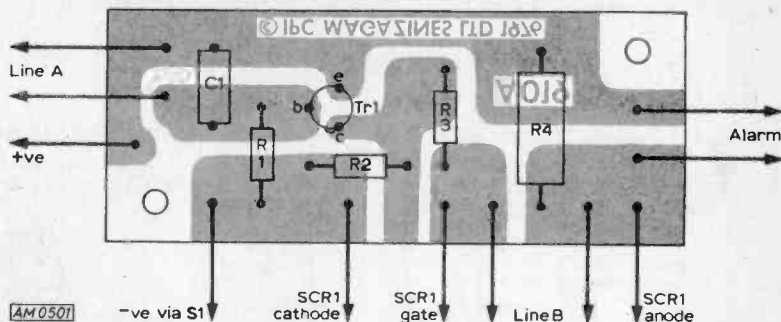


Fig. 2: The PCB shown above was designed to fit into a case, together with the alarm and switch. The sensing switches—pressure mats etc. are external to the unit, and placed where most useful.

of the thyristor is around 30mA, as without it, the SCR will reset. The only way to stop the alarm after it has been triggered, is to interrupt the supply i.e. switch the unit off and then back on again to reset. One could add a key switch to stop anyone but the owner resetting the unit, but if its well hidden the author felt that the extra cost was prohibitive.

## SETTING UP

To set up the alarm it only needs a battery, the normally closed circuit connected to 1 and 2 (line A), and/or normally open circuit to 3 and 4 (line B). These switched circuits can be of any design such as pressure mats or window contacts. The alarm itself, should be connected between the anode of SCR1 and the positive supply.

The unit should now be switched on, and as long as the circuit on line A is closed or line B open, the alarm should not sound. However, if either of these two circuits are in the reverse mode, the alarm will be activated. After this, switch off, reset the contacts that were broken and switch back on again. The unit is now back to its standby mode.

## CONSTRUCTION

All the components except the alarm, switch and SCR1 are mounted on the PCB shown in Fig. 2. The two former components are screwed to the case together with a connecting block, while the SCR is fitted to a piece of aluminium for heat sinking. Two holes are drilled in the lid, a small one for the external wiring and a larger one for the alarm to sound through.

## CONCLUSIONS

While the unit is in the standby mode it is only taking a few milliamps and will give good life to an HP1 battery.

The battery should be capable of delivering up to a few amps for the alarm, since this will be the only time there will be a large drain.

When the unit is complete, with sensors in position, attention should be made to hide the cables and position the unit in an effective but unobtrusive position.


THE FOUR PCB'S SHOWN IN THIS CAR SUPPLEMENT ARE OBTAINABLE FROM THE READERS PCB SERVICE. FULL DETAILS AND COST CAN BE FOUND ON PAGE 576 OF THIS ISSUE.




# PROJECT SERIES



# CAR



# ELECTRONICS

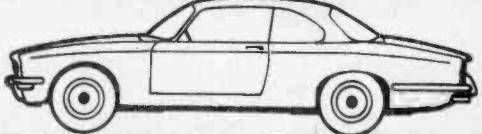

# DFM prescaler

## & MODIFIED DISPLAY BOARDS

T.J. JOHNSON

THE Frequency Meter described in the June/July issues of PW, had certain limitations, one being the upper frequency limit, typically 28MHz. This is obviously no use if it is desired to measure the frequency, of say, an amateur 2m transmitter, where the limit is 146MHz. To overcome this limitation a prescaler is used to divide the input frequency by 10, thus extending the range up to 280MHz.

### Circuit description

The circuit of the prescaler is shown in Fig. 1, and comprises integrated circuit IC1, capacitor C2, which provides a small amount of smoothing on the power

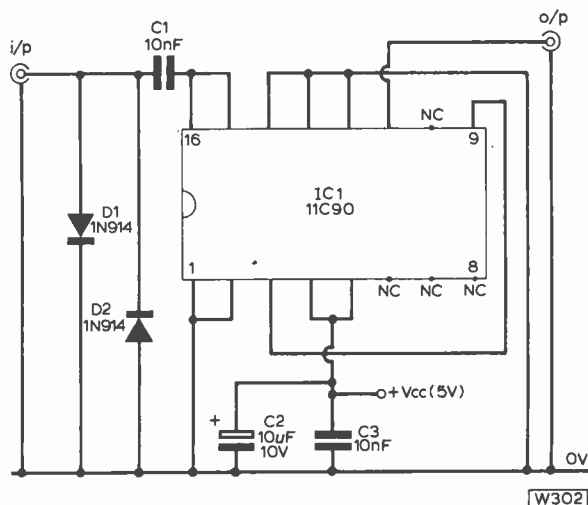


Fig. 1: Circuit diagram showing the small number of components required for this project. When used with this circuit, the DFM's frequency coverage is extended up to 280 MHz.

supply, and C3 which smooths any RF noise. The input signal is AC coupled to the IC via C1, while the two diodes protect the IC from excessive input voltage.

The IC is one from a range of prescalers manufactured by Fairchild, and designated 11C90, and is capable of operating up to 650MHz, although the limit of the DFM reduces this to 280MHz.

### Construction

The use of a PCB is a must if instability is to be avoided, the one shown in Fig. 2 is to be recom-

mended, but on no account use veroboard.

It is also advisable to use an IC socket, the price of the socket just does not compare with the price

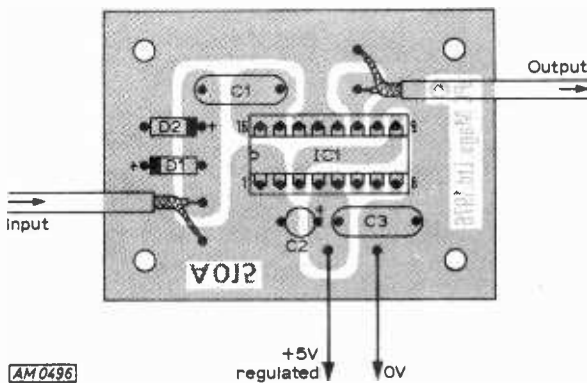
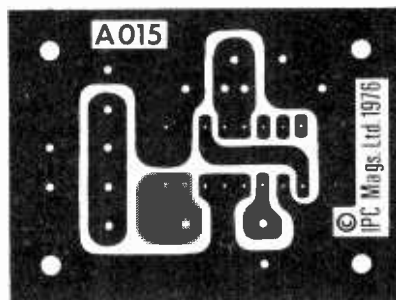


Fig. 2: Full size drawings of the PCB required for this project. This design is recommended if instability is to be avoided.

### ★ components list

#### Capacitors

C1 10nF C3 10nF  
C2 10µF 10V

#### Semiconductors

D1 1N914 IC1 11C90 (Fairchild)  
D2 1N914

#### Miscellaneous

PCB 50 x 38mm, 18 pin DIL socket. Length of single core screened cable. Length of wire for supply. DPDT switch.

of a damaged IC! The input and output are connected via screened leads, the length of which should be as short as possible.

## Use

It is up to the constructor as to whether the prescaler is to be used inside the main DFM or external to it. When used in the main DFM, the power supply may be taken from any convenient point on the main circuit board. If used externally, then it is advisable to screen the power leads, and to keep them as short as possible.

When used in the DFM, the circuit board may be mounted near the input socket and a small switch used to change over the inputs. A suitable system is shown in Fig. 3.

The minimum operating voltage is 350mV pk to pk sinewave, although tests carried out found

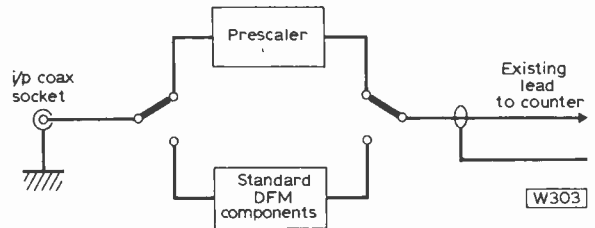


Fig. 3: The prescaler should be connected in parallel with the standard input wire (between SK1 and S2), and either one of these two inputs selected by a DPDT switch.

the prescaler reliable down to 100mV, for a range from 100kHz to 100MHz. It was also found that operation below 100kHz was too erratic, but since this type of frequency can be measured direct on the DFM this is no set back. In all cases a sinewave was used.

## MODIFIED DISPLAY BOARDS

OWING to the demand for the four Doran display boards for the DFM (June/July '76), stocks have run short, and we are now able to offer these boards in the PW readers PCB service (page 576).


Although all four boards are the same in design,

(6) Lead from pin 4 IC8 to board 4 (pins 4/13 IC15).


(7) Lead from S4J/ON to DP on board 2.

(8) Lead from S3J/ON to DP on board 3.

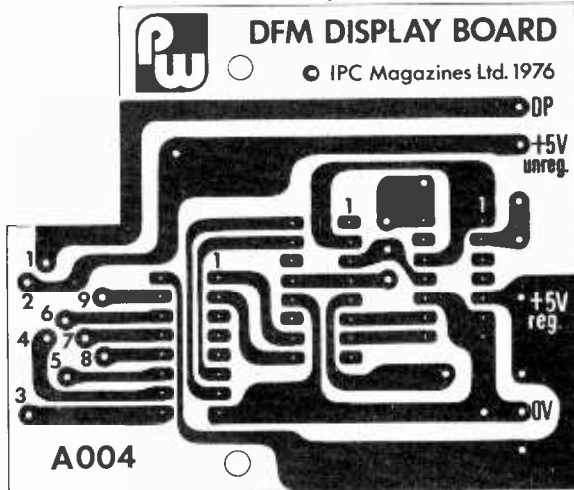(9) Lead from pin 1 IC9 to board 1 (pin 2 IC14), and then links taken from this board to the other three.



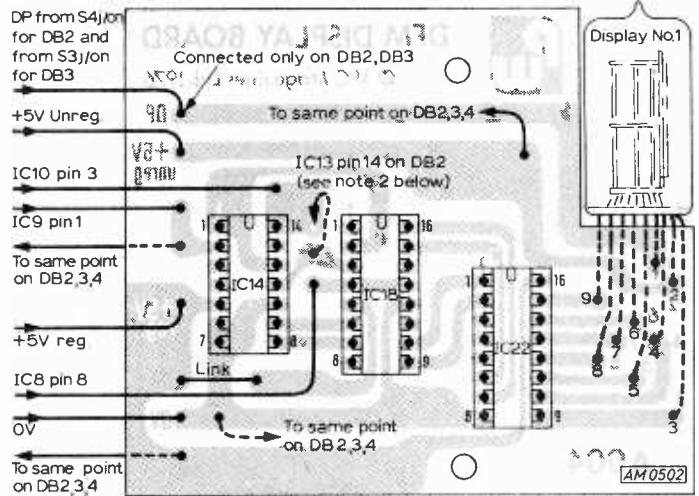Component and foil side views of the modified display boards for use in the PW DFM as published in June/July 1976.



connections to these boards differ. Below is listed the connections to the main board and power supply board and the links required between the display boards themselves.

(1) +5V regulated, +5V unregulated and 0V to board 1, and then links taken from this board to the other three via the holes ready drilled. Also links on all boards bridging the 0V track near pins 7/8 of the 7490.

(2) Input lead from pin 3 IC10 to board 1 (pin 14 IC14) and links taken from pin 11 IC14 to pin 14 IC13; from pin 11 IC13 to pin 14 IC12, and from pin 11 IC12 to pin 14 IC11 (refer to Fig. 8, DFM, July '76).

(3) Lead from pin 8 IC8 to board 1 (pins 4/13 IC18).

(4) Lead from pin 6 IC8 to board 2 (pins 4/13 IC17).

(5) Lead from pin 2 IC8 to board 3 (pins 4/13 IC16).

**AVAILABLE NOW!**

**REPRINT OF PW's**

**TELE-TENNIS SERIES**

**July-November 74**

Send 75p + 10p (post & packing) to: Chief Cashier  
(PW Tele-Tennis), IPC Magazines, Tower House,  
Southampton St., London, WC2E 9QX.

# HOTLINES

ON RECENT DEVELOPMENTS

## WHITER THAN WHITE

Have you ever seen those advertisements on the telly where some dolly bird leers at the lens displaying a mouthful of dazzlingly white gnashers—like a piano keyboard with no black notes? Well, those teeth are going to be twice as white soon, thanks to the Japanese.

A new colour television tube which is claimed to be almost twice as bright as its earlier brothers will be marketed later this year by Hitachi. The increase in whiteness/brightness is achieved by persuading twice the number of electrons to get to the phosphor dot screen via the shadow mask. This in turn has been managed by applying a voltage between the mask and the screen. Interesting that the system calls for some 24kV for the electron guns. Clearly a method with great potential!

## DEATH CODE

Say the word 'Crypt' during a conversation and there will probably be a grave silence—smokers may even start coffin! But leave off the letter 't' and you've got something quite different.

Cryp is the name of a new range of communications security equipment which uses digital techniques for voice transmissions. It can be used with data transmission and other types also.

Some systems operate by stretching out and compressing the voice data. Time-element scrambling is one title often used.

Cryp makes things very difficult for the 'enemy' i.e., the unauthorised listener. It takes the message data and mixes it all up with long, long digital code sequences. These digital sequences are generated on a completely random basis.

For the eavesdropper the statistics of making what he hears intelligible are truly horrendous. For example, if he's looking for a sequence so that he can synchronise his own equipment and thus pick up the start of a sequence of code, the manufacturers guarantee that the encrypted sequences will not recur or recycle in less than 17 thousand million bits. Even worse: every customer has the

option of something like 10 thousand million unique settings for his code. Someone with a mathematical bent has worked out that even if you were able to check out each different code taking only one single second to do it—it would still take you 300 years to check them all. Well 10111001 me!

## SMALLER FINGERS WANTED

Now that just about everyone has an electronic calculator, and prices have sunk to almost nothing for simple four-rule machines, I thought that this area of electronics would remain quiet. After all, what else was there.

Just to prove me wrong, a Japanese company has produced a tiny little calculator which measures 61 x 43 millimeters and is only 15 millimeters thick. Price in Japan is around the £17 mark. Not only does this mighty midget give addition, subtraction, multiplication and division, it also offers calculation by powers, division and multiplication by a constant and it has floating decimal point. Liquid crystal displays are used and the power drawn is only one hundredth of one Watt. It uses a single silver-oxide type battery and this will give over 60 hours of use. Commenting on the calculator, the company believes that it is the smallest size calculator which can be operated by bare hands. To go smaller is possible, but one is limited by the size of human fingers.

## CHIPS WITH EVERYTHING

The conservation of power has been highlighted in recent times and I learn with great interest of what appears to be the ultimate—an electronic circuit which doesn't use a battery, just light. It is a tiny chip which is intended for use in the new Kodak Fast Development Camera. A minute photodiode supplies power to a tiny oscillator. The greater the light intensity, the higher the frequency of the oscillator. Output from this oscillator feeds an "ever so tiny" converter which in turn shows its gratitude to the oscillator by pro-

ducing around 500mV of output. Frequency of the oscillator varies (with light intensity) from just over 100Hz up to nearly 1MHz. The photodiode receives its light through the lens and is, therefore, proportional to the scene being actually photographed. Now the chip manufacturers, realizing this, were not slow to see greater possibilities for their baby chip (the light-to-frequency converter measures only 36thou by 12thou).

For the Kodak Instant type of camera, the photodiode chip and a linear IC are packaged together. This little bundle indicates when the light levels are too low, gives warning that the battery in the camera (used for other things) gets low, it also looks at ambient light levels at the time of taking the photograph and automatically selects the aperture, and finally it times the automatic shutter. Now that's what I call the efficient use of energy.

## STERILE BEAM

I hear that the laser continues to find new tasks—carrying out light work no doubt. One manufacturer is using a laser beam to cut out shapes of ceramic used in the manufacture of electronic circuits. The substrates are held on an X-Y table which is computer controlled, and thus the substrate is moved under a stationary laser beam which does the cutting. The power of the laser is only around 100W continuous wave but this still works out at 10MW (ten million Watts) per centimetre. It is also reported that the same laser is being modified so that the beam itself can be guided very precisely by hand. The application here is to use the beam for surgery. The beam has the advantage of being completely sterile and would cauterize blood vessels instantly.

It's nice to know that someone is shedding a little light on the internal workings of the human body.





# PW 'Easybuild'

# VIDEO-WRITER

## PART 4

M. J. HUGHES M. A., C. Eng. MIERE

The first 3 sections have covered the General Concept, the Power Supply and the Sync Pulse Board.

This section deals with the Address Counters and Registers in theory and practice.

As explained in Part 1 we have to produce discrete sets of binary codes which designate portions of the television display raster to the different character cells. These are called the Character "Column" and "Row" Addresses respectively. We have also to produce similar codes which designate portions within each character cell. You will remember that each cell comprises a matrix of 6 picture points in width by 8 picture points in height. Each of the six vertical picture point columns needs a code to tell the multiplexer the sequence in which they must appear when they are assembled into the final video signal. The Read Only Memory also needs to know which row of picture points (within the cell) it should be operating on hence eight binary codes are required to identify them.

These address codes have to be produced in a very regular fashion and in exact synchronism with the television raster so that they always relate to precise positions on the screen in the final display.

Fig. 14 is a schematic of the address code generators, which we call counters. The word counter is a perfect description because that is all they are. Within the circuit there are four fairly straightforward binary divider chains. They vary from ordinary divider chains in that some of them do not start at a count of zero and all of them are forced to reset before they have completed their natural counting cycle.

### MULTIPLEXERS

Take the Multiplexer Address Counter for instance. This is IC20, a four stage binary divider IC. The first stage is not used because we need to divide the 4MHz clock by 6 to define the codes for each of the six picture points within the width of the cell. To count on a scale of six only, a 3 stage counter is required which has a maximum range of eight. To get it to cycle on six we have to force it

into a reset condition after the count of "5". This is done by IC21b in conjunction with IC21a.


To ensure that the counter always starts at a count of zero at the beginning of a television raster line (this is to ensure synchronism) we use the line sync pulse (Line Drive) to override the internally generated reset. This is particularly important because there are a potential 256 picture points along a line (including the line sync period) and this number is not exactly divisible by six. Without an overriding reset at the start of each line the counter would precess relative to the lines of the display and the final result would be rubbish. IC21a accepts the line drive reset as well as the "scale of six" reset from IC21b and feeds a reset signal to IC20.

If you refer to Fig 15, you will see the waveforms that are generated by the three outputs of IC20. We call these the Multiplexer Address lines and they are designated Q21, Q22 and Q23. Notice that, apart from the reset to zero period when line drive is active, Q21 is simply a divide by two of the 4MHz clock. Q22 does not get a chance to take up its second "high" before the counter is reset on the scale of six and the "high" of Q23 is curtailed by the reset. This sequence requires 6 clock pulses after the line drive signal has ended and if the three address lines are looked at as binary numbers you can see the six discrete codes that they represent in the table under the region marked as the first "Cell Width". The code 000 describes the most left-hand picture along a row in the cell while 001 represents the second from the left and 101 represents the sixth. The counter is then reset to 000 and this describes the most left-hand picture point of the next cell and so on.
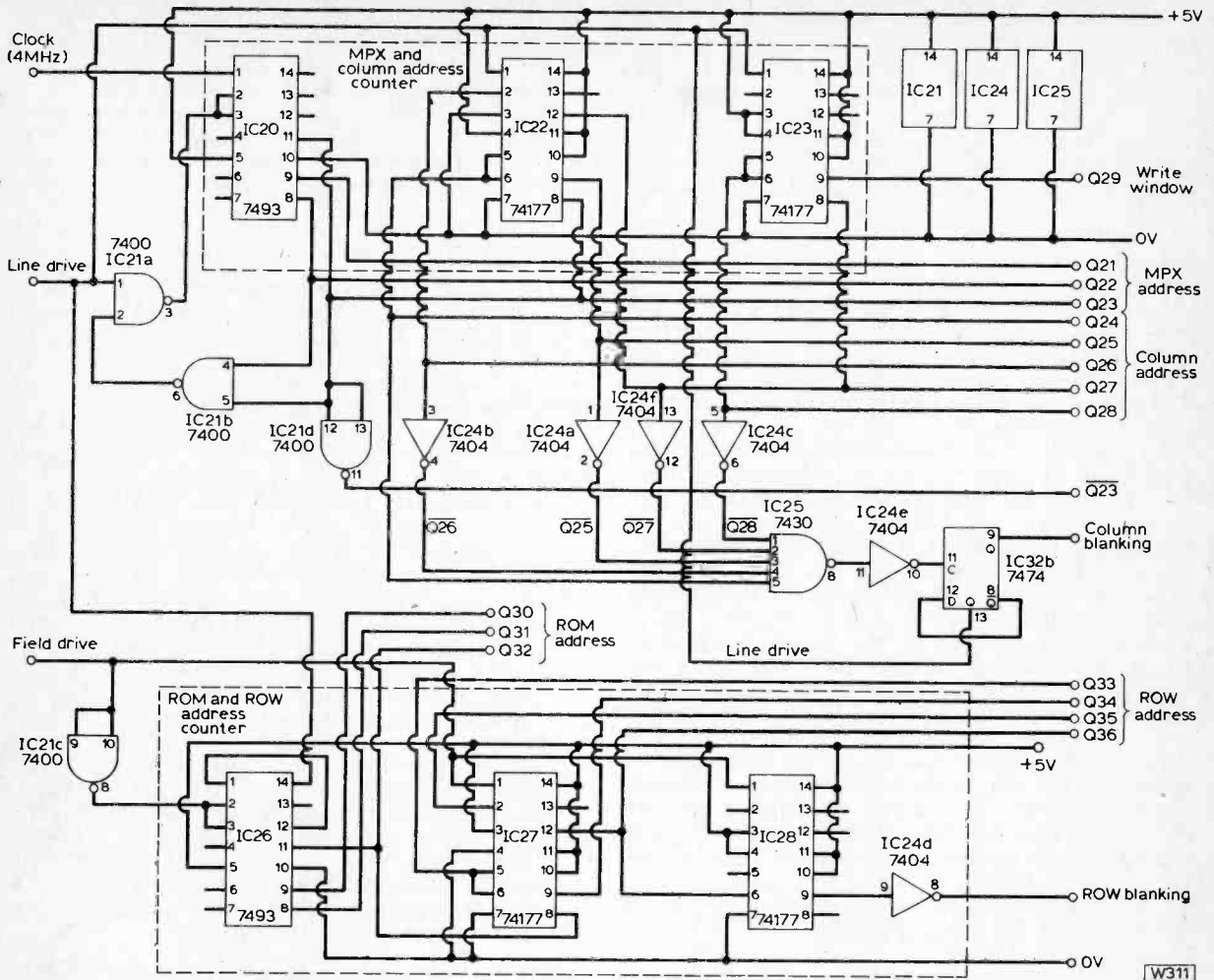
### COLUMN ADDRESS

A total of 39 complete cells can be described along a television raster line in this manner but, as mentioned before, there is an incomplete cell on the extreme right hand end of the raster line which only has three picture points. The line drive reset takes over in the middle of this cell and resets the counter in readiness for the next television line.


The first five cells along a raster line are not used for display as they form the left hand margin while the last two complete cells plus the forshortened cell form the right hand margin. The fact that the last



W311

▲ Fig. 14. Schematic diagram of the Address Counters.

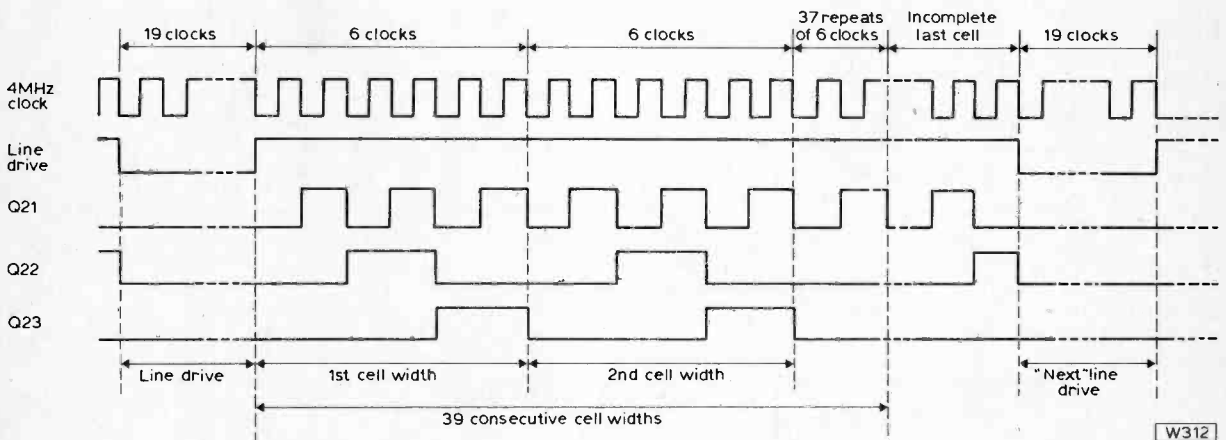▼ Fig. 15. The waveforms from IC20 (modulo 6 counter).



W312

Q21	0	1	0	1	0	1	} Repeated
Q22	0	0	1	1	0	0	
Q23	0	0	0	0	1	1	

Multiplexer address codes  
(used to serialise the picture point  
data provided by the ROM)



## MARGIN BLANKING

During the read cycle of the instrument the address counter will be going through all its code combinations and unless something is done about it we would get true addresses thrown up at the times of the left and right hand margins. The effect of this would be to repeat some of the characters (that have equivalent addresses) in the margins. In reality it does not matter if this happens as long as we don't see them, so we arrange to blank the video signal as we are going through the margin address positions. This is slightly complicated by the fact that we have to embody a character cell delay between addressing the Random Access Memory and displaying the information. This was mentioned in Part 1. The column blanking signal must therefore be one character cell delayed relative to the addresses. This is clearly seen in the bottom waveform of Fig. 16. This delayed waveform is generated by the circuitry associated with IC32b.

## ROM ADDRESS

Having defined the horizontal positions of the cells we now have to prescribe Addresses to them to designate their vertical positions and at the same time generate lower level address codes to denote which of the eight rows of picture points within the cell is active (this is needed for the Read Only Memory). It is the latter which we produce first and we call it the ROM Address. The counter which produces it is IC26. You should refer also to Fig. 17.

Because each row of picture points within a cell is made up of two raster lines the first thing we do is divide the line rate by two. This is done by the first stage of IC26. We have not given a designation to this half line frequency signal as it does not play any further part in the circuitry but, if you have an oscilloscope, it can be seen at pin 12 of IC26.

The following three stages of IC26 produce the ROM Address signals shown as Q30, Q31, and Q32 in Fig. 17. These three stages are reset to an "All Noughts" starting condition by the inverted field drive signal. This ensures synchronism with the field


rate of the television raster. Conventional binary division takes place with the counter of IC26 completing 19 full cycles. It then starts an extra cycle but is unable to complete it before the next field drive signal, which resets the counter in readiness for the next field. There will be a short delay (half a line period) before the start of cycling for the next field—due to the staggering of line drive pulses brought about by our locked interlace system. On the third field this delay will not occur, but on the fourth it will be present again and so on.

## ROW ADDRESS

One complete cycle of Q32 defines the height of a character cell and the eight codes generated by the Address lines are shown in the table of Fig. 17. As already mentioned we obtain "19 and a bit" cells; the top two and bottom "One and a bit" are reserved for top and bottom margins respectively so we require the Row Address for all the cells occurring on the THIRD row from top of the screen to be 0000.

An identical technique is used to that already described for the Column Address Counter. The four stages within IC27 give the Row Address as Q33, Q34, Q35 and Q36. Field drive is used to reset this counter to "All Ones" with the exception of Q33. Reference to Fig. 18 shows that this gives us an address of 0000 for the third row. The counter operates up to 16—producing the address for each row of cells—and then starts to re-cycle just before the next field drive pulse. For the same reasons as before we have to prevent the appearance of characters in the top and bottom margins so we use the first stage of IC28 to divide Q36 by two and this gives us (after inversion by IC24d) our Row Blanking signal. There is no need for this to be subjected to the delay that was needed in the case of the Column Blanking signal.

Fig. 17. The waveforms appearing at the outputs of IC26, the ROM Address Counter.

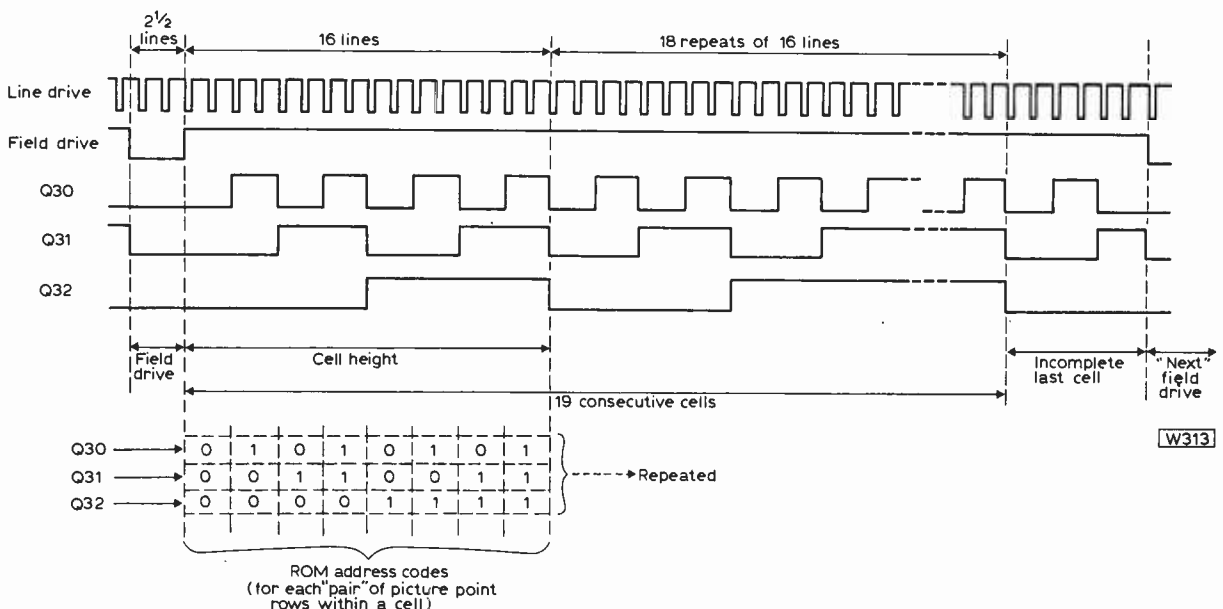

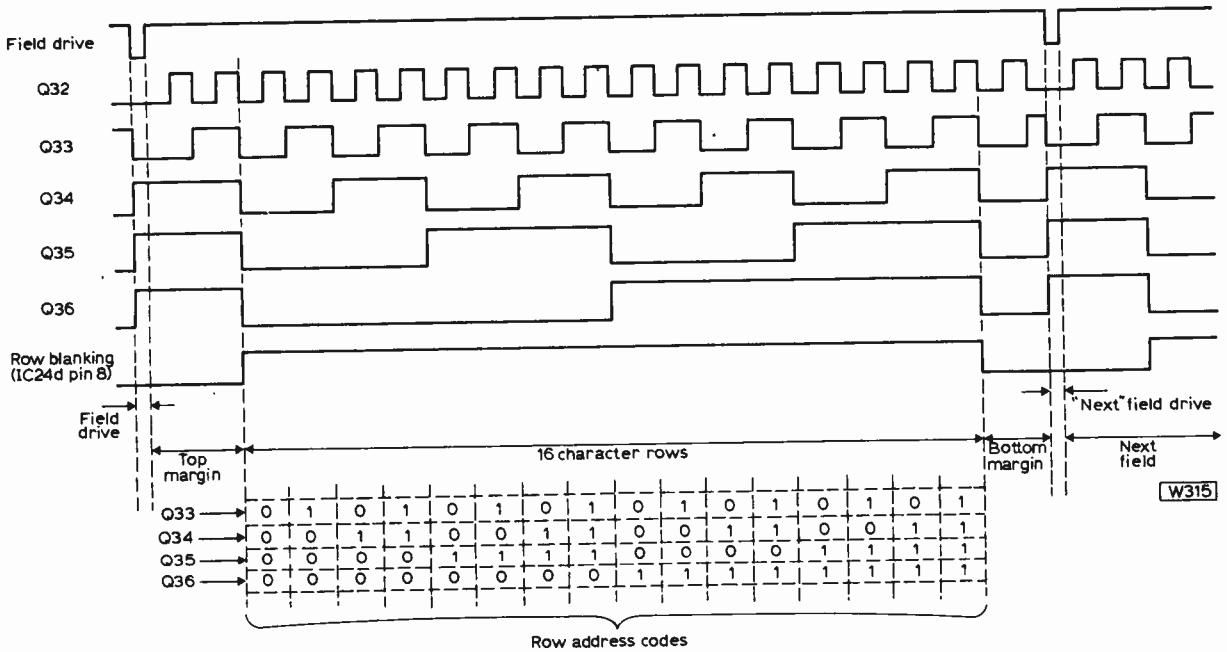


Fig. 18. The waveforms from the outputs of IC27 and IC28 (these form the Row Address Counter).

## ADDRESS ROUTING

As might be expected the MPX Address codes are fed directly to the multiplexer (which will be described later), the ROM Address codes go straight to the Read Only Memory and the Column and Row Address codes go to the Random Access Memory to call up the correct data to describe the character that should be occurring at the prescribed place on the screen. The Column and Row Addresses are also fed to the comparator (Fig 19) to start the process of generating a writing signal.

## CELL IDENTIFICATION

As explained in the first part of this series we have to keep a record of where on the screen we expect the next character to occur when we are typing into the system. Clearly every character cell can be described in terms of a Column and a Row Address code and a combination of any pair of these codes will be unique for a particular position on the screen. We can use a static register to hold any pre-determined code and compare its contents with the Column and Row Addresses as they are generated. Whenever the contents of the register exactly tally with the codes generated by the Address Counters we can say that the television raster is going through the cell that is designated by the code we have stored in the register.

## ADDRESS REGISTERS

To keep life simple, and practical, we have split the register into two logical portions. One is the Row Address Register and the other is the Column Address Register. In a typewriter we do not often wish to go to a particular place on the screen at random but usually follow a certain pattern. For example we usually want to step to the next character position along a line (towards the right) after we have typed the last character. At the end of a line we want to return to the start of a new line (i.e. a carriage return) and then to step down a line. It should be clear that stepping along a line from left to right is the same as moving from one

column address to the next higher one and stepping down the screen from one line to the next is simply an operation of incrementing the Row Address.

A carriage return is simply a means of telling the Column Address register to return to an address of zero. The registers are therefore nothing more than counters which react to asynchronous signals generated at the user's command.

## UP/DOWN FACILITY

To add flexibility we have chosen to make the counters reversible so that, if desired, we can step the address codes in the other direction—this enables back spacing and stepping UP the screen for correction purposes.

It would have been possible to incorporate a "tab" facility so that, at a touch of a button, the column address register would take up a pre-determined code which might be of help in compiling tables of numbers. We felt that this was an unnecessary luxury and although simple in theory would have complicated the wiring of the system.

The only condition we have built in, of this nature, is "Reset to Zero" which zeros the address codes for both columns and rows. This enables the user to do a rapid return to the top left hand corner of the screen to start a page of type.

IC35 forms the Row Address Register. Like all the counters used in this part of the circuit it is an UP/DOWN counter that receives its direction instruction at pin 5. In this case the instruction is generated by a flip flop (IC32a). One press of the Forward/Reverse key will make the counters operate in an UP mode and a second press will toggle the flip flop making them count down. A "0" on pin 11 of IC35 will reset it to zero in this circuit and this signal is obtained from SW2. Counting pulses (for stepping from one row to the next) are generated by the Line Feed key of the keyboard and this signal is detected by the keyboard interface



circuitry (to be described later) and fed to pin 14 of the Row Address Register.

## DEAD END COUNTERS

There are 16 discrete row address codes and the four binary stages within IC35 are a perfect match. This allows us to use another feature of this integrated circuit. It has a Maximum/Minimum count output at pin 12. When the counter reaches "All Ones" when counting UP this output goes to "1" and the same happens when the counter reaches "All Noughts" when counting DOWN. By feeding this signal back to the enable input of the circuit it allows us to turn the unit into a "Dead End Counter". This facility ensures that when the bottom row of the screen is reached a further depression of the line feed button does not set the counter back to zero—which would result in the writing position jumping back to the top row of the screen.

Because the outputs of this stage correspond to the Row Address Waveforms as generated by the Row Address Counter we give them similar designations suffixed by an "a". They are Q33a, 34a, 35a and Q36a. They are eventually compared with their equivalents Q33, 34, 35 and Q36 in the comparator comprising ICs 29 to 31 but more about this later.

The Column Address Register works on exactly the same principle. IC36 is a four stage UP/DOWN counter as is IC37 which provides the fifth bit of the comparison address. These two integrated counters are cascaded one into the next and both receive their direction instruction from the same flip flop as the Row Address Register. This register has to increment, every time a character key is depressed, on the release of the key. It also has to increment on receipt of the non-writing "Cursor Step" signal. These two signals are combined in the keyboard interface circuit and we see their combined signal (called Character Step) coming in to pin 14 of IC36.

To prevent the register cycling round to restart addresses for the row in question we again have to make it a "Dead End Counter". This is rather more complicated than for the Row Address Register because we cannot make use of the Maximum/Minimum signal from IC37 directly. This is because only its first stage is used. We therefore have the

Fig. 19. The schematic diagram of the "Up/Down" Counter, the Row Address Register, the Column Address Register, the Comparator and the "Direction Indicators".

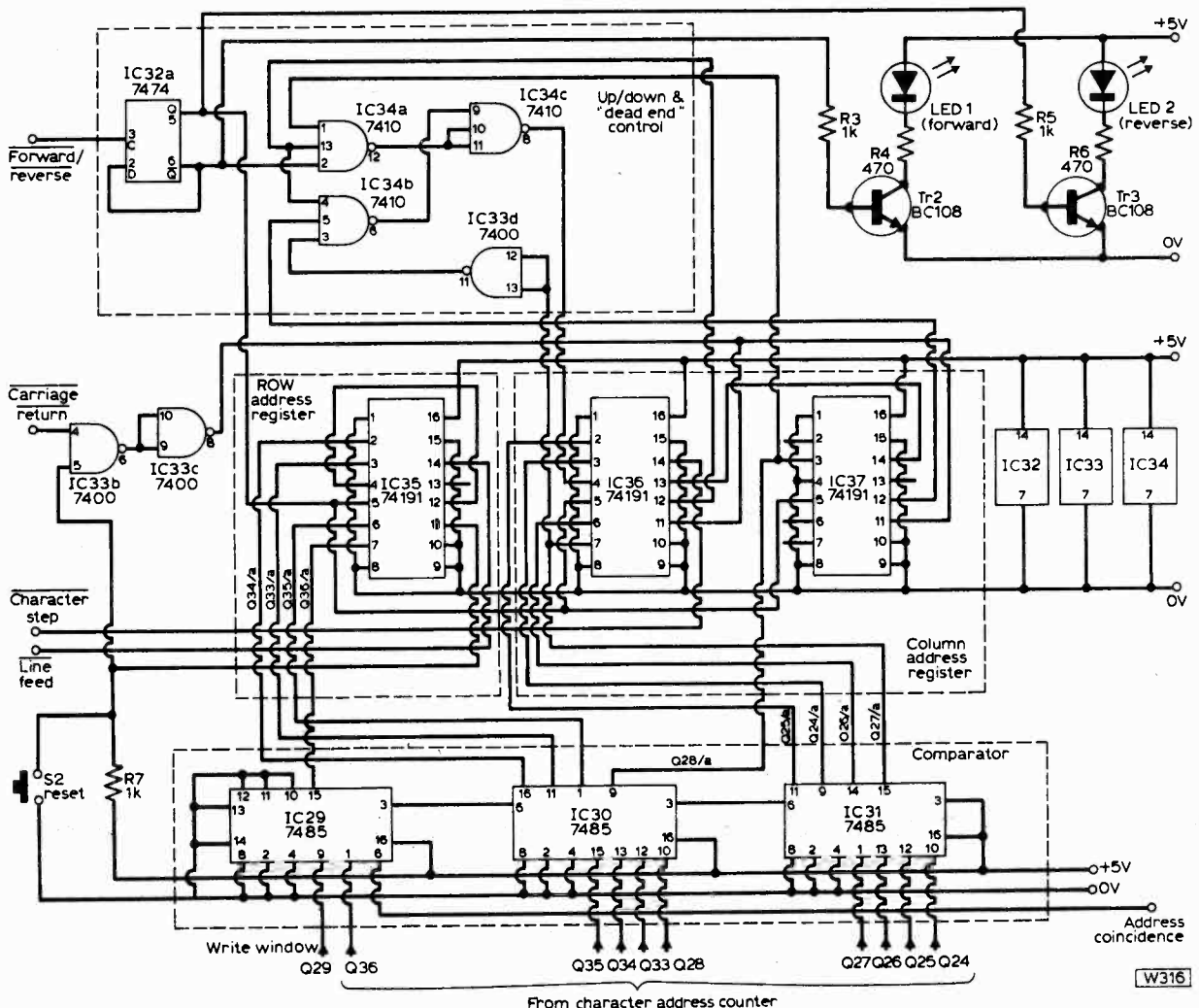


Fig. 20. The major portion of the wiring pattern on the etched board. The remaining pattern is on the component side of the board and can be seen as Fig. 21.


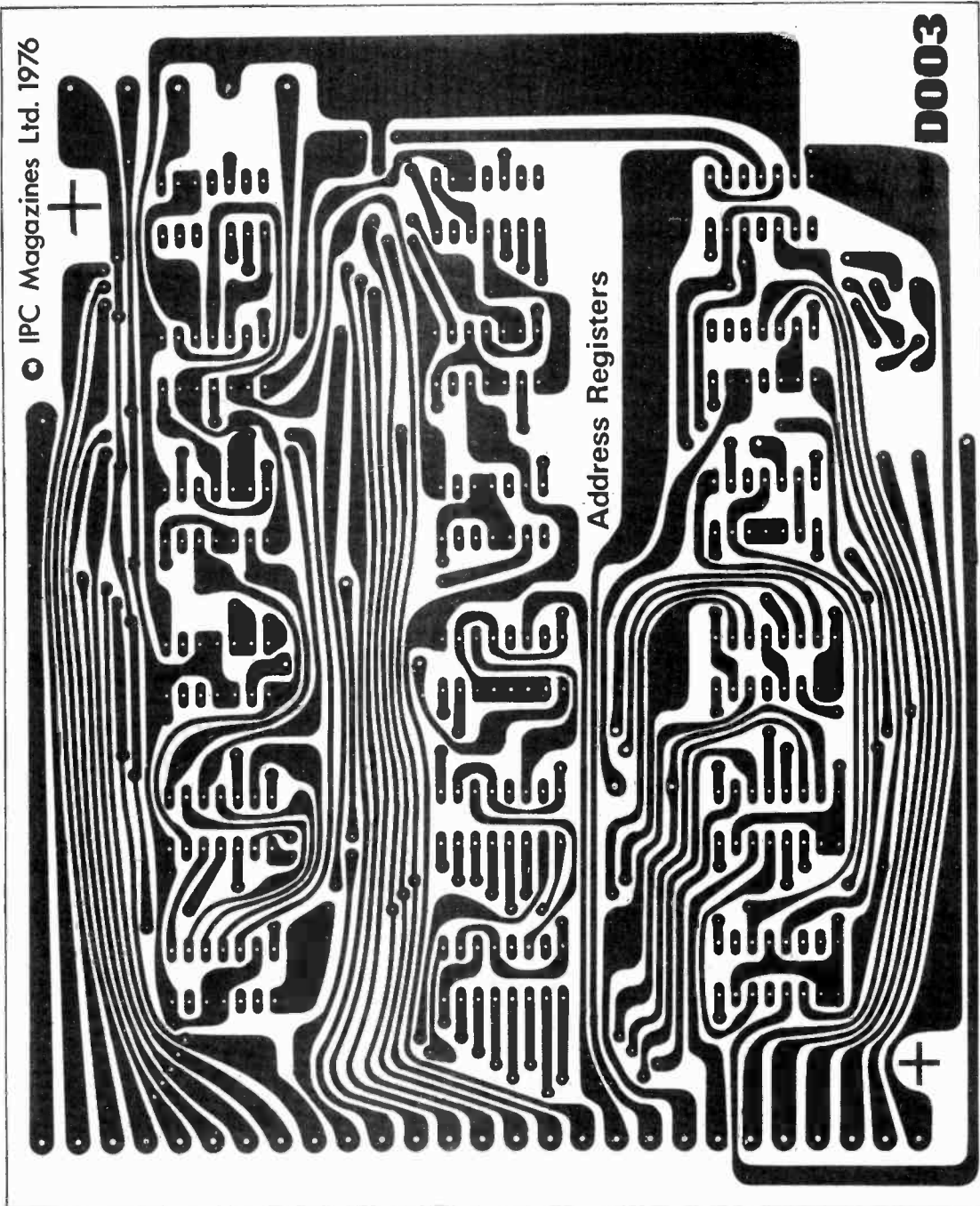


Fig. 21. The component locations on the board. Note that IC32 is reversed in orientation compared to all the other ICs on this board. Since R7 acts as a stake between the two sides of the board it is essential to solder both sides of both ends.

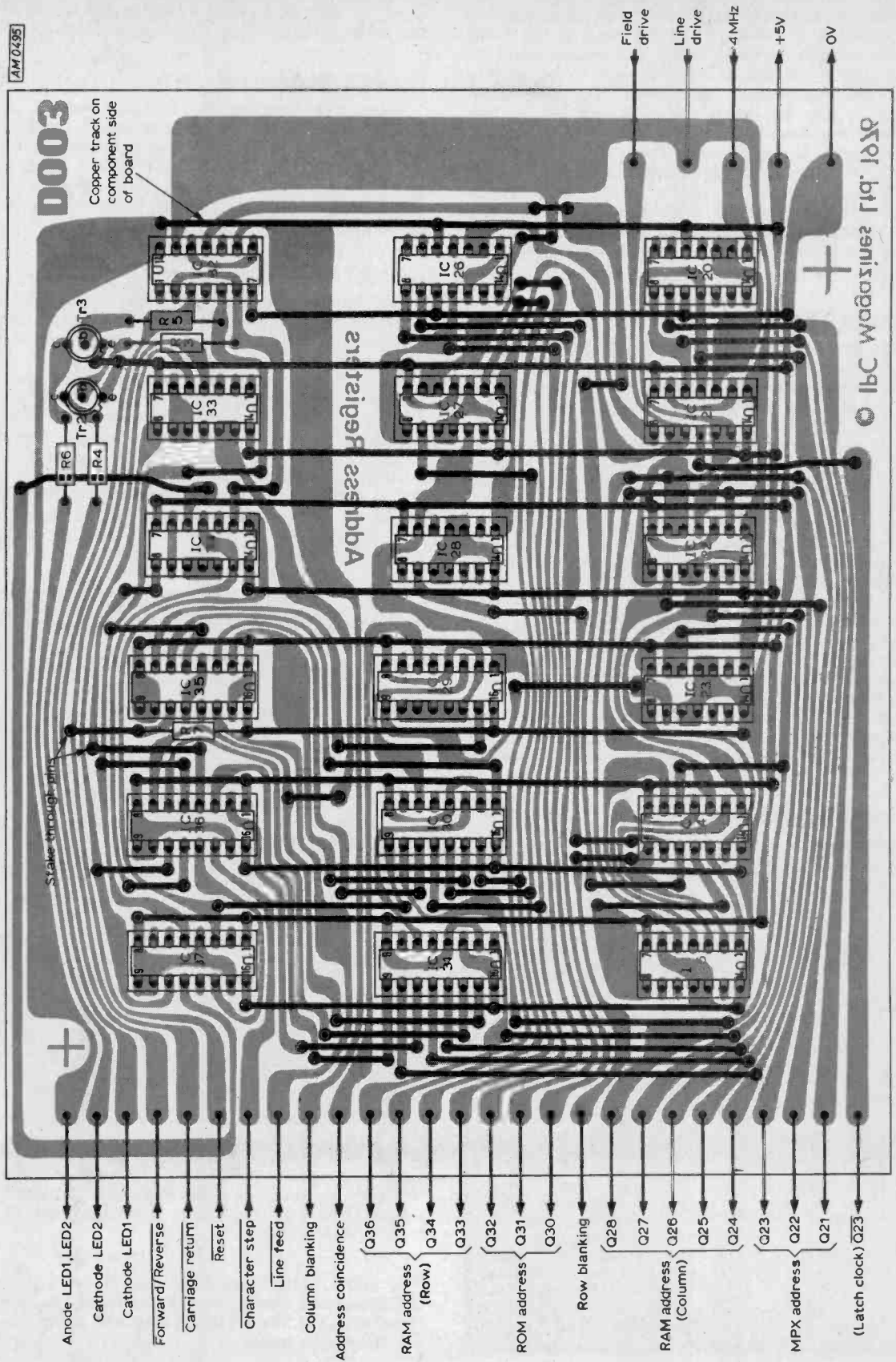

circuitry comprising IC33d and IC34a, b and c which detects the state of the counter and depending on the direction of counting and the state of the count it will activate, or de-activate, the enable input of IC36 (pin 4). Again it is convenient to be able to reset the register to "All Zeros" for an instant return to the left hand end of a row but in this instance we have to consider two sources of the reset signal. It might come from the reset button (SW2) which is used for starting from the top left hand corner of the screen or from the Carriage Return signal generated from the keyboard. These two signals are combined in IC33b and c before being fed to the reset inputs of the Column Address Register.

## COMPARATOR

The five outputs, Q24a, 25a, 26a, 27a and Q28a are fed to other stages of the comparator with their counterparts from the Column Address Counter. If we consider the four Row Address bits and the five Column Address bits together we can define any one of the 512 possible positions of character cells with a nine bit word. Provided we compare like bit with like (from the counter and register respectively) there will only be a perfect comparison of all nine pairs of bits when the Address Counter is addressing the cell position defined by the Register. Our comparator therefore has to be capable of handling nine pairs of variables and when coincidence occurs it must produce an output which is later used to generate the Write instruction.

We call the comparator's output "Address Coincidence." Note that we have one extra signal coming into the comparator at pin 9 of IC29; this is the Write Window which has already been described. We can use it at this stage to inhibit the generation of an Address Coincidence signal during the left and right hand margins by simply comparing

it against logic level "0". When the Write Window is at "0" and we have a perfect match of addresses the Address Coincidence signal goes "high".

## DIRECTION INDICATOR

Because a toggling flip flop is used to control the direction of the registers it would not be clear which way they were likely to go without some form of indicator. LEDs 1 and 2 are driven from the Q and  $\bar{Q}$  outputs of the direction change flip flop. When LED1 is lit it indicates "Forward" operation whereas LED2 indicates "Reverse" operation.

## CONSTRUCTION

The inter-component wiring for this unit is again provided by a double sided PCB. The major portion is shown in Fig 20, whilst the "overflow" is combined with the component layout of Fig 21.

From Fig 21 it is clear that most of the construction consists of inserting integrated circuits into their correct holes. However, we make no apology for repeating our previous warnings, namely:— check the orientation of the devices, ensure no pins are folded under, keep the heat from the soldering iron to a minimum and solder all the stakes on both sides. On the subject of stakes, note that R7 acts as a stake so each side of each end needs to be soldered.

### IMPORTANT CONSTRUCTIONAL NOTE

To prevent erratic logic conditions arising from current spiking—caused by the very high switching speeds of TTL and the heavy current drawn by its output during switching operations—it is usual to incorporate small value capacitors across the power rails. When the prototype was originally designed it was felt that these capacitors could be soldered across the power supply leads on the top of each board. As it turned out, there were no problems with spurious pulses hence the illustrations of the boards do not show the capacitors. If, after construction, there is any indication of erratic operation the constructor should connect four 0.22uF capacitors between the +5V and 0V rails at convenient positions on each board. These can be soldered directly to the topside printed wiring—if double sided boards are used. They should be distributed so that the de-coupling effect of each will affect as many of the IC packages as possible. There are no rules for this but, equally, there are unlikely to be any problems if the recommended layout is adopted.

You will notice that provision is made for flying leads to be taken to the two LEDs which should be mounted on the front panel in a convenient position. On the prototype there was room for them on the keyboard metalwork.

The third major board of the three, containing the Memories, the Keyboard Interface, The Cursor Generator and the Video Stages will be covered in our December issue.

## ★ components list

### Address Counter/Register/Comparator

#### Integrated Circuits

IC20 SN7493  
 IC21 SN7400  
 IC22 SN74177  
 IC23 SN74177  
 IC24 SN7404  
 IC25 SN7430  
 IC26 SN7493  
 IC27 SN74177  
 IC28 SN74177  
 IC29 SN7485  
 IC30 SN7485  
 IC31 SN7485  
 IC32 SN7474  
 IC33 SN7400  
 IC34 SN7410  
 IC35 SN74191  
 IC36 SN74191  
 IC37 SN74191

#### Resistors

R3 1k 10%, 1/4W  
 R4 470 10%, 1/4W  
 R5 1k 10%, 1/4W  
 R6 470 10%, 1/4W  
 R7 1k 10%, 1/4W

#### Semiconductors

Tr2 BC108  
 Tr3 BC108  
 LED1 MV5025 or similar  
 LED2 MV5025 or similar

#### Miscellaneous

Printed circuit board, code D003, from Readers PCB Service. DIL sockets, 12 off 14 way and 6 off 16 way (DIL strip sockets could be used). Tinned copper wire for staking. Board pins.

# How to get a reputation overnight for making Hi Fi equipment as good as ours.



To be perfectly honest, it's not that difficult.

Simply go out and buy a Goldring CK2 turntable construction kit. Follow the simple step by step instructions.

And in no time at all you'll be the proud owner of a superb, hand built, precision engineered deck.

Which can hardly fail to make your reputation amongst those who know about HiFi. And all achieved with the minimum capital outlay: around £28.00, plus V.A.T.

The Goldring CK2 kit is, in fact, based around the widely known G102 turntable.

The CK2 is belt driven, giving a wow and flutter reading of 0.15%, and rumble (weighted) -60dB.

The pick-up arm features a viscously damped raising and lowering device.


For the protection of your records, there's an anti-skate mechanism. And with an easily adjustable playing weight, the arm will accept a wide range of cartridges, such as

the Goldring G800.

A final touch is that both the on-off function and speed selection are via neat rocker switches.

If you fill in the coupon, we'll send you our free colour brochure, which describes the CK2 construction unit in detail.

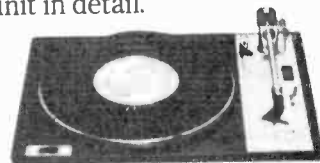And if you're serious about HiFi, you couldn't hope to ask for a better start than that.



To: Goldring Limited, Anglian Lane, Bury St. Edmunds, Suffolk IP32 6SS.  
Please tell me more about the Goldring CK2 Construction kit


Name \_\_\_\_\_

Address \_\_\_\_\_

FW1076

 **Goldring**  
Sound pure and simple



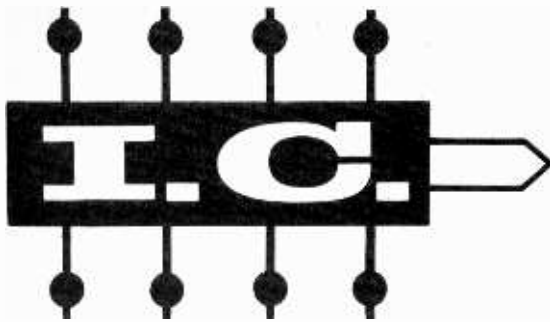

# OF THE MONTH

by BRIAN DANCE

Number 61

## MOTOROLA MC1339P STEREO PRE-AMP

THE Motorola MC1339P is a low-noise audio pre-amplifier package containing the two separate amplifiers required for a stereo system in a single 14 pin dual-in-line epoxy case. A power supply filter circuit is incorporated on the chip, whilst emitter follower circuits provide low output impedances.

### CHARACTERISTICS

The MC1339P is normally used with a 12V power supply, the supply current being typically 17.5mA (max. 22mA for any device) at this voltage. Although the absolute maximum permissible supply voltage is 16V, it is wise to use a somewhat smaller value to allow some margin of safety, since any momentary excursion above 16V can result in the destruction of the device. The maximum permissible internal dissipation is 625mW at 25°C.

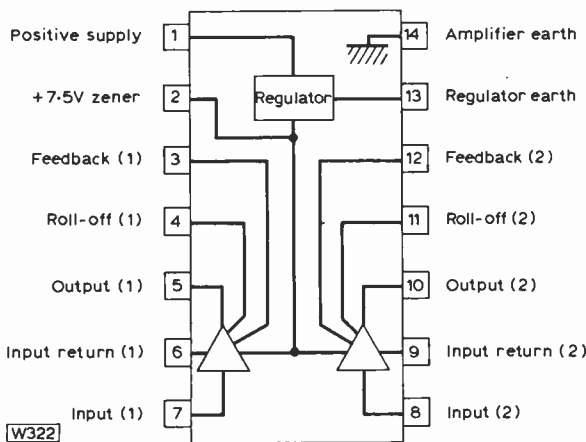


Fig. 1. The leadout connections for the MC1339P. The amplifiers are quite separate from each other.

The amplifiers of the MC1339P each have an open loop gain of typically 65dB. Their input resistance is about 250kΩ and the output resistance about 100Ω. The channel separation is typically 70dB whilst the internal circuit provides some 33dB power supply frequency rejection. The equivalent noise voltage at the input in the 100Hz to 10kHz range is about 0.7μV with a maximum of 3μV for any device.

The MC1339P is basically two operational amplifiers, with the connections shown in Fig. 1. It can be seen that various facilities are provided, such as a connection to pin 4 from which a by-pass capacitor can be connected to provide a rolling-off of the gain at high frequencies.

### TYPICAL AMPLIFIER

A typical general purpose pre-amplifier with a flat response over a wide frequency range is shown in Fig. 2. The input impedance is 10kΩ and the voltage gain 100 times (40dB) with the component values shown. The voltage gain is equal to  $(R3+R2)/R2$  and the values of these resistors may be adjusted for any reasonable value of gain. The frequency response rolls off below 100Hz, the gain falling to about 30dB at 15Hz. The high frequency response depends upon the value of C3. If the latter has a value of 500pF the response is flat to about 200kHz, whilst when C3 has a value of 1000pF the response is level to about 40kHz.

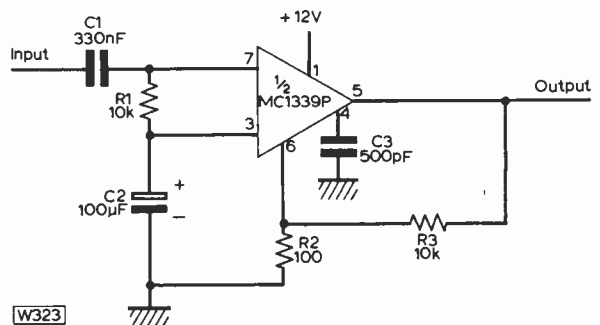


Fig. 2. Circuit of a wideband pre-amplifier using one half of the IC. The other half would be identical for stereo work.

The pin numbers shown are for the one amplifier of the MC1339P, but the other amplifier can be used in a similar circuit. This remark applies to the other circuits to be discussed.

### RECORD PLAYER

The output of a typical magnetic cartridge of a record player is about 2 to 12mV RMS to a pre-amplifier with an appreciable gain is required before

**Random FLASHER UNIT**



Wired ready for use  
Complete with three  
100 watt coloured lamps  
that flash independently  
at random

**£18.95**

**TWIN BANK 6 LIGHT UNIT**  
(less lamps) LENGTH 14 1/2 inches



B.C. Fitting **£9.55**  
E.S. Fitting **£10.35**  
EACH

**Sound to Light MASTER UNIT**



600 WATTS PER CHANNEL

**£30.95**

INCLUDING CHANNEL OUTPUT PLUGS AND MAINS INPUT SOCKET

**TYPE A SPOT**  
(less lamp)



B.C. Fitting **£1.95** EACH  
E.S. Fitting **£2.12** EACH

**TYPE B 3 BANK UNIT**  
(Less Lamps)



B.C. Fitting **£6.90** EACH  
E.S. Fitting **£7.26** EACH

**TWIN BANK 12 LIGHT UNIT**  
(less lamps) Length 31 1/2



B.C. Fitting **£15.60** EACH  
E.S. Fitting **£17.00** EACH

100 WATT SPOT LAMPS  
RED, YELLOW, GREEN  
BLUE, CLEAR

Maximum 3 lamps

**£1.18** each **£3.54**


B.C. or E.S. Fitting

ALL PRICES INCLUDE V.A.T. and POST & PACKING (Please allow 2 weeks for the United Kingdom only)

Send Zip for illustrated leaflet & price list

**ALBEN ENGINEERING CO. LTD.**  
DEPT. P.W. THE CRESCENT, WORSTHORNE,  
BURNLEY, LANCS. Tel: Burnley 20940

# Brush up on your record care

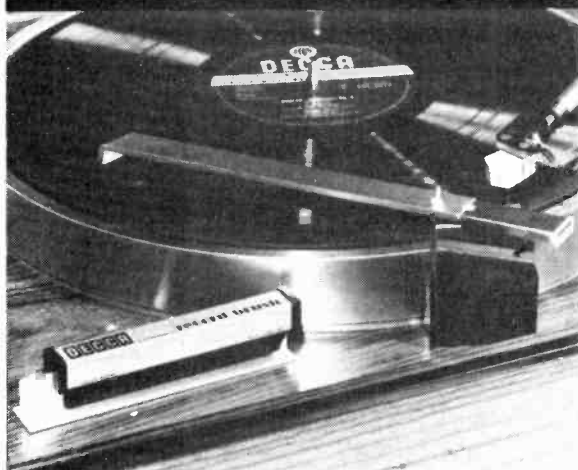

Presenting two superb cleaners from Decca Special Products in the Decca Record Brush and the Decca Record Cleaner. Two different designs but both using the same miracle conductive fibre with a diameter which can clean right to the bottom of your record grooves, overcoming both your static and dust problems without any need of anti-static fluids.

The Record Brush consists of a handbrush using a million tiny fibre 'bristles'. Each sweep of the record surface thus allowing upwards of a thousand bristles to enter each groove in order to clean it.

The Record Cleaner consists of an electrically conducting arm carrying a brush made from the same unique fibrous material.

The Decca Record Brush or the Decca Record Cleaner; two ways of ensuring that your valuable record collection is kept in excellent condition.




Decca Special Products  
Ingate Place, Queenstown Road,  
London SW8 3NT

## Build circuits in minutes using the low-cost modular breadboard S-DeC

An S-DeC is a breadboard which allows components to be inserted into it without soldering. Holes are numbered for identification and re-use purposes. Electronic components are plugged into the holes via their leads. Beneath the holes are metal sockets connected together electrically in accordance with a pattern shown on the upper surface of the S-DeC. By plugging in the components, you can build electronic circuits in minutes—without using a soldering iron. When you have built your circuit, simply unplug the components and use them over and over again to build other circuits on your S-DeC.

With every S-DeC you receive a free booklet showing how to build nine super circuits. There is also a free control panel to accommodate things like tuning capacitors and variable resistors.

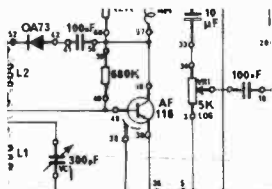The S-DeC, booklet and control panel costs only £1.98p plus 37p postage, packaging and VAT. Send your cheque/PO now and start building electronic circuits the easy way.



**P.B. Electronics (Scotland) Ltd.**

57 HIGH STREET, SAFFRON WALDEN, ESSEX CB10 1AA.  
Telephone: Saffron Walden (0799) 22876. PWO

# TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH

**NO HIDDEN EXTRAS**—Prices include VAT and P & P. EXCEPT

↑ WHERE CARRIAGE WILL BE ACCORDING TO WEIGHT & DISTANCE—BRS. Electropoil, Audio accessories, semiconductors, Panel Meters & Multi-Meters

CALLERS WELCOME (MON.-FRI.) OR SEND STAMP FOR LISTS.

## MAINS ISOLATING

Prim. 120/240V  
Sec. 120/240V  
Centre tap with screen

Ref.	VA	(Watts)	£
07*	20	4.57	
149	60	6.68	
150	100	7.65	
151	200	11.95	
152	250	14.47	
153	350	17.14	
154	500	19.73	
155	750	27.25	
156	1000	37.97	
157	1500	43.33	
158	2000	48.34	
159	3000	76.36	

\*115V or 240V Sec. only.

## 12 and or 24 Volt

PRIMARY 240-250 VOLTS

Ref.	12v	24v	£
111	0.5	0.25	2.30
213	1.0	0.5	3.01
71	2	—	3.69
68	3	—	5.10
18	4	—	4.56
85	5	—	5.61
70	6	3	6.36
108	8	4	7.34
72	10	5	7.86
116	12	6	8.39
17	16	8	10.48
115	20	10	15.42
187	30	15	19.50
226	60	30	21.94

## HIGH VOLTAGE

Mainly Isolating

Prim.	200/220 or 200/240	Sec.	100/120 or 200/240	P & P	£
VA	Ref.	£			
60	243	6.62			
350	247	18.23			
1000	250	32.68			
2000	252	54.80			

## AUTO TRANSFORMERS

Ref	VA	Auto Taps	(Watts)	£
113	20	0-115-210-240	2.81	
64	75	—	4.65	
4	150	0-115-200-220-240	8.62	
66	300	—	8.62	
67	500	—	13.10	
84	1000	—	19.70	
93	1500	—	23.62	
95	2000	—	31.56	
73	3000	—	45.76	

## CASED AUTO TRANSFORMERS

240V mains lead input & USA 2 pin outlets.

20VA	£	Ref
113W	4.95	113W
150VA	8.94	4W
500VA	15.11	67W
1000VA	22.84	84W
2000VA	43.66	95W

Electronic Construction Kit  
10-Project (including electronic organ)  
ideal gift at £8.63.

## 50 VOLT RANGE

Prim. 200-240V  
Sec. 0-19-25-33-40-50V

Ref.	No.	Amps	£
102	0.5	4.07	
103	1.0	5.27	
104	2.0	7.17	
105	3.0	8.77	
106	4.0	11.26	
107	6.0	17.29	
118	8.0	18.62	
119	10.0	22.04	

## SCREENED MINIATURES

Ref	mA	Volts	£
238	200	3-0-3	2.50
212	1A, 1A	0-6, 0-6	2.97
13	100	0-9, 0-9	2.28
235	330, 330	0-9, 0-9	2.39
207	500, 500	0-8-9, 0-8-9	3.14
208	1A, 1A	0-8-9, 0-8-9	4.51
236	200, 200	0-15, 0-15	2.28
214	300, 300	0-20, 0-20	3.22
221	700 (DC)	20-12-0-12-20	3.66
206	1A, 1A	0-15-20, 0-15-20	5.37
203	500, 500	0-15-27, 0-15-27	4.77
204	1A, 1A	0-15-27, 0-15-27	6.00
5112	500	12, 15, 20, 24, 30	3.15

## C1000 MINI-MULTIMETER

DC-1000V AC-1000V 1000Ω/V  
DCI-100mA RES-150kΩ  
BARGAIN AT £4.59

**ANTEX SOLDERING IRONS**  
15W £3.57 18W £3.31 25W £2.99  
**SOLDERING IRON KIT**  
£4.48 STAND FOR ABOVE £1.49

**MAGNETIC TO CERAMIC CARTRIDGE CONVERTOR**  
OPERATING VOLTAGE 20-45V  
ONLY £3.17.

## COMPONENT PAKS

200 Mixed value resistors (count by weight)  
150 Mixed value capacitors (count by weight)  
30 Mixed value precision resistors  $\pm$  2%  
15 Assorted pots & pre-seets  
10 Reed switches  
3 Micro Switches  
2 Assorted tag strips  
PLEASE STATE PAK REQUIRED  
90p PER PAK.

## HIGH QUALITY MODULES

3 Watt RMS AMPLIFIER	£2.78
5 Watt RMS AMPLIFIER	£3.17
10 Watt RMS AMPLIFIER	£3.81
25 Watt RMS AMPLIFIER	£4.67
125W RMS AMPLIFIER	£17.50
PRE-AMP for 3-5-10W	£7.50
PRE-AMP for 25W	£15.79
POWER SUPPLIES 3-5-10W	£1.54
POWER SUPPLIES 25W	£3.56
TRANSFORMER 3W	£2.77
TRANSFORMER 5-10W	£3.22
TRANSFORMER 25W	£3.56

## AUDIO KIT 25W

2+25W Amplifiers  
1+Pre-Amp  
1+Power supply  
1+Transformer  
1+Front Panel  
1+Kit of parts to include on-off switch, neon ind. Stereo headphone socket. Plus instructions book £32.18.

## TEAK AUDIO KIT 25W

Teak veneered cabinet  
16 $\frac{1}{2}$ "x11 $\frac{1}{2}$ "x3 $\frac{1}{2}$ ", aluminium chassis, heat sink and front panel brackets plus back panel and sockets etc. £11.21

## BSR MINI-DECK

4 Speed Single-or Auto-changer (chassis) £7.61  
BSR P128R Single and Auto (Chassis) £20.54  
GARRARD SP25 IV ("") £21.36

## NEW STEREO 30

Complete Stereo Chassis inc.:  
7+7w RMS, Amp, Pre-amp, Power Supply, Front Panel, Knobs (only needs Mains Trans.).  
Stereo 30 £17.99, Mains Trans £3.56. Teak veneered cab. £4.54.

## CARTRIDGES

Magnetic Sonotone 100 £5.31  
Ceramic E.E.I.C.S 2000 £2.72  
ACOS GP93-1 £2.11  
TCC AT-55 £4.42

## 30 VOLT RANGE

Prim. 200-240V  
Sec. 0-12-15-20-24-30V

Ref.	Amps	£
112	0.5	3.15
79	1.0	4.00
3	2.0	5.35
20	3.0	6.87
21	4.0	7.93
51	5.0	9.55
117	6.0	10.69
88	8.0	14.15
89	10.0	14.31

## 60 VOLT RANGE

Prim. 200-240V  
Sec. 0-24-30-40-48-60V

Ref.	Amps	£
124	0.5	3.94
126	1.0	5.43
127	2.0	7.63
125	3.0	11.00
123	4.0	13.07
40	5.0	14.20
120	6.0	16.64
121	8.0	19.56
122	10.0	24.09
189	12.0	25.16

## NEW TRANS CASES

Combined wall and floor mounting. Send for details.

## BRIDGE RECTIFIERS

200V	2A	0.67
400V	2A	0.72
200V	4A	0.89
500V	10A	2.70

## TEST METERS

AVO 8 MK5	£67.33
AVO 72	£26.86
AVO MM5	£23.48
AVO TT 169	£27.34
U4315	£13.93

(USSR) inc. Steel carry case.

## POWER UNIT

CC12-05 Output Switched  
3-4.5-6-7.5-9-12V  
at 500mA. £5.18.

## STEREO FM TUNER fitted with Phase-lock Loop

4 Pre-selected stations supply 20-35V. 90mA Max. £22.72


## Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ  
TELEPHONE: 01-488 3316/7/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST
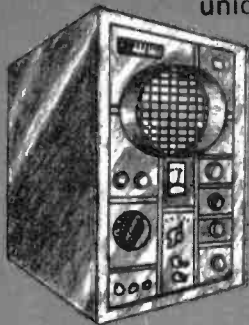
# 1. Understand electronics.


Step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered using our unique Lerna-Kit course.



- (1) Build an oscilloscope.
- (2) Read, draw and understand circuit diagrams.
- (3) Carry out over 40 experiments on basic electronic circuits and see how they work.
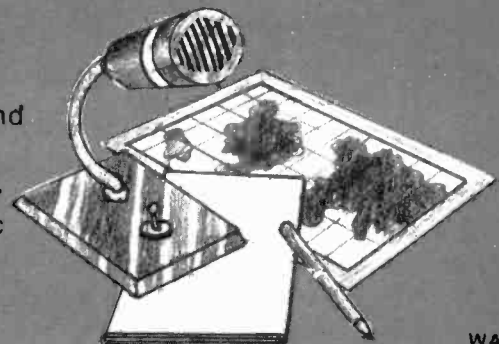
# 2. Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.



Free!

Brochure, without obligation to:  
**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**  
P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

Block caps please

the main amplifier. This pre-amplifier must also have the required response to match the RIAA recording characteristic used by record manufacturers. In contrast, crystal and ceramic pick-up heads are not usually used with a pre-amplifier, since they provide a much higher output voltage than magnetic cartridges.


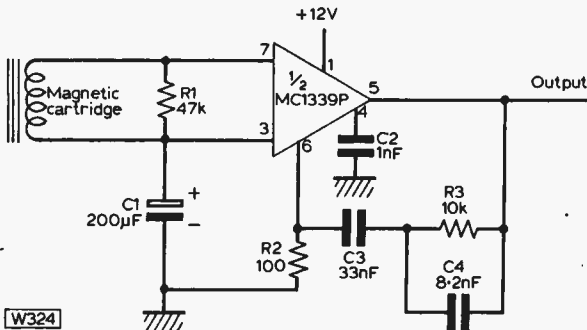


Fig. 3, above, in this application the MC1339P is used as an amplifier with a magnetic cartridge.

Fig. 4, below, the response to be expected from the circuit of Fig. 3 together with the ideal RIAA curve.

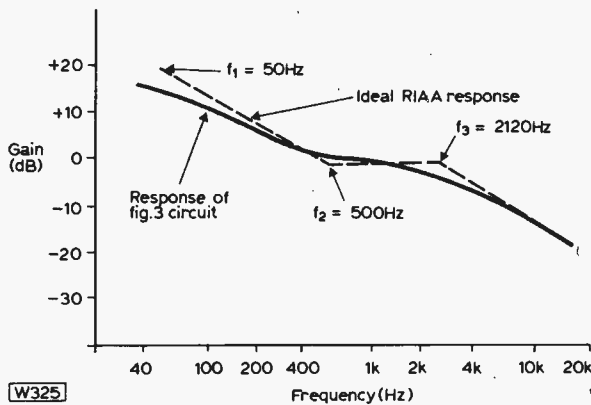

A pre-amplifier for use with a magnetic cartridge is shown in Fig. 3. This provides the response shown in Fig. 4 which is very close to the ideal RIAA response shown dotted in Fig. 4. The values of the two 'corner' frequencies  $f_2$  and  $f_3$  are determined by the values of  $C_3$  and  $C_4$  respectively. The low frequency response is determined by the value of  $C_1$ .

$$f_2 = \frac{1}{2\pi R_3 C_3} \quad f_3 = \frac{1}{2\pi R_3 C_4}$$

### PLAYBACK AMPLIFIER

A low noise, high gain tape playback amplifier is shown in Fig. 5. This provides the special frequency compensation required to produce the NAB standard playback equalisation curve of Fig. 6. The output is about 100mV with an input from a tape head of 2.2mV at 1kHz. The low frequency response is determined by the value of  $C_2$ , whilst  $C_3$  provides the bass frequency boost. The minimum high frequency gain is set by the ratio  $(R_3 + R_2)/R_2$ .

### TAPE RECORDER AMPLIFIER

The frequency response of a tape recording amplifier must be the mirror image of the NAB


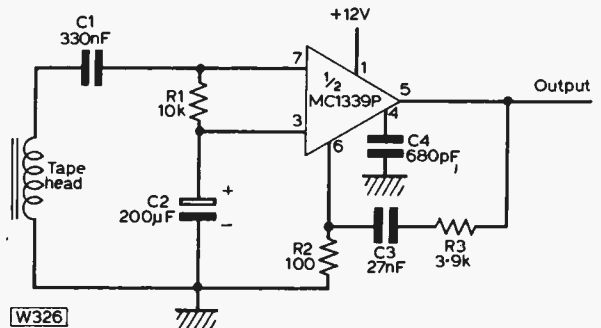


Fig. 5, above, a tape playback amplifier incorporating NAB equalisation. Fig. 6, below, illustrates the frequency response of Fig. 5.

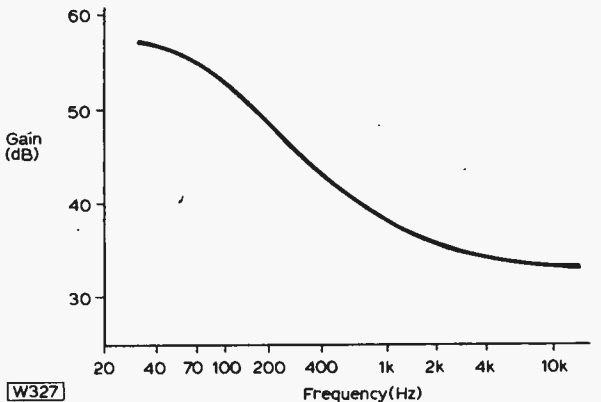

playback equalisation characteristic in order that the overall record/playback response shall be flat. The circuit shown in Fig. 7 will produce the required recording characteristic of Fig. 8.

The parallel inductance-capacitance circuit at the output of this amplifier forms the bias trap and must resonate at the bias oscillator frequency. It prevents the bias signal from passing to the output of the recording amplifier. Any reasonable inductance and capacitance values can be used, but the Q factor should be reasonably high for good bias rejection.

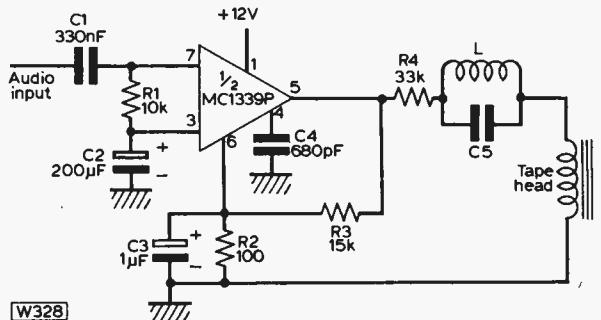


Fig. 7. Amplifier circuit for feeding a signal to a tape head during recording. Capacitor  $C_5$  resonates with inductor  $L$  at the bias frequency employed in the recorder.

This circuit is, for example, suitable for amplifying the 10mV output from a microphone to provide the 30µA recording current required by a typical tape recording head. The 30µA current is simulated by a 1V RMS signal at the output pin 5, feeding the head through the 33kΩ resistor  $R_4$  at 1kHz. The voltage gain required at this frequency is thus 100 (40dB)

but the value of R3 is chosen to give a somewhat greater low frequency gain, since the open-loop gain of the amplifier is not infinite.

The response of a typical quarter track head at a tape speed of 3 $\frac{3}{4}$  i.p.s. is typically 3dB down at 1770Hz. The value shown for C3 provides the required compensating boost at this frequency. One might feel a resistor would be needed in series with C3 to roll off the high frequency gain at frequencies over 20kHz, but this is not necessary since the fall in the open loop gain of the amplifier itself provides the required roll off. The low frequency response is determined by the value of the coupling capacitor C1.

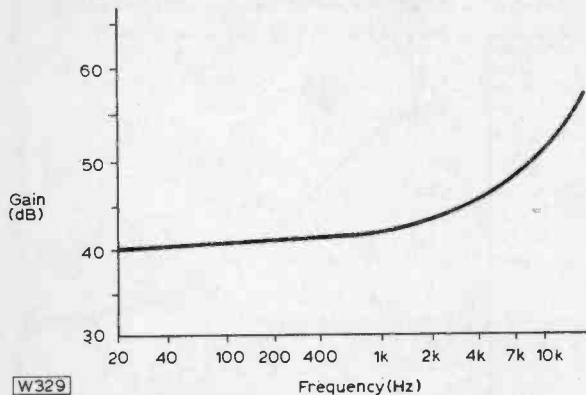


Fig. 8. Frequency response of the circuit in Fig. 7.

The MC1339P is available from Trampus Electronics Ltd., 58-60 Grove Road, Windsor, Berkshire SL4 1HS and from Chromasonic Electronics, 56 Fortis Green Road, Muswell Hill, London, N10 3HN.

## Mail Order Protection Scheme


The Publishers of *Practical Wireless* are members of the Periodical Publishers Association which has given an undertaking to the Director General of Fair Trading to refund monies sent by readers in response to mail order advertisements, placed by mail order traders, who fail to supply goods or refund monies owing to liquidation or bankruptcy. This arrangement does not apply to any failure to supply goods advertised in a catalogue or in a direct mail solicitation.

In the unhappy event of the failure of a mail order trader readers are advised to lodge a claim with *Practical Wireless* within three months of the date of the appearance of the advertisement, providing proof of payment. Claims lodged after this period will be considered at the Publisher's discretion. Since all refunds are made by the magazine voluntarily and at its own expense, this undertaking enables you to respond to our mail order advertisers with the fullest confidence.

For the purpose of this scheme, mail order advertising is defined as—

'Direct response advertisements, display or postal bargains where cash had to be sent in advance of goods being delivered.' Classified and catalogue mail order advertising are excluded.

# PW TECHNICROSS PUZZLE No.16

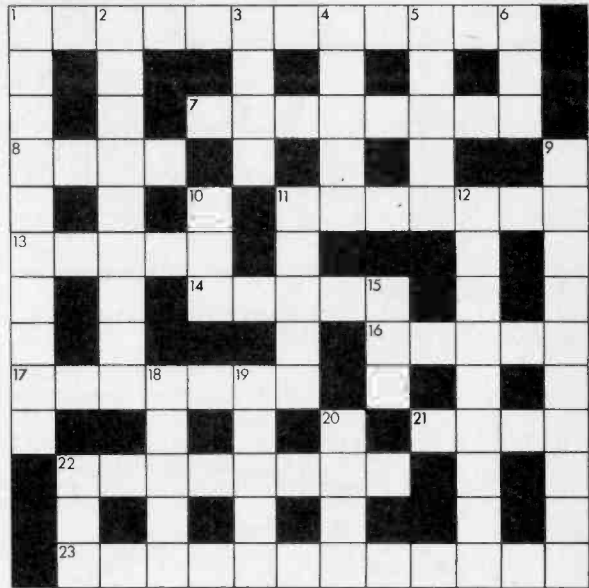

### ACROSS

- 1 Utmost faith in such audio systems? (4, 8)
- 7 Trades 10 modulators for a wireless? (5-3)
- 8 Length of tape to make you look sideways, backwards! (4)
- 11 Bubbles to see Seth's changed hook-up? (7)
- 13 Then a transformer could be in a Welsh town? (5)
- 14 Skill in his comeback as conductor is zero! (5)
- 16 Disc that's taped as an honour? (5)
- 17 Blow-out in tin adaptor and you need percipience? (7)
- 21 Marconi made two starters for Mum? (4)
- 22 He's been given the target of transmission? (8)
- 23 Quite obvious it's like cats-whisker reception! (7, 5)

### DOWN

- 1 Amplifier with a built-in listener? (7-3)
- 2 Makes a powerful contribution? (9)
- 3 Solid state based on oil in hair antennae? (4)
- 4 Battery-makers team with 500 between points (5)
- 5 Plan corner piece as a radio component? (5)
- 6 Your superhet outside still? (3)
- 9 Current source for your choice of stable relaxation? (10)
- 10 He's oscillating with her! (3)
- 11 Fish for reconditioned parts? (5)
- 12 Impedances in switching—in theory, anyway (9)
- 15 Initial label that made the dog spin! (3)
- 18 Object about old aerial and why sound irritating? (5)
- 19 Raise to his modulation? (5)
- 20 The Ringer recorded by Edison? (4)
- 22 Fabulous bird makes electro-coil centres? (3)

FOR AMUSEMENT ONLY  
ANSWERS NEXT MONTH



## 20x20 Watt STEREO AMPLIFIER

Superb Viscount IV unit in teak-finished cabinet. Black fascia with aluminium rotary controls and pushbuttons, red mains indicator and stereo jack socket. Function switch for mic, magnetic and crystal pick-ups, tape, tuner, and auxiliary. Rear panel features two mains outlets, DIN speaker and input sockets, plus fuse 20+20 watts rms, 40+40 watts peak.

**HOW YOU CAN SAVE £29<sup>90</sup>**  
+ p & p £2.10

### SYSTEM 1B

For only £80, you get the 20+20 watt Viscount IV amplifier; a pair of our 12-watt-rms Duo Type IIb matched speakers; a BSR MP 60 type deck complete with magnetic cartridge, de luxe plinth and cover.

**£80<sup>00</sup>**  
+ p & p £6.50

### SYSTEM 2

Comprising our 20+20 watt Viscount IV amplifier; a pair of our large Duo Type III matching speakers which handle 20 watts rms each; and a BSR MP 60 type deck with magnetic cartridge, de luxe plinth and cover.

**£92<sup>00</sup>**  
+ p & p £7.60

Carriage surcharge to Scotland: System 1b £2.50, System 2 £5



**SPEAKERS** Two models— Duo IIb, teak veneer, 12 watts rms, 24 watts peak, 18 1/2" x 13 1/2" x 7 1/4" approx.

**£34** PER PAIR  
+ p & p £6.50


Duo III, 20 watts rms, 40 watts peak, 27" x 13" x 11 1/2"

**£48** PER PAIR  
+ p & p £7.50

**TURNTABLE** Popular BSR MP 60 type, complete with magnetic cartridge, diamond stylus, and de luxe plinth and cover.

**£24<sup>00</sup>**  
+ p & p £3.50

**VALUE**

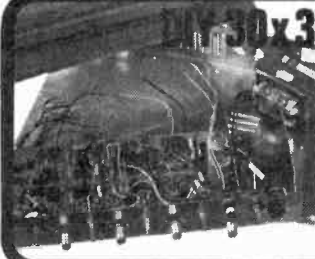

## 30x30 AMPLIFIER KIT

Specially designed by RT-VC for the experience constructor, this kit comes complete in every detail. Same facilities as Viscount IV amplifier. Chassis is ready punched, drilled and formed. Cabinet is finished in teak veneer. Black fascia and easy-to-handle aluminium knobs. Output 30+30 watts rms, 60+60 peak.

**£29<sup>00</sup>**  
+ p & p £2.10

## STEREO CASSETTE DECK KIT

Again, this kit is specially designed for the experienced constructor — for mounting into his own cabinet. Features include solenoid-assisted AUTO-STOP, 3-digit counter, record/replay PC board, mains transformer and input and output controls. AC BIAS AND ERASE.

**£32<sup>50</sup>**  
+ p & p £1.50

## DELUXE ACCESSORY KIT

Comprises of a matched pair of dynamic mics, and two replacement slider level controls. P & P FREE WHEN PURCHASED TOGETHER WITH ABOVE ITEM

**£3.95** + p & p £1.00



## DIY STEREO SYSTEM

COMPLETE WITH SPEAKERS

Here's real value in DIY! Comprises ready-built amplifier module, 3-speed Garrard auto-return deck, and teak-veneered simulate cabinets with clear plastic top. Easily built by hobbyists.

**£26<sup>95</sup>**  
+ p & p £4.05



## TURNTABLES BY BSR

Big value from RT-VC! Two units COMPLETE WITH PLINTHS. First, the popular MP 60 type semi-professional deck.

**£17<sup>50</sup>** + p & p £2.50

Second, the lower-cost C141 automatic unit, fitted with a stereo ceramic cartridge.

**£11<sup>95</sup>** + p & p £2.55

Both units have plinths finished in superb teak veneer. Either way, you're on to a bargain from RT-VC.

## STEREO AMPLIFIER KIT

Build up a 4-watts rms per channel stereo amplifier with Unisound MK2 modules. For only £9.95

you get pre-amp, power amp, and all the control panel parts. Features include IC power chips for low distortion. For the experienced constructor only.

**£9<sup>95</sup>**  
+ p & p £1.55



## 35-WATT DISCO AMP

Here's the mono unit you need to start off with. Gives you a good solid 35 watts rms, 70 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.

**£27<sup>50</sup>** + p & p £1.50


## 70 and 100 WATT DISCO AMPLIFIERS

Brilliantly styled for easy disco performance! Sloping fascia, so that you can use the controls without fuss or bother. Brushed aluminium fascia and rotary controls. Five smooth-acting, vertically mounted slide controls — master volume, tape level, mic level, deck level, PLUS INTER-DECK FADER for perfect graduated change from record deck No 1 to No. 2, or vice-versa. Pre-fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. 70 watts rms, 140 watts peak output.

**£49<sup>00</sup>**  
+ p & p £3.00

All the big features as on the 70-watt disco amplifier, but with a massive 100 watts rms, 200 watts peak output power.

**£65<sup>00</sup>**  
p & p £4.00

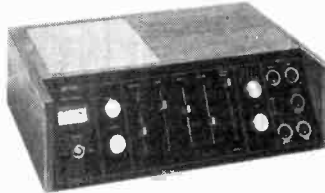

## PORTABLE DISCO CONSOLE with built-in pre-amplifiers

Here's the big-value portable disco console from RT-VC! It features a pair of BSR MP 60 type auto-return, single-play professional series record decks. Plus all the controls and features you need to give fabulous disco performances. Simply connects into your existing slave or external amplifier.

**£55<sup>00</sup>**  
+ p & p £6.50



## EASY-TO-BUILD, WITH ENCLOSURE

Specially designed by RT-VC for cost-conscious hi-fi enthusiasts, these kits incorporate two teak-simulate enclosures, two EMI 13" x 8" (approx.) woofers, two 3 1/4" (approx.) tweeters and a pair of matching crossovers. Easily constructed, using a few basic tools. Supplied complete with an easy-to-follow circuit diagram, and crossover components. Input 15 watts rms, 30 watts peak, each unit. Cabinet size 20" x 11" x 9 1/2" (approx.).

**£25<sup>50</sup>** PER PAIR  
+ p & p £5.50

## 15-WATT KIT IN CHASSIS FORM

When you are looking for a good speaker, why not build your own from this kit. It's the unit which we supply with the above enclosures. Size 13" x 8" (approx.) EMI woofer, 3 1/4" (approx.) tweeter, and matching crossover. Power handling capacity 15 watts rms, 30 watts peak.

**£7<sup>50</sup>** PER SET  
+ p & p

## 20-WATT HI-FI KIT IN CHASSIS FORM

For extra power, choose this super RT-VC kit! EMI 13" x 8" (approx.) triple-laminate-coned woofer with massive 5" (approx.) magnet, plus 5" (approx.) mid-range unit with concentric 2" parasitic tweeter and 2 3/4" (approx.) magnet. Complete with circuit diagram and crossover components.

**£10<sup>50</sup>** PER SET  
+ p & p £2

## DIY SPEAKER KITS

### 'COMPACT' FOR TOP VALUE

How about this for incredible bookshelf value from RT-VC! A pair of high efficiency units for only £7.50 — just what you need for low-power amplifiers. These infinite baffle enclosures come to you ready mitted and professionally finished. Each cabinet measures 12" x 9" x 5" (approx.) deep, and is finished in simulated teak. Complete with two 8" (approx.) speakers for max. power handling of 7 watts.

**£7<sup>50</sup>** PER PAIR  
p & p £1.70

## ELECTROLYTIC CAPACITORS AT BARGAIN PRICES

all brand new from reputable international manufacturers.  
**PACK 1** Containing 30 mixed Electrolytics, values from 4.7 mfd to 47 mfd. Minimum 16V working. 55p + 20p p&p.  
**PACK 2** Containing 17 mixed Electrolytic valves from 100 mfd to 2200 mfd. Minimum 16V working. Majority 40V working. 75p + 20p p&p.

## ALL PRICES INC. VAT AT CURRENT RATES

GOODS NOT DESPATCHED OUTSIDE UK  
All items subject to availability.  
Price correct at 1st September 1976 and subject to change without notice.

For further information, please send stamped addressed envelope



21C HIGH STREET, ACTON, LONDON W3 6NG  
323 EDGWARE ROAD, LONDON W2  
Personal Shoppers EDGWARE ROAD, 9 a.m.—5.30 p.m.  
Half day Thurs.  
ACTON, 9.30 a.m.—5 p.m. Closed all day Wed.



Minimum order on Access and BarclayCards £15

DO NOT SEND CARD  
Just write your order giving your credit card number

# TANDY

**START 'EM  
RIGHT WITH  
SCIENCE FAIR  
P-BOX KITS**

## IC MW RADIO KIT

Like all Tandy P-Box kits, they build the 'pro' way—by 'bread-boarding'. Easy to follow instructions aid in building a great MW sound from speaker or plug-in earphone.




**SUPER  
£4.49  
VALUE**

28-111
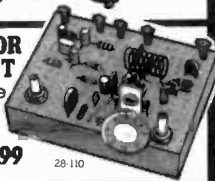
## 3-TRANSISTOR SW RADIO KIT

Brings you the world on 4.5-50 MHz.  
**NEW LOW PRICE £6.99**



28-110

## MORE EXCITING P-BOX KITS

MORSE CODE KIT (28-105)	£3.29	NIGHT-LIGHT KIT (28-125)	£1.99
SIREN KIT (28-107)	£3.99	BURGLAR ALARM KIT (28-128)	£4.69
PHONE BOOSTER KIT (28-116)	£4.99	ELECTRONIC ORGAN KIT (28-101)	£4.95
ELECTRONIC METRONOME (28-118)	£2.95	METAL LOCATOR KIT (28-134)	£4.99
"COOPY-LITE" FLASHER KIT (28-130)	£3.99		

Batteries necessary for all kits are extra. All offers subject to availability.

## P-BOX KIT VOUCHER

(as advertised)

Name \_\_\_\_\_

Address \_\_\_\_\_

**£1  
OFF**

FOR TANDY

*Bob Gault*

PW3

Fill in your name and address and take this voucher to any Tandy store. It's worth £1 off any P-Box Kit advertised above. 1 per customer. Offer ends 30.11.76

Available from any of our 150 stores

# TANDY

Nationwide supermarket of sound!

# PRECISION PETITE LTD.

119A HIGH STREET, TEDDINGTON, MIDDX. TEL. 01-977 0878

Now with the

## • NEW MK. II DRILL •

10,000 r.p.m., 120 cmg.

**"MORE  
POWER—  
MORE  
TORQUE"**

12v. - 14v. DC

**DRILL ONLY £8.79**  
(P.P. 35p)

**STAND £4.40**  
(P.P. 35p)  
Incl. VAT

(Together 50p P.P.)

SAE for illustrated leaflet and order form



## 4-STATION INTERCOM



**£18.30**

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 85p.

## MAINS INTERCOM NEW MODEL

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £29.24 per pair P. & P. 85p.

## NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER




**ONLY £12.95**  
VAT £1.04

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/Off switch, volume. Direct tape recording model at £18.95 + VAT £1.12 P. & P. 70p, 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (PW10)  
169 KENSINGTON HIGH STREET, LONDON, W8

## INTER-LOCKING PLASTIC STORAGE DRAWERS

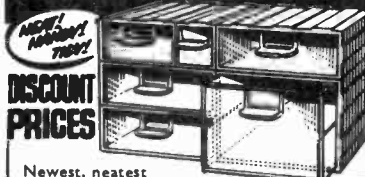

**DISCOUNT PRICES**

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

AS SUPPLIED TO POST OFFICE, INDUSTRY & GOVERNMENT DEPTS.

**SINGLE UNITS (1D)** (5ins x 2½ins x 2½ins) £2.50 DOZEN.  
**DOUBLE UNITS (2D)** (5ins x 4½ins x 2½ins) £4.40 DOZEN.  
**TREBLE (3D)** £4.20 for 8.  
**DOUBLE TREBLE 2** drawers, in one outer case (6D2), £6.50 for 8.  
**EXTRA LARGE SIZE (6D1)** £5.50 for 8.  
**PLUS QUANTITY DISCOUNTS!**  
Orders over £20, less 5%;  
Orders over £60, less 7½%.

**PACKING/POSTAGE/CARRIAGE:** Add 75p to all orders under £10. Orders £10 and over, please add 10% carriage.

**QUOTATIONS FOR LARGER QUANTITIES** Please add 8% V.A.T. to total remittance

All prices correct at time of going to press

## FLAIRLINE SUPPLIES

(Dept PW11)  
124 Cricklewood Broadway, London NW2  
Tel. 01-450 4844



## AMATEUR BANDS

by Eric Dowdeswell G4AR

**B**ACK in harness again, in dirty old London! I rather liked lying in the garden all day at home, gazing up at the swallows resting awhile on the aerial wires. Still, I'm fit and reasonably well again so there's nothing for it but to get back to the daily slog!

There are several readers this month writing in for the first time. One thought that I must get very fed up answering questions from beginners. Not at all OM! I have now been doing this feature long enough to see what were beginners a couple of years back, now getting their amateur transmitting licences, generally at the first attempt. It is very gratifying to me and, of course, it is a continuous process.

Judging by the Home Office figures on current amateur licences more people are joining the ranks than are leaving it which is a very healthy sign. However, the figures do not reveal how many of the licences are actually being used. Unfortunately the percentage is very low indeed, probably due to TVI problems, in the main. TVI can be cured so it behoves the TVI-troubled amateur, especially the newly licensed one, to persevere and get it cleared up rather than to give up the ghost at the first setback. For sound practical advice on TVI there is no better source than the RSGB.

The logs and letters continue to come in so obviously a lot of people have decided to enjoy our own fantastic weather rather than chance it abroad! **Paul Barker** BRS34898 of Sunderland is in the throes of moving across town so holidays are probably far from his thoughts. However, he seems to have kept the receiver and the SSTV gear on the boil although he considered it a poor month from the latter angle, nothing logged outside Europe. Asia on 20m seemed the best for Paul and his best catch was KJ6DL on Johnston Is. First newcomer this month is **John Beer** of Barnstaple who has acquired a BC348 set and coupled it to a 100ft aerial via a home-made ATU to "PW specification" as John puts it. On 20m John managed an HK9 and some JA's which is not too bad for a start.

**Steven Larkins** in Wellingborough sent a list of stuff heard via the Cambridge repeater on 2m so Uncle Eric has had to send a nice little letter explaining that real amateur radio is something quite

different and hoping he, Steve, will see the light very soon. Steven nearly died laughing when a very new G8+3 was called by "SK1RT" for his first "DX" QSO! **Robin Bayley** A9203 near Wolverhampton splits his time between studying for his RAE, building an all-bands receiver and listening on his Marconi R1475, finding 80 and 20m quite good but 40m very poor. Second newcomer is **Peter Bowyer** residing in Kettering, Northants, who has a Heathkit SW717G plus a "modified" Windom plus a 50ft dipole. What about making the 50ft into 66ft OM and getting the best out of it on both 7 and 21MHz? Peter, like several others, comments on the jamming station that seems to sit on 20m all day and night although I gather that it has moved off lately. I should not be surprised if those who operate these polluters of our ether find the amateur bands a good place to "park" their transmitters while they are finding some poor broadcaster for their attention!

**Neil Braeman** is our third newcomer, hailing from Southwater in Sussex. He is another who is starting the hard way with an old four-valve Pye superhet to which he added a BFO although this was not very successful. Coupling arrangements have to be just right, especially for SSB, so perhaps your lack of success is hardly surprising, Neil. He now uses a signal generator but even so SSB is hard to resolve. Neil aspires to the RAE in December, plus the morse test, so he's got a lot to do in the meantime. His way of learning Morse has a lot to commend it. He sat down with a copy of "Treasure Island" and hummed the letters to himself until he knew them by heart. Now he can do 16 wpm on a key, "buzz" at 32 wpm (!) but copy only at 5 wpm! This is where another and experienced operator is absolutely essential.

Old timer (to the column) **Alan Doherty** BRS34968 in Portrush, N. Ireland, is now off to ZL land for a few months but he promises to keep in touch. I don't know if it's business or pleasure but I reckon he'll want to stay there! His best catch recently has been VK9XI on Christmas Is. **Mr. P. Moore** only started his listening in April, on a Heathkit Mohican receiver, and is pleased with the 400 or so calls logged to date mostly on 80m SSB. At Fairwater, Cardiff he uses a long wire or a telescopic aerial. Now, more Moores! **John Moore** of Leicester is not really a newcomer since he used to dabble some five years ago until music and photography got a hold on him! Now he's back in the fold with a CR100, 2m converter and 132ft long wire. He's built another set using the Plessey SL600 IC's and copied over 90 countries on 20m in a few weeks. He says "the amount of pleasure I get from hearing DX on a receiver I have built myself is tremendous" which only confirms what I have always been saying! Build



it yourself! John comments on the many new prefixes which have been inflicted on us in recent years, quoting an AC3 thought to be in Sikkim but turning out to be Pennsylvania! What a let-down!

Brian Harrison uses an AR88 in Hastings, spending a bit more time on 10m than most, but 20 and 80m also get some attention. J. Hodgson of Morpeth, Northumberland is getting the hang of things now and learning to sort out the "goodies" from the rubbish on 20m SSB. His full-wave end fed wire feeds a Mini Clipper set but he'd like PW to publish a series on constructing a good communications receiver with explanatory details as the project went along. As he says, it would also help to spread the cost over a period of a few months.

### Log Extracts (All SBB)

**B. Harrison:**—10m 7X4MD JY9TR 8R1J 6W8AAD; 20m HL9TX OA4GM VR3HA 3B8DR 5U7BA 8R1X 9L1JM 9N1MM 9X5RK.

**J. Moore:**—20m AH3FF (US Samoa) KC4AAC KH6OT VP5SL 3D2AJ (Fiji) 4W9GR 5J3SB.

**P. Moore:**—80m CR5AK CX7BH HI1NR.

**A. Doherty:**—20m VK9XI VQ9HCS 9M2SV 9V1NR.

**P. Bowyer:**—20m CO2FR FM7AU FR7BI HK0LE HR3JJR JY9HQ VP1MPW VP2KAA YA3DO 5W1AX; 15m CE3RC JA6XMM LU9VAB YB2VE ZD7SD 6W8AAD 9Q5SW 9V1SR.

**R. Bayley:**—20m DU1DBT FP8DH HK0COP TG9HL VP8AA 80m A2GCO EA6CF KL7KV PY7HS PZ1DR.

**J. Beer:**—20m HK9BBJ VE8OMC 9K2DP.

**J. Hodgson:**—20m HC2LF HI8MVF HK6MA HP7XJS JY9HQ KV4AM VP1PTL VP2MAI YN1WB.

**P. Barker:**—20m A4XGQ (Masirah Is.) KJ6DL YB0IN 5N2NAS 7Z1AB 9L1JM 9V1NR 20m SSTV DF1KJ HB9ADD I4EXY OK3TDH.

**S. Budd:**—80m CE3EZ FM7AV VP8PB ZE2KF ZS5LB; 40m HK1CMO VK7CK 6W8FP; 20m AH3GK (KS6) FW8CO HC8RG HK0LE (San Andres Is.) KG4SC PY0AW (Trinidad Is.) YB8ACK; 10m CT6CAL TI2TB.



### SHORT WAVE BROADCASTS

by Derek Bell

THE holiday period is over at last and DXers can now settle down to the long winter nights with the dark hours giving reception from early evening to well into the late morning. For those

that took a portable on holiday with them the change of QTH perhaps filled in some of the blanks in their log books. Robin Bayley of Albrighton was one such who while in Yorkshire with his Grundig Prima Boy logged:—

9570 Radio Australia at 0815  
 9860 Radio Peking at 1600  
 11780 Radio Nacional de Brazillia at 2000  
 11920 TWR Bonaire at 0100  
 15430 NHK Japan at 0800.

For those who were lucky enough to get abroad with a portable they were perhaps involved with the Customs who are always interested in one's possessions! So take along the bill from the shop that sold the receiver. Alternatively ask the Customs to give you a statement that you are taking the set out of the country. In fact it is always a good idea to have a note of the vital statistics of your equipment, such as the serial number, since should you be unlucky enough to have it stolen then such details can be a great help to the police.

Operating a short wave set from a hotel bedroom is fraught with problems. Indeed, operating from any room without access to a space for a decent aerial puts the DXer at a distinct disadvantage. John Timms of Manor House is in that position living in a bedsitter in the heart of London which is hardly conducive to good interference-free listening. He already has a 40ft wire draped round the room but this produces no results at all.

Two readers have passed on items of mail, the first relating to the recent on/off/on again overseas service of Radio New Zealand and sent by Tom Mahoney of Callander, Perthshire and is the official press statement from the New Zealand Minister of Broadcasting. Couched in the usual diplomatic language it makes clear that the funding for the service will now come from the Ministry of Foreign Affairs and be cheaper than the Telex and tape services that were planned to replace it. The statement says that the service is of "particular use to the island communities with which New Zealand had special relations." One concession to the wider world of DXing was made in the final paragraph which said that the new service would enable contact to be maintained with "New Zealanders in the South Pacific, with scientific staff in the Antarctic as well as with listeners in other parts of the world." This cut in the service must have drawn protests from all over the world. Anyway, the service is now restored with the bonus that being a relay of the internal service we can now hear what the New Zealanders hear. I would be interested to know if anyone pulls in Arthur Cushen's DX programme as it would be a shame if that were to be axed.

The second item is from R. E. White of Wallasey who takes issue with me on the old discussion regarding the value of the literature sent out by broadcasting stations. Mr. White presents a very cogent argument in favour by saying that these items are of particular use to the novice DXer. However, the questions and answers in publications such as the news bulletins of the Radio Budapest DX Club, that Mr. White used to back his argument, tend to be repetitive and do not give all round education in matters DX. The main argument against is that many stations send not items that improve the DXers knowledge of the hobby but political propaganda. Recently Radio Berlin International asked me if I

### ROOM THERMOSTAT

Famous Satchwell, elegant design. Intended for wall mounting. Will switch up to 20 amps at mains voltage, covers the range 0-30°C. Special snip this month £2-90, post and VAT paid.




### NUMICATOR TUBES

For digital instruments, counters, timers, clocks, etc. Hi-vac. KN11 Price £1-25 each. Post and VAT paid.
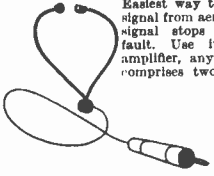
### RADIO STETHOSCOPE

Easiest way to fault find, traces signal from aerial to speaker, when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything. Complete kit comprises two special transistors and all parts including probe tube and crystal earpiece, £2-95, twin stetho-set instead of earpiece VAT and postage incl.



### MAINS TRANSISTOR PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PF1, PF2, PF4, PF6, PF7, PF9 and others. Kit comprises: main transformer rectifier, smoothing and load resistor condensers and instructions. Real snip at only £1-90 including post and VAT.

### MOTORIZED DISCO SWITCHES

With six 10 amp changeover switches. Multi adjustable switches are rated at 10 amp each so a total of 2000w's can be controlled and this would provide a magnificent display. For mains operating £4-25 post & VAT Paid. Ditto 9 switch £4-95 post & VAT Paid. DITTO BUT 12 SWITCH £5-75 POST AND VAT PAID.

### MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fans, blower, heaters, etc. New and perfect. Snip at 95p + VAT & Postage 35p. 1 1/2" stackmotor £1-56 + VAT & postage 35p. 1 1/4" stackmotor. £2 + VAT and Postage 40p.



### WINDSCREEN WIPER CONTROL

Vary speed of your wiper to suit conditions. All parts and instructions to make. £3-75 post and VAT paid.



### EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic feet per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc. It is so quiet it can hardly be heard. Compact. 5 1/2" casing comprises motor, fan blades, sheet steel casing, pull switch, mains connector and fixing brackets. £3-25 INCLUDING POST & VAT Monthly list available free; send long stamped envelope.



### 28 RPM GEARED MAINS MOTOR

This is a substantial motor (1 1/2" stack induction type) quite powerful definitely large enough to drive a rotating display or a tumbler for polishing stone etc. Approximate overall size 4" x 3 1/2" x 2 1/2" these are ex-unsued equipment, carrying our normal ex-equipment guarantees. PRICE £2-95 POST AND VAT PAID.

### SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450w). Unit in box all ready to work. £7-95 plus 95p VAT and postage.



### TELESCOPIC AERIALS

for portable car radio or transmitter. Chrome plated—six sections, extending from 7 1/2 to 47 1/2" 50p + 15p. Post & VAT.

KNUCKLED MODEL FOR F.M. 80p + 17p Post and VAT.

### NEED A SPECIAL SWITCH

Double lead contact. Very slight pressure closes both contacts 15p each. Plastic pushrod suitable for operating. 10p each, 10 for 68p.



### MULLARD UNILEX

A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost any one in easy-to-assemble modular form and complete with a pair of Goodmans speakers this should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £14-00 including VAT and postage.



### PP3/PP9 BATTERY ELIMINATOR

Made in Japan for Bush Radio. This is very neat little transformer driven full wave unit totally enclosed with input mains and output leads. This power supply unit which was originally marketed by Bush at over £6 is offered at this month's snip. PRICE £2-60 INCLUDING POST & VAT.

### TWIN OUTPUT POWER PACKS

These have two separate R.C. smooth out outputs so can operate two battery radios or a stereo amp without cross modulation (they will of course operate one radio/tape cassette/calculator, in fact any battery appliance, and will save their cost in a few months). Specs: Full wave rectification, double insulated mains transformer—total enclosed in a hard P.V.C. case—three core mains lead terminal output—when ordering please state output voltage 4v, 6v, 7 1/2v, 9v, 12v, or 24v. Price £3-95. Post and VAT included.



### INFRA RED BINOCULARS

Made for military purpose during and immediately after the last war to enable snipers, vehicle drivers, etc. to see in the dark. The binoculars have to be fed from a high voltage source (5KV approx.) and providing the objects are in the rays of an infra-red beam then the binoculars will enable these objects to be seen. Each binocular eye tube contains a complete optical lens system as well as the infra-red cell, technical data on which is available. The binoculars are unused, believed to be in good working order, in fact they were never issued and are still in original cases, but since they were made a long time ago they can hardly be called new. Sold without guarantee. Price £17-60 per set + £1 carriage.

### THIS MONTHS SNIP

This is a Satchwell thermostat. It is highly sensitive and can be set to control temperature within 1°C. Like most other very sensitive thermostats it is of low current rating so if you require it to switch heaters or similar then you will have to use a thermostat to switch a relay, the relay will switch the heaters. (We have supply suitable relays £1-00 + 8p each. These have three 10 amp changeover contacts so that with this the thermostat can control up to 6kw's of heating). This is wall mounting thermostat with white ventilator cover, regular price of this is probably £3 or £4. We are offering this month at £1-60 + 12p. Our total stock is over 1,000 and anyone wishing to make an offer, bulk quantities up to £1,000, are invited to do so.

### MICRO SWITCH BARGAINS

Rated at 5 amps 250 volts, ideal to make a switch panel for a calculator and for dozens of other applications. Parcel of 10 for £1-00 VAT AND POST PAID.



### HONEYWELL PUSH BUTTON PANEL MOUNTING MICRO SWITCH

1-2-3-Bank, each bank consisting of the changeover micro switch rated at 10 amps 250 volts. Through panel fixing by 2 lock nuts complete with black 1" diameter knob. Prices:—1 bank 40p—2 bank 55p—3 bank 70p.



### SMITHS CENTRAL HEATING CONTROLLER

Push button gives 10 variations as follows: (1) continuous hot water and continuous central heating (2) continuous hot water but central heating off at night (3) continuous hot water but central heating on only for 2 periods during the day (4) hot water and central heating both on but day time only (5) hot water all day but central heating only for two periods during the day (6) hot water and central heating on for 2 periods during the day time only—then for summer time use with central heating off (7) hot water continuous (8) hot water day time only (9) hot water twice daily (10) everything off. A handsome looking unit with 24 hour movement and the switches and other parts necessary to select the desired programme of heating. Supplied complete with wiring diagram. Originally sold we believe at over £15. We offer these while stocks last at £7-50 each INCLUDING VAT and Postage.



### SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19, 25, 31, 29 metre bands—Kit contains chassis front panel and all the parts £1-60—crystal earphone 65p including VAT and Postage.



### ONLY £1-50 FOR SEVEN ELECTRIC MOTORS

7 powerful batt. motors as used in racing cars and power models. Output and types vary for use in hundreds of projects—Tools, toys, models, etc. All brand new reversible and for 1 1/2-12v batts. Wiring diag. inc. VAT, Post PAID.



TERMS: Where order is under £5 please add 40p surcharge to offset packing expenses

**J. BULL (ELECTRICAL) LTD.**  
(Dept. P.W.), 103 TAMWORTH ROAD,  
CROYDON CR9 1SG.

### ITS FREE!

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—its an interesting list and its free—just send S.A.E. Below are a few of the Bargains still available from previous lists.

Remember 7.029P (again available). Electricians of the old school most certainly will, and most will agree how much better this is than its modern replacement 2-5mm. It has greater current carrying capacity (20 amps against 13 amps) and being stranded it will not break so easily and being larger it is easier to use. A fortunate buy enables us to offer 3 core 7-029 cheaper than we could offer 3 core 2-5mm, namely £9-50 against £11-50. If you are contemplating installing a ring main, an immersion heater, storage heaters or fires, then you should definitely buy some of this cable. It is p.v.c. covered, correctly colour coded and up to all British standards; in fact, was made by one of our most famous cable companies. Price £9-50p + 76p per 100 metre coil. Carriage £2-50 + 20p.

Remember 3.029P This would not be much good today as most installations call for a trailing earth wire as well as L. & N., however a special offer this month is 3 core 1-5mm at only £5-60p + 44p per 100 metres. Post £1-60p + 12p.

NCE Accounting Computer. This we understand was in working order immediately before being dismantled and delivered to us, but as we have no means of testing it and as also we don't have any spares for it, we cannot give any guarantee. If you buy it then you will have to use a calculator. The computer is American made, it weighs over 1 ton, has an alphabetical numerical keyboard. We cannot see any type number on it but the numbers that do appear are as follows: Class 390-990-1. It comprises three main units with interconnecting leads, the first unit is a 10kv isolating same as the 416 amp described as well as a very handy transformer and new would cost at least £200. The second major unit is the computer control panel, this weighs nearly a ton and is full of components and hardware. The third unit is the desk with the alphabetical and numerical keyboards. The price we are asking for this computer is £2375 and we feel certain that even if it could not be got going again it would realise a lot more than this if broken down and sold for its component parts. Important Note: Owing to its size this computer is not at our Croydon address. If you wish to view this please be prepared to travel into Sussex just off the Brighton Road and telephone us for the address and so that a mutually convenient time can be arranged. Tele No. 688 1833.

7kv EIT Transformer. This is made by Parmeko, this is a "cc" core construction totally enclosed in black enamelled sheet steel case. The primary consists of two separate windings each 125 volts tapped with two 10 volt steps so it could be used on 115 volts or 230/240 volts. The secondary is centre tapped with further tapping to give voltages as follows: 2-5kv-0-2-5kv, 3kv-0-3kv, 3-5kv-0-3-5kv. The current rating of the secondary is 245 ma r.m.s. Price £30 + £2-40p. Carriage £2 + 16p.

Isolation Transformer. Very high current 416 amps, primary 0-280 volts, last 60 volts in 10 volt steps so this transformer can be used to step up voltages for use at the end of a long cable run. Secondary, centre tapped 120v-0-120v so this transformer will isolate and step down or will isolate at normal mains in and normal mains out or finally it will isolate and step up. A big transformer completely enclosed in sheet steel with weighing about 300 lbs. Price £100 + £8. Carriage as with but we would prefer you to collect this. (This is at Croydon).

5 Bank Switch Panel. This is a Government Surplus item so it is very well made and contains switches which will break 15 amps DC. The 5 switches are completely separate so may be used to control separate circuits or they may be ganged together to bring in 5 heaters in parallel suitable for mains or battery power. Size of the switch is approximately 5 1/2 x 1 1/2 x 1 1/2 and operation is by nickel plated toggles. Price 75p each + 6p. Post 20p + 2p.

Cooling Thermostat. The thermostat switches off as the temperature in the room rises. It is, therefore, suitable for controlling electric room heating. We have a similar stat but with contacts which switch on as the temperature rises. These are for air conditioning or cooling circuits. Contacts again rated at 20 amps and these have changeable contacts so they can be used for cooling or heating or both but as their original function was intended for cooling they are set and calibrated for 12-40°F. Price £3-60p + 26p.

Simmerstats. Often confused with thermostats the function of simmerstat is to pulse the supply into a heater or cooker. The longer the pulse is the greater will be the amount of heat dissipated and vice versa. The length of the pulse is determined by a control knob which in the case of a cooker is usually engraved—simmer, boil, fry. We have Sunvic Simmerstat as used in many high grade cookers as well as industrial heaters. Current rating is 15 amps @ 200/250 volts AC. Price £1-75p + 14p. Post 20p + 2p.

Flash Ernie is the name we have given to our latest disco light display because it is a random flasher and is very effective especially with coloured bulbs. Kit consists of motorised stud switch, master control switch, anti spark caps, 9 lamp holders, connecting wire and wiring diagram. Price £5 + 40p. Post 60p + 6p.



**T.T.L. 74 I.C.'s. Prices include Postage and V.A.T. plus BIG QUANTITY DISCOUNTS**

7400 12p	7413 30p	7432 25p	7454 15p	7480 35p	74121 25p	74139 100p	74156 70p	74174 100p	74189 350p
7401 12p	7414 00p	7437 25p	7480 15p	7491 75p	74122 40p	74141 60p	74157 70p	74175 75p	74190 100p
7402 12p	7416 30p	7438 25p	7470 30p	7492 45p	74123 60p	74142 270p	74160 90p	74176 100p	74191 100p
7403 12p	7417 30p	7440 15p	7472 25p	7493 40p	74125 50p	74143 270p	74161 90p	74177 100p	74192 120p
7404 12p	7420 15p	7441 65p	7473 30p	7495 60p	74126 50p	74144 270p	74162 90p	74178 140p	74193 120p
7405 12p	7422 20p	7442 65p	7474 30p	7496 70p	74130 130p	74145 75p	74163 90p	74179 140p	74194 100p
7406 35p	7423 25p	7445 80p	7475 30p	74100 95p	74131 100p	74147 230p	74164 125p	74180 100p	74195 75p
7407 35p	7425 25p	7446 85p	7476 30p	74104 40p	74132 65p	74148 100p	74165 125p	74181 200p	74196 100p
7408 15p	7426 25p	7447 75p	7483 85p	74105 48p	74135 100p	74150 120p	74166 125p	74182 75p	74197 100p
7409 15p	7427 25p	7448 70p	7485 100p	74107 30p	74136 80p	74151 65p	74167 325p	74184 150p	74198 100p
7410 12p	7428 40p	7450 15p	7486 30p	74108 50p	74137 100p	74153 85p	74170 200p	74185 150p	74199 185p
7411 20p	7430 15p	7453 15p	7489 250p	74120 90p	74138 125p	74155 70p	74173 150p	74188 350p	74199 185p

**SPECIAL OFFER ALL 22 I.C.'s FOR P.W. DIGITAL FREQUENCY COUNTER FOR £7.50**

**POPULAR BRANDED TRANSISTORS**

**BC147 — BC148 — BC149 — BC157 — BC158 — BC159 — BF194 — BF195 — BF196 — BF197**  
7p each. 100 for £6.00. Type numbers may be mixed for quantity discount.

Bulk Purchase I.T.T. IN4148 10 for 30p, 100 for £1.50

1 Amp Diodes IN4001, IN4002, IN4003 4p each, 30 for £1.00  
IN4004, IN4005, IN4006 6p each, 30 for £1.50

Zener Diodes BZY88, 400MW 3V to 33V 7p each, 100 for £6.00

**NEW LOW PRICE**  
741 OP Amps  
ANY QUANTITY 20p each  
555 TIMERS  
ANY QUANTITY 35p each

**TRANSISTORS, etc.**

AC128 12p	MTCHN PR	AF117 18p	BC148 7p	BC182L 12p	BC212L 12p	BCY72 16p	BF180 30p	BFX85 25p	2N3702 12p
AC176 12p		BC107 9p	BC149 7p	BC183 10p	BC547 12p	BD124 70p	BF182 30p	BFX87 25p	2N3704 12p
AD149 45p	AF114 18p	BC108 9p	BC157 7p	BC183L 11p	BC548 12p	BD131 35p	BF183 30p	BRX39 35p	1N914 3p
AD161 35p	AF115 18p	BC109 9p	BC159 7p	BC184 11p	BC549 12p	BD132 35p	BF200 30p	BRX56 35p	BY100 15p
AD182 35p	AF116 18p	BC147 7p	BC169 12p	BC184L 12p	BCY70 16p	BD135 50p	BF244 16p	BSX20 16p	BY126 10p
			BC182 11p	BC212 12p	BCY71 16p	BD137 40p	BFX84 25p	2N3055 50p	BY127 12p

**PLEASE NOTE THAT ALL PRICES INCLUDE POSTAGE AND V.A.T. AT 8 OR 12½% AS APPROPRIATE**

**MAIL ORDER ONLY  
XEROZA RADIO**

**1, EAST STREET, BISHOPS TAWTON, BARNSTAPLE, DEVON**

**TAMBA ELECTRONICS**

QUALITY PRODUCTS  
FOR HI-FI, DISCO,  
P.A. GROUP AND CLUB USE

**A BRAND NEW RANGE OF AMPLIFIER MODULES 5 to 100 WATT/RMS**

Choose the power you need from these five pure complementary amplifiers  
Two-year guarantee

All amplifiers feature a pure complementary symmetry output stage for low distortion and high reliability—the highest grade components (by Mullard—Texas, Plessey—RCA, etc.) used throughout



TAM50 5W RMS 25V supply	£3.20
TAM100 10W RMS 35V supply	£3.75
TAM250 25W RMS 45V supply	£4.25
TAM500 50W RMS 45V supply	£6.95
TAM1000 100W RMS 65V supply	£9.80
(all modules carriage free)	

- Suits loads 4-16 ohms (optimum load 8 ohms, TAM50/100/250, 4 ohms TAM500/1000)
- Low distortion (0.1%)
- 20-20,000 Hz ± 1dB
- Silicon circuitry throughout
- Inherently open circuit proof
- Four simple connections

- High sensitivity—100mV
- Low profile (1in high 3½in x 3in)
- 75% efficient
- Glass fibre printed circuit board
- Accepts most mixers/pre-amplifiers

**POWER SUPPLIES**

For 1 or 2 TAM50/100	£4.25 (carr 50p)
For 1 or 2 TAM250/500	£6.95 (carr 50p)
For 1 or 2 TAM1000	£9.80 (carr 50p)

You may order as follows: C.W.O. (crossed cheques, P.O.s, M.O.s, etc.) C.O.D. (50p extra). We accept Access and Barclaycard—send or telephone your number—do not send your card. Add VAT at 8% to orders for 50-100W units and a 12½% for 5-25W units

Hours, 9.30 a.m.—5 p.m.  
Monday—Saturday.  
Callers welcome.  
Tel: (01) 684 0098

**TAMBA ELECTRONICS**

**BENSHAM MANOR ROAD PASSAGE, BENSHAM MANOR ROAD, THORNTON HEATH, SURREY**



was still interested in their RBI Journal, which is 99 per cent propaganda and only devotes a few column inches to DXing.

However, to get away from the problems of the world let us turn to **Andrew Linton** who had a Meridian superhet via Santa Claus last Christmas. Having hung it on the end of a 90ft wire and got used to all the knobs Andrew has logged the following:—

- 0590 Radio Norway at 1400
- 9701 Vatican Radio at 1131
- 11710 Radio Israel at 2000
- 11940 WYFR at 2200.

Andrew has one or two questions to ask, namely the location of WYFR and of the 7235 service of Radio Australia. WYFR is an American evangelist network with the call sign that happily translates into "Your Family Radio" and around 1973 or so if memory serves bought another gospel network "Radio New York Worldwide" in order to get some shortwave access. Their present address is: 290 Hegenberger Road, Oakland, California 94621. The Radio Australia transmitters are at Shepperton, Lyndhurst, Brisbane and Darwin.

To continue with the latest transmitter news I hear that Liechtenstein is awaiting the delivery of a 500kW transmitter and will be on the air around 1979 probably on 1386. **Niels Montanana** from Camberley mentions the Standard Frequency time signals that are so handy for calibrating the receiver. These usually consist of a morse signal identification with perhaps an announcement at regular intervals. To take one example, Turin comes in on 5000 with 5kW on the last quarter of each hour, from 0645 to 1800, in English, French and Italian and the call sign is IBF. With that I must declare the innings closed and wish 73s to you and yours.

## BROADCAST BANDS

### MEDIUM WAVE DX

by *Charles Molloy*

**A**N interesting log of North American DX comes from Mirfield in Yorkshire where **Harold Emblem** at the controls of his Eddystone 730 and medium wave loop pulled-in CKCM in Grand Falls, Newfoundland on 620kHz, CKVO Clareville, Newfoundland on 710kHz, WNEW New York City on 1130kHz, WCAU Philadelphia on 1210kHz, CFGO

Ottawa on 1440kHz and WMEX in Boston on 1510 kHz. Harold must surely have the last word over Istanbul when he claims that the site of the 1016kHz transmitter is on the Asiatic side of the Bosphorus which makes this station an Asiatic broadcaster without any doubt.

Medium wave stations often identify themselves over the air by the name of the town or city where the studios are located. Information on actual transmitting sites is not readily available and consequently a DXer who hears WCKY on 1530kHz announce itself as being in Cincinnati will count this one as being in the State of Ohio, not knowing that the transmitter is really in Kentucky. Vatican Radio on 1529kHz transmits from a site at Santa Maria di Galeria some 18km north of Rome and the Vatican State. This station is really in Italy! Collectors of "States Heard" will be disturbed to learn that some of the high power New York City outlets such as WINS on 1010kHz, WHN on 1050kHz and WNEW on 1130kHz transmit from an area of swamp land across the Hudson in New Jersey and should really count as belonging to that state. WNBC 660 kHz is on Long Island and WCBS 880kHz is on Columbia Island (in Long Island Sound) so these two do count as New York.

### BROADCAST BANDS

**Short Wave Reports** by the 15th of the month to **Derek Bell**, c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

**Medium Wave Logs** to **Charles Molloy**, 132 Segars Lane, Southport, PR8 3JG.

### AMATEUR BANDS

Logs covering any amateur band/s in band/ alphabetical order by the end of the month to **Eric Dowdeswell G4AR**, **Silver Firs**, **Leatherhead Road, Ashstead, Surrey, KT21 2TW**.

The writer enjoys his DX without worrying too much about the exact location of his quarry. DX clubs though, like to encourage competition among members by running "ladders" or tables of States, Provinces, Countries or Continents heard which can, now and again, lead to quite unexpected difficulties.

**F. A. Ainsley** reports from Hartlepool with details of his homebrew receiver which, he claims, performs better than an AR88 on the medium waves. Two RF stages and a mixer are followed by a 4-pole ceramic filter at 455kHz and two IF amplifiers, a detector and an audio stage. The receiver was specially made for medium wave DXing and is used with a medium wave loop, FET differential amplifier and a two stage RF sensing unit. Preferred time for DXing during the summer is at sunrise on a Sunday morning when local QRM is light. Stations heard between 0200 and 0400 include Trans World Radio on the island of Bonaire in the Caribbean on 800kHz, WBZ in Boston on 1030kHz, WOKO in Albany, New York on 1460kHz (not often heard), WTOP in Washington DC on 1500kHz and WQXR, the serious music station in New York City on 1560kHz. The latter is



owned by the New York Times and broadcasts programmes similar to those of BBC Radio 3.

Sunday morning is a good time for DXing on the medium waves at any time of the year in the UK. Stations in time zones to the east start to sign-on from 0300 onwards and during the week, DXing becomes difficult by 0500 owing to QRM. On Sundays however, many broadcasters make a late start which gives the DXer the chance to find a few spaces in the band to look for DX. This is the time to look for KOMO in Seattle on 1000kHz and WCFL in Chicago which is on the same frequency.

Ralph Newman who lives in Reading, has been experimenting with a loop and homemade FET loop amplifier. The amplifier, which uses a 2N5459 (MPF105) FET and two BC168 transistors, has an output emitter follower stage. With this set-up connected to an ordinary 6 transistor portable, CBN on 640kHz, CJON on 930kHz, WINS on 1010kHz and WCAU on 1210kHz were heard. How was the loop amplifier joined to the portable receiver Ralph? Readers would be interested in details. When the loop plus amplifier was used with a Barlow Wadley receiver Bagdad on 760kHz and the Voice of America relay in Thailand on 1580kHz were logged.

Reception was during last winter. Ralph points out that you do not need a coupling winding on a loop when it is joined to an FET amplifier. Long leads between the loop and the amplifier should be avoided though, otherwise a poor null will be obtained due to the leads picking up signal. The amplifier was literally hung on the loop tuning capacitor to avoid this.

A long and interesting letter from Fred Pilkington, G3IAG, mentions medium and long wave DX on board ship during his seafaring day. Droitwich 200 kHz was heard during the day, half way across the Atlantic and as far south as Sierra Leone. After dark European longwave stations are heard regularly by DXers on the east coast of the United States. The range of the ground wave varies inversely with frequency. Even on the medium waves this effect can be observed. On a winters' afternoon start tuning from the LF end of the band, where North Africa can be heard in daylight, towards the HF end. At the writer's QTH long range reception peters out by the time 1200kHz is reached. After dark, long wave signals are reflected by the ionosphere and the range is considerably extended, just as on the medium waves.

Fred mentions a holiday in south Spain and his attempts to hear Radio Gibraltar on 1484kHz. The station, in a letter, admits that it is difficult to put out a decent signal from the rock (probably because of the difficulty obtaining a good earth). Radio Gibraltar, which transmits on one of the two international common frequencies, is on the air daily from 0655 until 2300 but so far as the writer is aware, it has not been heard in the UK. Pw

## CONTINUOUS DISPLAY LCD WATCHES

We now have available the choice of our unique alternating display feature or a full six digits display.

### Models 1113/10 and /20 (Gold)

Displays hours, minutes, months, date and seconds. Alternating display feature where display shows time for two seconds and then months and date for two seconds and continues to alternate until re-set to the normal mode of operation which is: continuously displaying time in hours and minutes with months, date and seconds on demand.

Models 1113/10 also available with a stainless-steel bracelet.

### Also available model 2000/10

This is a full six digit display which continuously shows: hours, minutes AND seconds OR hours, minutes and day of the month (date). To change seconds to day of the month simply operate command button once. To revert back to initial display mode operate command button once again. This watch is only available with stainless-steel bracelet.


Prices: Model 1113/10 or 20 **£34.50**

Model 2000/10 **£37.95**

These prices are inclusive of VAT and P and P and all models are complete with back-light, matching bracelet, presentation case and one full year's guarantee and instructions.
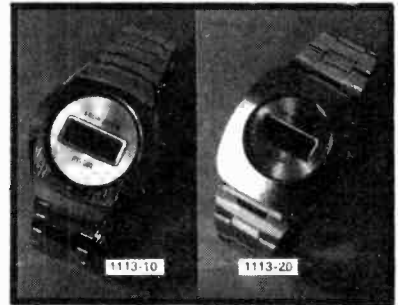
# Leetronic

Watch Division, Lee Instrumentation Ltd.,  
Bedwas, Newport, Gwent NP1 8YZ  
Tel. (0222) 885756-7-8. TELEX: 497084  
Reg. No. 639437. VAT Reg. No. 133 8154 80



To: Leetronic, Lee Instrumentation Ltd., Newport, Gwent NP1 8YZ  
Print — FREPOST — no stamp required.

Please forward.....(qty) model .....at.....each TOTAL £.....  
I enclose



Name ..... cheque .....

Address ..... postal order .....

..... money order .....

Signed .....

Barclay/Access No.....

## QUALITY STEREO SOUND

ALMOST **1/2 PRICE OFFER!** SOLENT AUDIO SYSTEM  
**£7.50**

MADE TO SELL AT  
DOUBLE THE PRICE  
IN CABINET FORM

OUR PRICE **£69.95**

**down**

Solent Mark II Stereo Tuner Amplifier chassis with AM/FM radio covering long medium short and Stereo FM wavebands. Separate Bass and Treble controls. 30 watts total power output (frequency response 25-20,000 Hz) AFC Switching Tape record and playback facilities. Dimensions 18½" x 9" x 3½". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price £69.95. Credit Sale £7.50 deposit 9 monthly payments of £8.00 (Total Credit price £79.50). P. & P. £4.00. Send £11.50 today.

Chassis only available for cash at £49.00 + p. & p. £3.00.

Full 12 months Guarantee.

CALLERS WELCOME.

Access and Barclaycard Orders Accepted by Telephone

**FREE!** Stereo headphones supplied with every complete order

**LEWIS radio** PW/11/76.100 CHASE SIDE SOUTHGATE  
LONDON N14 5PL Telephones: 01-882-1644

# Complete the coupon and we'll send you our complete, new catalogue.



The new Heathkit catalogue is now out. Full as ever with exciting, new models. To make building a Heathkit even more interesting and satisfying.

Clip the coupon now (enclosing a 10p stamp for postage) and we'll send you your copy to browse through.

With the world's largest range of electronic kits to choose from, there really is something for everyone.

Including our full range of test equipment, amateur radio gear, hi-fi equipment and many general interest kits.

And, if you happen to be in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.

Heath (Gloucester) Limited, Dept. PW-116 Bristol Road, Gloucester, GL2 6EE. Tel: Gloucester (0452) 29451.

**Wire Wound Resistors.** Our selection of mixed values. 30 for £1.40. 100 for £3.50.

**Audio Amplifier Module.** Mullard LP1173. Output nominal 10 watt. Supply voltage +24vt. With data and circuit £2.30.

**Varicap Control Selector.** 4 way 25K. £1.50. 6 way 14.5K. £2.00.

**Mains Droppers.** 10 mixed values £1.00.

**Edge-wise Level Meters.** 200µA. Size ½" overall 50p.

**15 Assorted Switches.** Micro, push button, etc. £1.00.

**Tag Strips.** 3 way to 7 way. 50 for £1.15.

**Chrome Plastic Knobs.** 3 Types 4 of each with spring clip. £1.25.

**Ferguson Stereogram Chassis.** Model 3357. All transistor. Med/LW, FM. 3 watts per channel S/M. With connection data. Less tuning scale. £18.00. P/P free.

**Ferguson Stereogram Chassis.** MW, LW, FM. With tuning scale (5+5 watts sine wave) 15 ohms £26.25. P/P free.

**Copper Clad Laminate.** 8" x 7"—3 boards £1.00 + 8%.

**Ferric Chloride.** 1lb 65p + 8%.

**Crystals HC8U.** (MHz) 12700; 12891.6; 9455.55; 9530.55; 9087.5; 9456.25; 52.01667; 52.02500; 37.7625; 51.56667; 52.03333; 9090.62; 9531.04; 9533.33. 50p each.

**Electrolytics.** 32/32/32µF. 325v. 2" x 1½" 35p; 80µF 150v 1½" x 1" 20p; 2000µF 30v. 2½" x 1" 25p; 2000µF 35v 3" x 1" 30p; 470µF 100v 3" x 1½" 25p; 2000/2000µF 25v 2" x 1½" 35p; 700µF 200v 3½" x 1½" 30p; 16/16µF 275v 1½" x 1" 20p; 4500/900/900µF 30v 2½" x 1½" 50p; 2500µF 40v 3" x 1½" 40p; 470µF 25v 1½" x 1½" 15p; 4,000µF 25v 3" x 1½" 40p; 32µF 450v 1½" x 1" 30p; 8µF 16µF 450v 1½" x 1" 30p; 1000µF 12v 1½" x 1" 15p; 8000µF 50v 2" x 1½" 50p; 150/200/200µF 300v 3" x 1½" 50p; 16/16/16µF 350v 2" x 1" 30p; 50/50µF 500v 3½" x 1½" 50p; 400µF 40v 1½" x 1" 20p.

Try our parcel of small capacitors 20 mixed values £1.50 + post.

**Miniature Presets**—Selection of various values 10 for 65p.

**Coil Formers.** 50 mixed. £1.25.

**Slider Volume Controls.** 1K Lin; 100K Log; 1 Meg Log; 25K Lin; 25K Log; 10K/100K Log; 100K/100K Log; 50K Log. 35p each.

**Aluminium Chassis.** 7½" x 5½" x 2½" 65p. 10" x 7½" x 2½" 75p. 11" x 7½" x 2½" 85p + 8%.

**Thorn TA/28.** Slide synchroniser for 4 track reel to reel recorders. 6 pin DIN socket models. £4.50.

**BSR Single Play Decks with Cue.** Fitted stereo cartridge. P146 £11.00. P153 £12.00.

Please add 10% P.P. Unless stated free P/P. VAT 12½% to be added to total order unless stated 8%. No goods despatched outside U.K.

## SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON LU3 1JD, BEDS.

**The new Heathkit catalogue. Out now. FREE.**

To: Heath (Gloucester) Limited, Dept. PW-116 Gloucester GL2 6EE. Please send me a Heathkit catalogue. I enclose a 10p stamp for postage.

Name \_\_\_\_\_

Address \_\_\_\_\_

**FREE**  
SOLDERING IRON  
UP TO £11  
**£3.50**  
with all orders over  
£25

HEATH  
Schlumberger

EASY TO USE SOLDERING IRON WITH HEATHKIT WARRANTY AND BUILT-IN PLAN

# SINTEL FOR KITS - CMOS - DISPLAYS - MEMORIES - BOOKS - MICROPROCESSORS.

Components from leading manufacturers only

SINTEL

## DATABOOK and DATASHEETS: (may be photocopies)

New 1976 RCA CMOS and Linear IC Combined Databook	£4.95
New 1976 RCA 'Power Transistors, SCR's, Databook	£4.95
National Semiconductor 7400 series TTL Databook, c. 200 pages	£3.45
TTL Pin-Out Card Index. Set of cards with pin-outs (top and bottom views) of T.L. TTL range and many other T.L. IC's	£2.95
Intel Memory Design Handbook, c. 280 pages	£4.75
Intel 8080 Microcomputer Systems Users Manual, c. 220 pages	£4.85
Motorola McMOS Databook (Vol. 5 Series A) c. 500 pages	£2.77
Motorola M6800 Microprocessor Applications Manual, c. 650 pages	£12.45
Motorola M6800 Programming Manual, c. 200 pages	£6.85
Motorola Booklet Introducing Microprocessors	£1.50
National SC/MP Introkit Users Manual	£0.75
National SC/MP Programming and Assembly Manual	£6.30
National SC/MP Technical Description	£1.95
2850 Microprocessor Manual 220 pp	£24.50
<b>DATASHEETS on Microprocessors: (usually Xerox Copies)</b>	
Intersil IM6100 12 bit CMOS	£0.75
RCA CDP1802 8 bit CMOS	£0.35
National SC/MP 8 bit, Low cost	£0.75
Zilog Z80	£0.75
Signetica 2850 8 bit, Low cost	£0.75
Motorola MC6800	£0.75

## CMOS From the top manufacturers, mainly RCA and MOTOROLA

CD4000 0-16	CD4028 0 89	CD4053 0 97	CD4086 0 74	<b>CLOCK CHIPS</b>
CD4001 0-16	CD4029 1 18	CD4054 1 20	CD4089 1 61	
CD4002 0-16	CD4030 0 56	CD4055 1 37	CD4093 0 89	AY51202 2 89
CD4008 1 22	CD4031 2 24	CD4056 1 37	CD4094 1 94	AY51224 3 50
CD4009 0 17	CD4032 1 11	CD4057 27 95	CD4095 1 09	MK50253 5 60
CD4002 0-16	CD4033 1 45	CD4059 4 96	CD4096 1 09	
CD4009 0-56	CD4034 1 98	CD4060 1 16	CD4097 3 87	<b>FLAT CABLE</b>
CD4010 0-56	CD4035 1 22	CD4062 9 07	CD4099 0 90	20-w 1m. 1 00
CD4011 0 17	CD4036 3 18	CD4063 1 14	CD4502 1 29	10m. for 8 00
CD4012 0 17	CD4037 0 99	CD4066 0 64	CD4510 1 41	
CD4013 0 58	CD4038 1 22	CD4067 3 87	CD4511 1 62	<b>VEROCASES</b>
CD4014 0 16	CD4039 3 09	CD4068 0 22	CD4514 2 85	751410J 2 64
CD4015 1 05	CD4040 1 11	CD4069 0 22	CD4515 3 25	751411D 3 04
CD4016 0 55	CD4041 0 87	CD4070 0 60	CD4516 1 41	751237J 1 72
CD4017 0 99	CD4042 0 87	CD4071 0 22	CD4518 1 30	751238D 2 15
CD4018 0 99	CD4043 1 05	CD4072 0 22	CD4520 1 30	
CD4019 0 56	CD4044 0 97	CD4073 0 22	CD4527 1 64	<b>SUNDRY</b>
CD4020 1 19	CD4045 1 45	CD4075 0 22	CD4532 1 50	CA3130 1 14
CD4021 1 05	CD4046 1 39	CD4076 1 61	CD4555 0 94	uA 741 0 35
CD4022 1 00	CD4047 0 94	CD4077 0 80	CD4556 0 94	
CD4023 0 17	CD4048 0 58	CD4078 0 22	MC14528 1 18	<b>SOLDERCON</b>
CD4024 0 81	CD4049 0 55	CD4081 0 22	MC14553 5 24	PINS 0 50
CD4025 0 17	CD4050 0 55	CD4082 0 22	MC14552 8 05	1000 4 00
CD4026 1 19	CD4051 0 97	CD4085 0 74	IM6508 8 05	
CD4027 0 55	CD4052 0 97			

**FAST SERVICE.** We guarantee that Telephone Orders for goods in stock, received by 4.15 Mon-Fri, will be despatched the same day. Private customers use Access or Barclaycard (min. tel. order £5). Official orders no min.

**SINTEL** P.O. BOX 75F, Oxford, Tel. 0865 49781



## PW 'EASYBUILD' CAR CLOCK KIT, Oct '76

Everything included except battery—IN STOCK NOW



order as:

**"AUTOCLOCK KIT"**  
£17.85

only 40mm x 154mm x 85mm

**FULLY AUTHOR-APPROVED KIT** (We wrote the article) ● Only high quality components used—Pihler resistors, roller tinned fibreglass PCB's etc. ● Full instructions included. Simple but sophisticated circuitry gives you good performance at low cost. You benefit from our experience in clock kit design. After sales service available at very reasonable cost. Uses our own crystal timebase kit. Also available less case, order as: "AUTO-MODULE-KIT" £16.45

Send for **FREE CATALOGUE** giving details of our complete range of **Clock kits, Led displays, Cases** and other components

## memory ic's and microprocessors

Please: Microprocessors should only be bought by experienced constructors. Sorry, we cannot answer technical queries or supply data other than from our data selection.

IM6100CCDL	£58.00	MP1's	6820	£17.67
8080A (2µS)	£43.65		6850	£17.67
6800	£33.87		8224	£9.76
ISPA1500 (SC/MP)	£18.75		8228	£12.16
2850	£27.00		8251	£17.67
			8255	£17.67

**MEMORY IC's**  
Intel 2102A-6 (new version of 2102-2). 16 pin IC. TTL compatible. Single +5V supply, 650nsec., 1024 x 1 bit Static NMOS RAM. £3.35  
Intel 2112-2 650nsec. 256 x 4 bit Static NMOS RAM. £4.78  
Intersil IM6508C CMOS 1024 x 1 bit Static RAM. £8.05

Add 8% VAT + 25p p&p on all orders. Phone orders see "Fast service" for details. Export orders welcome, but you must contact us first for special order form and postage rates. **OFFICIAL ORDERS WELCOME.**

**SINTEL**

## VALVE BARGAINS

Any 5-54p, 10-£1.00, 50-£4.50. Your choice from the list below.

ECC82, EF80, EF183, EF184, EH90, PCF80, PCF802, PCL82, PCL84, PCL85, PCL86, PCL805, PL504, PY81/800, PY88, 30PL14, 6FZ8.

Large stock of older types of TV Valves. Brand new 35p each.

Colour Valves—PL508, PL509, PL519, PY500/A. All tested. 30p each.

Press Button UHF Tuners—4 Button Transistor—British made—£2.50 each.

## 50p BARGAIN PACKS

All Packs Un-used Parts—PK1-40-C280 (Mullard) Axial Lead Capacitor mixed values from .01µF to .47µF (250V/W). PK2-30-C281 (Mullard) Radial Lead Capacitors mixed values from .015µF to 1.5µF (250V/W). PK3-6 Co-ax. plugs. PK4-6 Co-ax connectors. PK5-8-5m/m formers with slugs, PK6-25-AC128 Transistors. PK7-3 BF200 (VHF) Transistors. PK8-2 BF182 (UHF) Transistors. PK9 Any 6 Transistors BC108, BC113, BC135, BC153, BC171, BC172, BF194, BF195, BF196, BF197. PK10 8-1 amp 400 volts rectifiers. PK11 4-5 pin din plugs (180°). PK12-5 PP3 Battery Connectors.

All prices include VAT. P&P 20p per order. Please send uncrossed P.O. or Cheques for returning if we are out of stock of Bargain Packs or older types of new valves.

## ELECTRONIC MAILORDER LTD.

62 BRIDGE ST., RAMSBOTTOM, BURY, LANCS. TEL. RAMS. (070 682) 3036

## AERIAL BOOSTERS


Aerial boosters can produce remarkable improvements on the picture and sound, in fringe or difficult areas.

**B11** For TH stereo and standard VHF/FM radio.

**B12**—For the older VHF television—Please state channel numbers.

**B45**—For Mono or colour this covers the complete UHF Television band.

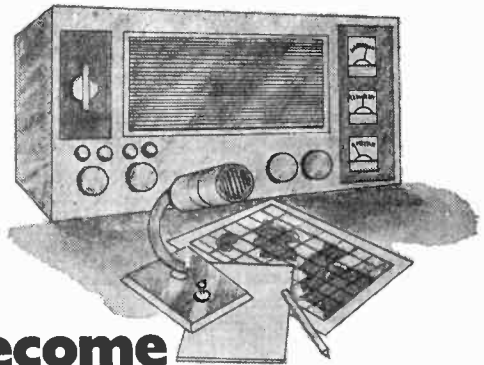All boosters are complete with battery with Co-ax plugs & sockets. Next to the set fitting. £3.60



## Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

**Free!** WAA  
Brochure, without obligation to: WK11  
**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**  
P.O.Box 156, Jersey, Channel Islands.  
NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_ (Block caps please)



# NEW MULLARD & MAZDA VALVES

All individually boxed.  
Full trade discounts to bona fide companies.  
Prices on application.

**EXPRESS POSTAGE**

15p per 1 Valve.  
Each additional Valve add 2p in UK

DM70	0.69	EF80	0.92	PCC84	0.84	PL504	1.44	30C15/	
DY88/7	0.70	EF83	1.10	PC835	1.02	PL508	1.74	AAZ15	0.12
DY802	0.53	EF85	0.70	PCC88	0.98	PL509	2.34	AAZ15	0.10
EB91	0.97	EF86	1.73	PC839	0.97	PL802	2.34	AC107	0.51
EB91	0.89	EF89	1.73	PCC189	1.22	PY33	0.74	AC126	0.51
EBF80	0.63	EF91	1.35	PCF80	0.84	PY81/800	0.72	AC137	0.25
EBF83	0.64	EF92	1.51	PCF82	1.37	PY82	0.73	AC128	0.15
EBF89	0.50	EF183	0.93	PCF86	0.97	PY86/7	70p	AC176	0.25
EC86	0.82	EF184	0.93	PCF200	1.50	PY88	0.84	AC187	0.21
EC89	0.86	EH90	1.22	PCP201	1.50	PY88	0.84	AC188	0.20
EC90	0.94	EH90	1.22	PCF801	0.97	PY800A	1.30	AC176	0.25
EC97	0.69	EL34	1.40	PCF802	1.02	PY801	0.72	AC187	0.21
EC98	0.70	EL36	1.50	PCF806	0.97	U26	1.22	AD140	0.50
EC98	0.70	EL84	0.70	PCH200	1.73	U191	1.17	AD149	0.78
EC98	0.70	EL95	1.02	PCL82	0.84	U193	0.58	AD161	0.44
EC98	0.63	EM81	1.24	PCL83	0.97	UBC81	0.80	AD162	0.44
EC98	1.22	EY61	0.89	PCL84	0.98	UBF89	0.85	AF116	0.25
EC98	1.22	EY86	0.50	PCL85	0.72	UC385	0.65	AF116	0.25
EC98	1.22	EY86/87	0.70	PCL86	0.97	UC81	1.73	AF117	0.24
EC98	0.68	EZ50	0.81	PCL805/850/97	0.97	UC81	1.22	AF186	0.48
EC98	0.90	EZ50	0.81	PD500	2.82	UC82	1.02	AF239	0.44
EC98	0.76	EZ81	0.70	PFL200	1.23	UL84	1.23	AGY27	0.40
EC98	1.73	GY501	1.73	PL36	1.40	U850	0.73	ABY28	0.25
EC98	1.08	GZ34	1.22	PL81	1.23	30PL12/		BA102	0.25
EC98	1.50	OC83	0.80	PL81A	1.40	30PL13/		BA115	0.10
EC98	1.02	PC86	1.40	PL82	0.48	ECC804	1.20	BC107	0.10
EC98	0.69	PC88	1.40	PL83	1.73	6P23/EF812		BC108	0.12
EC98	0.63	PC97	0.70	PL84	1.02	30C11/PCF80		BC118	0.15
EC98	0.62	PC90	0.84	PL500	1.40			BC117	0.21

# NEW VALVES

Individually boxed and guaranteed but of European or other origin at greatly reduced prices. Quotations for any valve not listed.

PY500	1.10	6J5M	0.65
PY81/800	0.60	6J6G	0.45
PY801	0.55	6J6	0.25
8P41	3.00	6J7G	0.80
8P81	0.25	6J7M	0.85
T41	1.50	6K6GT	0.80
U14	0.75	6K7G	0.85
U25	1.00	6K7M	0.45
U28	0.85	6K8G	0.45
U191	0.78	6K8M	0.70
UABC80	0.60	6K25	1.00
UAF42	0.75	6L6G	1.25
UBC41	0.80	6L6GC	0.80
UBC81	0.80	6Q7G	0.40
UBF80	0.80	6Q7M	0.80
UBF89	0.80	68L1T	0.80
UC385	0.65	68N7GT	0.55
UCH42	0.80	68Q7GT	0.80
UCH81	0.80	6U5G	1.50
UCL82	0.40	6V6G	0.80
UCL83	0.20	6V6GT	0.60
UD41	0.75	6X4	0.45
UD89	0.80	6X6G	0.60
UL41	0.25	6X6GT	0.55
UL84	0.50	7B6	0.80
UY41	0.55	7B7	0.80
UY85	0.45	7C5	2.00
VR105/30	0.40	7C5	1.00
VR150/30	0.48	7H7	0.80
1R5	0.80	7B7	1.30
1R8	0.45	7B7	2.25
IT4	0.75	7Y4	0.80
384	0.80	12AT6	0.45
SV4	0.85	12AT7	0.45
6K4GY	1.50	12AU6	0.50
6U4G	1.55	12AU7	0.80
6U40G	0.70	12AX7	1.00
6Y30T	0.45	12BA6	0.50
6Z4G	0.85	12BE6	0.50
6/30L2	0.60	30C1	0.40
6AK5	0.45	30C15	1.00
6AM5	2.60	30C17	1.00
6AQ5	0.80	30C18	0.90
6A87G	1.90	30F5	1.30
6AT6	0.40	30FL1	1.00
6AU6	0.40	30FL2	1.00
6BA6	0.38	30FL14	1.00
6BE6	0.48	30L15	0.95
6BH6	0.78	30L17	0.95
6BJ6	0.78	30P4MR	1.30
6BQ7A	0.88	30P12	1.00
6BR7	1.30	30P19	0.95
6BS7	1.40	30P11	0.95
6BW6	1.30	30P13	1.10
6BW7	1.30	30P14	1.10
6C4	0.40	35W4	0.70
6CD6G	1.50	35Z4GT	0.80
6CW6	2.20	30CD6G	1.50
6CW7	4.20	60W	1.50
6F23	0.90	8131TT	17.50
6F25	1.00	813USSR	7.00
6F28	0.75	866A	2.00

# TRANSISTORS-INTEGRATED CIRCUITS

**EXPRESS POSTAGE**

15p per order in UK

All transistors, I.C.'s offered are new and branded. Manufactured by Mullard, Texas, RCA, Ferranti, Motorola, ITT, Fairchild, Lucas, etc. Quantity discounts on application.

AA119	0.07	RD131	0.42	AA91	0.07	ZTX500	0.13	2N2004	0.20
AA213	0.12	BD132	0.50	AA900	0.08	ZTX501	0.15	2N2004A	0.20
AAZ15	0.10	BF115	0.20	AA202	0.06	ZTX503	0.18	2N2005	0.25
AC107	0.51	BF167	0.25	OC16	1.00	ZTX531	0.25	2N2905A	0.25
AC126	0.51	BF173	0.25	OC20	2.00	ZTX550	0.18	2N2906	0.20
AC137	0.25	BF179	0.35	OC23	1.25	1N914	0.08	2N2936	0.12
AC128	0.15	BF180	0.35	OC28	1.00	1N4001	0.08	2N3003	0.18
AC176	0.25	BF181	0.35	OC29	0.75	1N4002	0.07	2N3005	0.15
AC187	0.21	BF194	0.10	OC36	0.60	1N4003	0.08	2N3025	0.21
AC188	0.20	BF195	0.18	OC42	0.40	1N4004	0.08	2N3044	1.90
AC176	0.25	BF197	0.15	OC44	0.20	1N4005	0.10	2N3051	0.05
AD140	0.50	BF200	0.32	OC45	0.20	1N4006	0.18	2N3702	0.11
AD149	0.78	BF209	0.25	OC71	0.25	1N4007	0.18	2N3703	0.18
AD161	0.44	BFW10	0.41	OC71	0.25	1N4009	0.06	2N3704	0.14
AD162	0.44	BFX29	0.28	OC72	0.25	1N4148	0.06	2N3705	0.18
AF116	0.25	BFX68	0.24	OC76	0.30	18921	0.07	2N3707	0.18
AF116	0.25	BFY50	0.20	OC81	0.55	18923	0.30	2N3708	0.37
AF117	0.24	BFY51	0.20	OC81Z	0.28	189100A	0.80	2N3709	0.18
AF186	0.48	BFY52	0.20	OC83	0.60	189100A	0.80	2N3710	0.11
AF239	0.44	BR100	0.40	OC70	1.50	2N696	0.18	2N3711	0.11
AGY27	0.40	BY100	0.27	OC170	0.80	2N697	0.18	2N3819	0.08
ABY28	0.25	BY126	0.14	OC171	0.80	2N706	0.18	2N3820	0.50
BA102	0.25	BY127	0.12	OC200	1.00	2N706A	0.10	2N3821	0.18
BA115	0.10	BZX61 series		OC201	1.50	2N1131	0.25	2N3822	0.15
BC107	0.10			OC202	1.50	2N1132	0.25	2N3823	0.18
BC108	0.12			OC203	1.25	2N1133	0.25	2N3824	0.18
BC118	0.15	CR81-05	0.45	OC204	1.50	2N1134	0.25	2N3825	0.18
BC117	0.21	CR81-40	0.85	OC205	1.25	2N1135	0.25	2N3826	0.18
BC148	0.20	CR83-05	0.40	OC206	1.50	2N1136	0.25	2N3827	0.18
BC147	0.10	CR83-40	0.85	OC207	1.50	2N1137	0.25	2N3828	0.18
BC148	0.08	MJE340	0.47	OC208	1.50	2N1138	0.25	2N3829	0.18
BC160C	0.18	MJE370	0.88	OC209	1.50	2N1139	0.25	2N3830	0.18
BC162	0.18	MJE320	0.65	OC210	1.50	2N1140	0.25	2N3831	0.18
BC82L	0.18	MJE2955	1.27	OC211	1.50	2N1141	0.25	2N3832	0.18
BC184L	0.18	MJE3055	0.75	OC212	1.50	2N1142	0.25	2N3833	0.18
BC338	0.15	MPP102	0.40	OC213	1.50	2N1143	0.25	2N3834	0.18
BOY32	0.85	MPP103	0.88	OC214	1.50	2N1144	0.25	2N3835	0.18
BOY33	0.85	MPP104	0.85	OC215	1.50	2N1145	0.25	2N3836	0.18
BOY34	0.45	MPP105	0.88	OC216	1.50	2N1146	0.25	2N3837	0.18
BOY70	0.18	NE555	0.42	OC217	1.50	2N1147	0.25	2N3838	0.18
BOY71	0.18	NE555	0.42	OC218	1.50	2N1148	0.25	2N3839	0.18
BOY72	0.18	NE555	0.42	OC219	1.50	2N1149	0.25	2N3840	0.18
BOY73	0.18	OA5	0.78	OC220	1.50	2N1150	0.25	2N3841	0.18
BOZ11	0.65	OA10	0.40	OC221	1.50	2N1151	0.25	2N3842	0.18
BD121	1.00	OA79	0.10	OC222	1.50	2N1152	0.25	2N3843	0.18
BD124	0.65	OA81	0.18	OC223	1.50	2N1153	0.25	2N3844	0.18

**VAT**  
To be added to all orders  
Valves & Plastic Transistors 1 1/2%  
Integrated Circuits & Metal Can Transistors 8%

# THIS MONTH'S

• OSCILLOSCOPE TUBES  
Types CV 1526,  
DG 7-5, VCR 139A  
All at £8.00 each, + p & p 50p.  
Add 8% VAT

# SPECIAL OFFER

TERMS OF BUSINESS: C.W.O. A/c's available to approved companies on application. Telephone and telex orders accepted. Export and trade enquiries welcomed. Open daily to callers 9 a.m.-5 p.m. Monday to Friday. Prices correct when going to press. Prices on application for any types not listed. Obsolete valves a speciality.

# RST VALVE MAIL ORDER CO.

Climax House, Fallsbrook Rd.,  
Streatham SW16 6ED

**JC12 AMPLIFIER**  
6W IC audio amp with free data and printed circuit £2-25\*



**DELUXE KIT FOR JC12**  
Contains extra parts for the pcb and volume and tone controls. Mono version £2-33. Stereo £4-95.

**JC12 POWER KIT**  
Supplies 25V 1Amp £3-55.

**JC12 PREAMP KITS**  
Type 1 for magnetic pickups, mics and tuners. Mono £1-50. Stereo £3-00. Type 2 for ceramic or crystal pickups. Mono 85p. Stereo £1-76.

**LOUDSPEAKERS FOR JC12**  
8 x 5in 8 ohms 5W £2-48  
SEND SAE FOR FREE LEAFLET ON KITS

**SINCLAIR IC20**  
IC20 10W + 10W stereo integrated circuit amplifier kit with free printed circuit + data £4-95.  
PZ20 Power supply kit for above £3-95.  
VP20 Volume, tone-control and preamp kit £7-95.  
SP20 10W 4 ohm speaker for IC20 £2-95.  
CS20 11 x 6 x 3 in attractive case for IC20 £2-95.  
SEND SAE FOR FREE LEAFLET.

**FERRANTI ZN414**  
IC radio chip £1-44. Extra parts and pcb for radio £3-85. Case 90p. Send sae for free data.

**SINCLAIR PROJECT 80 AUDIO MODULES**  
FM Tuner £13-75. Q16 £9-50. PZ5 £4-95. PZ6 £8-70. Z40 £5-75. Stereo 80 £11-95. Project 80SQ £18-95.

**BI-PAK AUDIO MODULES**  
S450 Tuner £18-95. AL60 £4-33. PA100 £13-45. MK60 audio kit £27-20. Teak 60 £10-95. Stereo 30 £15-95. TC30 £4-60. AL260 £16-15. Send sae for free data.

**SAXON ENTERTAINMENTS AUDIO MODULES**  
SA1208 £18-95. SA1204 £13-30. SA608 £11-95. SA604 £10-30. PM1201/8 £11-45. PM1202/8 £14-95. PM1202/4 £14-95. PM1201/4 £11-45. PM601/8 £9-95. PM301/8 £8-70. Send sae for free leaflet.

**JC40 AMPLIFIER**  
New integrated circuit 20W amplifier kit complete with chip, printed circuit and data. £4-45. Send sae for free leaflet.

**PRINTED CIRCUIT KIT £3-95\***  
Make your own printed circuits. Contains etching dish, 100 sq ins of pc board, 1 lb ferric chloride, etch resist pen, small drill bit, laminate cutter.

**SINCLAIR BLACK WATCH**  
Fully assembled  
With free stainless steel bracket £20-95\*



**S-DECS AND T-DECS\***  
S-DeC £2-24. T-DeC £4-05.  
u-DeCa £4-45. u-DeCB £7-85.  
IC carriers:—  
16 dil: plain £1-07.  
with socket £2-21.  
10T05: plain 99p. with socket £1-95.



**SINCLAIR CALCULATORS\***  
Cam. Univ. £6-60. Cambridge Scientific £11-45. Oxford 300 £13-30. Programmable Scientific with free mains unit £24-95. Mains adaptors are available for all models (state model) £3-20.

**CBM CALCULATORS\***  
897D 8 digit 1/4 function memory N/A. SR7919D 8 digit or 5 + 2/memory/trig/log/pl/powers £10-95. SR1800 10 digit scientific £17-95. Mains adaptors £3-20.

**NOVUS CALCULATORS\***  
835 Model 8 digit 1/2 sq. root/cont/4 function memory £4-95. Mains adaptors £4-20.

**MISTRAL I DIGITAL CLOCK KITS\***  
Includes pcb, power supply, case, 1/2" display, chip and all parts. Kit £10-95. Built £11-95. Also Mistral 2, deluxe assembled version with alarm and tilt sleep-over facility N/A.  
SEND SAE FOR OUR DIGITAL CLOCK LEAFLET

**BATTERY ELIMINATOR BARGAINS**  
**STABILIZED POWER UNITS\***  
Millenia series. Switched 1 to 30V in 0-1V steps. 1A output: Kit £11-45. Kit + case £14-40. Built £18-40. 2A output: Kit £13-95. Kit + case £16-90. Built £20-95.

**6-WAY SPECIAL £5-20**  
Switched output of 3, 4½, 6, 7½, 9, 12V at 500mA



**6-WAY DOUBLE RADIO MODEL £6-20**  
Switched output 3+3/4+4+6/6/7/3+7½/9+12+12V at 250mA. Also 15/18/24V single.

**J-17V MODEL**  
Switched output of 6/7½/9V at 250mA with 4-way multi-jack plug £2-95\*

**RADIO MODELS**  
50mA with press-stud battery connectors. 9V £3-25. 6V £3-45. 9+9V £4-95. 6+6V £4-95. 4+4½V £4-95. Also 9V 300mA £3-95.

**CASSETTE MAINS UNITS**  
7½V output with 5 pin DIN plug. 50mA £3-45. 300mA £3-95.


**CAR CONVERTORS**  
Input 12V DC. Output 6/7½/9V DC 1A regulated £4-75\*

**BATTERY ELIMINATOR KITS**  
Send sae for free leaflets on range.  
100mA radio type with press-stud battery terminals. 4½V £1-95. 6V £1-95. 9V £1-95. 4½V + 4½V £2-60. 6V + 6V £2-60. 9V + 9V £2-60.  
100mA cassette type with 5 pin DIN plug. 7½V £1-95.  
Transistor stabilized 8-way type for low hum. 3/4½/6/7½/9/12/15/18V. 50mA £3-15. 1A £6-50.  
Heavy duty 13-way types 4½/6/7½/11/13/14/17/21/25/28/34/42V. 1 Amp Model £4-40. 2 Amp Model £6-95.  
Car Converter kit Input 12V DC. Output 6/7½/9V DC 1A regulated £1-95.

**MAINS TRANSFORMERS**  
6-0-6V 100mA £1. 9-0-9V 100mA £1. 18V 1A £1-95. 0/12/15/20/24/30V 1A £3-60. 12-0-12V 100mA £1. 0/12/15/20/24/30V 2A £4-95. 20V 2½A £2-25. 6-0-6V 1½A £2-16. 9-0-9V 1A £2-45. 12-0-12V 1A £2-95. 15-0-15V 1A £2-95. 30-0-30V 1A £3-60. 6-3V 1½A £1-95. 0-24V twice 100mA £1-65.

**SWANLEY ELECTRONICS**  
Dept. PW, PO BOX 68,  
SWANLEY, KENT.

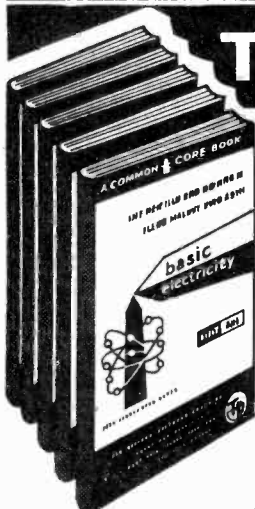Post 30p on orders under £2, otherwise free. Prices include VAT. (Overseas customers deduct 7% on items marked\*, otherwise 11%). Official orders welcome.



# The Pictorial Method

## BASIC ELECTRICITY (5vols) BASIC ELECTRONICS (6vols) BASIC TELEVISION (3vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

**YOUR 100% GUARANTEE**

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

**WHAT READERS SAY**

I didn't know this subject could be so easily presented.  
*J. K., Earlsfield*  
Pleased to say how understandable your books are—I now have a sound knowledge of the subject.  
*A. K., Hull*  
Invaluable for my training as a Technician.  
*W. J., Stockport*  
They have an easy approach to learning that a mathematical idiot like myself can easily understand.  
*K.L.Y., Ashton-u-Lyme*  
Thank you for the excellent publication: the best in form and type I have ever come across.  
*T.L.O., Shanklin*  
I find the Basic Manuals the best in their class and a real help in my work in prototype electronics.  
*C.L.P., Cardiff*

**To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP**

Please find enclosed P.O./Cheque value £.....

BASIC ELECTRICITY 5 parts £8-00

BASIC ELECTRONICS 6 parts £9-50

BASIC TELEVISION 3 parts £5-00

Tick Set(s) required. Prices include Postage

**YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.**

NAME .....

BLOCK LETTERS .....

FULL POSTAL .....

ADDRESS .....

**POST NOW FOR THIS OFFER!**

# 15—240 Watts!


## HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

**FEATURES:** Complete pre-amplifier in single pack—Multi-function equalization—Low noise—Low distortion—High overload—Two simply combined for stereo.

**APPLICATIONS:** Hi-Fi—Mixers—Disco—Guitar and Organ—Public address

**SPECIFICATIONS:**  
**INPUTS:** Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV; Auxiliary 3-100mV; Input impedance 4-7k $\Omega$  at 1kHz.  
**OUTPUTS:** Tape 100mV; Main output 500mV R.M.S.  
**ACTIVE TONE CONTROLS:** Treble  $\pm$  12dB at 10kHz; Bass  $\pm$  at 100Hz.  
**DISTORTION:** 0-1% at 1kHz. Signal/Noise Ratio 68dB.  
**OVERLOAD:** 38dB on Magnetic Pick-up. **SUPPLY VOLTAGE**  $\pm$  16-50V.  
**Price** £4.75 + 59p VAT P&P free.

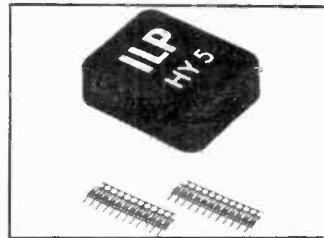

## HY30 15 Watts into 8 $\Omega$

The HY30 is an exciting New Kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

**FEATURES:** Complete Kit—Low Distortion—Short, Open and Thermal Protection—Easy to Build.

**APPLICATIONS:** Updating audio equipment—Guitar practice amplifier—Test amplifier—audio oscillator.

**SPECIFICATIONS:**  
**OUTPUT POWER** 15W R.M.S. into 8 $\Omega$ ; **DISTORTION** 0-1% at 1-5W.  
**INPUT SENSITIVITY** 500mV. **FREQUENCY RESPONSE** 10Hz-16kHz—3dB.  
**SUPPLY VOLTAGE**  $\pm$  18V.  
**Price** £4.75 + 59p VAT P&P free.



Available  
June '76

## HY50 25 Watts into 8 $\Omega$

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

**FEATURES:** Low Distortion—Integral Heatsink—Only five connections—7 amp output transistors—No external components

**APPLICATIONS:** Medium Power Hi-Fi systems—Low power disco—Guitar amplifier

**SPECIFICATIONS:** **INPUT SENSITIVITY** 500mV  
**OUTPUT POWER** 25W RMS into 8 $\Omega$  **LOAD IMPEDANCE** 4-16 $\Omega$  **DISTORTION** 0-04% at 25W at 1kHz  
**SIGNAL/NOISE RATIO** 75dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB.  
**SUPPLY VOLTAGE**  $\pm$  25V **SIZE** 105 50 25mm  
**Price** £6.20 + 77p VAT P&P free.




## HY120 60 Watts into 8 $\Omega$

The HY120 is the baby of I.L.P.'s new high power range. Designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

**FEATURES:** Very low distortion—Integral heatsink—Load line protection—Thermal protection—Five connections—No external components

**APPLICATIONS:** Hi-Fi—High quality disco—Public address—Monitor amplifier—Guitar and organ

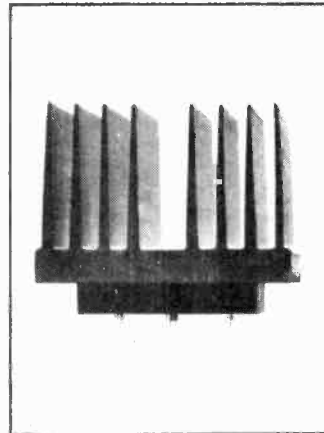**SPECIFICATIONS:**  
**INPUT SENSITIVITY** 500mV.  
**OUTPUT POWER** 60W RMS into 8 $\Omega$  **LOAD IMPEDANCE** 4-16 $\Omega$  **DISTORTION** 0-04% at 60W at 1kHz  
**SIGNAL/NOISE RATIO** 90dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**  $\pm$  35V  
**SIZE** 114 50 85mm  
**Price** £14.40 + £1.16 VAT P&P free.




## HY200 120 Watts into 8 $\Omega$

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

**FEATURES:** Thermal shutdown—Very low distortion—Load line protection—Integral heatsink—No external components

**APPLICATIONS:** Hi-Fi—Disco—Monitor—Power slave—Industrial—Public Address

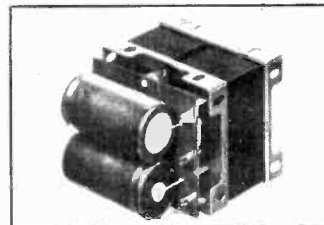**SPECIFICATIONS:**  
**INPUT SENSITIVITY** 500mV  
**OUTPUT POWER** 120W RMS into 8 $\Omega$  **LOAD IMPEDANCE** 4-16 $\Omega$  **DISTORTION** 0-05% at 100W at 1kHz.  
**SIGNAL/NOISE RATIO** 96 dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**  $\pm$  45V  
**SIZE** 114 100 85mm  
**Price** £21.20 + £1.70 VAT P&P free.




## HY400 240 Watts into 4 $\Omega$

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 $\Omega$ ! It has been designed for high power disco address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

**FEATURES:** Thermal shutdown—Very low distortion—Load line protection—No external components.

**APPLICATIONS:** Public address—Disco—Power slave—Industrial

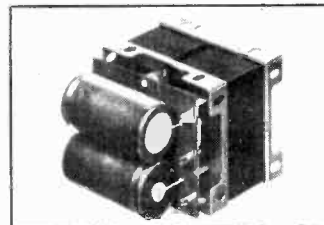**SPECIFICATIONS:**  
**OUTPUT POWER** 240W RMS into 4 $\Omega$  **LOAD IMPEDANCE** 4-16 $\Omega$  **DISTORTION** 0-1% at 240W at 1kHz  
**SIGNAL/NOISE RATIO** 94dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**  $\pm$  45V  
**INPUT SENSITIVITY** 500mV **SIZE** 114 x 100 x 85mm  
**Price** £29.25 + £2.34 VAT P&P free.



## POWER SUPPLIES

PSU36 suitable for two HY30's £4.75 plus 59p VAT. P/P free.  
 PSU50 suitable for two HY50's £6.20 plus 77p VAT. P/P free  
 PSU70 suitable for two HY120's £12.50 plus £1.00 VAT. P/P free.  
 PSU90 suitable for one HY200 £11.50 plus £0.92 VAT. P/P free.

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd.  
 Crossland House  
 Nackington, Canterbury  
 Kent CT4 7AD  
 Tel. (0227) 63218

Please Supply \_\_\_\_\_  
 Total Purchase Price \_\_\_\_\_  
 I Enclose Cheque  Postal Orders  Money Order   
 Please debit my Access account  Barclaycard account   
 Account number \_\_\_\_\_  
 Name and Address \_\_\_\_\_  
 Signature \_\_\_\_\_

# ambit international

## Coils, ICs for RF&AF, Tuners, Modules for AM FM & TV.

### complete tuner kits

Laresholt Signalmaster Mark 8....the most stylish FM tuner kit that is available today. Suitable for even the relatively inexperienced in electronics construction, with clear and concise point-to-point details. Performance matches the excellent looks. £86.95

International Mark 2....A flexible system, with cabinet, chassis and panel designed to accommodate a variety of tuner electronics. The standard system is built around the Laresholt 7253 tuner set, includes two meters 6 preset stations, manual tune, balanced LED tuning, PSU etc. £65.00

The above tuners are supplied with prealigned RF and IF stages.

AM/FM.....a new low cost MW/LW and FM stereo tuner, with muting, mechanical drive, teak effect cabinet. £41.95

TV sound.....the 7700 TV sound module in a chassis and cabinet that matches the AM/FM tuner. £36.95

Please remember to include an extra £3 carriage on complete tuner kits.

Radio ICs	Misc. regs etc.	Transistors
CA3089E FM IF 1.94†	7805UC 5v 1A 1.55*	ZTX107 0.14
CA3090AQ mpx 3.75†	78M12 12v ½A 1.20*	ZTX108 0.14
MC1310P mpx 2.20†	TDA1412 ... 0.95*	ZTX109 0.14
SN76660N FM IF 0.75	7815UC 15v 1A 1.55*	ZTX212 0.16
TBA120AS FM IF 1.00	78M20 20v ½A 1.20*	ZTX213 0.16
MC1350 AM/FM IF 0.70	78M24 24v ½A 1.20*	ZTX214 0.16
HA1197 AM system 1.40	uA723 5-35v 0.80*	ZTX413 0.18
TBA651 AM system 1.81	NE550A do. 0.80*	ZTX551 0.18
uA720 AM system 1.40	TAA550B 32v. 0.50*	ZTX451 0.18
	uA741 op amp 0.40*	BF224 0.22
	LM3900 quad amp 0.68*	BD165 0.50
	MC3401 do. 0.68*	BD166 0.54
	8038 wave gen. 3.10*	BD535 0.52
	NE555 timer 0.70*	BD536 0.53
	NE560B PLL 2.50	BD609 0.70
	NE561B PLL 3.50	BD610 1.20
	NE562B PLL 2.50	40673 0.50
	NE565A PLL 2.50	MEM680 0.75
	NE566V VCO 2.55*	BF256L 0.38
	NE567V tone trigger 2.50*	

**Tunerheads for VHF FM and UHF TV (All varicap types)**

EF5800	6 circuit high quality 88-108MHz tunerhead	14.00
EF5600	5 circuit high quality 88-108MHz tunerhead	12.50
EC3302	3 circuit (sime spec to LP1186) VHF tunerhead	5.50
5700	UHF TV tunerhead 38MHz IF with 4 way preset	8.00

**Modules for IF, decoders etc. (Also available built & tested)**

7020 kit	10.7MHz FM IF with mute, AFC, AGC, meter ops	5.25
7030 kit	10.7MHz linear phase low distortion FM IF	7.67
92310 kit	Stereo decoder with full pilot tone filtering (PLL)	5.35
93090 kit	Stereo decoder, low noise and distortion	6.40
7252	FM tuner set, built - 1uV in, Audio out with mute and all HiFi tuner features. Varicap tuned.(mono)	24.00
7253	FM tuner set, built 1.2uV in, stereo out, with mute and all Hi Fi tuner features. Varicap tuned.	24.00
71197 kit	Varicap tuned MW radio module. The best AM tuner, with 75dB AGC, 0.3% THD.	9.65
8001 kit	55kHz low pass, birdy, filter for stereo radio	1.75
2020 kit	TDA2020 stereo amplifier, with special heatsinks	9.35

**Famous TOKO COILS, Mechanical filters, ceramic filters, chokes etc.**

455/470kHz IF coils	0.30	M41T 4kHz/455kHz Mech filt.	1.65
(1st, 2nd & 3rd)IFTs	0.70	M71T 7kHz/455kHz Mech filter	1.65
10.7MHz IFTs	0.32	C455B 8kHz/455kHz ceramic filt 0.55	
Variable signal chokes:		C455C 6kHz/455kHz ceramic filt 0.55	
2mH, 23mH, 36mH, 7mH		C050D 6kHz/470kHz ceramic filt 0.60	
11.75mH	0.33	CF5107 10.7MHz cer. FM filter	0.50
Fixed chokes: (uH)		SFE6.0 6MHz TV sound IF filter	0.80
1.0, 4.7, 10, 33, 47, 100,		3132A linear phase FM IF filter	2.25
22, 33, 470, 1000	0.16	SFD470B 470kHz ceramic filter	0.75

PLEASE REMEMBER TO INCLUDE VAT - thank you !!

If you have read this far, you probably appreciate that AMBIT tends to specialize in the areas of wireless and TV that most component sources do not include. Our catalogue and price list continue this theme with coils, linear ICs etc. Catalogue 40p, price list free with SAE. Post is 22p per order - unless otherwise stated.

**37a HIGH STREET,  
BRENTWOOD ESSEX  
telephone 0277 216029**

## CMOS WITH DISCOUNTS!

Any mix: Discount 10%, 25+, 25%, 100+, 33%, 1000+



## CUS 4 CMOS!

4000	0.20	4099	3.09	4081	0.24	14505	4.38	E <sup>2</sup> LED Displays
4001	0.20	4060	1.19	4082	0.24	14506	0.57	DL-704E 0.3" 79p
4002	0.20	4041	0.93	4085	0.30	14507	0.60	DL-707E 0.3" 79p
4006	1.31	4042	0.93	4086	0.30	14508	3.08	DL-728E 2 x 0.5" 1.50
4007	0.20	4043	1.12	4089	1.74	14510	1.51	DL-727E 2 x 0.5" 1.50
4008	1.07	4044	0.94	4093	0.39	14511	1.74	DL-727E 2 x 0.5" 1.50
4009	0.60	4045	1.58	4094	2.08	14512	1.03	DL-750E 0.6" 1.50
4010	0.60	4046	1.48	4095	1.16	14514	3.47	DL-747E 0.6" 1.50
4011	0.20	4047	1.01	4098	1.16	14515	3.47	DL-747E 0.6" 1.50
4012	0.20	4048	0.90	4097	4.13	14516	1.51	Red Leds
4013	0.99	4049	0.90	4098	1.22	14517	4.02	0.1" 15p
4014	1.12	4050	0.90	4099	2.93	14518	1.30	0.2" 15p
4015	1.12	4051	0.94	4010	1.78	14519	0.57	Clock Chips
4016	0.99	4052	1.04	40102	2.16	14520	1.39	AY-1224A 3.50
4017	1.12	4053	1.04	40103	2.16	14521	2.77	MK0253 5.50
4018	1.12	4054	1.20	40104	2.20	14522	2.15	Soldercon Pins
4019	0.99	4055	1.46	40107	0.98	14526	2.15	100 Pins
4020	1.24	4056	1.46	40108	6.18	14527	1.70	1200 4.00
4021	1.12	4057	1.00	40109	2.21	14528	1.22	2500 8.75
4022	1.07	4059	0.20	40181	4.30	14529	1.72	DIL Sockets
4023	0.20	4060	1.24	40182	1.73	14530	0.05	14/16 Pin 15p
4024	0.97	4061	25.60	40194	2.20	14531	1.74	Red Acrylic Filter
4025	0.20	4062	10.10	40207	2.20	14532	1.38	For LED displays
4026	1.92	4063	1.22	4700	1.75	14534	0.00	157 x 29 x 3mm 78p
4027	0.99	4076	0.98	7083	4.25	14536	0.00	Push Switches
4028	1.00	4067	4.13	14160	1.18	14537	13.17	Type SW9 15p
4029	1.27	4068	0.24	14161	1.18	14539	1.24	Op-Amps
4030	0.80	4069	0.24	14162	1.18	14541	1.82	CA3140
4031	2.46	4070	0.65	14163	1.18	14543	1.82	(COS/MOS) 1.00
4032	1.10	4071	0.24	14174	1.90	14544	4.16	CA3140
4033	1.85	4072	0.24	14178	1.04	14552	10.50	(BI/MOS) 85p
4034	2.11	4073	0.24	14194	1.17	14553	4.66	741 Minidip 25p
4035	1.31	4075	0.24	14490	6.51	14554	1.87	
4036	3.09	4076	1.71	14501	0.20	14555	1.91	
4037	1.06	4077	0.85	14502	1.38	14556	1.81	
4038	1.20	4078	0.85	14503	0.75	14557	4.65	

Terms: C.W.O. Add VAT to all prices at 8%. Post etc. U.K. 25p + 2p - 27p per order. All orders processed same day. Official Govt. 'Varsity', Poly etc. orders (written or telephoned) welcome.

## GREENBANK ELECTRONICS (Dept. WIIP)

94 New Chester Road, New Ferry, Wirral, Merseyside  
L62 5AG Tel: 051-645 3391

**Capacitor Discharge IGNITION**

■ MAXIMUM PERFORMANCE  
■ MAXIMUM ECONOMY  
■ EASY COLD START

**SYSTEM I**

Professional photoelectric ignition using L.E.D. light source and reflective disc. This machined aluminium disc gives a timing accuracy far superior to other methods and is simple to fit. Unit housed in diecast box 4 1/4" x 3 3/8" x 2 1/4" Price £18.90 (Kit £18.90) State car/model/measurement across cam lobes.

**SYSTEM II**

Contact breaker model as above less sensor. Price £12.90 (Kit £10.00) M/C Twin unit Price £15.00. S.A.E. for descriptive leaflet - ALL UNITS IN STOCK. Mail orders to CDI Electronic Systems Ltd, 276 Vale Road, Ash Vale, Aldershot, Hants. Demonstration/Callers to Hillside Motors, 292 Carshalton Road, Carshalton, Surrey. telephone 01-642 9973.

51 Deptford Broadway, London SE8 4PH Telephone: 01-692 4284

## INDUSTRIAL RF SERVICES

H.F. WELDING INDUCTION & ELECTRICAL ENGINEERS

Suppliers of Surplus Electronic Components and Test Equipment

5 panels approx 5" x 12" packed with diodes, transformers, coils, ICs TTL transistors capacitors resistors etc. all 1975 gear limited quantity only £2.50 pp 80p

Grundig dictating machines slightly soiled and untested only £5.00 pp £1.50.

Small 2 waveband radios new boxed but sold as not working only £1.00 inc pp.

Everbrite multicore solder 18avg 23 KIL0 reels only our price £9.50 pp 90p.

Adcolia holding Irons 240V 23W New Boxed Our price £2.65 pp 50p.

10 LARGE panels Approx 10" x 12" Packed with condensers diodes transistors resistors etc £3.00 pp 90p.

Vernier dials 2" 0-100 £1.50 1 1/2" 0-10 £1.10 pp 50p

10 mixed computer panels £1.50 pp 50p

Transformers 25-0-25 1 amp £1.40 pp 60p 24 volt 1 amp £2.75 pp 80p.

METERS Talyco Edgewise no scale readings just markers miniature 50-0-50 micro amp £1.00 pp 40p.

Taylor Edgewise 50 micro amp and 100 Ma £1.00 pp 40p.

VIDEO tape to clear 1" £1.00 each pp 80p.

Computer tape to clear 1/2" £1.00 each pp 80p.

Record player deck plinths £1.00 each pp £1.00.

Potentiometers 5lb parcel £1.00 pp 60p.

Ferrite rods 5 assorted sizes 85p pp 30p

Capacitors 32mf 450V 32p pp 20p 140mf 350V 54p pp 30p 10 plus P & P free.

## RETURN OF POST MAIL-ORDER SERVICE

JUST RELEASED

### R.C.S. 100 watt VALVE AMPLIFIER



Four inputs. Four way mixing, master volume, treble and bass controls. Suits all speakers. This professional quality amplifier chassis is suitable for all groups, disco, P.A., where high quality power is required. 5 speaker outputs. A/C mains operated. Slave output. Produced by demand for a quality valve amplifier. Send for details. Suitable carrying cabinet £14. Price **£85** carr. £2-50

### ANOTHER R.S.C. BARGAIN!

ELAC 9 + 5in. HI-FI SPEAKER TYPE 59RM  
This famous unit now available, 10 watts, 8 ohm.

Price **£3-25** Post 40p



### 8" ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-10,000 cps. Bass resonance 55 cps. 8 ohm impedance, 10 watts. Post 40p **£3-95**

10in round £4-95.

### TEAK VENEER HI-FI SPEAKER CABINETS

MODEL "A". 30 x 18 x 12in. For 12in. dia. or 10in. speaker. Illustrated. Price **£13-50** 95p

MODEL "B". For 18 x 8in. or 8 in. speaker. Price **£7-50** Post 75p

MODEL "C". 30 x 20 x 12in. Reflex cabinet will accept 1-12in. bass unit, 1-8in. mid range, 1-8in. tweeter. Teak finish. Grooved front. Price **£21-50** Carr. £3

LOUDSPEAKER CABINET WADDING 18in. wide, 25p. it.

### GOODMANS CONE TWEETER

9 1/2in. diam. 18,000 C.P.S. 25 WATTS 8 Ω **£3-25**  
8 inch woofer 15 watts £6-75.

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated. Price **£5-20**

STEREO VERSION OF ABOVE £6-85.

BARGAIN 8 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. Mains Supply £2-95. Price **£3-95**

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER. Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/240V. Leadset S.A.E. Price **£3.95** Post 40p

### WATER HEATING ELEMENTS

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 1 1/2 x 2 1/2 x 1/2 in. Operating voltage 200/250V, a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe block heat. Suitable for use in photocopyers and print drying equipment. Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Convectro Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the garage—preventing frozen radiators or soiling as oil sump heater. Use in greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY **40p** EACH (FOUR FOR £1-50)  
ALL POST PAID—Discounts for quantity.

### BAKER MAJOR 12" £10-35



Post 60p  
30-14,500 c/s. 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 146,000 Maxwells. Bass resonance 40 c/s raised 85 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£13**

Please state 3 or 8 or 15 ohms. Post 60p

### BAKER SPEAKERS "BIG SOUND"

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass resonance 55 cps.

GROUP "25" **£8-95**  
12in 30 watt  
3, 8 or 15 ohms. Post 50p

GROUP "35" **£10-50**  
12in 40 watt  
3, 8 or 15 ohms. Post 50p

GROUP "50/12" **£14-50**

12in 60 watt professional model. 8 ohms or 15 ohms. With aluminium pressure dome. Post 50p

GROUP "50/15" **£19-50**  
15in 75 watt  
8 or 15 ohms. Post 90p

### BAKER 150 WATT QUALITY TRANSISTOR MIXER/AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4-way mixing. Output 8 Ω ohm. A.C. mains. Separate treble and bass controls. Guaranteed. Details S.A.E. Professional amplifier using advanced circuit design. Ideal for disco, groups, P.A. or musical instruments. 4 inputs 4 way mixing. Master treble, bass and volume controls. 3 speaker output sockets to suit various combinations of speakers. 4 to 16 ohm. Slave output. A/C mains. Guaranteed. Details S.A.E. Latest 50 watt Model **£49**

### 100 WATT DISCO AMPLIFIER CHASSIS

MADE BY JENNINGS MUSICAL INSTRUMENTS **£52**  
4 speaker outputs, vol., treble, bass controls  
CAN BE USED AS 100WATT SLAVE Carr. £1

### QUALITY LOUDSPEAKER ENCLOSURE

Teak veneered 3/4in thick wood cabinet. Size 18 1/2in x 15 1/2in x 8 1/2in. Weight 22lb. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horn. The fully sealed bass compartment is cut out for 6in Woofer. £7-50. Carr. 85p. Rosewood Version £8-50. Carr. 85p. Baffle could be cut for larger speaker.

### P.W. SOUND TO LIGHT DISPLAY

Complete kit of parts with R.C.S. printed circuit. Three channels. 800 to 1,000 watt each. As featured in December Practical Wireless. Price **£12-50**  
Cabinet extra £3.

8 inch PHILIPS LOUDSPEAKER **£1-95**  
4 ohm. 4 watt. ceramic magnet  
General purpose replacement unit.

### MAINS TRANSFORMERS

Post 50p  
6 VOLT 1 AMP. £1-00 3 AMP. £1-40  
12 VOLT 300 MA. £1-00 750 MA. £1-80  
24 VOLT 1 AMP. £1-75 3 AMP. £2-45  
20 VOLT 1 AMP. £1-75 3 AMP. £2-00 8 AMP. £2-20  
20-0-20 VOLT 1 AMP. £2 80 VOLT 1 AMP. £1-75  
0-20-40-80 VOLT 1 AMP. £2-50

### E.M.I. TAPE MOTOR

4 pole, 240 v. Size 2 1/2 x 2 1/2 in. 1200 rpm. Spindle 1/4 in. diameter. 120v version £1. Price **£1-85** Post 45p

### E.M.I. GRAM MOTOR

240V a.c. 2,400 rpm. 2-pole. Size 2 1/2 x 2 1/2 in. Collaro gram motor 120v. 75p. Price **£1-25** Post 35p

### BAKER DISCO SPEAKERS HIGH QUALITY—BRITISH MADE

#### 2 x 12" CABINETS

for Disco or PA all fitted with carrying handles and corners. Black finish. Other cabinets in stock. SAE For leaflet

**50 WATT R.M.S. £43**

Carr. £2

**70 WATT R.M.S. £46**

Carr. £2

**100 WATT R.M.S. £59**

Carr. £2



1 x 15" + 1 x 12" 100 WATT CABINET  
Size 36" x 24" x 15" **£65-00.** Carr. **£5**  
Ideal for Disco, Ogran or PA work. High quality. Full range.

### SUPERB HI-FI

12in 25 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register. Price **£16-30** Post 80p

### AUDITORIUM

12in. 35 watts

A full range reproducer for high power, Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Discotheques. Price **£15-50** Post 80p

### AUDITORIUM

15in. 45 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home Hi-Fi. Price **£19-50** Post 90p

Hi-Fi Enclosure Manual containing plans, designs, crossover data and cubic tables, 63p

## RADIO COMPONENT SPECIALISTS

Minimum post 30p. Components Lists 10p.

Cash price includes VAT

337 WHITEHORSE ROAD, CROYDON  
Open 9—6 Wed. 9—1 Sat. 9—5 (Closed for lunch 1.15—2.30)  
Access & Barclay cards welcome. Rail Selhurst. Tel. 01-684 1665

Practical Wireless, November 1976







# NOW-just when you need it most!

**BI-PRE PAK'S  
ONCE-IN-A  
LIFETIME**

# SALE

**PACKS  
COMPONENTS  
MODULES  
SUNDRIES  
BOOKS**

**SEE  
BELOW**

## MANY ITEMS AT HALF PRICE AND LESS PAKS DOWN FROM 60p TO 30p EACH

● **TESTED PAKS all at 30p each.**

- Pak No. Contents**
- TP10** 2 Light dependent resistors. 400 ohms light, 1 megohm dark.  $\frac{1}{2}$ " dia.
  - TP11** 10 Transistors XB102 & XB112 equiv. to AC126 AC156, OC81/2, OC72, etc.
  - TP13** 5 OCP71 Light sensitive transistors.
  - TP14** 20 OC71 germanium PNP audio pre amp transistor, black glass type
  - TP15** 20 OC81 germanium PNP audio output transistor, white glass type
  - TP17** 20 1 watt zener diodes, mixed 6.8 to 43 volts
  - TP20** 10 Mullard OC45 transistors. I.F. amp PNP germanium
  - TP21** 30 Short lead ( $\frac{1}{2}$ " approx) transistors, NPN silicon planar types Ex radio manufacturer, all good but production line changes.
  - TP22** 8 Integrated circuits. 4 gates BMC962 and 2 flip flops BMC945.
  - TP27** 5 Germanium PNP high frequency transistors, unmarked similar to OC170/171. AF115/6/7/3 lead TO-1.
  - TP28** 5 2N918 UHF/VHF silicon transistors. NPN 4 lead TO-18 uncoiled.
  - TP35** 4 3B19E transistors. N channel FETs these are 2N3819s in plastic cases.
  - TP38** 8 Integrated circuits. DTL data supplied. Mixed types flip flops.
  - TP40** 15 Transistors, these are brand new manufacturers surplus items.

● **UNTESTED PAKS all at 30p each**

- Pak No. Contents**
- UT2** 150 Germanium diodes. miniature glass type
  - UT3** 100 Silicon diodes miniature glass type, similar to 1N4148
  - UT4** 100 Silicon diodes. miniature glass type, similar to 1N914/6.
  - UT5** 40 Zener diodes, 250mW OAZ240 range, average 50% good
  - UT6** 25 Zener diodes. 1-1 $\frac{1}{2}$  watt top hat type, mixed voltages.
  - UT7** 30 Silicon rectifiers. 750mA BY 100 type, top hat, mixed voltages.
  - UT10** 15 Power transistors, PNP germanium and NPN silicon, mostly TO-3 but some plastic and some marked.
  - UT11** 30 OA47 gold bonded diodes, polarity marked.
  - UT12** 10 2N3819 10-channel FETs plastic case type.
  - UT13** 15 integrated circuits. experimenters pak, dual in line 10-5, TTL, DTL, marked and unmarked, some definitely good but old types.
  - UT14** 15 AC128 transistors PNP germanium audio output.

● **COMPONENT PAKS all at 30p each**

- CP1** 150 Capacitors, mixed bag of paper, silver mica electrolytic, etc. Approx No. counted by weight.
- CP2** 200 Resistors, mixed types and wattages, including HI-stability Approx No. counted by weight.
- CP5** 5 Earphones, single low impedance for transistor radios, cassettes, etc. No plugs
- CP7** 25 Heat sinks, to fit SO-2 (OC72) and TO-1 (AC128) etc.
- CP8** 500 Cable clips for G.P.O.  $\frac{1}{4}$ " dia cable. Nylon with hardened steel pin (probably tungsten) sealed box of 500.
- CP12** 10 Reed relay inserts,  $\frac{1}{4}$ " long  $\frac{1}{2}$ " dia. will operate from external magnet or coil. For magnets see PAK CP13.
- CP13** 10 Magnets various sizes for operating reedswitches in PAK, CP12. ideal for burglar alarms on doors and windows, etc.
- CP16** 5 P.C. boards each containing a BF180 UHF amplifier transistor. A good basis for building a TV aerial pre-amp
- CP17** 25 Electrolytic Capacitors, various values and voltages, many useful types, from T.V. to transistor radio & Hi-Fi.
- CP18** 1 Light activated SCR, 50 volts 1-6 A type L9F. Ready mounted on PCB with gate resistor & leads fitted. Full data & circuits for 14 projects. Inc. slave photo flash unit, burglar alarm, etc.
- CP19** 3 Micro switches 1 pole change over, standard model  $1\frac{1}{2}$ " x  $\frac{1}{4}$ ".
- CP21** 200 Square inches copper laminate P.C. board in approx. 8 pieces.
- CP23** 4 switches, miniature, push to make, single pole.

**FIRST EVER: QUARTZ CRYSTAL PAK**

Containing ten quartz crystals. 2-pin plug-in types. Easily dismantled from housing for inducting to different frequencies. Add 10p per pack to postage charge. **50p**

**BUMPER I.C. PAK** **50p**  
50 I.C.s at one penny each!  
50 assorted integrated circuits including many brand new marked devices.

## MISCELLANEOUS—Your chance to save pounds

**PRINTED CIRCUIT PANELS (Ex Equipment)**

**TYPE L4** Ex cash register board. Equipped with 8 x SN7490N decade counters. 11 x SN15846N quad 2 input NAND/NOR gate. 1 x SN7413 dual schmidt trigger £1.50

**TYPE L5.** A stabilised power supply board for I.C.s Equipped with 4 x SN7413N dual schmidt triggers 1 x TVR2001 tenor I.C., 1 x 2N3738 power trans. various resistors & capacitors. 76p

**UHF TUNER UNITS**

We have sold thousands of these units brand new and made by a world famous manufacturer. Covers 625 line T.V. channels 21 to 65 Standard T.V. IF frequency output ideal for making a Hi Fi television sound receiver. £1.50

**HIGH VOLTAGE (12KV) DIODES**

Replacements for colour TV triplers, only 5 for 50p

**ON-OFF ROCKER SWITCHES**

2 pole 1 way mains push cut: 7 for hole size  $\frac{1}{2}$ " x  $\frac{1}{4}$ " each 15p.

**8U.D.C. MOTORS**

Stabilised speed regulated. Ideal for portable record or cassette players. Size  $\frac{1}{2}$ " dia. x  $\frac{1}{4}$ " plus spindle. Brand new and boxed 75p

**SUNDRY POST OFFICE (G.P.O.) ITEMS**

**EX G.P.O. telephone dials**, as used in 700 and 300 type phones. Complete 35p

**EX G.P.O. telephone handsets** with lead, black. (Additional P & P. 25p) 40p

**EX G.P.O. buzzers**, 12/24 volt operation, clean condition 20p

**EX G.P.O. push button key switches**, 2 pole change over. Brand new. 15p

**EX G.P.O. counter units** 0000-9999. 10 per second (24-48v. operation) 20p

**INSTRUMENT CASES**

Beautifully finished in stove enamelled grey crackle, in heavy gauge aluminium with internal racking and heavy gauge panels (suitable as heatsinks). Ideal for P.A. systems, bench power supplies, oscilloscopes, metered instruments, etc. **BRAND NEW AND BOXED.**

**SIZE "A"** 14" x 15" x 6" deep £5.50 + additional 25p for P/P.

**SIZE "B"** 17" x 16" x 12" deep £6.50 + additional £1 for P/P.

**A FASCINATING & UNUSUAL OFFER VARIABLE PRE-SET VOICE DECODERS**

Brand new, but sold essentially for component value

4 stages, 7 position control knobs. On 10" x 12" P.C.B. in plastic tray

Contains 35 I.C.S. viz. 8 x 7493, 5 x 7420, 7 x 7400, 4 x 7404, 2 x 7430, 2 x 7410, 2 x 7442, 2 x 7401, 1 x 7413, 1 x 7474 and 1 x 7490 (total 35) plus 35 transistors, 4 miniature rotary switches, voltage stabilizer and various other components. **£4.00** + additional 50p for P/P

**PUSH BUTTON SELECTOR ASSEMBLIES**

for varicap tuning systems as used in VHF/FM radio receivers of UHF/TV tuners. With indicators on each stage. **£1.25\***

4 button assemblies. **£2.00\***

7 button assemblies with A.F.C. switch

**STEREO DECODERS (FM)**

I.C. operated units for use in negative earth systems **£1.95\***

Transistor operated unit for use in positive earth systems. **£1.75\***

L.E.D.s can be added to the above

**12 RELAYS £1 ONLY**

Ex GPO and others; various voltages and coil impedances, non-specified but extremely useful to keep for when wanted. Add 35p per pack to postage charge.

**TECHNICAL BOOKS**

Dozens and dozens of titles of NEWNES-BUTTERWORTH, BABANI PRESS, BERNARD PUBLISHERS All at **25% OFF PUBLISHERS PRICES** S.A.E. brings full list

**VAT 8%**

**ON EVERYTHING EXCEPT ITEMS MARKED \*** At 12% Please add appropriate amount to total value of your order.

**MINIMUM ORDER** for items sent by post £3 excluding VAT and postage.

**POSTAGE** Please add 50p for P/P to all orders unless stated otherwise. Where additional postage and packing is quoted this is to be added to the basic 50p charge.

**CALLERS WELCOME—ORDER WITHOUT DELAY—OFFERS CANNOT BE REPEATED**

Originators of and first with component paks in U.K. and still leading

# BI-PRE-PAK

**BI-PRE-PAK LTD Dept. PW.S**  
220-224 WEST ROAD, WESTCLIFF-ON-SEA  
ESSEX SSO 9DF Telephone Southend (0702) 46344

# VALVES

A1065	1-25	ECL80	0-40	GY501	5-00	PL50R	0-95	U25	1-00	UL84	0-50	3V4	0-85	6AM6	0-60	6C4	0-40	6K6GT	0-55	7B7	0-80
AR2	0-80	ECL83	0-40	KT88	0-50	PL509	1-35	U26	0-80	UY41	0-50	5B/254M	0-50	6AN8	0-70	6C8	0-50	6L6M	1-00	7Y4	0-80
AR3	0-80	ECL83	0-40	KT88	0-50	PL802	1-45	U27	1-00	UY85	0-50	5000	5-00	6A05	0-55	6CB6	0-50	6L7G	0-40	9D2	0-80
ATP4	5-00	ECL86	0-40	KT88	0-50	PL802	1-45	U28	0-80	VR105/30	0-50	5B/255M	0-50	6A05	0-55	6CH6	1-60	6SA7	0-55	9D6	0-80
B12H	3-00	EF85	0-85	KT88	0-50	PL802	1-45	U29	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6CL6	0-75	6SC7	0-75	11E2	0-60
DAF96	0-80	EF37A	1-10	KT88	0-50	PL802	1-45	U30	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6D6	0-50	6SG7	0-55	12A6	0-60
DF96	0-80	EF40	0-70	KT88	0-50	PL802	1-45	U31	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6E8	0-75	6SU7	0-60	12AT6	0-45
DK96	0-75	EF40	0-70	KT88	0-50	PL802	1-45	U32	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6F7	1-10	6SUTG	0-45	12AU7	0-45
DL92	5-00	EF83	1-25	KT88	0-50	PL802	1-45	U33	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6G8	0-75	6SUTG	0-45	12AX7	0-35
DL96	0-70	EF83	1-25	KT88	0-50	PL802	1-45	U34	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6H6	0-75	6SUTG	0-45	12BA6	0-50
DY86/87	0-85	EF85	0-40	KT88	0-50	PL802	1-45	U35	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6I6	0-75	6SUTG	0-45	12BE6	0-55
	0-45	EF86	0-40	KT88	0-50	PL802	1-45	U36	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6J6	0-75	6SUTG	0-45	12BH7	0-55
DY802	3-45	EF89	0-35	KT88	0-50	PL802	1-45	U37	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6K6	0-75	6SUTG	0-45	12C8	0-90
EB8CC/01	1-30	EF91	0-60	KT88	0-50	PL802	1-45	U38	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6L6	1-25	6SUTG	0-45	12E1	0-75
	0-45	EF92	0-50	KT88	0-50	PL802	1-45	U39	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6M6	0-75	6SUTG	0-45	12F3	0-75
E180CC	1-00	EF93	0-45	KT88	0-50	PL802	1-45	U40	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6N6	0-75	6SUTG	0-45	12G7	0-50
E182CC	3-00	EF1200	0-75	KT88	0-50	PL802	1-45	U41	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6P6	0-75	6SUTG	0-45	12K8GT	0-75
EA50	0-40	EL34	0-70	KT88	0-50	PL802	1-45	U42	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6Q6	0-75	6SUTG	0-45	12Q5GT	0-50
EABC80	0-40	EL35	0-70	KT88	0-50	PL802	1-45	U43	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6R6	0-75	6SUTG	0-45	12SA7GT	0-80
	0-40	EL37	0-20	KT88	0-50	PL802	1-45	U44	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6S6	0-75	6SUTG	0-45	12SG7	0-80
EAF42	0-70	EL37	0-20	KT88	0-50	PL802	1-45	U45	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6T6	0-75	6SUTG	0-45	12SJT	0-55
EB91	0-30	EL41	0-90	KT88	0-50	PL802	1-45	U46	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6U6	0-75	6SUTG	0-45	12T4	0-40
EB93	1-00	EL81	0-90	KT88	0-50	PL802	1-45	U47	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6V6	0-75	6SUTG	0-45	12U6	0-40
EB94	0-80	EL84	0-80	KT88	0-50	PL802	1-45	U48	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6W6	0-75	6SUTG	0-45	12V6	0-40
EB95	0-75	EL85	0-80	KT88	0-50	PL802	1-45	U49	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6X6	0-75	6SUTG	0-45	12W6	0-40
EB96	0-40	EL86	0-50	KT88	0-50	PL802	1-45	U50	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6Y6	0-75	6SUTG	0-45	12X6	0-40
EB97	0-40	EL86	0-50	KT88	0-50	PL802	1-45	U51	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6Z6	0-75	6SUTG	0-45	12Y6	0-40
EB98	0-40	EL91	1-00	KT88	0-50	PL802	1-45	U52	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6AA6	0-75	6SUTG	0-45	12Z6	0-40
EC32	0-40	EL95	0-70	KT88	0-50	PL802	1-45	U53	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6AB6	0-75	6SUTG	0-45	12AA6	0-40
ECC81	0-45	EL95	0-70	KT88	0-50	PL802	1-45	U54	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6AC6	0-75	6SUTG	0-45	12AB6	0-40
ECC82	0-35	EL94	0-80	KT88	0-50	PL802	1-45	U55	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6AD6	0-75	6SUTG	0-45	12AC6	0-40
ECC83	0-35	EL94	0-80	KT88	0-50	PL802	1-45	U56	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6AE6	0-75	6SUTG	0-45	12AD6	0-40
ECC84	0-35	EL94	0-80	KT88	0-50	PL802	1-45	U57	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6AF6	0-75	6SUTG	0-45	12AE6	0-40
ECC85	0-45	EM80	0-55	KT88	0-50	PL802	1-45	U58	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6AG6	0-75	6SUTG	0-45	12AF6	0-40
ECC86	1-25	EM84	0-55	KT88	0-50	PL802	1-45	U59	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6AH6	0-75	6SUTG	0-45	12AG6	0-40
ECC87	0-50	EM87	1-00	KT88	0-50	PL802	1-45	U60	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6AJ6	0-75	6SUTG	0-45	12AH6	0-40
ECC88	0-50	EM87	1-00	KT88	0-50	PL802	1-45	U61	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6AK6	0-75	6SUTG	0-45	12AJ6	0-40
ECC89	0-50	EM87	1-00	KT88	0-50	PL802	1-45	U62	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6AL6	0-75	6SUTG	0-45	12AK6	0-40
ECF80	0-45	EM87	1-00	KT88	0-50	PL802	1-45	U63	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6AM6	0-75	6SUTG	0-45	12AL6	0-40
ECF82	0-45	EM87	1-00	KT88	0-50	PL802	1-45	U64	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6AN6	0-75	6SUTG	0-45	12AM6	0-40
ECF801	0-75	EY88	0-50	KT88	0-50	PL802	1-45	U65	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6AO6	0-75	6SUTG	0-45	12AN6	0-40
ECF804	2-50	EZ40	0-70	KT88	0-50	PL802	1-45	U66	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6AP6	0-75	6SUTG	0-45	12AO6	0-40
ECF842	0-85	EZ41	0-75	KT88	0-50	PL802	1-45	U67	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6AQ6	0-75	6SUTG	0-45	12AP6	0-40
ECF841	0-80	EZ80	0-35	KT88	0-50	PL802	1-45	U68	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6AR6	0-75	6SUTG	0-45	12AQ6	0-40
ECF84	0-80	EZ81	0-35	KT88	0-50	PL802	1-45	U69	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6AS6	0-75	6SUTG	0-45	12AR6	0-40

PL50R	0-95	U25	1-00	UL84	0-50	3V4	0-85	6AM6	0-60	6C4	0-40	6K6GT	0-55	7B7	0-80
PL509	1-35	U26	0-80	UY41	0-50	5B/254M	0-50	6AN8	0-70	6C8	0-50	6L6M	1-00	7Y4	0-80
PL802	1-45	U27	1-00	UY85	0-50	5000	5-00	6A05	0-55	6CB6	0-50	6L7G	0-40	9D2	0-80
PL802	1-45	U28	0-80	VR105/30	0-50	5B/255M	0-50	6A05	0-55	6CH6	1-60	6SA7	0-55	9D6	0-80
PL802	1-45	U29	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6CL6	0-75	6SC7	0-75	11E2	0-60
PL802	1-45	U30	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6D6	0-50	6SG7	0-55	12A6	0-60
PL802	1-45	U31	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6E8	0-75	6SU7	0-60	12AT6	0-45
PL802	1-45	U32	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6F7	1-10	6SUTG	0-45	12AU7	0-45
PL802	1-45	U33	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6G8	0-75	6SUTG	0-45	12AX7	0-35
PL802	1-45	U34	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6H6	0-75	6SUTG	0-45	12BA6	0-50
PL802	1-45	U35	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6I6	0-75	6SUTG	0-45	12BE6	0-55
PL802	1-45	U36	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6J6	0-75	6SUTG	0-45	12BH7	0-55
PL802	1-45	U37	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6K6	0-75	6SUTG	0-45	12C8	0-90
PL802	1-45	U38	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6L6	1-25	6SUTG	0-45	12E1	0-75
PL802	1-45	U39	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6M6	0-75	6SUTG	0-45	12F3	0-75
PL802	1-45	U40	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6N6	0-75	6SUTG	0-45	12G7	0-50
PL802	1-45	U41	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6P6	0-75	6SUTG	0-45	12K8GT	0-75
PL802	1-45	U42	0-80	VR150/30	0-45	5B/258M	0-50	6A05	0-55	6Q6	0-75				

# GREENWELD

443 Millbrook Road Southampton  
SO1 0HX Tel: (0703) 772501

All mail order and callers (OPEN 9-5 MON-SAT.) to this address please  
—callers only to 2 Deptford Broadway, SE8 (Tel. 01-692 2009), and 38 Lower  
Addiscombe Road, Croydon (Tel. 01-888 2950).

**NEW 44 page CATALOGUE FREE with orders over £2. (Send 10p if under, or 20p stamps for just catalogue).**

## DEVELOPMENT PACKS

50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1000pF, total 210 caps. £2.78  
CR25 carbon film 1/3rd watt resistors, 5%, 10 of each value 10 ohms to 1M Total 810 resistors £8.00. Electrolytics, wire ended 25V working 10 each of: 1, 2, 2, 4, 7, 10, 22, 47 and 100mfd. 70 capacitors for £3.29. 400mV zeners 5% 10 each 3V to 30V, 260 in all. Only £14.00.  
1 watt Metal Film resistors, 5% 10 off each value 27R to 10M, E12 series. Total 680 resistors £19.00. Polystyrene capacitors 160V, 21% 10 of each value from 10pF to 10,000pF. Total 370 capacitors £12.50.

## COMPUTER PANELS

Large quantity always available: 3lb asstd. £1.75; 7lb £3.05; 56lb £18. Pack with about 500 components inc. at least 50 transistors £1.00. Pack with 12 High quality panels, inc. IC's, power transistors, multitrans trim pots hundreds of small signal transistors, resistors, zeners, capacitors, etc. Only £2.75.  
7400 IC pack—20 74 series IC's on panels £1.20.

## FERRIC CHLORIDE

Anhydrous technical quality in 1lb double sealed packs. 1lb £1.00; 3lbs £2.18; 10lbs £8.00; 100lbs £39.00.

## VEROBORD

100sq Ins asstd. sizes and pitches, about 8 pieces (All 0-1" if requested) £1.30.

**PC ETCHING KIT Mk II**  
Contains 1lb Ferric Chloride, 100 sq Ins copper clad board, D.A.I.C. Quick Dry Etch resist em, abrasive cleaner, 2 miniature drill bits, etching dish and instructions. £3.65

## 7lb BARGAIN PARCELS

Hundreds of new components—pots, resistors, capacitors, switches, PC Boards with transistors, diodes and zeners, loads of odds and ends. NOW REDUCED TO £2.90

## TRANSISTOR PACKS

200 asstd. mainly out of spec. transistors, mostly unmarked. PNP plastic; TO3, TO18, PNP AF Small signal and TO3 power devices. About 75% useable devices. Only £1.00. 100 unmarked BC108, untested £2.10. 10 out of spec. 2N3055 £1.30

## 12V 12A REGULATED POWER SUPPLY

Brand new boxed fully stabilized PSU, complete with instruction manual. Load regulation 0-15%. Thermal & Electronic overload protection. £11.00

## BULK BUYERS CORNER

Disc ceramic caps: 33pF. 100pF £8/1000; .02uF 30V £1.50/100; .1uF 50V £2.50/100; .5uF 3V £3/100. Polystyrene 160V 5%; 47, 120, 180, 390, 470pF £2/100.  
Electrolytics: 10,000uF 6-3V £8.50/100; 1000uF 10V £7/100; 2200uF 10V £9/100; 5uF 15V £2/100; 2.5uF 16V £1.50/100; 1uF 25V £2.50/100; 2.2uF 25V £2.50/100; 1uF 25V Tant bead £6.50/100.  
Zeners: 400mV 47V, 5V, 7.5V, 12V, 9V1, 10V, 11V, 12V, 15V, 30V. All £3.50/100. 12V 1.8W (ZC2012) £12/100; 33V 1W (S233C) £12/100; 47V 21W (VR475) £10/100; 22V 3V (BZ270) £10/100.  
Diodes: 1N4001 £2.70/100; 1N4004 £3.80/100; 1N4007 £3/100; BYX94 (1200V 1A) £7/100.

Transistors and IC's: BC107, 8, 9 £7.50/100; BC119 £13; BC139 £15; BC148 £7; BC149 £8; BC157 £8; BC158 £8; BC159 £8; BC172 £8; BC184 £7; BC208 £7; BC212 £7; BC213 £7; BC214 £8; BC252 £8; BC328 £10; BC347 £8; BCX33 £9; BCY70 £9; BF173 £14; BF181 £19; BF182 £19; BF194, 5, 6 £7; BF245 £17; BFY51 £10; BFY52 £10; B5X20 £11; B5Y95A £7; ZTX341 £9; 2N3055 (RCA) £36; 2SC538 £5.  
All price per 100

**SEE PRACTICAL ELECTRONICS FOR INDIVIDUAL COMPONENT PRICES**  
All prices quoted include VAT and UK/BFPO postage. Most orders despatched on day of receipt. SAE with enquiries please.  
Send 10p for Multimeter catalogue—free on request on orders over £3. Official Orders accepted from Schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Surplus components always wanted.

## MULTIMETER MODEL LT22



Probably one of the lowest priced meters featuring a mirror scale, overload protection and 20000 ohms per volt sensitivity. A modern styled meter with unusually clear scale markings. Ranges: DC Volts 0-0.5-2.5-10-50-250-1000 AC Volts 0-10-50-250-1000 DC Current 0-50uA-25mA-250mA Resistance 0-50k-500k-5M (Mid Scale 300-3k-30k) db's 4 ranges —20db to +42db. Size 130 x 90 x 42mm. £19.95.

## VEROBEXES & CASES

Case type 1410, 205 x 140 x 40mm £3.00  
1411, 205 x 140 x 75mm £3.25  
1412, 205 x 140 x 110mm £4.20

Plastic Boxes—Professional quality, two tone grey polystyrene boxes with threaded inserts for mounting PCB boards.

Type 2518, 120 x 65 x 40mm £1.85;  
2520, 150 x 80 x 50mm £2.20; 2522, 186 x 110 x 60mm £2.85; Slotted front type: 220 x 174 x 100/52mm £5.20.

## COMPONENT PACKS

400 asstd. carbon resistors £1.35  
200 asstd P.C. resistors 60p  
100 Wirewounds 2-15W £1.90  
200 Miniature resistors, 1/2, 1 and 1W, mostly carbon film £1.20  
200 poly, mica, ceramic caps £1.10  
100 polyester, .01-2.2uF £1.00  
200 miniature electrolytics, but many unmarked so only £1.00

## TRANSFORMERS

All have mains primaries: 0-0-6V 100mA 90p; 0-0-9V 100mA 97p; 12-0-12V 50mA PC mtng 85p; 12-0-12V 100mA £1.00; 24-0-24V 500mA £2.05; Multitapped transformer to give 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 or 30V, or 12-0-12, or 15-0-15V. 1A version £3.15; 2A version £4.45; 30-0-30V 1A £3.80; 6-0-6V 1A £2.30; 12-0-12V 1A £2.85; 25V 1A £2.00; 29V 50mA 75p; Type LGC: 17V @ 2-4A, 15-7V @ 1-25A, 12V @ 1/2 A. Only £2.90.  
Type JBS: 110V Primary; 31V 300mA Sec. Use 2 (Series srl) to get 31V @ 600 mA, or 62V @ 300mA. Price for 2 £1.05. Type SMS: 12V 130mA, 5-0-5V 120mA, 11-0-11V 10mA £1.20. Few only, 16V 20A £8.50.

## RELAYS

Miniature Plug-in types: 1250 ohm 4c/o 40p; 700 ohm 4c/o 50p. PC 3000 type 650 ohm with 5 heavy duty c/o contacts (Ex-equip) 75p; 10 for £4.00. 6 1/2" easily removable reeds in 3500 ohm coil 50p; Plug in relay: BTG Base 17mm dia x 42mm long 10k coil c/o contact 40p. Omron MK3P plug in relay. 230V AC coil, 3 sets 10Ac/o contacts. £1.20. Same with 12V coil £1.20. Bases 30p.

## REED INSERTS

Min. type, body length 1", 10 for 50p; 100 £3.50; 1000 £25.00.

## ODDS AND ENDS

Edge Connectors, gold plated 0-1" 40 way single sided 60p; 78 way double sided 80p. Heatshrink sleeving, 1m length 0-125" dia 16p. Spiral binding 3m x 2.2mm 20p. 100mfd 10V Tantalum Caps, 10 for 50p, 3kV or 1-8k 1% resistors, 20 for 25p. Polythene connector blocks, 12 way 2A, or 5A 20p; 10+18p; 25+18p. Insulation tape—Red, Black, Blue, Yellow, Green, White or Brown. 5yds x 0-75" 10p per reel, 10+ 9p; 25+ 8p. 1 1/2" Quick blow fuses 1, 1 1/2, 2, 3, 5, 10 or 15A 30p per doz of one value, 10 doz mixed £2.50. 2000mfd 10V capacitors vert mtng, 1000 leads 14 for £1.00. 20 ohm GPO balanced armature telephone insert 30p. 250V 2 1/2A bridge rect 50p. Ex-computer tape: 10 1/2" NAB reels of high grade 1/2" magnetic tape. £2. 10 reels £13, 100 reels £75. Much cheaper to callers.  
BC348B transistors—40V, 100mA, 300mW, Hfe 200 @ 2mA, 12 for 95p; 100 for £6.50.

# Join the Digital Revolution

Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation . . .

Each of the 6 volumes of this self-instruction course measures 11 1/2" x 8 1/2" and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers.

Design and Digital Systems.



## £6.20

plus 80p packaging and surface post anywhere in the world.

Payments may be made in foreign currencies.

Quantity discounts available on request.

VAT zero rated.

Also available—a more elementary course assuming no prior knowledge except simple arithmetic.

Digital Computer Logic and Electronics

In 4 volumes:

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flipflops and Registers

## £4.20

plus 80p P. & P.

Offer Order both courses for the bargain price £9.70, plus 80p P. & P.

### Designer Manager Enthusiast Scientist Engineer Student

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

**Guarantee—no risk to you**

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

To: Cambridge Learning Enterprises (Dept. CIR)  
FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR

\* Please send me . . . set(s) of Design of Digital Systems at £7.00 each, p & p included.

\* or . . . set(s) of Digital Computer Logic and Electronics at £5.00 each, p & p included

\* or . . . combined set(s) at £10.50 each, p & p included.

Name .....

Address .....

\* delete as applicable  
No need to use a stamp—just print FREEPOST on the envelope. PW11



### NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

## Receivers and Components

**BRAND NEW COMPONENTS BY RETURN.** Electrolytics 16V, 25V, 50V-0.47 1-0, 2.2, 4.7, 10mfds.—5p 22, 47—5½p (50V—6p); 100—7p. (50V—8p), 220—8p. (50V—10p), 500—11p. (50V—16p), 1000/25V—18p. Subminiature bead-type tantalums, 0.1/35V, 0.22/35V, 0.47/35V 1.0/35V, 2.2/35V, 4.7/25V—11p. 10/25V, 22/16V, 47/6V, 100/3V—12p. Mylar Film 100V, 0.001, 0.002, 0.005—3p, 0.01, 0.02—3½p. 0.04, 0.05—4p. Mullard C280 series miniature polyester vertical mounting E6 series 0.01—0.1—4p, 0.15, 0.22—5p, 0.33, 0.47—8p, 1.0—15p, 1.5—20p, 2.2—24p. Mullard miniature ceramics 63V, 2%, E12 series 1.8 pf.—47 pf.—3p, 56 pf.—330 pf.—3½p. Plate ceramics 50V E12 series 22 pf.—1000 pf. E6 series 1500 pf.—47000 pf.—2p. Polystyrene 63V E12 series 10 pf.—1000 pf.—3p, 1200 pf.—10000 pf.—4p. Miniature Highstab carbon film resistors ½W E12 series 5% (10% over 1MΩ) 1½—10MΩ—1p. IN4148—3p. IN4002—5p. IN4006—7p. IN4007—8p. Postage 10p. Prices VAT inclusive. The C. R. Supply Co., 127, Chesterfield Rd., Sheffield S8.

**6BA Spacer Pack.** 50 assorted length clearance and threaded through types (brass and alloy) 55p per pack.  
**4BA Spacer Pack.** 50 assorted length clearance and threaded through types heavy duty (brass and alloy) 60p per pack.  
**6 BA Screwpack.** 50 assorted length screws various heads some plated. 30p per pack.  
**Radio Tuning Pulley Pack.** 25 assorted diameter pulleys in brass and alloy, can be fitted to any thickness panels by suitable 6BA screw and nut. 90p per pack.  
**Extension Shaft and Coupler.** Standard size 6.35mm, ¼ dia. shaft 76mm long with rigid coupler complete with grub screws. Heavy brass construction. 35p per pack.  
**Trimmer Convertors.** Enables a standard 6.35 mm control knob to be fitted to "TP" type trimmers (brass) 10p each.  
**Front Panel Steadies.** To fit above ext shafts and convertors or any standard 6.35mm shaft. Complete with lock washer and nut. (brass). 19p each.  
 All the above components are new and carry our unconditional guarantee. Please add 20p postage per order. Mail order only. Trade inquiries invited.  
**Electro-Mech Products, 7 Chantry Avenue, Bideford, Devon. Precision Engineers to the Electronics Industry.**

**MULLARD COMPONENTS.** Send s.a.e. for free list to P.M.S., Dept. PW1, P.O. Box 6, Crawley, Sussex RH10 6LH.

# SMALL ADS

The prepaid rate for classified advertisements is 17 pence per word (minimum 12 words), box number 40p extra. Semi-display setting £14.00 per single column inch (2.5cm). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

## CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

## SOUTH AFRICAN HOBBYISTS

FOR ALL YOUR COMPONENT REQUIREMENTS WRITE TO

### SEFRA TV & ELECTRONICS

P.O. BOX 415 SILVERTON 0127

FOR QUOTE BY RETURN POST

### 300W TOUCH SWITCH KITS

**T8300K** Contains Triac, IC, Diodes, Resistors F.C.B. Frontplate, etc. Replaces conventional light switch with NO REWIRING. TOUCH one insulated plate for ON, another for OFF. Complete with instructions—ONLY 22-97.

**ALSO T8A00K AUTOMATIC** as above but with only ONE TOUCHPLATE. TOUCH for ON and light stays on for a preset time. Ideal for stairs and hall. Complete with instructions—ONLY 22-97.

**300W LIGHT DIMMER KIT** replaces conventional light switch—41-95.

### THIS MONTH'S SPECIAL OFFER

10 TRIACS TAG250 400V/10A for only 22-00.

CMOS	TRIACS	400V	T0220	BC148	8p*
4000	Case 6-5A isolated tab	74p	BC158	11p*	
4001	10A (TAG250)	70p	2N3055	36p	
4002	(3+87P)	2N8027			
4003	Isolating Kit	5p	(put)	30p	
4007	Disc	20p			
4011	NE555 8 pin DIL	44p	IN4004	6p	
4013	741 8 pin DIL	24p	IN4148	4p*	
4015	RESISTORS ¼W 5% E12 22 Ω				
4016	10M Ω				
4017	LDR ¼ dia. 400 Ω to 1M Ω light				
4018	to dark				
4019	NEON wire-ended				
4020	Choke 1½amp				
4021	Rocker switch white SPST				
4022	1A/250V				
4023	MINI MAINS TRANSFORMERS				
4024	100mA 6-0-6V				
4025	12-0-12V				

ADD 8% VAT (\*121%) PLUS 20p P&P. Mail Order Only to:

### T.K. ELECTRONICS

106 Studley Grange Road, London, W7 2LX.

**COMMUNICATIONS RECEIVER modules.** Small superhet circuit boards requiring only controls and tuned circuits. 9 volt. Mosfet mixer, IC IF, BFO, Prod. Det. Excellent AM/CW/SSB results reported by delighted users. From £11-50. SAE details. PR Lodge Electronics, Millend, Stonehouse, Glos.

## VINTAGE RADIO

1920 to 1950

Receivers, valves, components, service data, historical research, books, magazines, repairs and restorations. A complete service for the collector and enthusiast of vintage radio.

S.a.e. with enquiries and for monthly newshet. Full 1976 catalogue, 50p post paid.

**TUDOR REES (Vintage Services), 64, Broad Street, Staple Hill, Bristol, BS16 5NL. Tel. Bristol 565472.**

**LARGE SELECTION of surplus electronic components, speakers, cabinet hardware, etc. Offers invited. Lists available from: C.S.R. Ltd., Dawkins Road, Hamworthy, Poole, Dorset. Tel: 02015 78989.**

### Precision Polycarbonate Capacitors

440V AC RANGE	All High Stability	extremely Low Leakage	63V DC RANGE	Value (µF)	Dimensions (mm)	Price each	±1%	±2%	±5%
0.1µF	L	D	0.01-0.2	11-23	75p				
0.15µF	27	12-7	0.22-0.47	11-23	77p				
0.22µF	33	16	0.68µF	11-44	84p				
0.25µF	33	16	1.0µF	11-56	91p				
0.33µF	33	16	1.5µF	11-74	116				
0.47µF	33	19	2.2µF	11-98	132				
0.5µF	33	19	3.3µF	12-40	160				
0.68µF	33	19	4.7µF	12-82	188				
1.0µF	50-8	19	6.8µF	13-48	220				
1.5µF	50-8	25-4	10µF	14-54	260				
2.0µF	50-8	25-4	15µF	15-54	288				
			22µF	16-60	324				

**TANTALUM HEAD CAPACITORS**—Value available: 0.1, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2, 3.3, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. All at 12p\* each, 10 for 11-10\*, 50 for 45\*, 100 for 49\*.

TRANSISTORS & I.C.'s	BC107/8/9	8p	*BC121/212L	12p	2N3055	50p
	*BC114	12p	*BC219/213L	11p	OC44/45	90p
	*BC147/8/9	10p	*BC214/214L	11p	OC71/2	20p
	*BC153	16p	*BF194/5	12p	NE555 Timer	61p
	*BC154/7/8/9	12p	BFY50/1/2	20p	741C 8 pin DIL	33p
	BC182/182L	11p	AF178	40p	ZN414	11-16
	*BC181/181L	11p	AF239	38p	8N76013ND	
	*BC184/184L	12p	2N3702/4	11p		21-50

**POPULAR DIODES**—1N914 6p, 8 for 45p, 18 for 90p, 1N916 8p, 6 for 45p, 14 for 90p, 1844 5p, 11 for 50p; 26 for 41.00, 1N4148 5p, 6 for 27p, 12 for 48p; 1N4001 5p; 002 6p; 003 6p; 004 7p; 005 7p; 006 8p; 007 8p; 008 8p.

**LOW PRICE ZENER DIODES**—400mW, Tol. ±5% at 5mA. 3V: 3V3; 3V6; 4V7; 6V1; 5V6; 6V2; 6V8; 7V8; 8V2; 9V1; 10V; 11V; 12V; 13V; 13.4V; 15V; 16V; 18V; 20V; 22V; 24V; 27V; 30V; 33V. All at 7p each, 5 for 33p, 10 for 65p, 50 for 83-12. SPECIAL OFFER: 100 Zeners (may be mixed) for 26-00.

**RESISTORS**—High stability, low noise carbon film 5%, ¼W at 40°C, ¼W at 70°C. E12 series only—from 2.2 Ω to 2.2M Ω. ALL at 1p\* each, 8p\* for 10 of any one value, 70p\* for 100 of any one value. SPECIAL PACK: 10 of each value 2.2 Ω to 2.2M Ω (730 resistors) 45\*.

**SILICON PLASTIC RECTIFIERS**—1.5 amp, wire-ended D027: 100 P.I.V. 7p (4 for 26p); 400 P.I.V. 8p (4 for 30p). **BRIDGE RECTIFIERS**—2½ amp: 200V 40p; 350V 45p; 600V 55p.

**SUBMINIATURE VERTICAL PRESETS**—0.1W only: All at 5p\* each; 50; 100; 220; 470; 680 ohm; 1k; 2k; 4k; 6.8k; 10k; 15k; 22k; 47k; 100k; 200k; 500k; 1M; 2M; 5M.

PLEASE ADD 20p POST AND PACKING ON ALL ORDERS. EXPORT—ADD COST OF SEA/AIRMAIL. Add 8% VAT to all items except those marked with \*

Send S.A.E. for additional stock lists. Wholesale price lists available to bona fide companies.

### MARCO TRADING (Dept. P4)

The Old School, Edinstown, Wm. Stephenson.

Tel: Whitnall 464/465 (STD 094 878).

(Proprs. Minicoat Trading Ltd.)

## VALVES

Radio-TV Industrial Transmitting  
2200 Types, 1930 to 1975, many obsolete. List  
20p. S.A.E. for quotation. Postal export service.  
We wish to purchase all types of new and boxed  
valves. Wholesaler's, Dealer's, etc., stocks  
purchased.

**COX RADIO (SUSSEX) LTD., The Parade,  
East Wittering, Sussex. West Wittering 2923**

**500 COMPONENTS.** Resistors, capaci-  
tors, diodes, transistors, pots, coils,  
etc. Identified, formed leads, fall-out,  
and surplus. Good value at £1.75. All  
inclusive (UK postal rates only). CWO  
please to L. Penseny (PW) Bankhead  
Farm, South Queensferry, West  
Lothian.

**DIODES** IN914E 2p ea. £1.30/100, £10/  
1,000 5% Zeners 2.7-36v 5p ea £4/100,  
800V 1 amp Low VF 5p ea £4/100 20p  
p & p. Bale Electronics, 'Nanock'  
Dalton, Dumfriesshire.

### SPECIAL OFFER

1 — ZN1040E Inc. data	£6.00
2 — ZN1040E Inc. data	£11.00
1 — 1040E(R) unmarked reject of above	
Counts / Displays / Resets OK	£2.75
7489 Fully functional 64-bit	
Read / Write Memory — Speed Failures	
1 at 75p, 2 at £1.30, 3 at £1.65, 4 + at 50p each	
All prices inclusive (mail order only).	

### GJD ELECTRONICS

105 Harper Fold Road, Radcliffe, Manchester  
M26 0RQ

**RESISTORS GALORE:** ½ W 5% Carbon,  
E24 Range 910R-820K, 4p for 5 of one  
value, ½ W 1% Metal Oxide, E24 range  
3K3-15K, 5p each. CWO only, P&P  
15p/100 Resistors. D. Korman, 41 Sel-  
wood Road, Sutton, Surrey.

## Aerials

### G2DYM SWL AERIALS

All aerials custom built by G2DYM, Ex-  
B.B.C. Transmitter and Aerial Engineer.

#### DIPOLAS

10, 11, 13, 15, 16, 19, 20, 25, 31, 40, 49,  
or 80m £10 each. Shipping or 160m £15 ea.

#### WIDEBAND

10-160m £15 all c/w 25m Bal-twin feeder  
or with Anti-Colour TV QRM. Braided  
Screened Bal-twin 25m feeder £5 ea. extra.  
P. & P. £1 per aerial. VAT 12½% (except  
export). Design and Technical Consultant  
Service for your "difficult" situation or  
problem, details SAE plus 3 6½p stamps.

**OLD SAWMILLS, WHITEBALL  
WELLINGTON, SOM. TA21 0LU**

SATISFACTION GUARANTEED OR MONEY  
BACK—NO ARGUMENT

## For Sale

**DISCOLIGHTS.** 3-channel soundlights  
£17.50! Strobes £22! Full catalogue  
from: Arvak Electronics, 12a (P)  
Bruce Grove, London N17 (01-808 8923).

P-W 1949-76, P-E 1964-76 15p each plus  
p.p. S.A.E. to Rutherford, 41 Anzio  
Close, Aldershot, Hants.

Please mention

## PRACTICAL WIRELESS

when replying to  
Advertisements

## Books and Publications

### START YOUR OWN BUSINESS REWINDING ELECTRIC MOTORS

This unique instruction manual shows step by  
step how to rewind motors, working part or full  
time, without previous experience. Everything  
you need to know easily explained, including  
where to obtain materials, how to get all the work  
you need, etc. A goldmine of information and  
knowledge.

Only £3-90 plus 26p P&P.

### Magnum Publications Dept PW5

Brinkway Trading Estate, Brinksway,  
Stockport SK3 0BZ.

Overseas Distributors wanted.

### BOOKS FOR THE CONSTRUCTOR PRACTICAL ELECTRONIC PROJECTS

75p+10p P & P

### PRACTICAL TEST EQUIPMENT

75p+10p P & P

### SHORT WAVE RECEIVERS FOR THE BEGINNER

60p+10p P & P

CALVERTON PUBLICATIONS LTD.  
8 Redgates Court, Calverton, Notts.

## Situations Vacant

### MRC NEUROLOGICAL PROSTHESES UNIT

## TECHNICIAN

to help develop and maintain Neuro-  
logical Prostheses (i.e. electronic  
therapeutic systems, parts of which  
are surgically implanted). The work is  
carried out both in the laboratory and  
in patients' homes. The successful  
applicant will have initiative, an  
enthusiasm for electronics and an  
ability to get on with people. Any  
specialised training necessary will be  
given.

Candidate should possess an HNC or  
University degree or City and Guilds  
Full Technological Certificate in a  
relevant subject. Salary on a scale  
rising to £3738 p.a.

Apply in writing to The Director,  
MRC Neurological Prostheses Unit,  
Institute of Psychiatry, De Crespigny  
Park, London SE5, marking the  
envelope M.T.

## Educational

**COURSES—RADIO AMATEURS  
EXAMINATION** City & Guilds. Pass  
this important examination and  
obtain your G8 licence, with an RRC  
Home Study Course. For details of  
this, and other courses (GCE, Pro-  
fessional Examinations etc) write or  
phone—THE RAPID RESULTS  
COLLEGE, Dept JX1 Tuition House,  
London SW19 4DS. Tel. 01-947 7272  
(Careers Advisory Service) or for a  
prospectus only ring 01-946 1102 (24hr  
recording service).

GO TO SEA as a Radio Officer. Write:  
Principal, Nautical College, Broadwater,  
Fleetwood FY7 8JZ.

### THEORY AND PRACTICE OF MODEL RADIO CONTROL

2nd edition with latest circuitry

Development of proportional digital systems  
explained. Gives practical examples of a modern  
digital system transmitter receiver / decoder and  
servo's.

£2-25 plus 35p p. & p. C.W.O.  
S.A.E. for lists.

**D. J. & D. MODELGEAR  
58 LOWTHER GROVE, GARFORTH, LEEDS  
LS25 1EN**

### FREE T.V. CIRCUIT DIAGRAMS

All main British T.V. sets (plus many foreign)  
comprehensively covered in our easy-to-follow  
T.V. Repair Manuals—4 mono and 3 colour.

Just send model no., if colour (mfrs. chassis  
type helps) with £4.50 and receive the manual  
covering your set—plus your sets circuit diagram  
on request free. Set of 7 only £27 post free.

British T.V. Circuit Diagram Manuals—the main  
mono (over 37 series) for £9.90 and virtually  
every colour for £17.50.

Full details of these and other publications from:

### T.V. TECHNIC

76 CHURCH ST., LARKHALL, LANARKS  
Tel. (0698) 883334. ML9 1HE

## Wanted

**WANTED—NEW VALVES, TRAN-  
SISTORS. TOP PRICES,** popular types.  
Kensington Supplies (C), 367 Kensing-  
ton Street, Bradford 8, Yorkshire.

**WE PAY £2 EACH** (plus postage) for  
clean copies of "Radio & TV Servicing"  
books from 1960-61 edition on-  
wards. Bells Television Services, 190  
Kings Road, Harrogate, N. Yorkshire.  
Tel: 0423 55885.

## Service Sheets

**SERVICE SHEETS,** Radio, TV, etc.,  
50p and s.a.e. Catalogue 20p and s.a.e.  
**HAMILTON RADIO,** 47 Bohemia Road,  
St. Leonards, Sussex.

## LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS,  
RECORD PLAYERS, TRANSISTORS,  
STEREOGRAMS, RADIOGRAMS,  
CAR RADIOS)

**ALL AT 75p EACH** (Except colour) & CAR RADIOS  
Please state if Circuit will do if Service Sheet not  
in stock.

**"PLEASE ENCLOSE LARGE S.A.E.  
WITH ALL ENQUIRIES & ORDERS"**

Otherwise cannot be attended to

(Uncrossed P.O.s please, original  
returned if service sheets not available.)

### PLEASE NOTE

We operate a "by return of post" service. Any  
claims for non-delivery should be made within  
7-days of posting your order.

### C. CARANNA 71 BEAUFORT PARK LONDON, N.W.11 6RX

We have the largest supplies of Service  
Sheets (strictly by return of post). Please  
state make and model number alternative.  
Free TV fault tracing chart or TV list on  
request with order.

Mail order or phone 01-458 4882

Large Stocks of Colour Manuals  
**NO OVERSEAS MAIL PLEASE**

**SERVICE SHEETS,** radio, TV etc.  
10,000 models. Catalogue 24p, plus SAE  
with orders, enquiries. Telray, 154  
Brook Street, Preston PR1 7HP.



# SERVICE SHEETS—COLOUR TV SERVICE MANUALS

LARGE SELECTION COVERING MOST MAKES—S.A.E. WITH ENQUIRIES PLEASE TO:

## BELL'S TELEVISION SERVICES

190 KINGS ROAD, HARROGATE, N. YORKSHIRE TEL. (CODE 0423) 55885

We also have a large stock of Books & Magazines on Radio, TV, etc. Free lists on request

### Miscellaneous

## TRANSMIT!

★ Unique **TRANSMITTER/RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £7.95 plus 20p post and packing.

★ Psychedelic **MINI-STROBE** Kit. Take a pocket-sized lightning storm to Disco's & parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too. Send £3.50 plus 20p post and packing.  
(All prices include V.A.T.)

Send remittance to:

**BOFFIN PROJECTS,  
4 CUNLIFFE ROAD,  
STONELEIGH, EWELL, SURREY**  
(Mail order U.K. only)  
Or for more details, send 20p for lists

### ENAMELLED COPPER WIRE

S.W.G.	1 lb reel	½ lb reel
10 to 19	£2.95	£1.60
20 to 29	£3.15	£1.80
30 to 34	£3.45	£1.90
35 to 40	£3.65	£2.10

All the above prices are inclusive of postage and packing in U.K.

### COPPER SUPPLIES

102 Parrwood Road, Withington,  
Manchester 20 Tel: 061-445 8753

**SUPERB INSTRUMENTS CASES** by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range, competitive prices start at a low 82p. Examples: width, depth, height, 8in x 5in x 3in, £1.70. 10in x 6in x 3in £2.42. 10in x 8in x 3in £3.02. 12in x 10in x 3in £3.96. 8in x 4in x 4in £1.98. 10in x 6in x 4in £2.97. 12in x 8in x 4in £3.96. 7in x 7in x 5in £2.91. 8in x 10in x 6in £3.96. 12in x 8in x 7in £4.40. 12in x 12in x 7in £4.84. Plus 85p carriage and 8% VAT. Over 400 models to choose from. Prompt despatch. Free literature (stamp would be appreciated). Bazelli, Dept No. 25, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.



**HELME**  
DO-IT-YOURSELF  
HI-FI STEREO  
SPEAKER KITS  
The best value around!  
Send for details  
**HELME AUDIO  
PRODUCTS LTD.**  
Dept. P.W.  
SUMMERBRIDGE  
HARROGATE YORKS  
Tel. Darley 279 (Std Code 0423-72)

### THE SCIENTIFIC WIRE CO

Copper - Nickel Chrome - Eureka - Manganin Wires.

Enamelled - Silk - Cotton - Tinned Coverings.

No minimum charges or quantities.  
Trade and Export enquiries welcome.

S.A.E. Brings List.

P.O. BOX 38, LONDON, E4 9BW



**BUILD THE TREASURE TRACER MK III Metal Locator**

- Varicap tuning
- Britain's best selling metal locator kit: 4,000 sold
- Weights only 22oz. Fitted with Faraday shield.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send stamped, addressed envelope for leaflet

Complete Kit £12.50 Built & tested £17.50  
Post 85p + £1.90 VAT 8% Post 85p + £1.40 VAT 8%

**MINIKITS ELECTRONICS,  
14 CLEVELAND ROAD,  
LONDON, E18 2AN** (Mail order only)

### MORSE IMPROVEMENT

#### C90 Cassettes

1-12 wpm with simple exercises.

12-24 wpm Computer produced professional level operator material including international symbols.

Price: complete with instruction and exercise booklets £4 each including postage. Overseas £1 extra.

Morse Key and Buzzer Unit suitable for sending practice and DIY tape preparation. Price £3 including postage. Overseas £1 extra.

### MHEL Electronics

12 Longshore way, Milton  
Portsmouth, (UK) PO4 8LS

### H. M. ELECTRONICS

275a FULWOOD ROAD, BROOMHILL,  
SHEFFIELD S10, 3BD.

REC CABINETS (Illus'd)

METAL CASES  
DRY TRANSFER LETTERING

Send 15p for leaflets (Refundable)  
Trade enquiries invited



**RECHARGEABLE NICAD BATTERIES.**  
Pencell, AA—£0.94p, Sub. 'C'—£1.16, 'C'—£1.92, 'D'—£2.59, PP3—£4.48, Chargers, £4.48, £4.48, £4.98, £4.98, £3.98 respectively. Others. All prices include VAT. Add 10% Post and Package. SAE for price list plus 25p for information booklet. Sandwell Plant Ltd., 1 Denholm Road, Sutton Coldfield, West Midlands. 021 354 9764.

## PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware, Aluminium sheet and sections. Printed circuit boards, top quality for individual designs. Prompt service. Send 15p for catalogue.

**Ramar Constructor Services,  
Masons Road, Stratford on Avon,  
Warwicks. Tel. 4879**

**COLCHESTER COMPONENTS SHOP.**  
Now open Sunday-Thursdays 12-6 p.m.  
J. K. Electronics, 11 Mersea Road,  
Colchester 64433.

## Musical Miracles!

by **Dewtron**®

Build your own synthesiser or musical effects using some of the huge range of DEWTRON modules. Or, build fuzz or waa-waa at budget prices using special kits.

Send 20p for Catalogue from—

**D.E.W. Ltd., 254 Ringwood Road, Ferndown,  
Dorset BH22 9AE.**

**AUDIO PLUGS** and sockets at discount prices. Send s.a.e. for details by return. Tape Equipment Supplies, 25 Nuthurst, Sutton Coldfield, West Midlands B75 7EZ.

### 10% OFF TTL THIS MONTH

7400/1/2/3/10/40 @ 11p. 7404/5 @ 13p.  
7408/20/30 @ 14p. 7432 @ 15p. 7411 @ 19p.  
7407 @ 24p. 7419/72 @ 22p. 7437/38/74 @ 25p.  
7413/73 @ 28p. 7478 @ 28p. 74107 @ 29p.  
7486 @ 30p plus many others.

Please deduct 10%, add 15p postage and 8% VAT or send SAE for catalogue to:—

**FRASER-MANNING LTD.**  
26 HERVEY STREET, IPSWICH, SUFFOLK

## 12 VOLT FLUORESCENTS

**35% OFF**  
RRP

MADE BY THORN LIGHTING. Ideal for Caravan, Boat, Tent, Emergency Lighting etc. All lamps guaranteed for 12 months.

21 ins  
13 watt

£4.90



12 Ins  
8 watt

£4.00

All lamps have On/Off Switch, Wrong Polarity Protection Device and Diffuser.

**C60 CASSETTES 32p** All Cassettes in Plastic Case with Index and Screwed Assembly.  
**C90 CASSETTES 45p**

All prices include VAT. Add Postage 5p In £1.

Quantity Discounts: **SALOP ELECTRONICS**  
10 Units 5% **23 WYLE COP**  
50 Units 7% **SHREWSBURY**  
100 Units 10% **Tel. 53206**

**LOW-COST I.C. MOUNTING** for any size DIL package. 100 Soldercon sockets 65p. 7 and 8 hole plastic supports 5p/pair. Quantity rates. SAE details and sample. Trial pack 65p. (P & P 10p/order). P.K.G. Electronics, Oak Lodge, Tansley, Derbyshire DE4 5FE.

### TOO MUCH QRM?

GET RID OF tiring whistles and CW interference FAST with a TUNABLE AUDIO NOTCH FILTER Goes between receiver and speaker. EASY to make, all parts, case, instructions etc., money back assurance, ONLY £5.30 inc. post, £6.50 airmail.

#### CAMBRIDGE KITS

45 (PL) Old School Lane, Milton, Cambridge

### GORSE'S

MAIN STOCKISTS FOR  
**GRUNDIG**

Satellit 2000, 21 Wave Band Radio, TK545 and TK745 Stereo Tape Recorders, Radios, Radio/Cassette Recorders, Cassette Recorders, Microphones, etc., etc.

Please write, phone or call for full details and prices.

42-44 CHURCH ST.,  
BLACKBURN  
Tel: 51682

77 THE MALL  
BURNLEY  
Tel: 35229

## LOW COST — HIGH EFFICIENCY AUDIO TEST OSCILLATOR £20




RANGE: 10Hz to 100kHz. OUTPUT: 1V, sine/sq. DISTORTION: less than 0.02%. 9V battery. Also available in Kit form at £16. Add 8% VAT, P. & P. and ins. 75p. Leaflet available, also F.M. Signal Generator, Millivoltmeter, freq. meter, THD analyser, P.S. Units.

#### TELERADIO ELECTRONICS

325 Fore Street, London, N9 0PE  
Tel. 01-807 3719

FOR A PROFESSIONAL FINISH to your projects use our engraved front panel service. S.A.E. for price list. Write to Box No. 134.

### MINI ACCUMULATORS

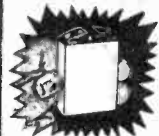

2 volt MULTI-USE Sealed Lead Acid Rechargeable Cells.

Size L650—1.4" X 1.1" X .44" 3 for £2.65  
Size GA2—1.7" X 1.3" X .5" 3 for £2.95  
"Add 25p P. & P. Any Qty"

Suits FI-Cord  
GARFIELDS, 295 Rye Lane, London, S.E.15

### Electrical

STYLI, CARTRIDGES and Audio leads, etc., for the best at keenest prices, send SAE for Free Illustrated List to: Felstead Electronics (PW), Longley Lane, Gatley, Cheadle, Cheshire SK8 4EE.

### Ladders

LADDERS. Varnished 25½ ft extended £26. Carriage £1.90. Leaflet. Alloy extending and Loft Ladders. The Ladder Centre (WLS) Halesfield (1) Telford, Salop. Tel: 586644. Order C.O.D.

## CLASSIFIED ADVERTISEMENTS

Your product or service can be successfully advertised through these columns—Details of how to send your instructions can be found on page 628

**ELECTRONIC  
BROKERS**

**ELECTRONIC BROKERS LTD**  
49/53 Pancras Road  
London NW1 2QB  
Tel: 01-837 7781

Computer parts for hobby, experimental, educational and professional use.

### KB6: 56-station standard Teletype layout

### AS RECOMMENDED FOR PRACTICAL WIRELESS VIDEO-WRITER PROJECT

ASCII-Coded TTL-compatible 4-bank alphanumeric reed-switch keyboard with ROM encoder chip, strobed output, two-key rollover and debounce. Standard 7-bit ASCII code (no parity). Supplied complete with circuit diagrams and code chart.

#### SPECIFICATIONS

Power Supply: +5VDC +/-5% 150mA; -12VDC +/-10% 10mA. Output Logic Levels: Data Bits 1 through 7: Ov "0" .45V; 2.6V "1"; 5.25V. Fan Out: One standard TTL load. Strobe: 2.6V "1" 5.25V; Ov "0" .46V. Fan Out: 10 standard TTL loads. Strobe signal delay 10 milliseconds nominal to allow data to stabilise.

Price **£35.00** plus £1.00 P&P + 8% VAT (Send £38.88)

#### ALSO AVAILABLE—SPECIAL LOW-COST KEYBOARD:

KB5: 3-bank alphanumeric Baudot-coded 36-station keyboard. TTL-compatible strobed output.

Price **£20.00** plus £1.00 P&P + 8% VAT (Send £22.68)

#### BURROUGHS SELF-SCAN DISPLAYS

16 display positions instructed by a 6-bit coded signal to display one of 64 pre-programmed characters as a 5 x 7 dot matrix. Each character 0.4" high. Input signal 6-bit data, clock, reset, etc. Power supplies +5V, -12V and +250V. External repertoire A-Z, 0-9 + special symbols. Size 8½ x 2½ x 1½ approx. Price: Ex-equipment £49.50, brand new £60.00 plus £2 P&P plus 8% VAT.



# WATFORD ELECTRONICS

(Continued from opposite side)

DIODES	*BRIDGE RECTIFIERS	SCR's Thyristors
AAZ15	15p	1A50V 38p
AEY11	60p	1A100V 42p
BA100	10p	1A200V 47p
BY126	12p	1A400V 52p
BY127	12p	1A600V 70p
OA9	9p	3A50V 38p
OA10	40p	3A100V 43p
OA47	8p	3A200V 49p
OA70	8p	3A400V 110p
OA79	12p	3A600V 99p
OA81	10p	5A400V 105p
OA85	12p	7A400V 125p
OA90	6p	C106D 55p
OA91	6p	MCR101 25p
OA95	8p	TIC44 25p
OA200	8p	2N4444 191p
OA202	8p	
PL4004	8p	
IN914	4p	<b>ZENERS</b>
IN918	5p	Rng. 3-3V-33V
IN4001/2	5p	400mV 9p
IN4003	6p	1-3V 17p
IN4004/5	6p	
IN4006/7	7p	<b>VARIABLES</b>
IN4148	4p	MVA1 270p
3A/100V	15p	MVAM2 105p
3A/600V	22p	BB105B 23p
3A/1000V	25p	Noise Diode Z5J 105p

OPTO ELECTRONICS*	VOLTAGE REGULATORS*
LED5 + Clip	DL704 75p
TIL209 Red14p	DL707 75p
0-2" Red 18p	DL727 180p
Yellow, Green	DL728 180p
Amber 21p	DL747 180p
OCF 70 40p	XAN345 3" 632
OCF 71 85p	Green 140p
ORP 12 58p	6" Green 190p
ORP 61 50p	MAN3610 170p
2N5777 36p	BB105B 170p
	Nitron
	3015F 110p

ALUM. BOXES with lid*	ALUM. PANELS*
23x5 1/2 x 1 1/2"	6 x 3 16p
4x4 1 1/2"	6 x 4 22p
4x2 1/2 x 1 1/2"	8 x 3 25p
4x5 1/2 x 1 1/2"	9 x 10 38p
4x2 1/2 x 2"	8 x 12 40p
3x2 1/2 x 1"	42p
6x4 1/2 x 2"	87p
7x5 1/2 x 2"	96p
8x6 3/4 x 3"	118p
10x7 3/4 x 3"	138p
12x8 3/4 x 3"	110p
12x5 3/4 x 3"	117p
12x8 3/4 x 3"	199p

SPEAKERS	COPPER CLAD BOARDS*
8Ω 0-3W	SRBP 8-75 x 9-5" 48p
2-25" 65p	Fibre Glass 6 x 6" 94p
2-5; 3" 58p	6 x 12" 115p
64Ω 2-5" 65p	
4Ω 4" 125p	
4Ω 7 1/2 x 5" 125p	
16Ω 5W	
7 x 4" 185p	

FERRIC CHLORIDE* 1lb bag	DALCO ETCH RESIST
Anhydrous 65p + 30p p. & p.	PEN* + spare tip 69p

VEROBOARD* Pitch	TRANSFORMERS*
0-1 0-15 (copper clad) (plain)	6-0-6V 100mA 90p
2 1/2 x 3 1/2 36p	9-0-9V 100mA 95p
2 1/2 x 5" 43p	12-0-12V 100mA 98p
3 1/2 x 3 1/2 43p	15-0-15V 100mA 185p
3 1/2 x 5" 48p	0-12-0-12V 150mA 140p
2 1/2 x 1 1/2 134p	0-6-0-6V 280mA 150p
3 1/2 x 1 1/2 173p	10-0-10V 0-5A 198p +
4 1/2 x 1 1/2 222p	24-0-24V 0-5A 198p +
Pin of 36 pins 28p	9-0-9V 1A 245p +
Spot face cutter 52p	0-12-0-12V 1A 245p +
Pin insertion tool 72p	15-0-15V 1A 245p +

KNOB'S* ft 1/2" shaft with grub screws, except K2 (push fit) & K8 (for sliders).	
K1 Black or White pointer type	9p
K2 Silver plated aluminium	10p
K4 Black serrated. Metal top with line Indicator 33mm diam.	22p
K4A As above but 25mm diam.	20p
K5 Black fluted metal top and skirt calibrated 0-10. 37mm diam.	26p
K6 PK2 as K5, pointer on skirt	26p
K7 Black, knurled, tapered. Metal top & skirt. Callib. 0-10. 30mm	25p
K8 Black or silvered for slider pot. Professional type, with etch line Indicator 16.5 x 12mm diam.	26p
K10 As above but tapered 18.5 x 17mm diam.	28p
K11 Aluminium, (Top Hat) Knurled body with 18.5mm skirt. Knotted Attractive	30p

PANEL METERS* Full scale	
1 x 46 x 35mm req. 1 1/2" hole	
0-50μA 0-100mA 50μA-0-50μA	
0-100μA 0-500mA 100μA-0-100μA	
0-500μA 0-1 Amp 500μA-0-500μA	
0-1mA 0-50V DC £3-25 each	
0-5mA 0-300V DC	
0-10mA "S"	
0-50mA "VU"	
Price £3-05 each.	
10 x 82-5 x 38mm req. 60mm panel hole	
0-50μA: 0-100μA: 0-500μA	£4-40

DUAL VU METERS (150μA approx) £4-65

TRANSFORMERS* (Mains Prim. 220-240V)	
6-0-6V 100mA 90p	18-0-18V 1A 275p +
9-0-9V 100mA 95p	30-0-30V 1A 295p +
12-0-12V 100mA 98p	6-0-6V 1.5A 240p +
15-0-15V 100mA 185p	9-0-9V 2A 270p +
0-12-0-12V 150mA 140p	Prim. 120/240V, Sec 20V @ 2-5A & 12V @ 1A 160p +
0-6-0-6V 280mA 150p	LT44 Mini. Driver. Pri. 20K, Sec. 1K 54p
10-0-10V 0-5A 198p +	LT700 Min. O/P Pri 1-2K, Sec. 3-2Ω 54p
24-0-24V 0-5A 198p +	MOT Min. O/P Pri 1-2K, Sec. 8Ω 42p
9-0-9V 1A 245p +	
0-12-0-12V 1A 245p +	
15-0-15V 1A 245p +	
30-24-20-15-12-0 1A	
Multi tappings 325p +	
30-24-20-15-12-0 1A	
2A mult tap 345p +	
(Please add 48p p&p charge to all prices marked +, above our normal postal charge.)	

JACK PLUGS	SOCKETS		
Screened chrome	Plastic body	Open metal	Moulded with break contacts
2-5mm 10p	8p	8p	8p
3-5mm 14p	10p	10p	10p
MONO 18p	15p	15p	15p
STEREO 28p	18p	18p	22p

DIN	Plugs	Sockets
2 pin Loudspeaker		
3, 4, 5 (180° & 240°)	12p	8p

CO-AXIAL (TV)	PHONO	BANANA
	assorted colours	4mm 2mm
	Metal screened	
		9p 11p
		10p 10p
		11p 11p

LAMP HOLDERS AND LAMPS*	
LES HOLDER Dome shaped, Red, Blue, Green, Yellow, White	14p
MES BULBS 6v and 12v	9p
LAMP HOLDERS Chrome cover, Red or Amber, Jewelled top	50p
MES BULBS 3-5V 6V 12V	9p
NEONS Mains, Sealed with Resistor, Sq. Top, Pear or Round Top Red 22p	
Neon with leads, 95V AC (No resistor) 9p	

SWITCHES*	SLIDE 250V:
TOGGLE: 2A, 250V	1A DP 10p
SPST 23p	1A DP C/O 12p
DPDT 29p	1A DP 9p
4 pole on/off 35p	4 pole/2 way 15p
SUB-MIN TOGGLE	PUSH BUTTON
SP changeover 48p	Spring loaded
SPST on/off 44p	SPST on/off 55p
DPDT 6 tag 69p	SPDT C/over 85p
DPDT Centre off 88p	DPDT 6 Tag 85p

SWITCHES* PUSH BUTTON:	
Miniature Non Locking	
Push to Make 15p	Push to Break 25p
ROCKER (white): 10A 250V	
SP changeover centre off	25p
ROCKER (black) on/off 10A 250V	20p
ROCKER: Illuminated (white)	
lights when on: 3A 240V	46p
ROTAARY: (ADJUSTABLE STOP) 1 pole	
12-way, 2p/2-6w, 3p/2-4w, 4p/2-3w 30p	
ROTAARY: Mains 250V AC, 4 Amp 28p	

## INDEX TO ADVERTISERS

A. H. Supplies	556
Alben Engineering	603
Ambit International	620
Astro Electronics	584
Babanipress	632
Bamber, B.	584
Barclay Electronics	551
Barrie Electronics	604
Bell's Television Services	628
Bentley Acoustic Corp.	548
B. H. Component Factors	622
Bi-Pak Ltd.	549
Bi-Pre-Pak Ltd.	623
Birkett, J.	550
Boffin Projects	628
British National Radio & Electronics School	552, 553, 562, 604, 616
J. Bull (Electrical) Ltd.	611
C.D.I. Electronics	620
Calverton Publications	627
Caranna, C.	627
Cambridge Kits	629
Cambridge Learning	625
Chromasonics	565
C.J.L. Ltd.	548
Copper Supplies	628
Cox Radio (Sussex) Ltd.	627
Crescent Radio Ltd.	562
Crofton Electronics	554
Decca Radio Ltd.	603
D.E.V. Ltd.	627
D.J. and D. Model Gear	566, 567
Doram	
Eagle International	546
Electro-Mech Products	626
Electronics Brokers Ltd.	629
Electronics Design Associates	550
Electronic Mail Order Ltd.	616
Electrospares	565
Electrovalve Ltd.	548
Express Components	627

Flairline	608
Fraser-Manning Ltd.	628
Garfields	629
G.J.D. Electronics	627
Golding	601
Gorses's	629
Greenbank Electronics	620
Greenway Electronics	554
Greenweld Electronics	625
H.A.C. Short-Wave Supplies	554
H.M. Electronics	628
Harversons Surplus	563
Heathkit	615
Helme Audio	628
Henry's Radio	555
Home Radio	564
I.L.P. Electronics Ltd.	619
Integrex	558
Intertext I.C.S.	546
Jostikits	579
Kinnie Components	624
Kramer & Co.	624
Lectronic	614
Lewis Radio	615
Linear Products	554
Lynx Electronics	580
Magenta Electronics	565
Magnum Publications	627
Maplin Electronic Supplies	cover iv
Marco Trading	626
Marshall, A. & Sons	558
M.H.E.L.	628
Minikits Electronics	628
Monolith Electronics	548
M.R.C.	627
Newmart Electronics	562
Orchard Electronics	546

Partridge Electronics Ltd.	565
P.B. Electronics	603
P.C. Radio (Colomar)	624
Precision Petite	608
Pulse Electronics	556
Radio Component Specialists	621
Radio Exchange Ltd.	cover iii
Ramar Construction Services	628
R.F. Services	620
R.S.C. (Hi-Fi)	547
R.S.T. Valve Mail Order Co.	617
Radio & T.V. Components Ltd.	607
Sales Team, The (Videomaster)	583
Salop Electronics	629
Saxon Entertainments	557
Scientific Wire Co., The	628
Sefra	626
Serlay Book Co.	618
Sintel	616
Sonic Hi Fi	580
Southern Valve Co.	632
Superelectronics	615
Swanley Electronics	618
Tamba Electronics	612
Tandy Corp.	556, 608
Technomatic Ltd.	622
Teleradio Electronics	629
T.K. Electronics	626
Trampus Electronics	cover ii
T.U.A.C.	560, 561
Tudor Rees (Vintage Services)	626
T.V. Technical Publications	627
Vero Electronics	550
Watford Electronics	630, 631
Web Europa	556
West London District Supplies	608
Williams, Mick	564
Wilmslow Audio	559
Xeroza Radio	612
Z. & I. Aero Services	632

Head Office and Warehouse  
44A WESTBOURNE GROVE  
LONDON W2 5SF  
Tel: 727 5641/2/3

# Z & I AERO SERVICES LTD.

Retail Shop  
85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel: 580 8403  
Open all day Saturday

Please send all correspondence and Mail-Orders to Head Office

## POWER TRANSISTORS

OC24	0-60...ASZ15	0-80
OC25	0-50...ASZ16	0-80
OC26	0-40...ASZ17	0-80
OC28	0-60...ASZ18	0-80
OC29	0-60...BD131	0-40
OC35	0-50...BD132	0-50
OC36	0-65...BD133	0-55
AD140	0-45...BD135	0-30
AD149	0-45...BD136	0-32
AD161	0-38...BD137	0-32
AD162	0-38...BD232	0-50
ADZ11	1-25...BU208	2-00
ADZ12	1-25...2N3055	0-60

**HIGH GAIN DARLINGTON PAIRS**  
Plastic 3-lead case encapsulated DARLINGTON pair. Typical current gain 30,000. Max. collector voltage V<sub>CB0</sub> 40V. Max. collector current 400mA. I<sub>CB0</sub> = 10nA.  
BC516-PNP £0-80.  
BC517-NPN £0-80.

**SILICON STUDMOUNTED POWER RECTIFIERS BYX25-1000R**  
1000 p.i.v. at 20A forward current, reverse polarity (i.e. Stud Anode).  
SPECIAL OFFER £0-55 each.

## FULLY GUARANTEED



OA2	0-45	6AS5	0-85	19AQ5	0-75
3V4	0-55	6AS6	0-80	30A5	0-70
OB2	0-45	6AS7G	1-00	30C15	1-00
OC3	0-45	6A76	0-60	30C17	1-10
OD3	0-45	6A78	0-50	30F5	1-00
1B3GT	0-35	6A78A	0-75	30F2	0-80
1L4	0-32	6A86	0-40	30FL12	1-10
1R4	0-50	6BA6	0-38	30PL14	0-90
1R5	0-55	6BE6	0-45	30P12	1-00
1S4	0-40	6BH6	0-75	30P19	0-95
1S5	0-40	6BJ6	0-75	30PL13	1-10
1T4	0-40	6BN6	0-80	30PL14	1-10
3A4	0-80	6BN8	0-85	30PL15	1-10
3A5	1-00	6B28	0-55	35A3	0-70
354	0-50	6B27	0-70	35A5	0-80
3V4	0-80	6C4	0-40	35B5	0-70
5R4GY	1-00	6C86	0-50	35C5	0-70
5U4G	0-55	6EA8	0-75	35D5	0-80
5Y2GT	0-65	6F6GC	0-80	35V4	0-80
5Z4GT	0-55	6GK5	0-70	50B5	0-85
6A84	0-50	6H8GT	0-80	50C5	0-70
6AC7	0-60	6J4	0-75	75C1	0-75
6AFAA	0-70	6J5GT	0-55	85A2	0-75
6AG5	0-35	6J6	0-35	90C1	0-85
6AG7	0-60	6SL7GT	0-55	90T	0-85
6AH6	0-70	6SN7GT	0-55	5763	1-50
6A15	0-45	12AT7	0-45	EABC80	0-40
6AK5	0-45	12AU7	0-50	EAC91	0-60
6AK8	0-70	12AX7	0-30	EAF42	0-70
6AL5	0-30	12BA4	0-90	EAF801	0-65
6AM6	0-65	12B6A	0-50	EC41	0-75
6AN5	2-50	12BE6	0-60	EBG81	0-90
6AN6	0-70	12BH7	0-60	EBF80	0-45
6AQ5	0-50	12X4	0-50	EBF89	0-40

## VALVES

EF92	0-75	PC86	0-65	PL519	1-55
EF97	0-70	PC88	0-65	PY81	0-45
EF98	0-90	PC900	0-60	PY82	0-45
EF183	0-35	PCC84	0-45	PY83	0-50
EF184	0-40	PCC85	0-45	PY88	0-50
EFL200	0-75	PCC88	0-65	PY800	1-10
EL41	0-80	PC289	0-55	PY801	0-55
EL81	0-60	PCF80	0-40	TY21	0-30
EL82	0-60	PCF82	0-40	TY22	0-30
EL83	0-60	PCF84	0-65	UC84	0-75
EL84	0-35	PCF86	0-65	UC85	0-50
EL86	0-50	PCF88	0-65	UC86	0-75
EL88	0-50	PCF200	0-60	UC87	0-70
EL95	0-70	PCF201	0-85	UC88	0-80
EL300	2-10	PCF202	0-55	UC89	0-80
EL504	0-80	PCF801	0-75	UC90	0-75
EL821	3-20	PCF802	0-55	UC91	0-80
EL822	3-50	PCF803	0-55	UC92	0-80
EM71	0-80	PCF804	0-55	UC93	0-80
EM80	0-55	PCF805	0-55	UC94	0-80
EM81	0-60	PCF806	0-55	UC95	0-80
EM83	0-50	PCF807	0-55	UC96	0-80
EM84	0-60	PCF808	0-55	UC97	0-80
EM85	1-00	PCF809	0-55	UC98	0-80
EM87	1-00	PCF810	0-55	UC99	0-80
EY51	0-45	PCF811	0-55	UC100	0-80
EY81	0-45	PCF812	0-55	UC101	0-80
EY84	3-50	PCF813	0-55	UC102	0-80
EY87	0-50	PCF814	0-55	UC103	0-80
EY88	0-50	PCF815	0-55	UC104	0-80
EZ20	0-30	PCF816	0-55	UC105	0-80
EZ21	0-35	PCF817	0-55	UC106	0-80
EZ34	0-80	PCF818	0-55	UC107	0-80
KT96	3-95	PCF819	0-55	UC108	0-80
KT98	4-30	PCF820	0-55	UC109	0-80

**HANDLING AND POSTAGE CHARGES.** When ordering through our Mail Order Service please add 20p in £ for postage and packing. Our new Catalogue 1976/1977 is now available. Please send £0-30 for your copy.

**VALUE ADDED TAX:** Prices are exclusive of VAT, at present rated at 12½%. This percentage must be added to the total value of the order including handling charges.

## SOUTHERN VALVE COMPANY

P.O. Box 144, Barnet, Herts. Tel: 01-440 8841

QUALITY Valves—90 day guarantee. ALL NEW & BOXED VALVES (incl. tax)—many makes. Radio Societies, trade etc. welcome.

AZ31	65p	PCC85	44p	PY801	41p
DY86/7	38p	PCC88	62p	UBF89	47p
DY802	42p	PCC89	60p	UC286	46p
EB91	15p	PCC189	65p	UCB42	72p
EC351	35p	PCF80	40p	UCH81	45p
ECC82	35p	PCF82	60p	UCL82	42p
ECC83	34p	PCF86	58p	UCL83	58p
ECC85	40p	PCF200	95p	UP41	68p
ECC88	48p	PCF801	50p	UP89	42p
ECH42	72p	PCF802	50p	UL41	72p
ECH31	35p	PCL84	47p	UL84	44p
ECH83	35p	PCF806	60p	UY85	35p
ECH84	52p	PCF808	£1-12	U25	72p
ECL80	52p	PCH200	77p	U26	65p
ECL82	47p	PCL82	37p	U191	70p
ECL83	65p	PCL88	60p	8/30L2	70p
ECL86	60p	PCL84	47p	95W7	65p
EF90	30p	6F6	62p	6F28	70p
EF85	37p	PCF805	62p	6F28	68p
EF86	58p	PCL86	60p	6V8	47p
EF89	38p	PCL200	£1-80	6L6 (near 90p	
EF183	37p	PD500	£2-25	equiv KT86)	
EF184	37p	PFL200	72p	20L1	80p
EH90	50p	PL39	62p	20P4	85p
EL34	85p	PL81	60p	30C1	40p
EL41	58p	PL81A	64p	30C15	78p
EL94	36p	PL82	38p	30C17	80p
EL90/1	47p	PL83	46p	30C18	£1-25
EM84	47p	PL84	46p	30F6	75p
EY61	47p	PL600	76p	30FL1	97p
EY86/7	35p	PL504	41p	30FL2	97p
EZ40/1	58p	PL608	83p	80L1	40p
EZ80	38p	PL609	£1-80	80L15	78p
EZ81	30p	PL619	£2-80	80L17	78p
GY501	80p	PL602	£2-00	80P12	75p
GZ80	40p	PY88	62p	80P19	70p
PC86	65p	PY618	41p	80PL1	£1-80
PC88	65p	PY88	41p	80PL13	78p
PC87	40p	PY500	£1	80PL14	85p
PC900	40p	PY600A	£1	80PL15	85p
PC84	40p	PY800	41p	80P4MR	90p

We offer return of post service. Post free over £10-00. Postage: 1st valve 9p, extra valves 6p. Max. 55p. Most types available, send see for lists. Discount Prices. All prices subject to alteration without notice due to market fluctuations etc. Trade: Representative calls certain areas. Telephone enquiries welcomed, see with enquiries PLEASE! C.W.O. ONLY. No C.O.D. Export enquiries welcomed. VAT invoices on request. Mail order only. (Large valves 2p extra).

Use your calculator  
however simple as a real  
scientific/mathematical device

## ELECTRONIC CALCULATOR USER'S HANDBOOK

by M. H. Babani B.Sc. (Eng)  
208 pages 4½ x 7½. 95p

Instant reference formulae, data, methods of calculating equations, trig. and hyperbolic functions, logs, square roots, etc., metric conversions, binary, etc. etc. (ISBN 0 85734 0368)

## HOW TO BUILD YOUR OWN METAL & TREASURE LOCATOR

by F. G. Rayer, T.Eng(CEI) Asstt. I.E.R.E.  
96 pages 4½ x 7½. 85p

Tells you progressively how to make your own locator stage by stage, so that beginner, and expert can enjoy using it. (ISBN 0 85934 035)


OBTAINABLE FROM most large branches of W. H. Smith, good bookshops, component dealers, mail order houses, etc. S.A.E. brings complete list.

**BABANI PRESS LTD.** The Grampians, Shepherds Bush Rd. London W6 7NF 01-603 7296/2581

Please mention  
Practical Wireless  
when replying  
to  
Advertisements



# NEW ELECTRONIC MASTER KIT

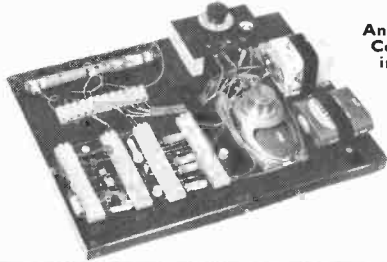

Another completely solderless Electronic Construction Kit with many more projects, including Transistor Radios of various types and wavebands. Amplifiers, Metronome, Sound Amplifier, Transistor Tester, Signal Generator, Quick check component Tester, Tuners, Crystal Set, Morse Code Practice Oscillator with Morse Key, A. F. Oscillator etc. etc., Also a special project V.H.F. Aircraft Receiver!!

**£14.99**

inc. P. & P. Complete kit of parts including construction plans.

And all these components!!

2 x Interchangeable Control Panels (ready drilled).  
4 x Solderless Construction Boards (ready drilled).  
Large 13 x 9 1/2" Baseboard. (ready drilled). Ready Wound Medium Wave, Long Wave, Short Wave, and V.H.F. Coils. 7" Ferrite Rod. Quality 5" x 3" Loudspeaker. Crystal Earpiece. Also!! Knobs, Dial, Wire, Sleeving, Capacitors, Resistors, Transistors, Battery Straps, Connector Clips, Screws, Nuts and Bolts, Potentiometers, Tuning Capacitors, Instruction Manual and Pictorial Diagrams.

## VHF AIR CONVERTER KIT

Build this Converter Kit and receive the Aircraft Band by placing it by the side of a radio tuned to Medium Wave or the Long Wave Band and operating as shown in the instructions supplied free with all parts. Uses a retractable chrome plated telescopic aerial, Gain Control, V.H.F. Tuning Capacitor, Transistor, etc.

All Parts including Case and Plans. **£3.95** P & P and Ins. 45p.



## NEW ROAMER TEN MODEL R.K.3.


MULTIBAND V.H.F. AND A.M. RECEIVER  
13 TRANSISTORS AND FIVE DIODES  
QUALITY 5" x 3" LOUDSPEAKER

WITH Multiband V.H.F. section covering Mobiles, Aircraft, T.V. Sound, Public Service Band, Local V.H.F. Stations, etc., and Multiband A.M. section with Airspaced Slow Motion Drive Tuning Capacitor for easier and accurate tuning, covering M.W.1. M.W.2. L.W. Three Short Wave Bands S.W.1. S.W.2. S.W.3 and Trawler Band. Built in Ferrite Rod Aerial for Medium Waves, Long Wave and Trawler Band, etc. Chrome Plated 7 section Telescopic Aerial, angled and rotatable for peak Short Wave and V.H.F. reception. Push Pull output using 600mw Transistors. Gain, Wave-Change and Tone Controls. Plus two Slider Switches. Negative Feedback circuit and SPECIAL POWER BOOSTER SOCKET AND RESISTOR, to virtually double gain if required. Powered by P.P.9.9 volt battery.

Complete kit of parts including carrying strap-Building Instructions and Operating Manuals.

**£13.99** inc. P & P.

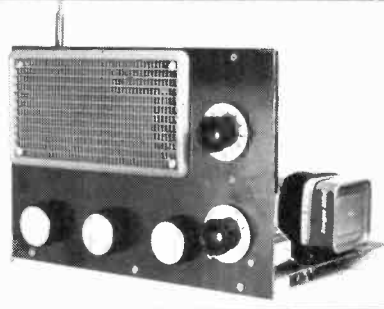
Case Enclosure Kit (if required) £1.80 inc. P & P.


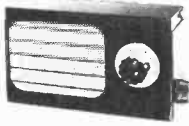
## POCKET FIVE

NOW WITH 3" LOUDSPEAKER

3 Tuneable wavebands. M.W., L.W., and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5 1/2" x 1 1/2" x 3 1/2" approx.



Total Building Costs **£4.50**

All Parts including Case and Plans. P & P + Ins. 60p.

## TRANS EIGHT

8 TRANSISTORS and 3 DIODES

6 Tuneable Wavebands: MW, LW, SW1, SW2, SW3, and Trawler Band. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for Short Waves, 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker.

Complete kit of parts including construction plans. P & P + Ins. 70p.

**£7.50**

## ELECTRONIC CONSTRUCTION KITS



**ECK 2** Self Contained Multi-Band V.H.F. Receiver Kit. 8 Transistors and 3 Diodes. Push/Pull output. 3" Loudspeaker, Gain Control. Superb 9 section swivel ratchet and retractable chrome plated telescopic aerial. V.H.F. Tuning Capacitor, Resistors, Capacitors, Transistors, etc. Will receive T.V. Sound, Public Service Band, Aircraft, V.H.F. Local Stations, etc. Operates from a 9 Volt PP7 Battery (not supplied with kit). Complete kit of parts including construction plans

**£7.95** P & P and Ins. 70p



**ECK 4** 7 Transistors, 6 tuneable wavebands, MW, LW, Trawler Band, 3 Short Wave Bands, Receiver Kit. With 5" x 3" Loudspeaker.

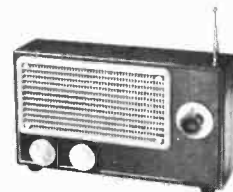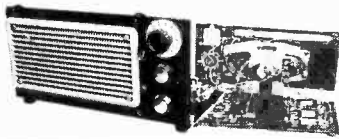Push/Pull output stage, Gain Control, and Rotary Switch. 7 Transistors and 4 Diodes. 6 section chrome-plated telescopic aerial. 8" Sensitive Ready Wound Ferrite Rod Aerial. Tuning Capacitor, Resistors, Capacitors, etc. Operates from a 9 Volt PP7 Battery (not supplied with kit). Complete kit of parts including construction plans. **£7.25** P & P and Ins. 70p.



**£7.10**

## ROAMER SIX

CASE AND LOOKS AS TRANS EIGHT

6 Tuneable Wavebands: MW, LW, SW1, SW2, Trawler band plus an extra Medium waveband for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Complete kit of parts including construction plans P & P + Ins. 70p.

## NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit. Build these projects without soldering iron or solder.

★ 4 Transistor Earpiece Radio ★ Signal Tracer ★ Signal Injector ★ Transistor Tester NPN-PNP ★ 4 Transistor Push Pull Amplifier ★ 5 Transistor Push Pull Amplifier ★ 7 Transistor Loudspeaker Radio MW/LW ★ 5 Transistor Short Wave Radio ★ Electronic Metronome ★ Electronic Noise Generator ★ Batteryless Crystal Radio ★ One Transistor Radio ★ 2 Transistor Regenerative Radio ★ 3 Transistor Regenerative Radio ★ Audible Continuity Tester ★ Sensitive Pre-Amplifier  
Components include: 24 Resistors ★ 21 Capacitors ★ 10 Transistors ★ 3in Loudspeaker ★ Earpiece ★ Mica Baseboard ★ 3 1/2-way connectors ★ 2 Volume controls ★ 2 Slider Switches ★ 1 Tuning Condenser ★ 3 Knobs ★ Ready Wound MW/LW/SW Coils ★ Ferrite Rod ★ 6 1/2 yards of wire ★ 1 Yard of sleeving, etc. Complete kit of parts including construction plans.

**£9.00**

Total Building Costs P & P + Ins. 85p.



## RADIO EXCHANGE LTD.,

61A HIGH STREET,  
BEDFORD MK40 1SA

Tel: 0234 52367

ALL PRICES INCLUDE VAT

Reg. No. 788372

★ Callers side entrance "Lavelle's" Shop.  
★ Open 10-1, 2.30-4.30. Mon-Fri. 9-12 Sat.

I enclose £.....

for .....

Name .....


Address .....

PW/11/76

# Make it with MAPLIN!


**ELECTRONIC COMPONENTS**  
WIDE RANGE • HIGH QUALITY • FAST SERVICE

## The 4600 SYNTHESISER

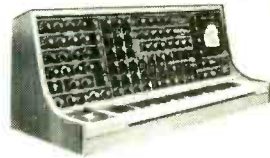

We stock all the parts for this brilliantly designed synthesiser, including all the PCB's, metalwork and a drilled and printed front panel, giving a superb professional finish. Opinions of authority agree the ETI International Synthesiser is technically superior to most of today's models. Complete construction details in our booklet now available price £1.50, or send SAE for specification.

## ELECTRONIC ORGAN

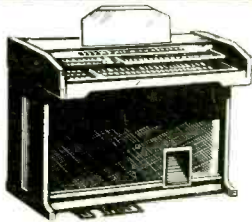


### BUILD IT YOURSELF ... IN STAGES

Get started with a 49 note instrument - features tremulant and reverburation. Ideal to learn on. Leaflet MES 51. Price 15p gives full details to build this complete instrument.

Extend the range of MES 51 by adding another keyboard and several new tone colours. Leaflet MES 52. Price 15p also shows how to use 61 note keyboards.

Fully controllable attack and decay controls (normally found only on the most expensive organs), up to seven footages on each keyboard, up to 70 controls including drawbars, and a 13 note pedalboard, make up the additions described in the step-by-step 32 page instruction leaflet MES 53. Price 35p.

## GRAPHIC EQUALIZER

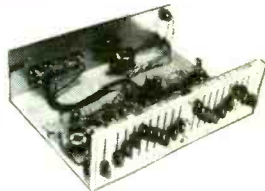

A really superior high quality stereo graphic equalizer featuring 9 octaves per channel. We stock all the parts (except woodwork) including the metalwork drilled and printed. 15p brings you a reprint of the article.

## DIGITAL CLOCK KITS

ONLY **£8.60** INC. VAT  
E/P/P



This is a fully constructed and tested electronic clock module as illustrated. Data sheet supplied. Simple to connect to alarm and your battery/mains radio. Smart case available. Data sheet available separately. Please send SAE.

- \* Bright 4 Digit 0.5" Display
- \* Flashing Colon (1Hz)
- \* Switch for Display Seconds
- \* Alarm Set Indicator
- \* P.M. Indicator
- \* Power Failure Indicator
- \* Sleep Timer
- \* Snooze Timer
- \* Time can be set accurately to within one second
- \* Leading Zero Blanking

SIMPLE CLOCK KIT - £9.38 ALARM CLOCK KIT - £10.99.  
ALARM CLOCK & RADIO CONTROLLER KIT - £11.51.  
SMART PLASTIC CASE with fully punched chassis - £2.49.  
Please send SAE for our Clock data sheet.



## 100 W PER CHANNEL STEREO DISCO

- \* Automatic voice operated fader
- \* Belt drive turntables
- \* Monitor facilities (Headphones and VU meters)
- \* Sound operated light show - plus many other advantages.

Send for our leaflet MES 41, giving full details for construction. Price 20p. Soon you'll be the Deejay everyone wants at their party!

## Get our FABULOUS NEW 1977/78 CATALOGUE

PUBLICATION DATE OCT. 28, 1976 ON APPROVAL

All new. Completely re-written. Hundreds of new lines. Lots of exciting new projects to build. PRICE 50p. SEND NO MONEY NOW. Overseas send 8 International reply coupons. Everyone ordering before publication date will receive a pack of ten super special offer coupons giving big discounts on ten different popular items—YOU COULD SAVE POUNDS!! SO DON'T DELAY FILL IN AND POST THE COUPON NOW.

JOIN OUR MAILING LIST NOW!  
Published every two months our Newsletter gives full details of our latest guaranteed prices. Send just 30p and we'll send you the next six news letters as they are published.

- \* SAVE ££'s ON SPECIAL OFFERS!
- \* DETAILS OF NEW PROJECTS AND NEW LINES

Please rush me a copy of your brand new 1977-78 catalogue the instant it is printed (October 28th, 1976). Only if I am completely satisfied that it is worth every penny will I send 50p within 14 days of receipt. If I am not satisfied I may return the catalogue to you within 14 days without obligation. I understand that I need not purchase anything from your catalogue should I choose to keep it.

NAME \_\_\_\_\_ PW

ADDRESS \_\_\_\_\_



MAPLIN ELECTRONIC SUPPLIES  
All mail to: P.O. Box 3, Rayleigh, Essex SS6 6LR

If you do not wish to cut magazine, write your request for catalogue on separate sheet

69 Rayd y Deford